
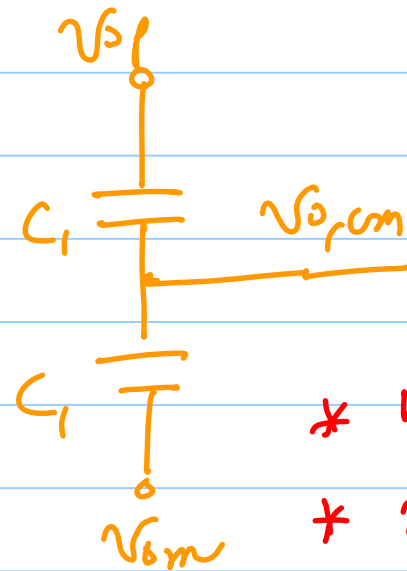


ECE 614 - Lecture 7

Note Title

9/16/2014

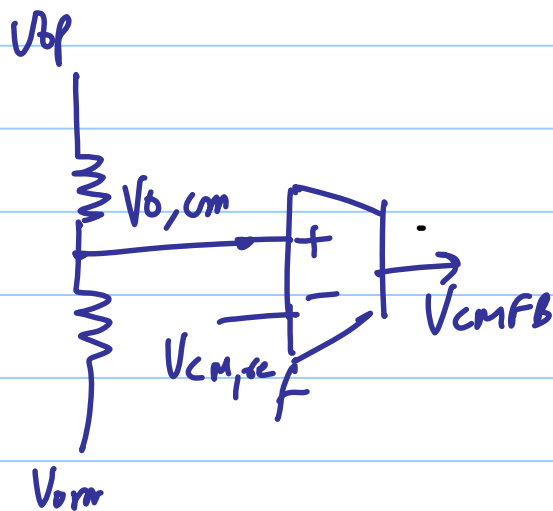CM-detectors $\rightarrow$ dual diff pair
 $\rightarrow$ Resistive averaging $\rightarrow$ load the output
but wide swing




* wide swing

* no resistive loading


* Can we use capacitive CM-detector?

Switched Capacitor Circuits

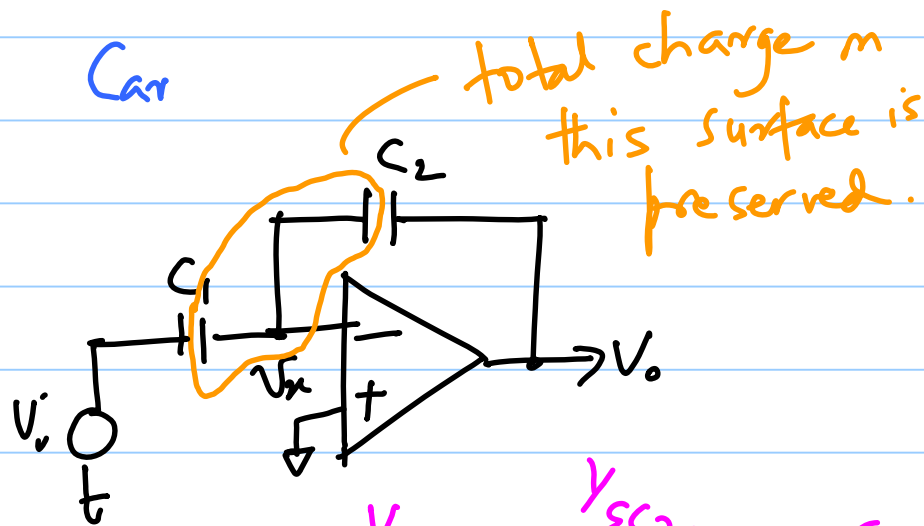


$$\frac{v_o}{v_i} = -\frac{V_{SC2}}{V_{SC1}} = -\frac{C_1}{C_2}, \quad \text{No resistive loading!}$$

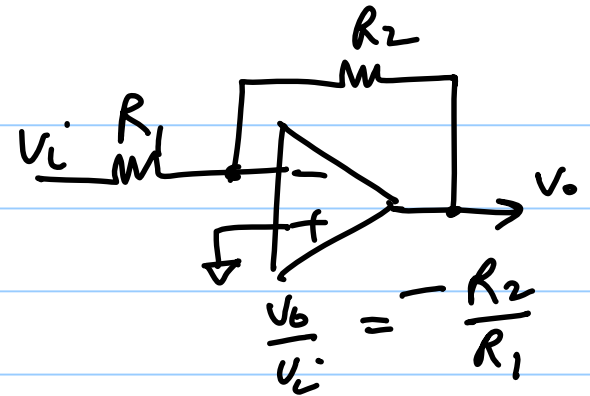
But, there is no DC feedback path.
↳ doesn't bias properly



Switched Cap Resistor

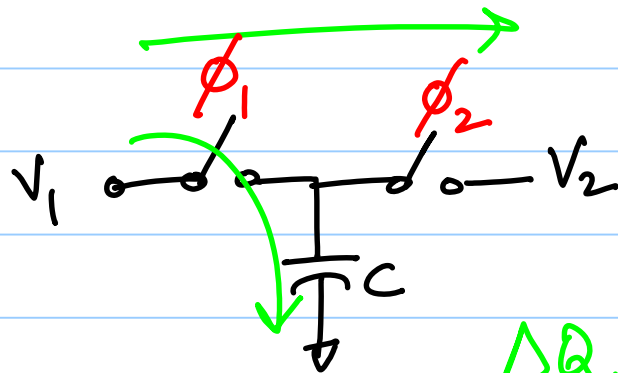


$$\Delta Q = C(V_1 - V_2)$$

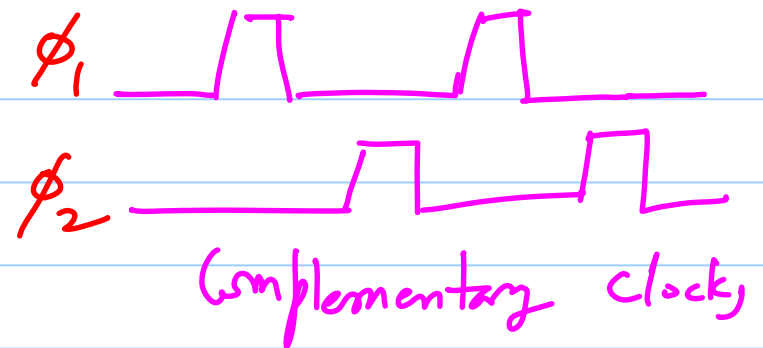

@ f_s




$$I_{av} = \frac{\Delta Q}{T_s} = f_s \Delta Q = f_s C (V_1 - V_2)$$

$$= \frac{V_1 - V_2}{\frac{1}{f_s C}}$$

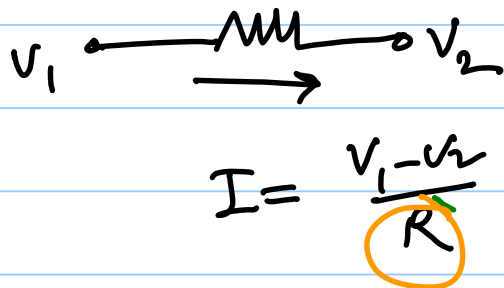

$$R = \frac{1}{f_s C}$$

X Discrete-time circuit

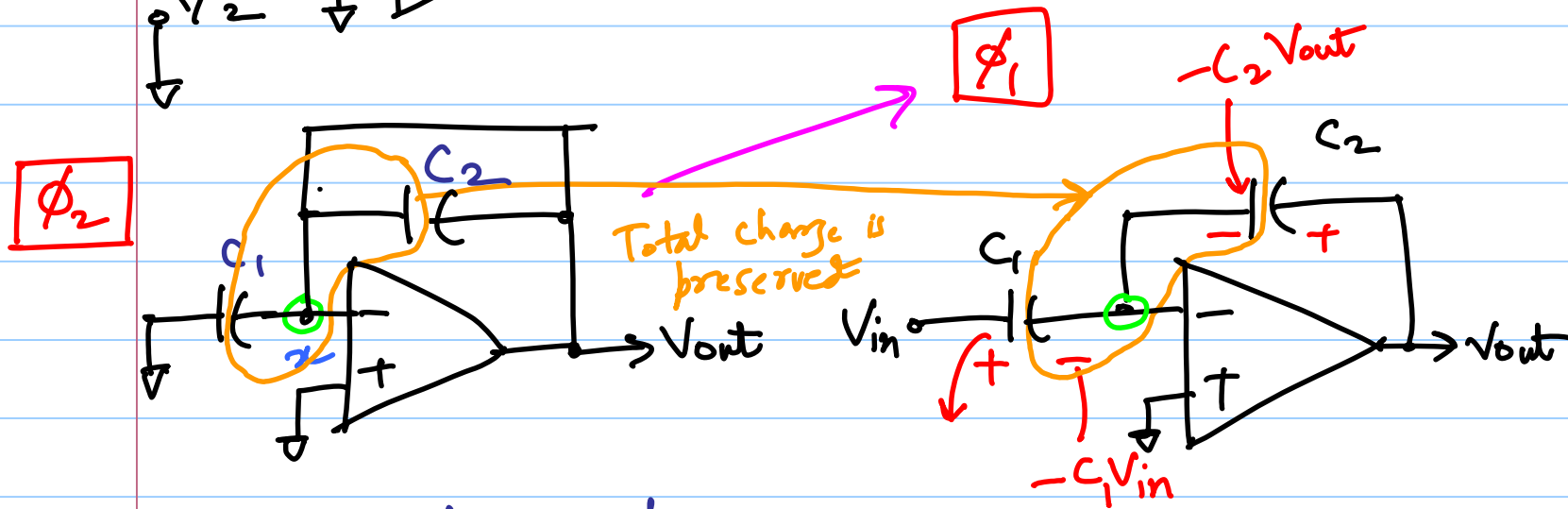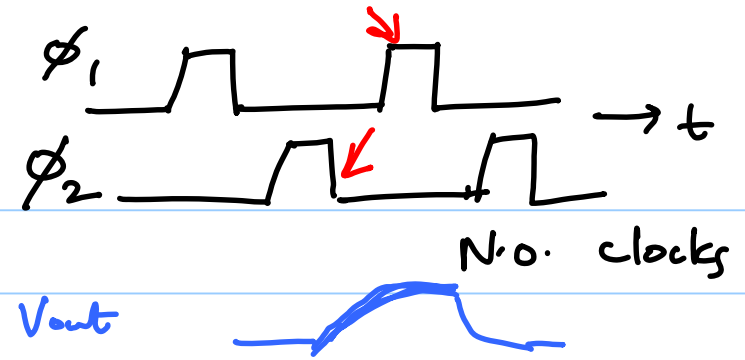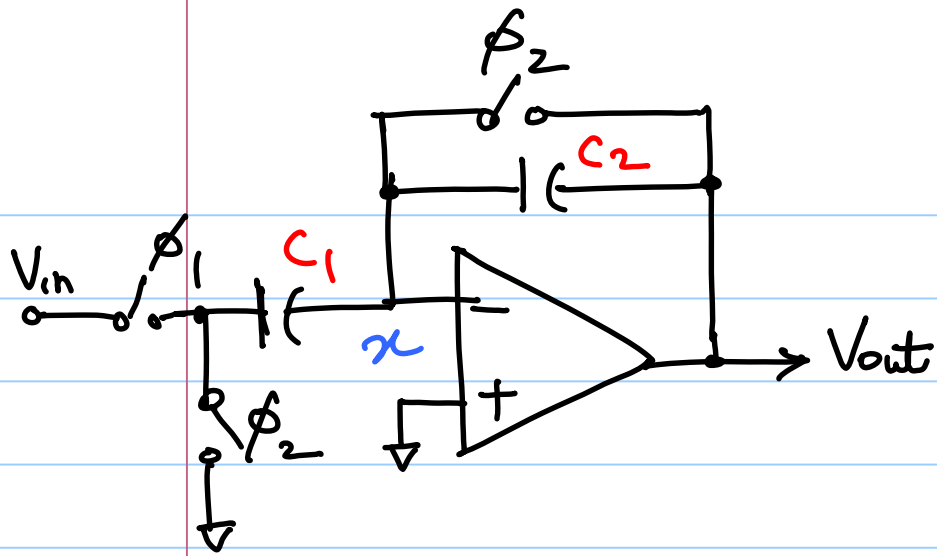

$V_n = 0$ due to the DC feedback



Input is sampled on C_1 & C_2
 * Since the charge on the virtual ground is preserved

$$Q = \underbrace{C_1(0) + C_2(0)}_0 = -C_1 V_{in} - C_2 V_{out} = 0$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = -\frac{C_1}{C_2} \quad \text{after settling occurs}$$


SC Integrator :

assume ideal switches

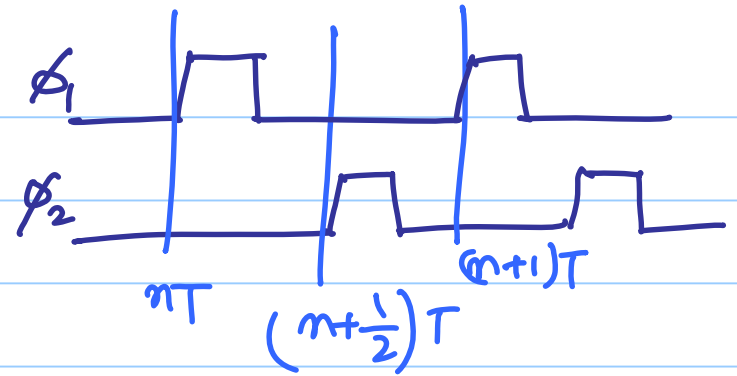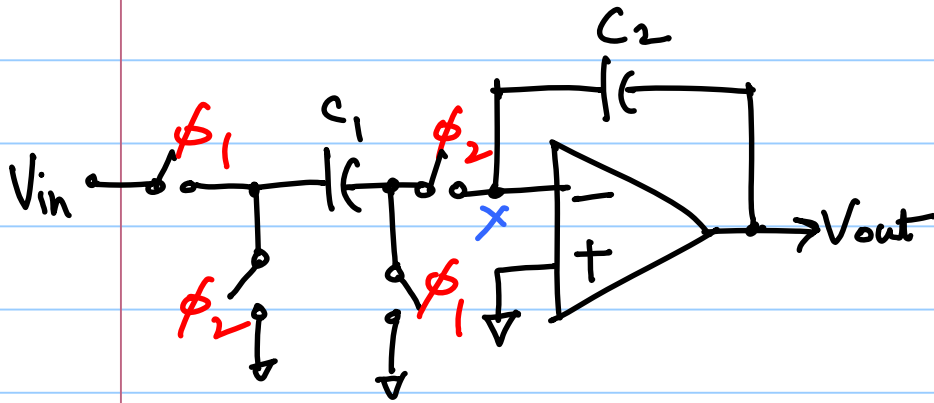


ϕ_1 : sampling phase

$$Q = -C_1 V_{in}[n]$$

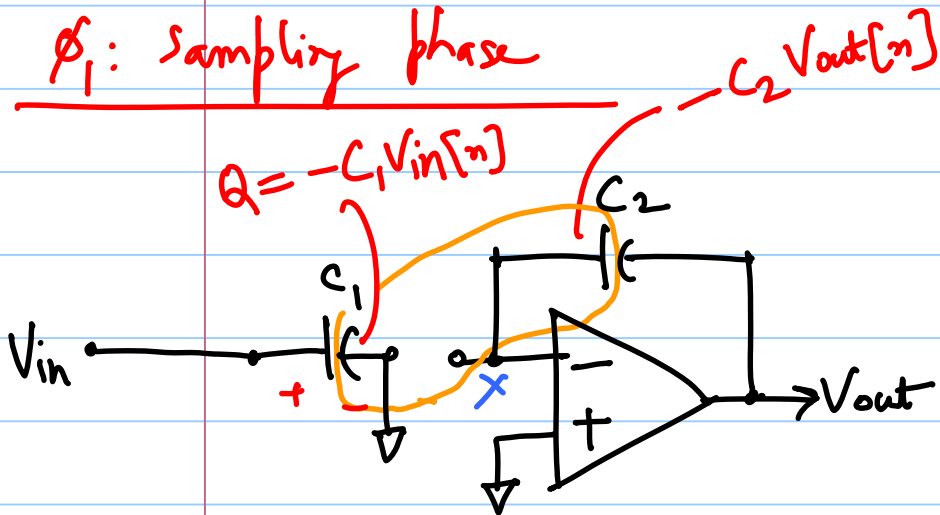

ϕ_2 : integration phase

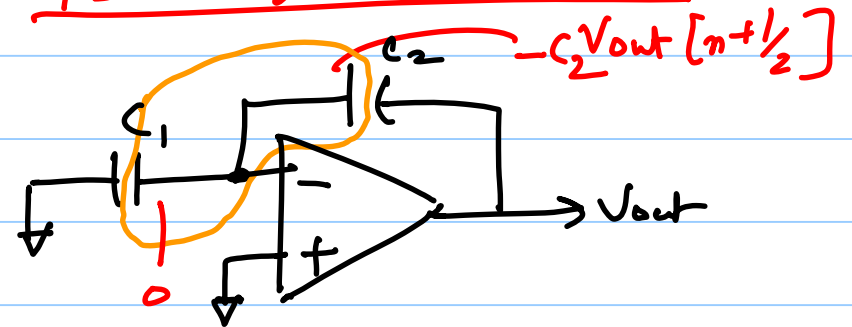

* charge stored in C_1 is transferred to C_2

Voltage across C_1 tracks V_{in}
 C_2 holds previous value

$$Q[n] = -V_{in}[n]C_1 + (0 - V_{out}[n])C_2$$

$$= -V_{in}[n]C_1 - V_{out}[n]C_2$$

$$Q[n+\frac{1}{2}] = 0 \cdot C_1 - V_{out}[n+\frac{1}{2}] \cdot C_2$$

* Since the charge at the plates connected to V_x is conserved

$$\Rightarrow Q[n+\frac{1}{2}] = Q[n]$$

$$\Rightarrow V_{out}[n+\frac{1}{2}]C_2 = V_{in}[n]C_1 + V_{out}[n]C_2$$



$V_{out}[n+1] \triangleq V_{out}[n+\frac{1}{2}] \leftarrow C_2$ is disconnected during ϕ_1

$$V_{out}[n] = V_{out}[n-1] + \frac{C_1}{C_2} V_{in}[n-1]$$


$$V_{out}(z) = z^{-1} V_{out}(z) + z^{-1} \frac{C_1}{C_2} V_{in}(z)$$

$$\frac{V_{out}}{V_{in}}(z) = \underbrace{\frac{C_1}{C_2}}_{\text{gain}} \cdot \frac{z^{-1}}{(1-z^{-1})}$$


Delaying Discrete-time integrator

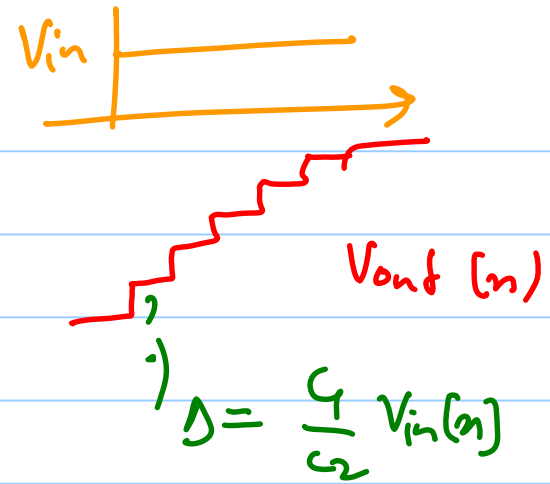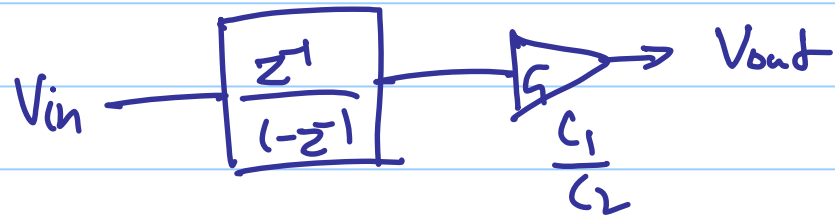


SC CMFB

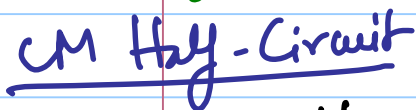


V_{CMFB}

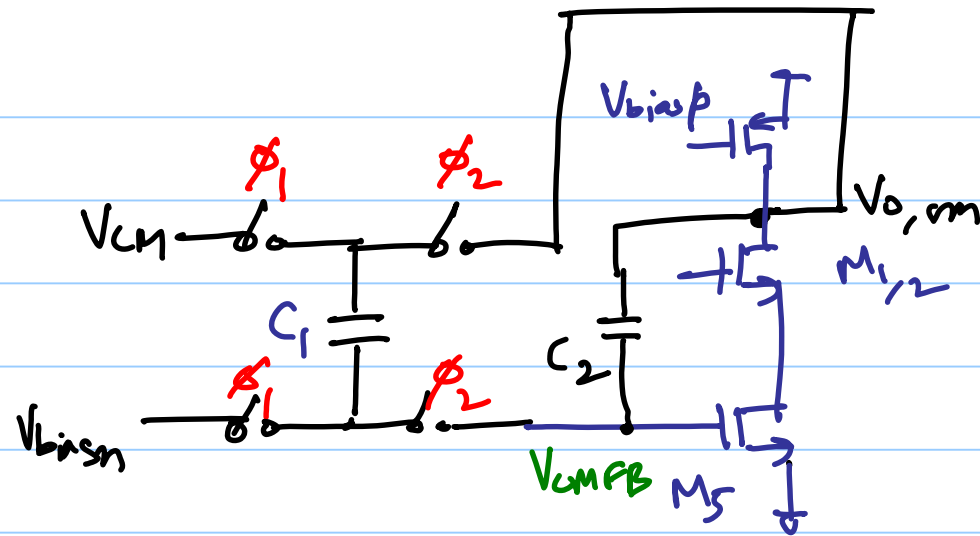


DT Integrator in a negative feedback

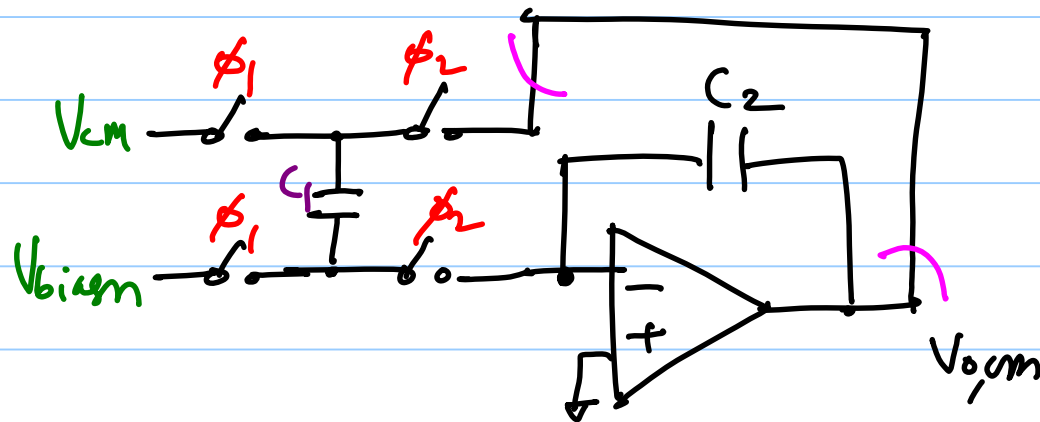

Assuming $|A_{cm}| \gg 1$

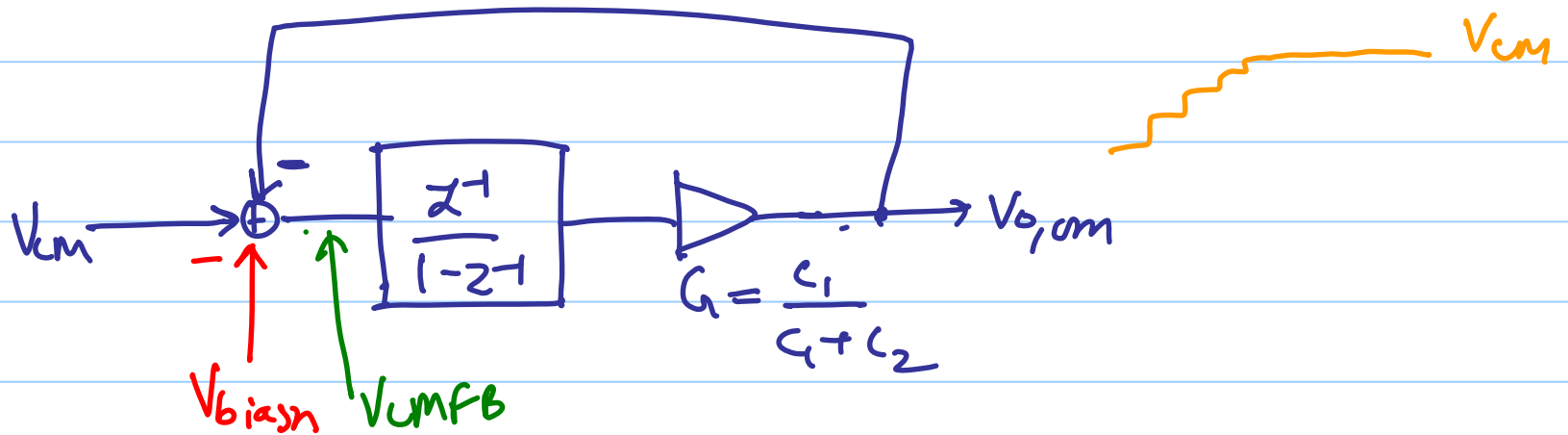


During ϕ_1

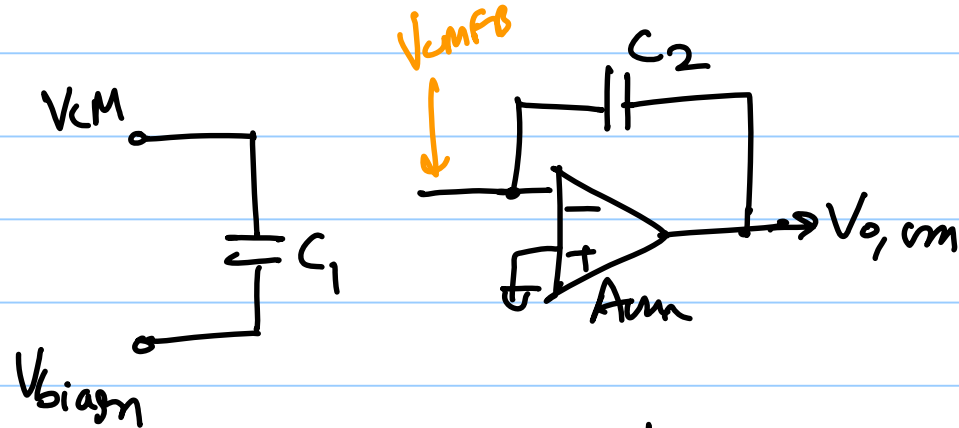

- * C_1 is charged to $V_{cm} - V_{biasn}$
- * $V_{O,cm}$ is undisturbed

During ϕ_2

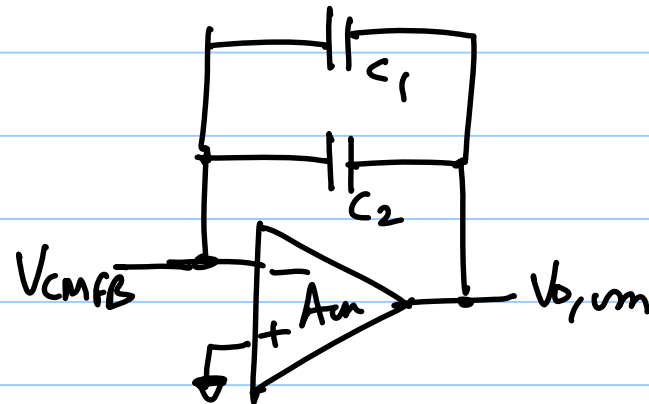

- * Charge sharing occurs b/w C_1 & C_2

In steady-state $V_{O,cm}$ becomes constant

$\Rightarrow C_1$ doesn't transfer any charge into C_2

$$\Rightarrow Q(\phi_1) \stackrel{D}{=} Q(\phi_2)$$

$$C_1 (V_{cm} - V_{biasn}) = C_1 (V_{o,cm} - V_{cmFB})$$

$\frac{V_{op} + V_{om}}{2}$



$$\Rightarrow V_{cm} - V_{o,cm} = \underbrace{V_{biasn} - V_{cmFB}}_{\text{systematic offset}}$$

If $V_{cmFB} \stackrel{D}{=} V_{biasn} \Rightarrow V_{o,cm} = V_{cm}$

If $V_{biasn} - V_{cmFB} = \Delta$

$$V_{o,cm} = V_{cm} - \Delta$$