
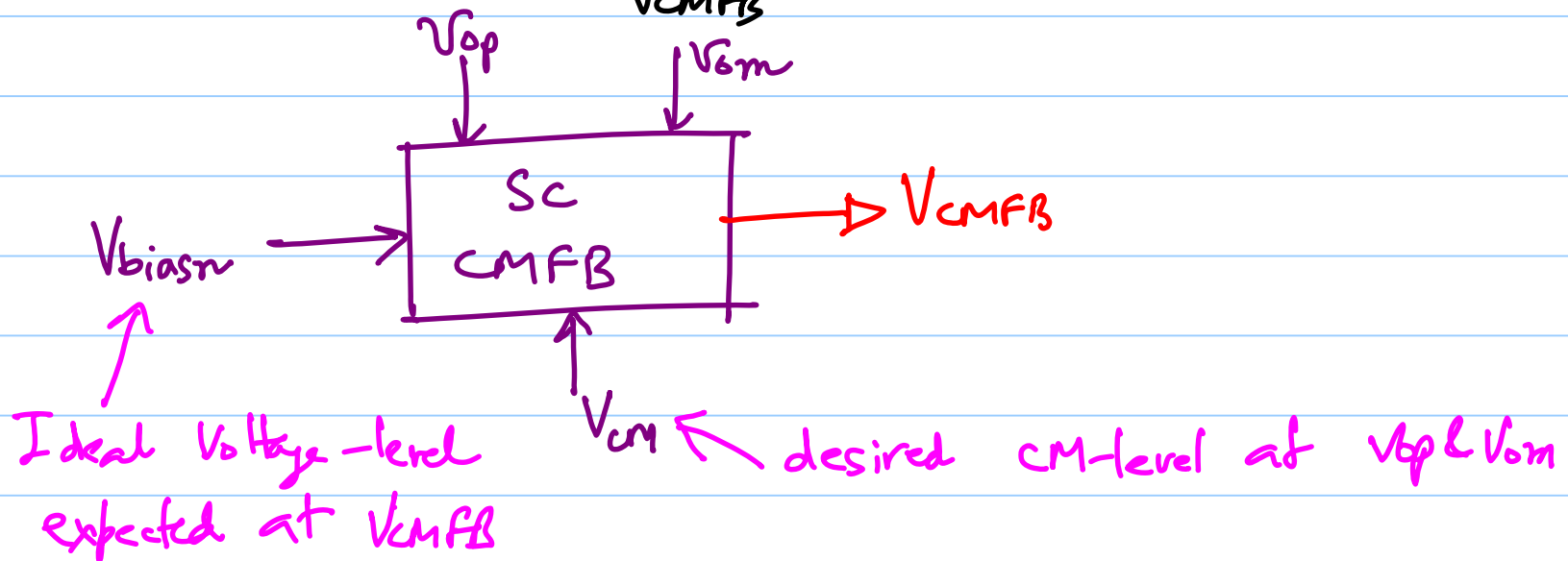



ECE 614 - Lecture 8

Note Title


9/18/2014

SC CMFB Circuit

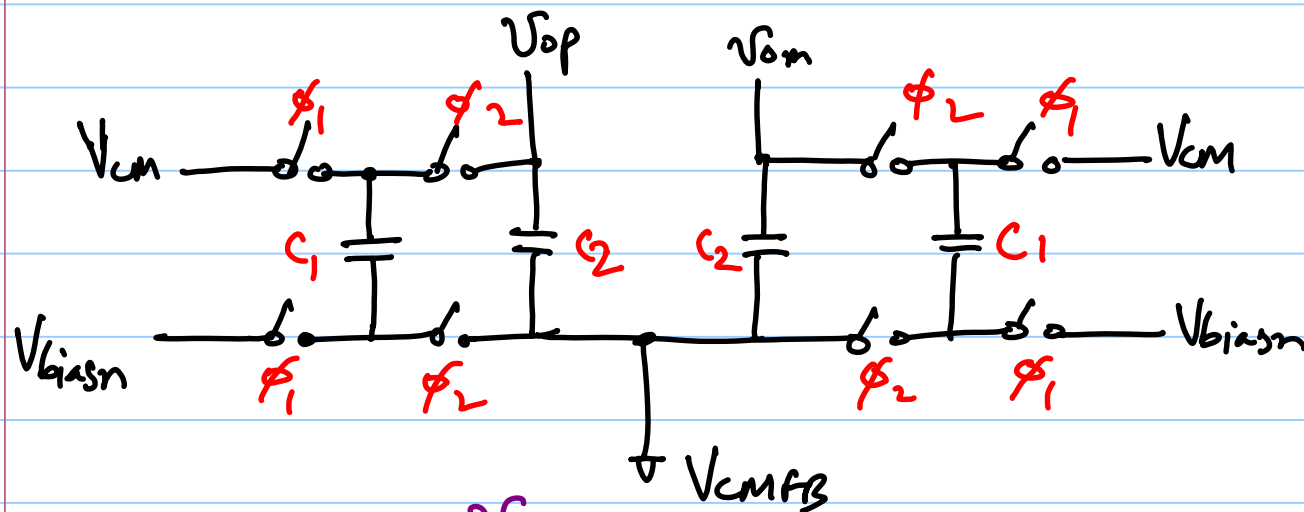


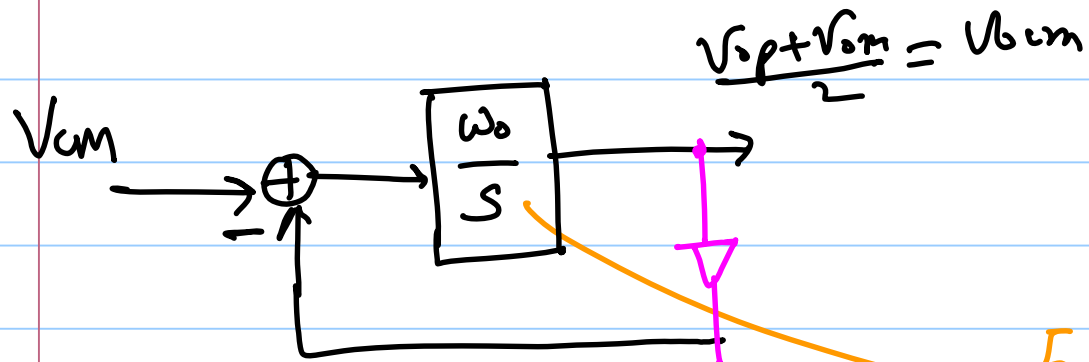


$$V_{opt} \rightarrow V_{cm}$$

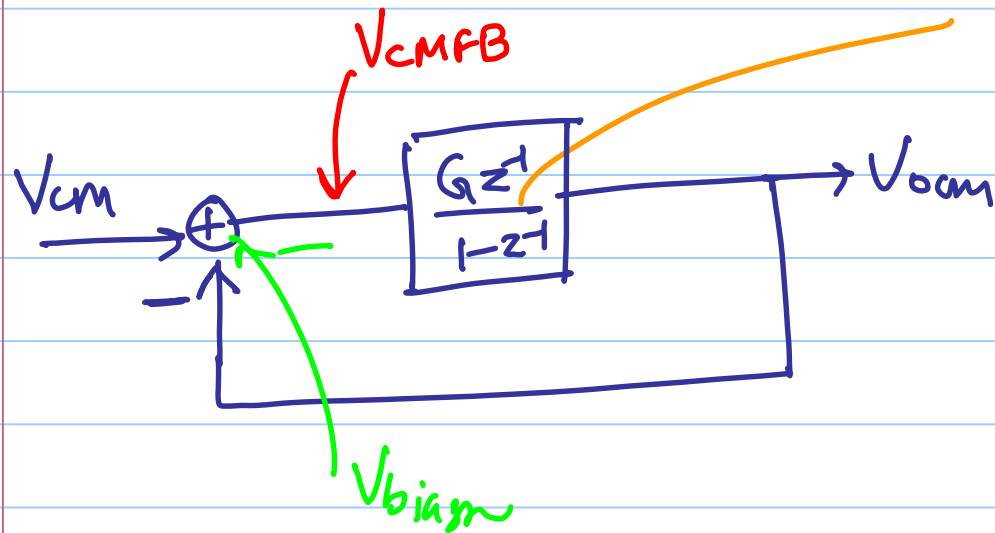

-ve feedback loop
that drives
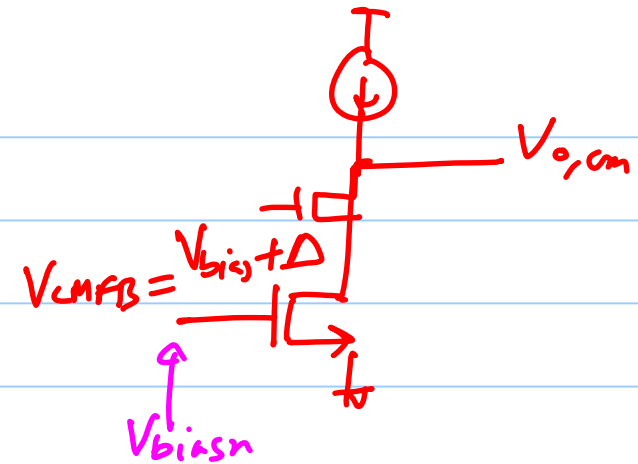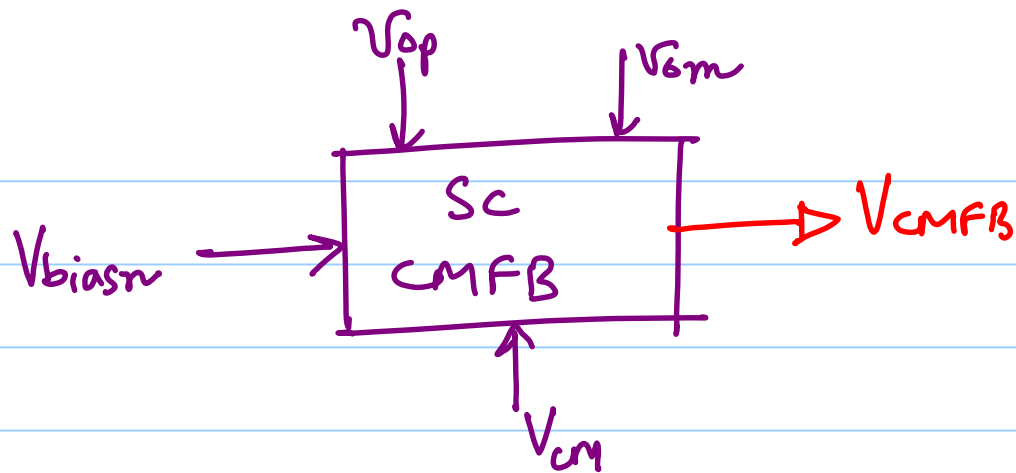
$$\frac{V_{opt} + V_{cm}}{2} \rightarrow V_{cm}$$




$$V_{error} = V_{cm} - V_{o,cm} = V_{biasn} - V_{cmFB} \Rightarrow 0$$

$\uparrow$
 $\left(\frac{V_{op} + V_{om}}{2} \right)$


$$V_{o,cm} = V_{cm} - \Delta$$

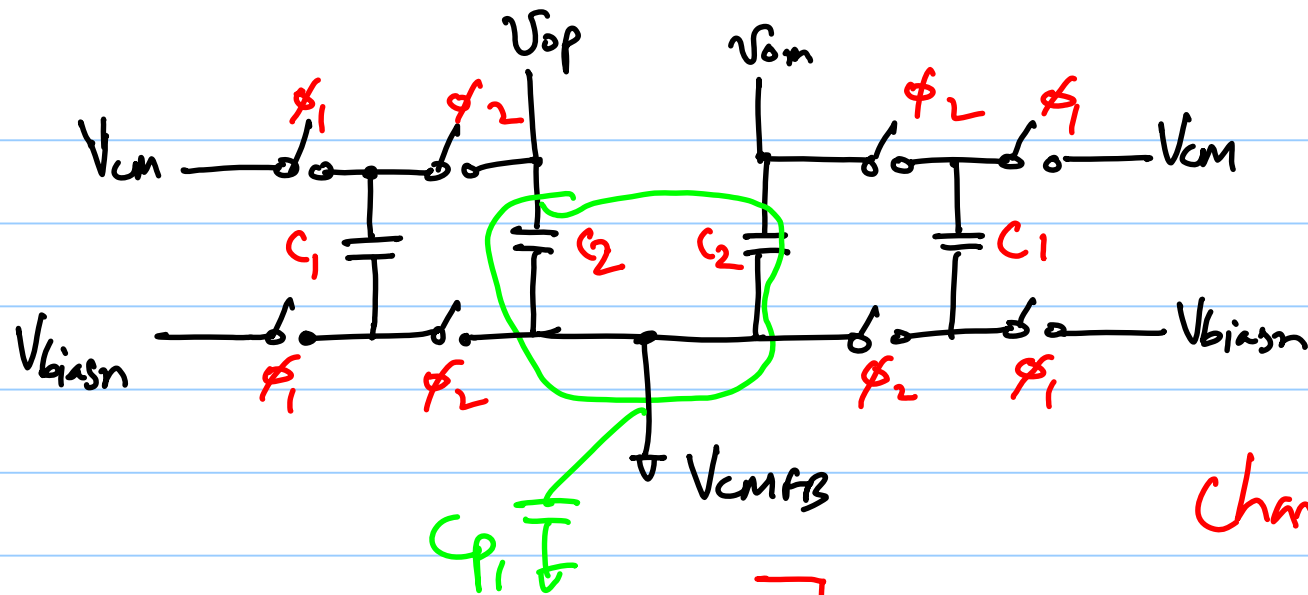Advantages: op swing is not limited by the CM-detector
& no resistive loading



Charge-injection

$$\Delta Q_I = WL C_{ox}'$$

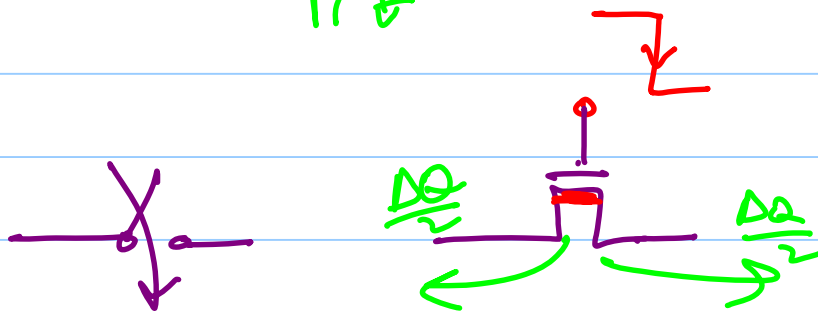

→ switches ϕ_1 inject charge into $C_1 \Rightarrow \Delta Q$

In steady-state

$$C_1 (V_{cm} - V_{biasn}) = C_1 (V_{o,cm} - V_{cmfb}) + \Delta Q$$

$$V_{cm} - V_{o,cm} = V_{biasn} - V_{cmFR3} + \frac{\Delta Q}{C_1}$$

induces an offset into $V_{o,cm}$

$V_{o,cm}$ is away from V_{cm} by $\frac{\Delta Q}{C_1}$

① $\because \Delta Q \propto W$, small WL $\Rightarrow$ switch resistance
 $\hookrightarrow R_C$ time constant

② $C_1 \uparrow$
 $\hookrightarrow$ reduce the offset due to C.I.


$\Rightarrow$ more loading on the outputs during ϕ_2 phase

Single-stage opamp

$$f_m = \frac{g_{m1}}{C_2}$$

Analysis:

$\frac{C_1}{C_2} \uparrow$

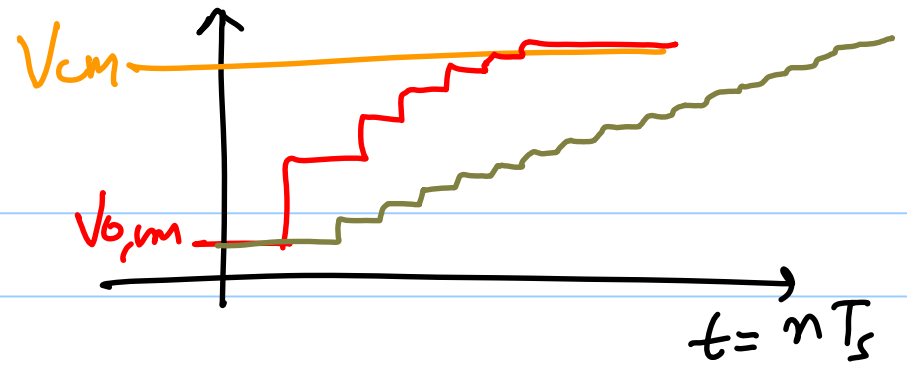

final value of $\frac{V_{O1} + V_{O2}}{2}$

$$V_{O,CM} = \frac{V_{CM} + \left[\left(1 + \frac{C_1}{C_2} \right) (V_{CM} - V_{biasn}) \right] - \frac{\Delta Q}{C_1} + \frac{I_{leak} \cdot T}{2C_1}}{1 + \frac{1}{A_{cm}} \cdot \left(1 + \frac{C_1}{C_2} \right)}$$

Step-size of settling depends on $\frac{C_1}{C_2}$

for $\frac{C_1}{C_2} \gg 1 \Rightarrow$ settling is fast

Excess loading on the amplifier

$$\phi_2 \Rightarrow C_1 + C_2 + C_{load}$$

$$\phi_1 \Rightarrow C_2 + C_{load}$$

Algorithm: choose C_2 such that

$$\omega_{u,CMFB} \supseteq \omega_{u,DM}$$





and choose $C_1 \Rightarrow$ 5 to 10 times of C_2
for faster settling

Example

$$C_2 \leq 10 \text{ fF}$$

$$C_1 = 50 \text{ fF}$$

Replica bias

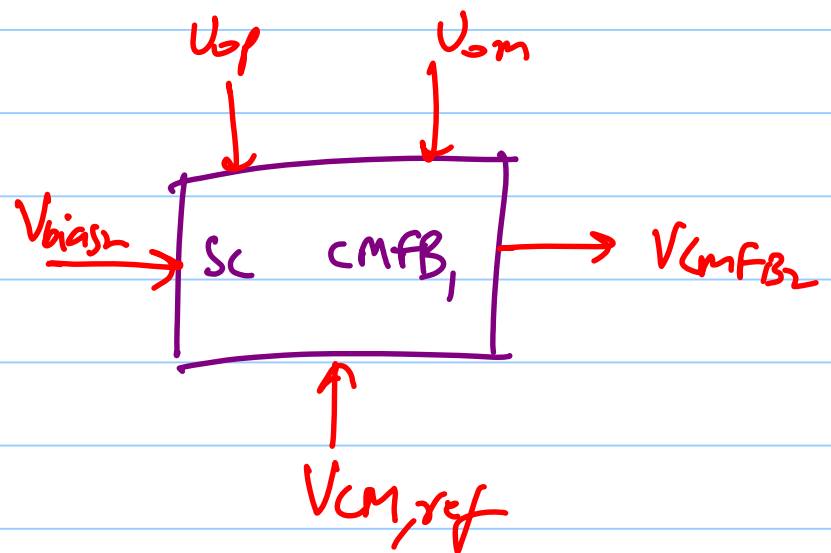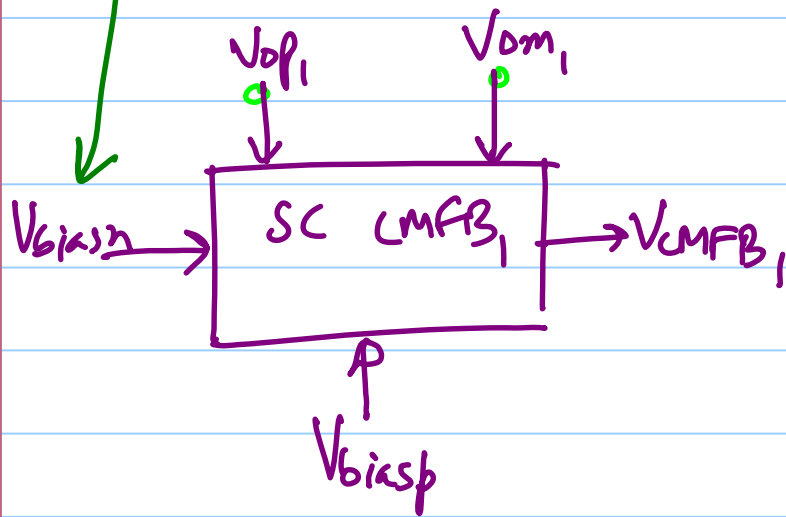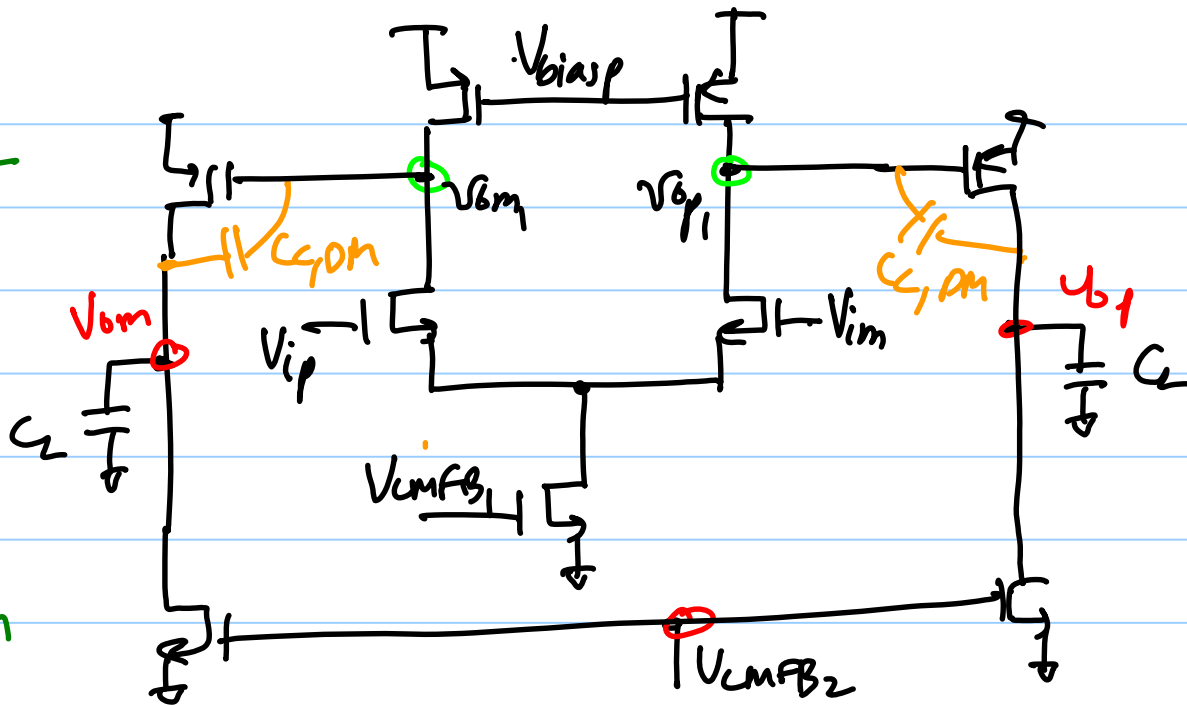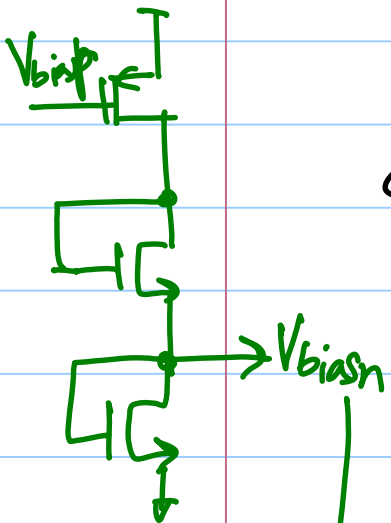

* A periodically switched system

Spec & RF

CT equivalent

periodic steady state $\Rightarrow$ PSS $\leftrightarrow$ operating point

periodic stability $\Rightarrow$ PSTB $\leftrightarrow$ STB



" AC response $\Rightarrow$ PAR $\leftrightarrow$ $X(e^{j\omega})$

" Transient "

$\rightarrow$ TSH parameter

Noise

Noise: Random process

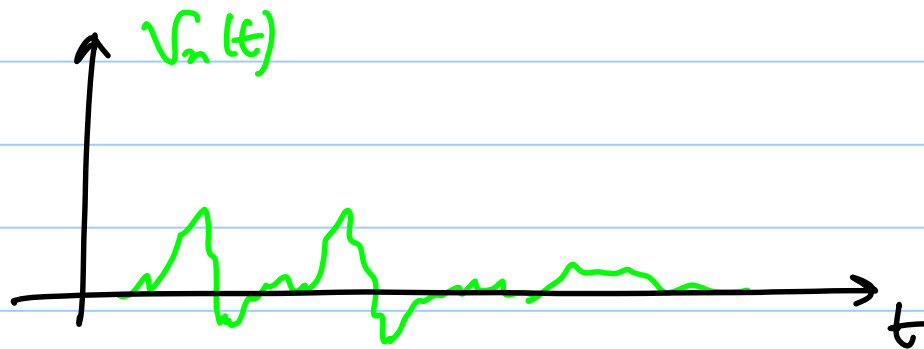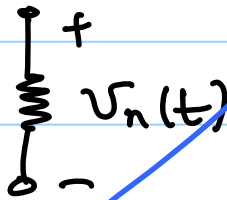



→ amplitude has a random distribution at any instance of time

→ need to look at it statistically

x Which properties of noise can be predicted?

⇒ In many cases, average power of noise is predictable

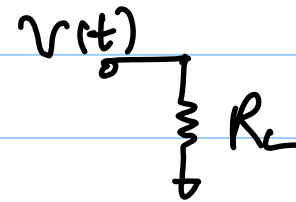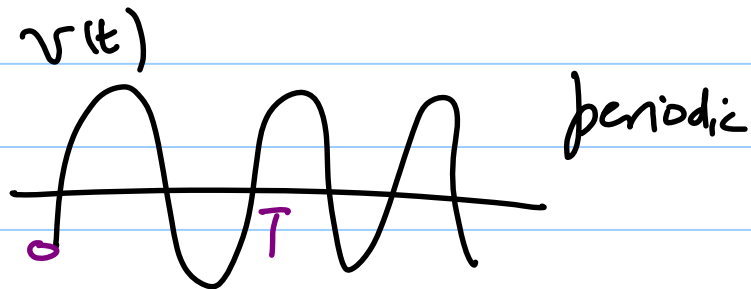↳ most noises in circuits fundamentally exhibit constant average power.



The average power delivered by a periodic voltage source $v(t)$ to a load R_L

$$P_{av} = \frac{1}{T} \int_{-T/2}^{T/2} \frac{v^2(t)}{R_L} dt = \frac{V_p^2}{2R_L} \text{ for sine}$$
$$\frac{V_{DC}^2}{R_L} \text{ for DC}$$

for a random signal $x(t)$

$$P_{av} = \lim_{T \rightarrow \infty} \frac{1}{T} \int_{-T/2}^{T/2} \frac{x^2(t)}{R_L} dt$$

