

**ECE1371 Advanced Analog Circuits
Lecture 7**

SWITCHED CAPACITOR CIRCUITS

Richard Schreier
richard.schreier@analog.com

Trevor Caldwell
trevor.caldwell@utoronto.ca

Course Goals

- **Deepen Understanding of CMOS analog circuit design through a top-down study of a modern analog system**
The lectures will focus on Delta-Sigma ADCs, but you may do your project on another analog system.
- **Develop circuit insight through brief peeks at some nifty little circuits**
The circuit world is filled with many little gems that every competent designer ought to recognize.


Date	Lecture		Ref	Homework
2008-01-07	RS	1	Introduction: MOD1 & MOD2	S&T 2-3, A Matlab MOD2
2008-01-14	RS	2	Example Design: Part 1	S&T 9.1, J&M 10 Switch-level sim
2008-01-21	RS	3	Example Design: Part 2	J&M 14, S&T B Q-level sim
2008-01-28	TC	4	Pipeline and SAR ADCs	J&M 11,13 Pipeline DNL
2008-02-04	ISSCC – No Lecture			
2008-02-11	RS	5	Advanced $\Delta\Sigma$	S&T 4, 6.6, 9.4, B CTMOD2; Proj.
2008-02-18	Reading Week – No Lecture			
2008-02-25	RS	6	Comparator and Flash ADC	J&M 7
2008-03-03	TC	7	SC Circuits	Raz 12, J&M 10
2008-03-10	TC	8	Amplifier Design	
2008-03-17	TC	9	Amplifier Design	
2008-03-24	TC	10	Noise in SC Circuits	S&T C
2008-03-31	Project Presentations			
2008-04-07	TC	11	Matching & MM-Shaping	
2008-04-14	RS	12	Switching Regulator	Project Report

ECE1371

7-3

NLCOTD: Schmitt Trigger

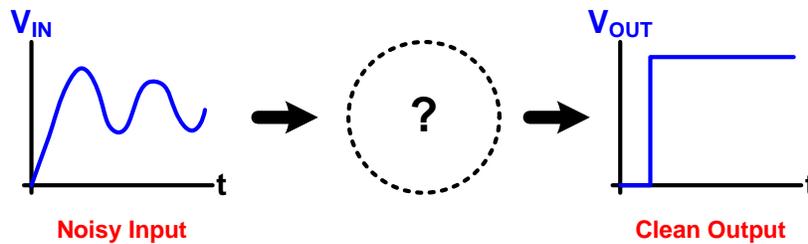Problem: Input is noisy or slowly varying



How do we turn this into a clean digital output?

ECE1371

7-4

Highlights

(i.e. What you will learn today)

1. **Motivation for SC Circuits**
2. **Basic sampling switch and charge injection errors**
3. **Fundamental SC Circuits**
Sample & Hold, Gain and Integrator
4. **Other Circuits**
Bootstrapping, SC CMFB

ECE1371

7-5

Why Switched Capacitor?

- **Used in discrete-time or sampled-data circuits**
Alternative to continuous-time circuits
- **Capacitors instead of resistors**
Capacitors won't reduce the gain of high output impedance OTAs
No need for low output impedance buffer to drive resistors
- **Accurate frequency response**
Filter coefficients determined by capacitor ratios (rather than RC time constants) and clock frequencies
Capacitor matching on the order of 0.1% - when the transfer characteristics are a function of only a capacitor ratio, it can be very accurate
RC time constants vary by up to 20%

ECE1371

7-6

Basic Building Blocks


- **Opamps**
Ideal usually assumed
Some important non-idealities to consider include:
 1. **DC Gain:** sets the accuracy of the charge transfer, how 'grounded' the virtual ground is
 2. **Unity-gain freq, Phase Margin & Slew Rate:** determines maximum clock frequency
 3. **DC Offsets:** circuit techniques to combat this and 1/f noise – Correlated Double Sampling, Chopping
- **Capacitors**
Large absolute variation, good matching
Large bottom plate capacitor adds parasitic cap

ECE1371

7-7

Basic Building Blocks

- **Switches**
MOSFET switches are good – large off resistance ($G\Omega$), small on resistance (100Ω - $5k\Omega$, depending on transistor sizing)
MOSFET switches have non-linear parasitic capacitors
- **Non-Overlapping Clocks**
Clocks are never on at the same time
Required so that charge is never lost/shared
Clock Generator previously discussed

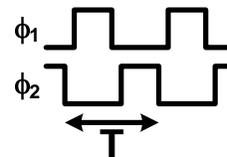

ECE1371


7-8

Basic Sampling Switch


- MOSFET used as sample-and-hold

When CLK is HIGH, V_{OUT} follows V_{IN} through the low-pass filter created by R_{ON} and C

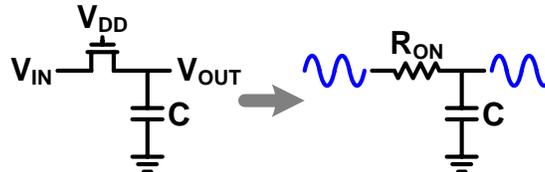R_{ON} varies depending on V_{IN} , V_{OUT} , and V_{DD}



When CLK is LOW, V_{OUT} holds the value on C

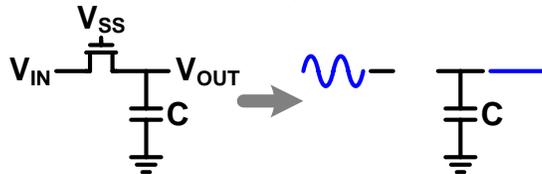


ECE1371

7-9

On-Resistance Variation

- With an NMOS sampling switch, as V_{IN} approaches $V_{DD} - V_{TH}$, R_{ON} increases dramatically
In smaller technologies, as V_{DD} decreases the swing on V_{IN} is severely limited
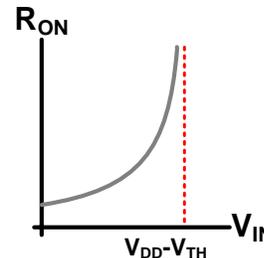
$$R_{ON} = \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{DD} - V_{IN} - V_{TH})}$$



Sampling switch must be sized for worst case R_{ON} so that the bandwidth is still sufficient

ECE1371


7-10

On-Resistance Variation

- PMOS switches suffer from the same problem as V_{IN} approaches V_T
- Complementary switch can allow rail-to-rail input swings

Ignoring variation of V_{TH} with V_{IN} , $R_{ON,eq}$ is constant with V_{IN} if

$$\mu_n C_{ox} \frac{W}{L} = \mu_p C_{ox} \frac{W}{L}$$

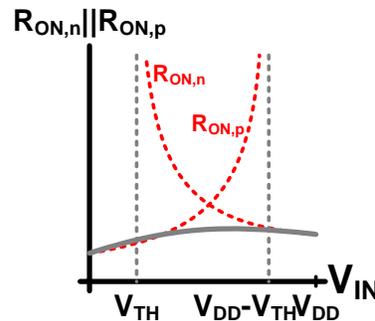

ECE1371

7-11

Settling Accuracy

- Two situations to consider
 - 1) Discrete-time signal
 - When analyzing a signal within the switched-capacitor circuit (for example, at the output of the first OTA)
 - 2) Continuous-time signal
 - When analyzing a signal that is sampled at the input

ECE1371

7-12

Settling Accuracy – DT


- Discrete-Time Signal

Settling Error = $e^{-T/4RC}$

For N-bit accuracy in T/4 seconds

$$R_{ON} C < \frac{T}{4N \ln 2}$$

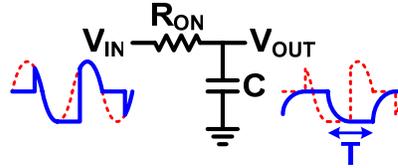This is the maximum R_{ON} (for a given C)



- Example:

Assume 1 GHz to 4 GHz variation of $\frac{1}{2\pi R_{ON} C}$
 Input sinusoidal signal at 50 MHz

For $f_s=100\text{MHz}$, $N=22$ bits with discrete-time signal
 (typically you are limited by the OTA)

Settling Accuracy – CT

- Continuous-Time Signal


$R_{ON} C$ acts as a low-pass filter and introduces amplitude and phase change

Variations in the input signal size cause variations in R_{ON} , causing distortion in the sampled signal

Both the amplitude and phase vary – which one causes distortion?

Amplitude Error

- **Less significant error**
Due to variation in magnitude of low-pass filter
At 50 MHz (with same $R_{ON}C$ variation as DT case),
maximum possible error is 0.1%

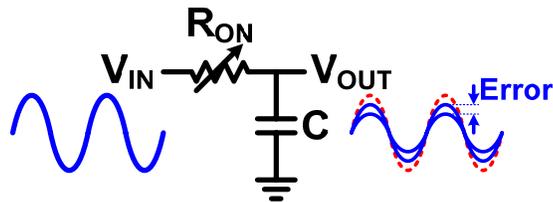


ECE1371

7-15

Distortion in sampled CT input

- **Input ~50 MHz, sampled at 100MHz**
Distortion at 57dB, or ~9 bits
This is larger than the maximum possible error due to
amplitude variation

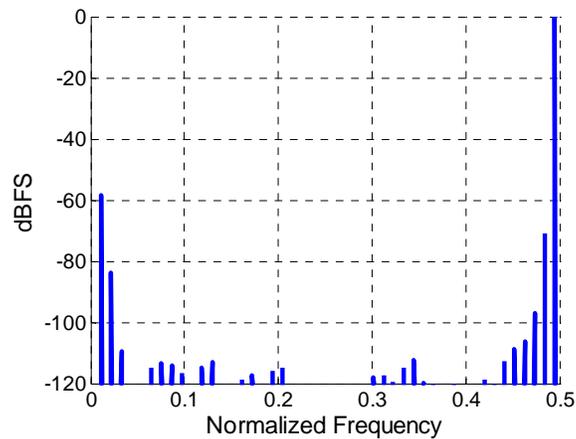


ECE1371

7-16

Phase Error

- **More significant error**
 Due to variation in phase of low-pass filter
 At 50 MHz (with same $R_{ON}C$ variation as DT case),
 maximum possible error is a few percent - error is
 less than that

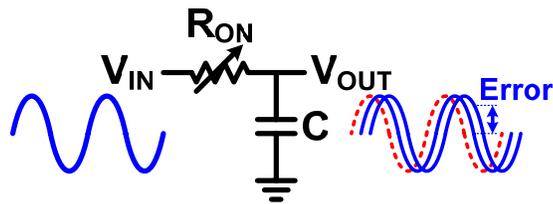


ECE1371

7-17

Charge Injection

- **When a transistor turns off, the channel charge Q_{CH} goes into the circuit**
 Doesn't exactly divide in half - depends on impedance
 seen at each terminal and the clock transition time
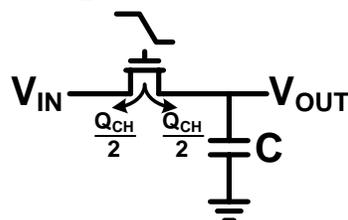
$$Q_{CH} = WLC_{ox}(V_{DD} - V_{IN} - V_{TH})$$
- **Charge into V_{IN} has no impact on output node**
 Doesn't create error in the circuit
- **Charge into C causes error ΔV in V_{OUT}**



$$\begin{aligned} \Delta V &= \frac{Q_{CH}}{2C} \\ &= \frac{WLC_{ox}(V_{DD} - V_{IN} - V_{TH})}{2C} \end{aligned}$$

ECE1371

7-18

Charge Injection

- In previous analysis, charge injection introduces a gain and offset error

This is still linear and could be tolerated or corrected

$$V_{OUT} = V_{IN} - \Delta V$$

$$= V_{IN} \left(1 + \frac{WLC_{ox}}{2C} \right) - \frac{WLC_{ox}(V_{DD} - V_{TH})}{2C}$$

- But...

V_{TH} is actually a function of $\sim \sqrt{V_{IN}}$

Introduces non-linear term that cannot be corrected in the circuit

Charge Injection vs. Speed

- Charge injection
Proportional to transistor size (WL)
- Speed
 R_{ON} inversely proportional to aspect ratio (W/L)
- Figure of Merit
Product of speed (1/ τ) and charge injection (1/ ΔV)

$$(\tau \Delta V)^{-1} = \left(\frac{C}{\mu_n C_{ox} (W/L) (V_{DD} - V_{IN} - V_{TH})} \right)^{-1} \left(\frac{WLC_{ox} (V_{DD} - V_{IN} - V_{TH})}{C} \right)^{-1}$$


$$= \frac{\mu_n}{L^2}$$

Clock Feedthrough

- **Overlap capacitance allows clock to couple from the gate to drain/source terminals**

Change in voltage ΔV independent of the input signal

Error is an offset voltage which is cancelled with differential operation

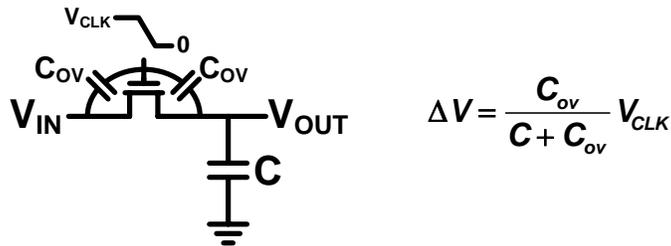

ECE1371

7-21

Charge Error Cancellation

- **Differential operation**
Cancels offset errors, depending on the matching between differential circuits

Applies to signal dependent portion of charge injection error, and clock feedthrough error

- **Complementary Switches**

Error cancelled for 1 input level

$$W_n L_n C_{ox} (V_{CLK} - V_{IN} - V_{THN}) = W_p L_p C_{ox} (V_{IN} - |V_{THP}|)$$

Clock feedthrough cancelled depending on similarity of overlap capacitance for PMOS and NMOS switches

ECE1371

7-22

Charge Error Cancellation

- **Dummy Switch**


Use second transistor to remove charge injection by main transistor

Inverted clock operates on dummy switch

Charge from M1: $q_{M1} = W_1 L_1 C_{ox} (V_{CLK} - V_{IN} - V_{TH1}) / 2$

Charge from M2: $q_{M2} = W_2 L_2 C_{ox} (V_{CLK} - V_{IN} - V_{TH2})$

If charge splits equally in M1 (not quite true), then with M2 half the size of M1, $q_{M1} = q_{M2}$

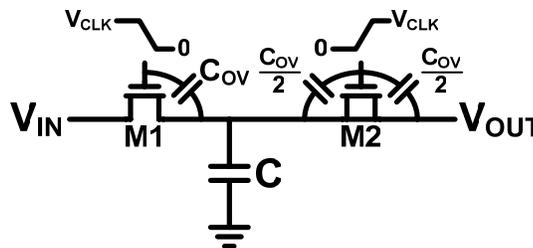

ECE1371


7-23

Sample and Hold Amplifier

- **Input dependent charge from S_1 onto C**

When S_1 turns off, charge q adds to C

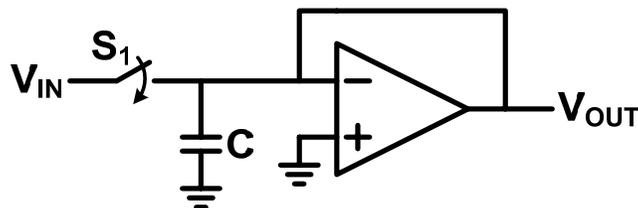V_{OUT} is then equal to $V_{IN} + q/C$ where q has a non-linear dependence on V_{IN}




We can improve on this by making V_{OUT} independent of sampling switch charge...

ECE1371

7-24

S/H Amplifier

- **Two phases**
 - Phase 1: S_1 and S_2 closed, V_{IN} sampled on C
 - Phase 2: S_3 closed, C is tied to V_{OUT}
- **Phase 1**
 - Charge on C is CV_{IN}
 - S_2 opens, injecting signal indep. charge at node X
 - Then S_1 opens, injecting signal dependent charge q onto $C + C_p$

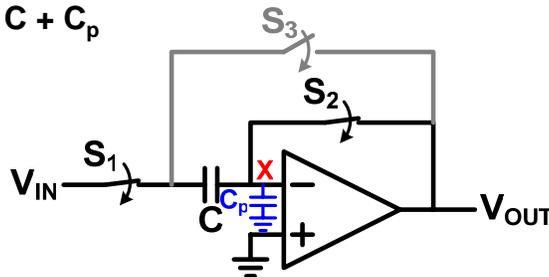


ECE1371

7-25

S/H Amplifier

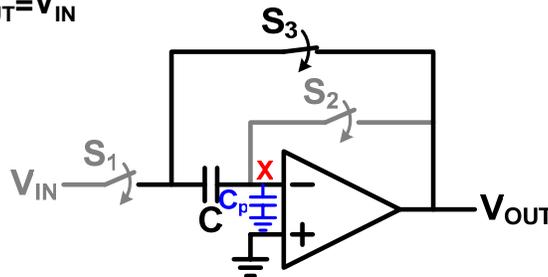- **Phase 2**
 - Node X is a virtual ground and charge on C_p is zero
 - Charge on C is still CV_{IN}
 - S_3 injects charge on X that must be discharged due to virtual ground node – it does not disturb charge on C
 - $\therefore V_{OUT} = V_{IN}$



S_1 / S_3 are non-overlapping, S_2 slightly ahead of S_1

ECE1371


7-26

Gain of the S/H

- Finite OTA gain reduces gain of sampler
 - On Phase 1, C charges to V_{IN}
 - On Phase 2, node X goes from 0 to $V_X = -V_{OUT}/A$
 - Charge comes from C, changing q_C to $CV_{IN} + C_p V_X$
 - $V_{OUT} - (CV_{IN} + C_p V_X)/C = V_X$

$$V_{OUT} = \frac{V_{IN}}{1 + \frac{1}{A} \left(\frac{C_p}{C} + 1 \right)}$$

$$\approx V_{IN} \left[1 - \frac{1}{A} \left(\frac{C_p}{C} + 1 \right) \right]$$

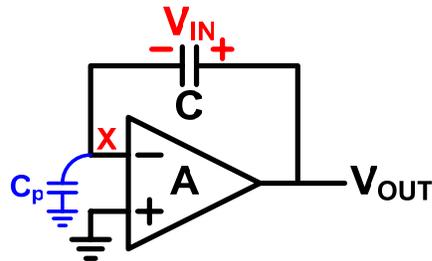


ECE1371

7-27

Speed of the S/H

- In sampling mode (Phase 1)
 - At node X, $R_X \sim 1/G_m$, $\tau_1 \sim (R_{on1} + 1/G_m)C$
- In amplification mode (Phase 2)
 - Replace charge on C by voltage source V_{IN} (like switching in voltage source at start of Phase 2)
 - After analysis, $\tau_2 = (C_L C_p + C_p C + C C_L)/G_M C$
 - Reduces to $\tau_2 \sim C_L/G_M$ if C_p is small

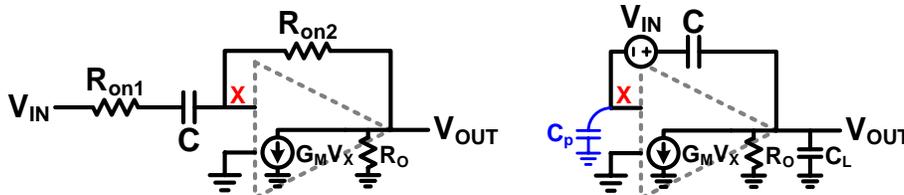


ECE1371

7-28

Basic Amplifier

- **Sampling phase when S_1 and S_2 closed**
Input signal sampled onto C_1
- **Amplifying phase when S_3 closed**
Charge on C_1 transferred to C_2 so that the final output is $V_{OUT} = \frac{C_1}{C_2} V_{IN}$

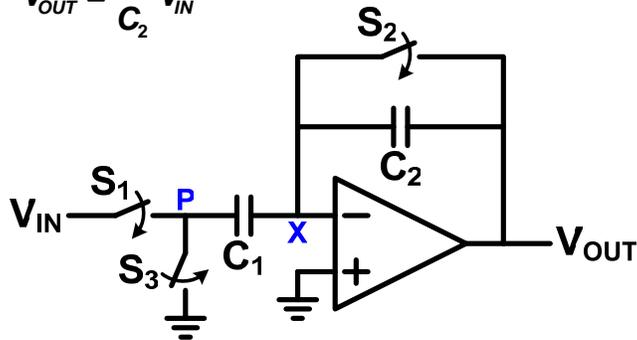


ECE1371

7-29

Basic Amplifier

- **S_2 must open before S_1 for the charge injection to be signal independent**
Charge from S_2 opening is deposited on C_1 , but is not signal dependent
Charge from S_1 opening causes glitch in V_{OUT}
When S_3 closes, V_{OUT} goes to final value, regardless of what happened between S_2 opening and S_3 closing

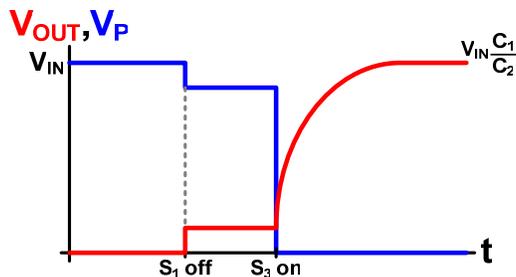


ECE1371

7-30

Precision Gain-2

- Sampling phase when S_1, S_2, S_3 closed
Input signal sampled onto C_1 and C_2
- Amplifying phase when S_4, S_5 closed
Charge on C_1 is transferred to C_2 , doubling the charge on C_2
Final output is $2V_{IN}$ since $C_1 = C_2$

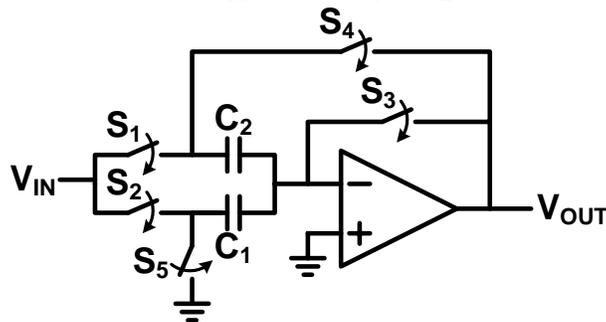

ECE1371

7-31

Precision Gain-2

- How is it more precise?
The feedback factor in both gain circuits is

$$\frac{C_2}{C_2 + C_1 + C_p}$$

In the precision Gain-2 circuit, $C_1 = C_2$, while the basic amplifier has $C_1 = 2C_2$, resulting in a smaller feedback factor and a slower circuit


The gain error is inversely proportional to the feedback factor, so the precision circuit is more accurate for a given amplifier gain A

$$\frac{V_{OUT}}{V_{IN}} \approx 2 \left(1 - \frac{C_2 + C_1 + C_p}{AC_2} \right)$$

ECE1371

7-32

Resistor Equivalence of SC

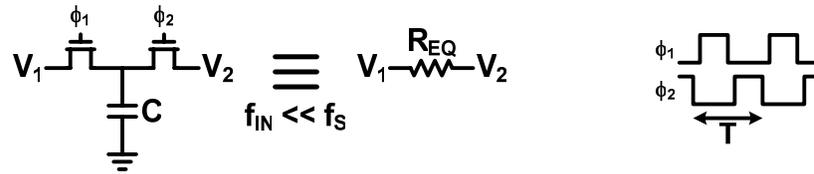

- Average current through switched-capacitor

$$\phi_1 : Q_1 = CV_1 \quad \phi_2 : Q_2 = CV_2$$

$$I_{AVG} = \frac{Q_1 - Q_2}{T} = \frac{C(V_1 - V_2)}{T}$$

- Equivalent current through a resistor ($f_{IN} \ll f_S$)


$$I_{EQ} = \frac{V_1 - V_2}{R_{EQ}}$$

$$R_{EQ} = \frac{T}{C} = \frac{1}{Cf_S}$$

ECE1371

7-33

Switched-Capacitor Integrator

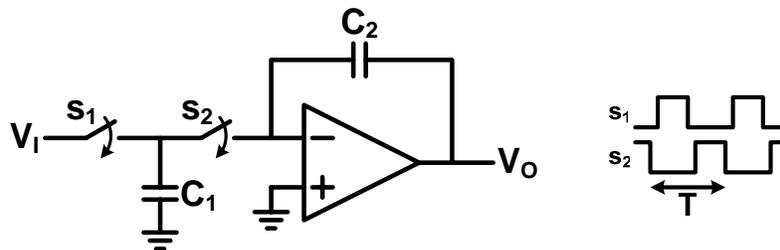

- Two non-overlapping clock phases control s_1, s_2


Phase 1: Sampling phase – input is sampled onto capacitor C_1

Phase 2: Integrating phase – additional charge is added to previous charge on C_2

ECE1371

7-34

Switched-Capacitor Integrator

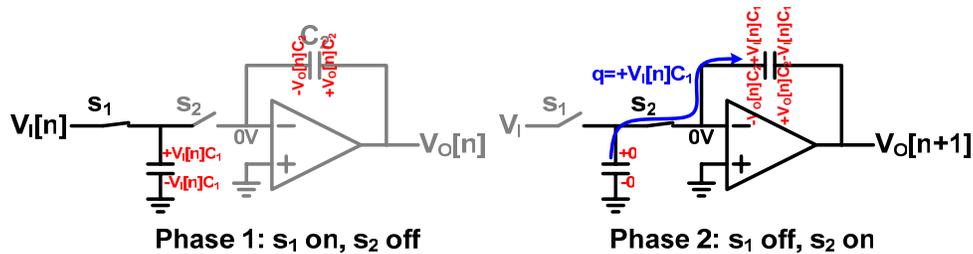

- Final charge on L.S. of C_2 is $+V_O[n+1]C_2$

$$+V_O[n+1]C_2 = +V_O[n]C_2 - V_I[n]C_1$$


$$zV_O(z)C_2 = V_O(z)C_2 - V_I(z)C_1$$

$$\frac{V_O(z)}{V_I(z)} = -\frac{C_1}{C_2} \frac{1}{z-1}$$

ECE1371

7-35

Parasitic Sensitive

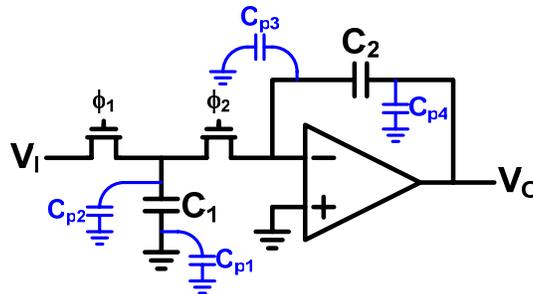


- Parasitic capacitances C_{p1} , C_{p3} and C_{p4} have no impact on transfer function
- C_{p2} in parallel with C_1 , changes transfer function

$$\frac{V_O(z)}{V_I(z)} = -\frac{(C_1 + C_{p2})}{C_2} \frac{1}{z-1}$$

ECE1371

7-36

Parasitic Insensitive

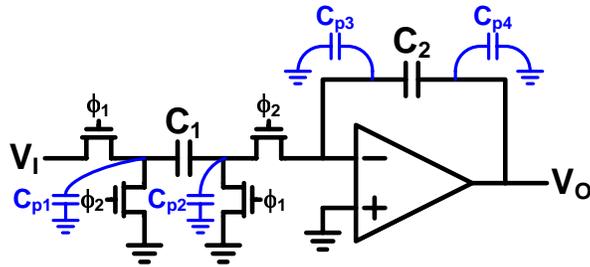

- Transfer function is non-inverting, delaying

$$\frac{V_O}{V_I}(z) = \frac{C_1}{C_2} \frac{1}{z-1}$$

ECE1371

7-37


Parasitic Insensitive

- Parasitics have no impact on transfer function
Better linearity since non-linear capacitors are unimportant
- Top plate on virtual ground node
Minimizes parasitics, improves amplifier speed and resolution, reduces noise coupled to node
- Two extra switches needed
More power to drive the switches for the same on-resistance

ECE1371

7-38

Delay-Free Integrator

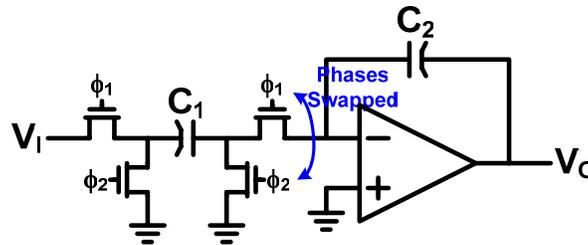

- Same structure, still parasitic insensitive
- Transfer function is inverting, delay-free

$$\frac{V_o}{V_i}(z) = -\frac{C_1}{C_2} \frac{z}{z-1}$$

Bootstrapping

- At low supply voltages, signal swing is limited
Maximum distortion determines the tolerable variation in R_{ON} , and this limits the signal swing
- Want to increase V_{GS} on the sampling switch
Can do this by increasing the supply voltage for the sampling switch, but this requires slower thick oxide devices
Alternatively, add a constant voltage to the input signal and use that as the gate voltage – keep V_{GS} constant, reducing the variation in R_{ON}


Bootstrapped Circuit

- **Basic operation**

ϕ_2 : C is charged to V_{DD} and gate of sampling switch is discharged to V_{SS} (turned off)

ϕ_1 : V_{IN} is added to voltage across C, sampling switch turns on, gate voltage of the sampling switch is $V_{IN} + V_{DD}$

Ideally, there is always $V_{GS} = V_{DD}$ for the sampling switch

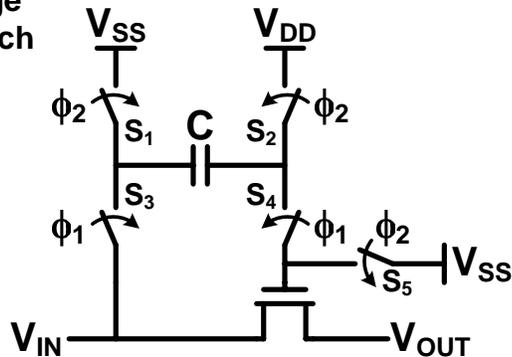

ECE1371

7-41

Bootstrapped Circuit

- C must be sized so that charge sharing between gate capacitance of switch is not significant

$$V_G = V_{IN} + \frac{C}{C + C_G} V_{DD}$$

- Rise time controlled by size of S_4 , fall time controlled by size of S_5
- Extra transistors required to limit gate-source voltages to V_{DD} and prevent overstress

See Dessouky, JSSC Mar.2001

ECE1371

7-42

Switched-Capacitor CMFB


- Two parts to the circuit
 - First, sense the common mode of the output
 - Second, compare the common mode to the expected common mode, and adjust the bias accordingly
- Sensing
 - Could use 2 resistors – they are either too small and reduce the gain, or they can get prohibitively large
 - Could use 2 capacitors – they don't reduce the gain, but the voltage across them is undefined
 - The voltage across them can be refreshed every clock cycle

ECE1371

7-43

Switched-Capacitor CMFB

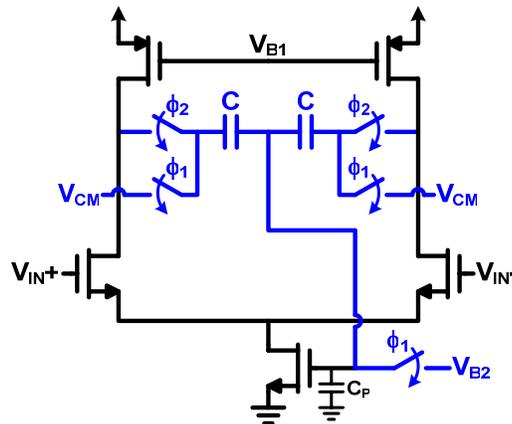- One alternative...
 - Phase 1: precharge capacitors to ideal value
 - Phase 2: sense the difference and adjust the bias accordingly



But... there may be large changes in the tail current bias


ECE1371

7-44

Switched-Capacitor CMFB

- **Solution: Part of the tail current source can be controlled by a constant bias voltage**

Will this work?

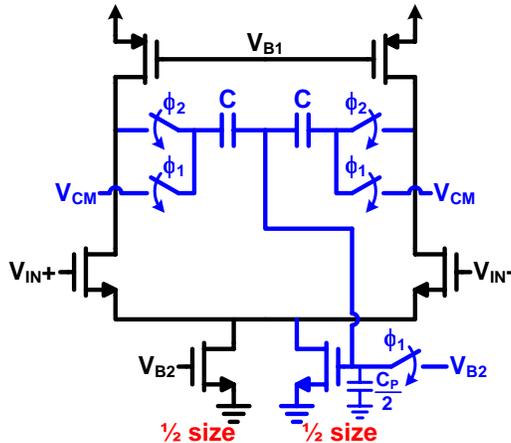


ECE1371

7-45

Switched-Capacitor CMFB

- **Alternatively, use 2 capacitors so that only a fraction of the charge is shared to adjust the bias voltage**

Typically, C_2 is 4-10 times C_1

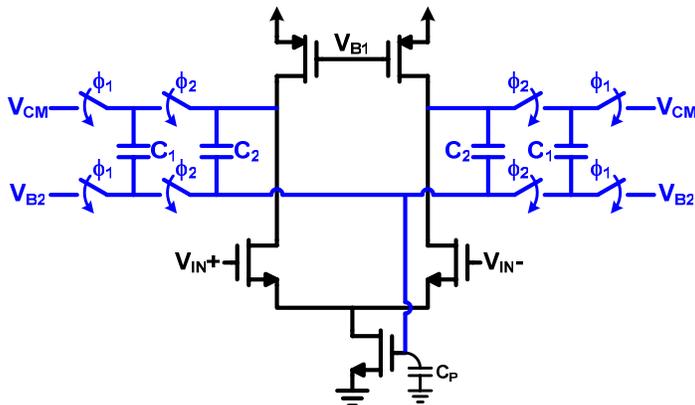

ECE1371

7-46

NLCOTD: Schmitt Trigger

ECE1371

7-47

What You Learned Today

- 1. Errors introduced with simple sampling switch**
RON variation, charge injection
- 2. Main SC Circuits – S/H, Gain and Integrators**
Parasitic Insensitive
Signal-independent charge injection
- 3. Bootstrapped Circuit**
- 4. Switched Capacitor CMFB**

ECE1371

7-48