


ECE615 Mixed-Signal IC Design

Discrete-Time $\Delta\Sigma$ Modulator Implementation



Vishal Saxena, Boise State University
(vishalsaxena@boisestate.edu)

Analog Mixed Signal IC Laboratory
Boise State University

Review: A $\Delta\Sigma$ ADC System


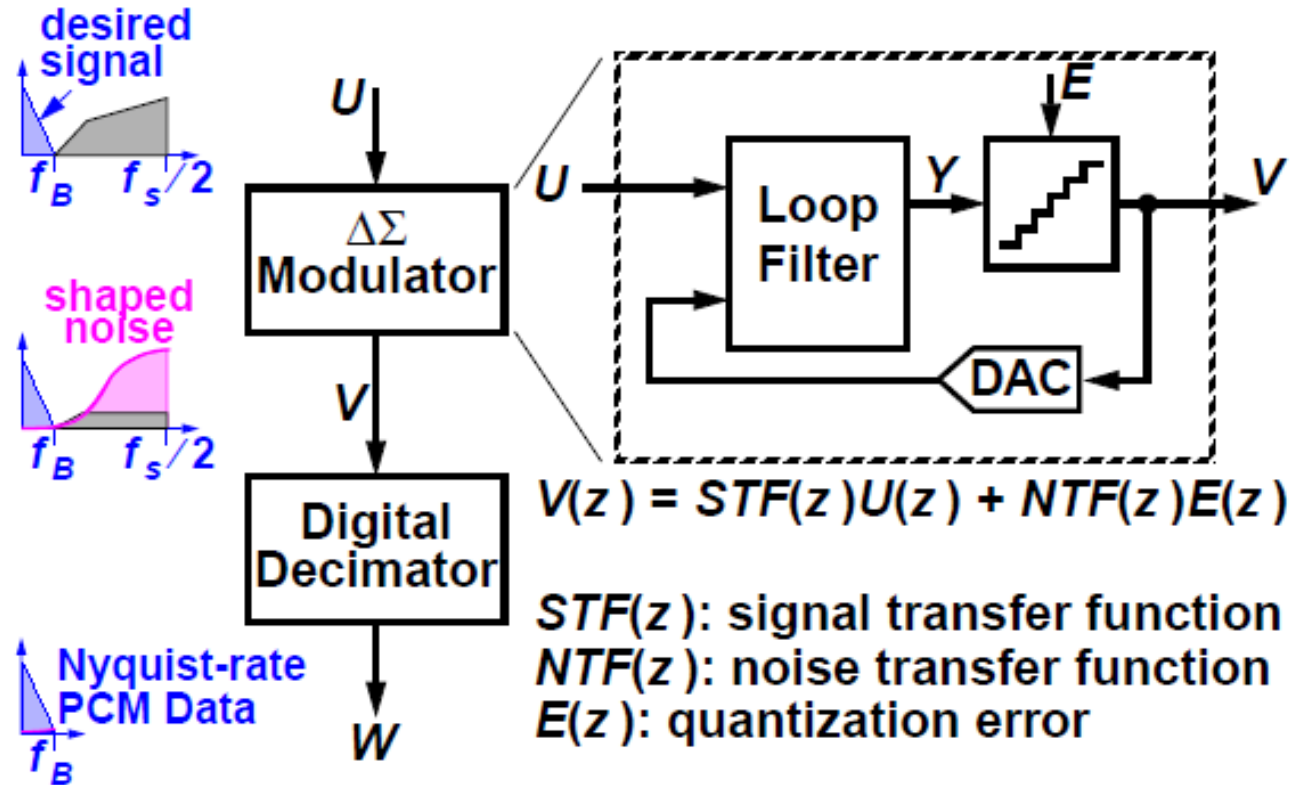


Review: MOD1

  

- Doubling OSR improves SQNR by 9 dB
Peak SQNR $\approx \text{dbp}(9 \cdot \text{OSR}^3 / (2\pi^2))$; $\text{dbp}(x) \equiv 10\log_{10}(x)$


Review: MOD2

  

- **Doubling OSR improves SQNR by 15 dB**
Peak SQNR $\approx \text{dbp}((15 \cdot \text{OSR}^5)/(4\pi^4))$

Review: Simulated MOD2 PSD

Input at 50% of FullScale

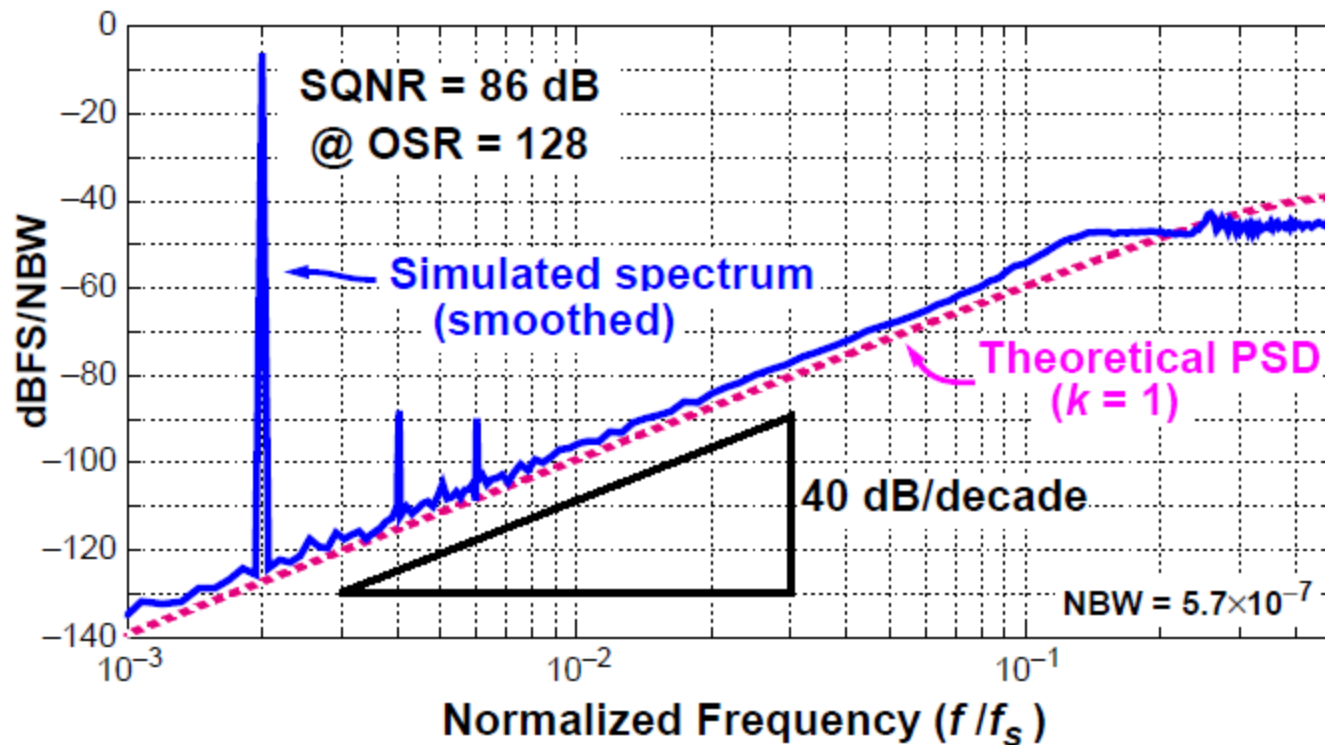

Example Design 1

- Clock at $f_s = 1 \text{ MHz}$.

Assume $BW = 1 \text{ kHz}$.


$$\square OSR = f_s / (2 \cdot BW) = 500 \approx 29$$

- MOD1: SQNR $\approx 9 \text{ dB/octave} \cdot 9 \text{ octaves} = 81 \text{ dB}$
 - MOD2: SQNR $\approx 15 \text{ dB/octave} \cdot 9 \text{ octaves} = 135 \text{ dB}$
- Actually more like 120 dB.

- SQNR of MOD1 is not bad, but SQNR of MOD2 is awesome!

MOD2 is usually preferred over MOD1 because MOD2's quantization noise is more well-behaved.


Block Diagram

 


- ❑ **Summation blocks**
- ❑ **Delaying and non-delaying discrete-time integrators**
- ❑ **Quantizer (1-bit)**
- ❑ **Feedback DACs (1-bit)**
- ❑ **Decimation filter (not shown)**
 - **Digital and therefore “easy”**

Switched-Capacitor Integrator

Single-ended circuit:

 


Timing:

 


Switched-Capacitor Integrator contd.


Single-ended circuit:

 


Timing:

 


$\phi 1$:

 

$\phi 2$:

 


Summation and Integration

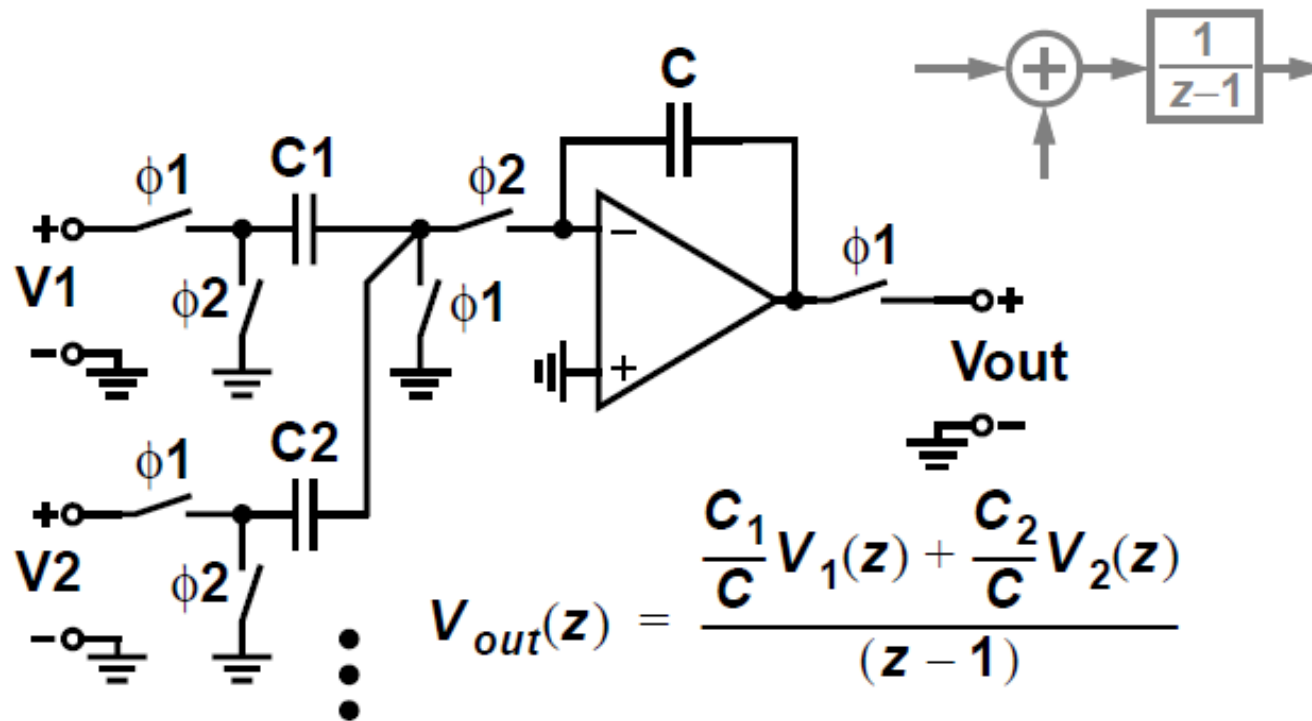


- Adding an extra input branch accomplishes addition, with weighting

1-bit DAC + Summation + Integration

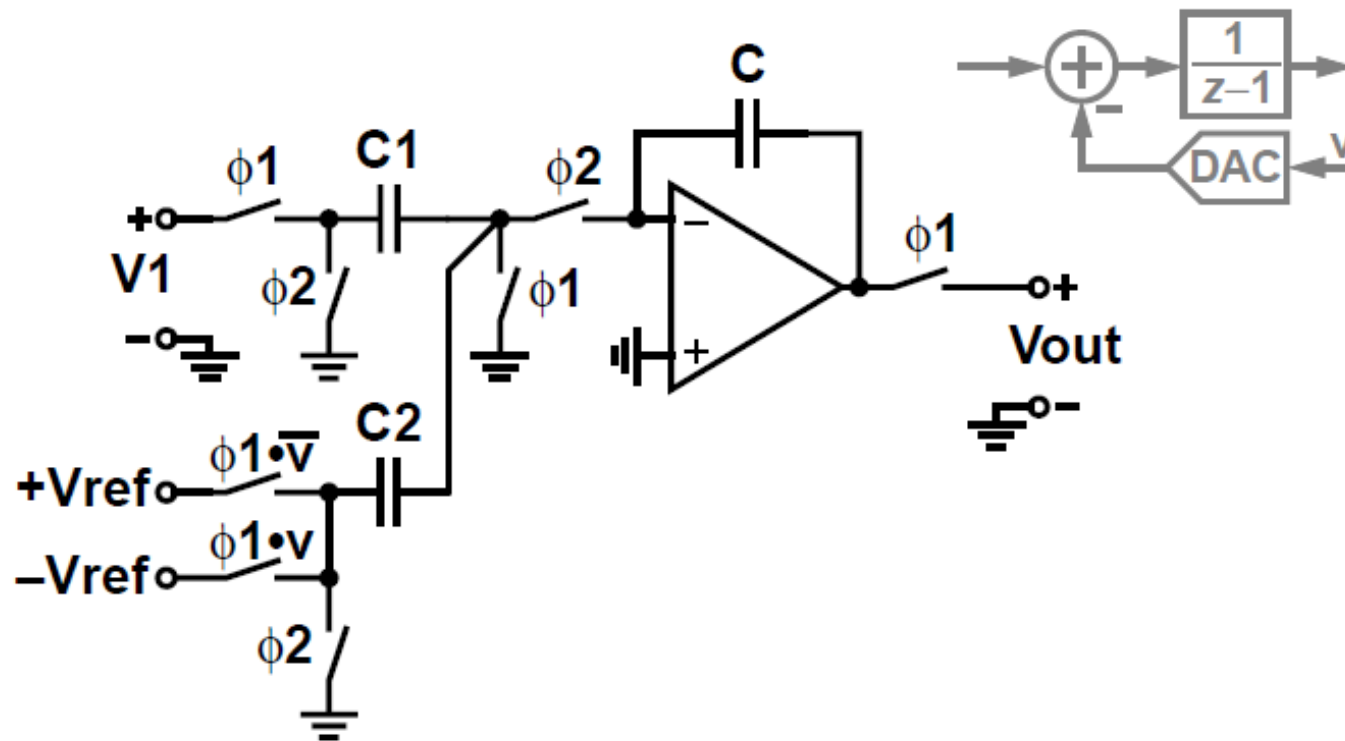


Fully-Differential Integrator

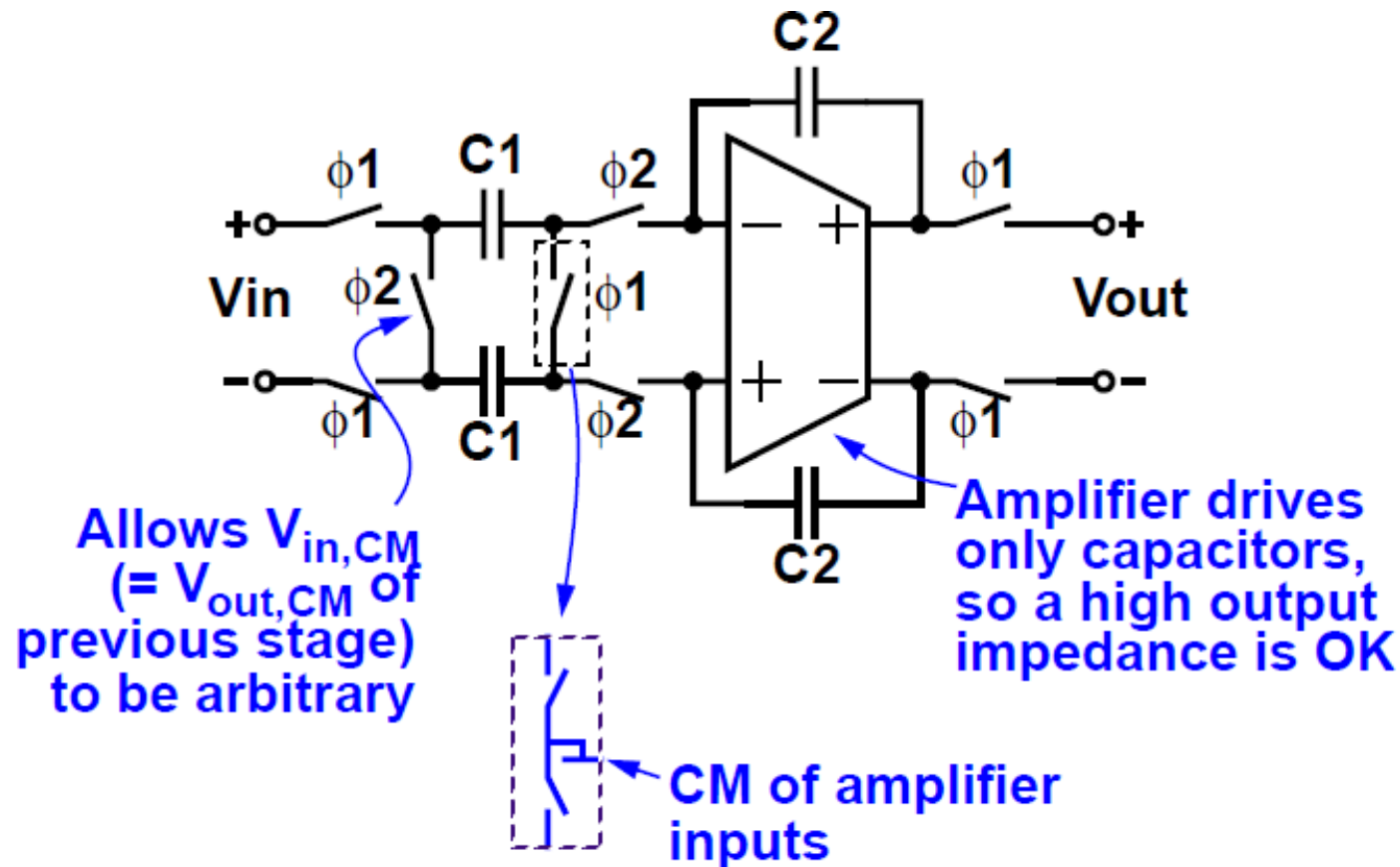


Non-Delaying Integrator

Single-ended circuit:

 


Timing:

 


Non-Delaying Integrator contd.


Single-ended circuit:

 


Timing:

 

$\phi 2$:

 

$\phi 1$:

 

Non-Delaying Integrator contd.

$$q_2(n+1) = q_2(n) - q_1(n+1)$$

$$zQ_2(z) = Q_2(z) - zQ_1(z)$$


$$\frac{Q_2(z)}{Q_1(z)} = -\frac{z}{z-1}$$

$$\frac{V_{out}(z)}{V_{in}(z)} = -\left(\frac{C_1}{C_2}\right)\frac{z}{z-1}$$


- **Delaying (and inverting) integrator**

Half-Delay Integrator

Single-ended circuit:

 

Timing:

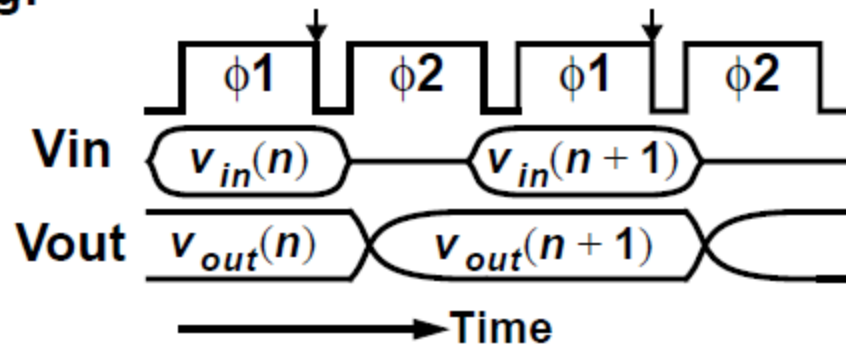

Half-Delay Integrator

- Output is sampled on a different phase than the input
- Some use the notation to denote the shift in sampling time


$$H(z) = \frac{z^{-1/2}}{z-1}$$

- An alternative method is to declare that the border between time n and $n+1$ occurs at the end of a specific phase, say ϕ_2
- A circuit which samples on ϕ_1 and updates on ϕ_2 is non-delaying, i.e. $H(z) = z / (z - 1)$

whereas a circuit which samples on ϕ_2 and updates on ϕ_1 is delaying, i.e. $H(z) = 1 / (z - 1)$


Timing in a $\Delta\Sigma$ Modulator

 - The safest way to deal with timing is to construct a timing diagram and verify that the circuit implements the desired difference equations
- E.g. MOD2:




- Difference Equations:
$$v(n) = Q(x_2(n))$$
$$x_2(n+1) = x_2(n) - v(n) + x_1(n+1)$$
$$x_1(n+1) = x_1(n) - v(n) + u(n)$$

Switched-Capacitor Realization

 

Timing

 

Timing looks OK!


Signal Swing

- So far, we have not paid any attention to how much swing the op amps can support, or to the magnitudes of u , V_{ref} , x_1 and x_2
- For simplicity, assume:
 - the full-scale range of u is ± 1 V,
 - the op-amp swing is also ± 1 V and
 - $V_{\text{ref}} = 1$ V
- We still need to know the ranges of x_1 and x_2 in order to accomplish *dynamic-range scaling*

Dynamic Range Scaling

- In a linear system with known state bounds, the states can be scaled to occupy any desired range

e.g. one state of original system:

 

state scaled by $1/k$:

