

ECE 615 → Lecture 14

Note Title

10/22/2013


* Single-loop Modulator

order ≤ 5

Low-OSR \Rightarrow large order
modulators

Complexity of 5th-order
modulator

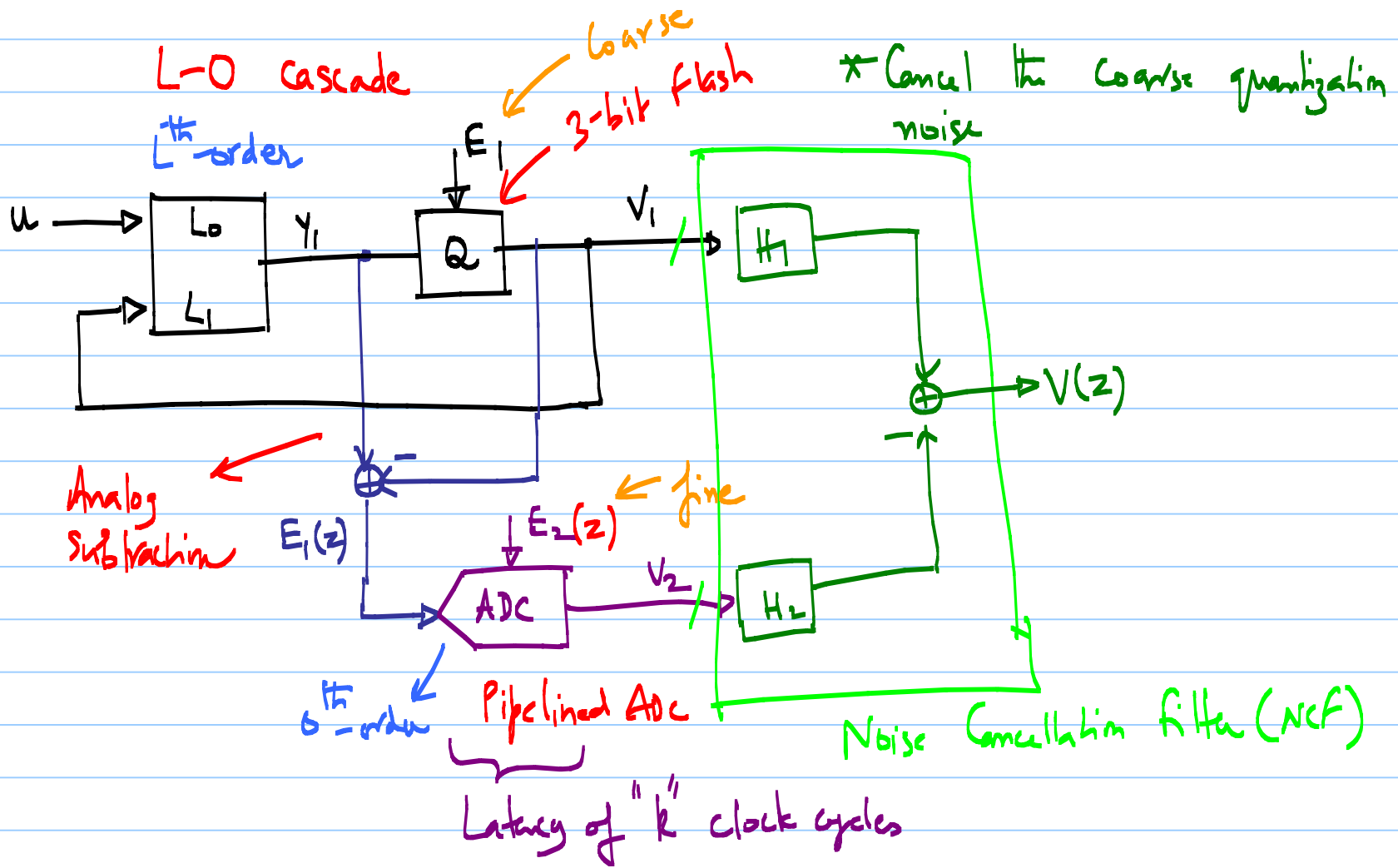Multi Stage Modulators (Cascaded $\Delta\Sigma$ Modulators)



* "Combine" V_1 & V_2 to obtain overall output V .

$$V_1(z) = STF_1 \cdot U + NTF_{1L} \cdot E_1 \longrightarrow \textcircled{1}$$

$$V_2(z) = z^{-k} (E_1(z) + E_2(z)) \longrightarrow \textcircled{2}$$

Design choice
 $H_1(z) = z^{-k}$

$$V(z) = H_1(z) \cdot V_1(z) - H_2(z) \cdot V_2(z) \quad \& \quad H_2(z) = NTF_{2L}(z)$$


$$= z^{-k} [STF_1 \cdot U + \underbrace{NTF_{1L}}_{\text{Analog}} \cdot E_1] - \underbrace{NTF_{2L}}_{\text{Digital}} [E_1 + E_2] \cdot z^{-k}$$

$$= z^{-k} [STF_1 \cdot U - NTF_{1L} \cdot E_2]$$

In general:

$$NTF_{1L}(z) \cdot NTF_{2L}(z) E_2(z)$$


for L_1 - L_2 cascade

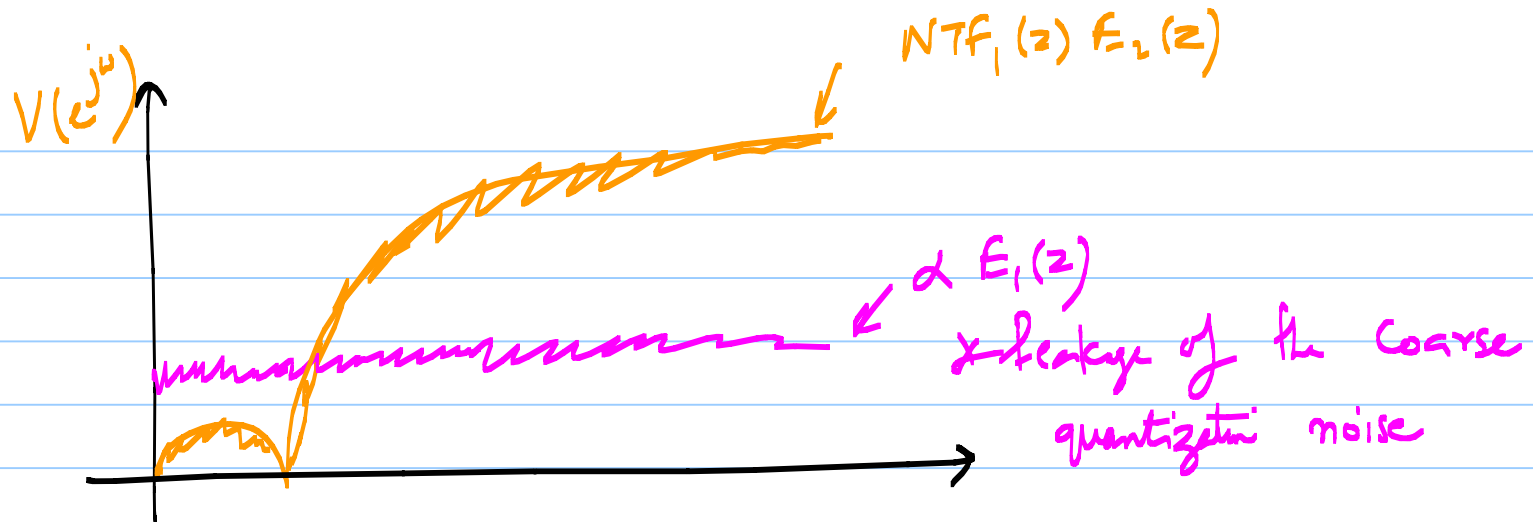

* Imperfect cancellation of the coarse quantization noise

Digital S/c Analog
 $H_2(z) = NTF_1(z)$

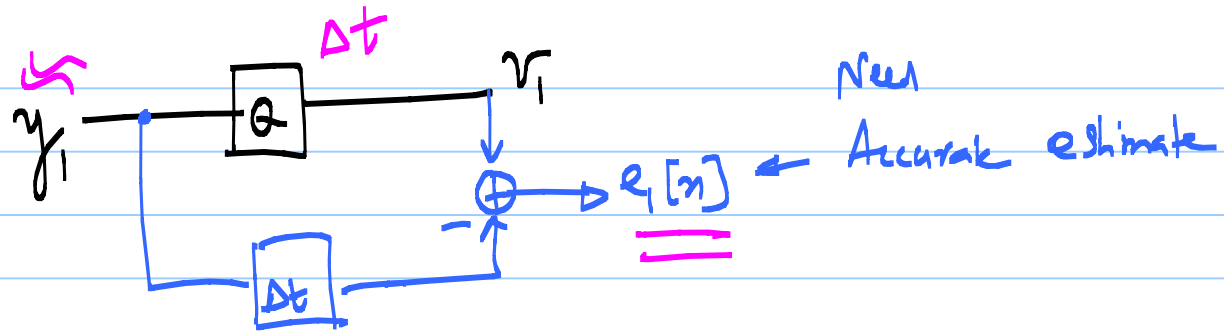
↑ Adaptability ← Calibration b/w Digital and Analog TFs



* To avoid the analog subtraction, use y_1 as the input to the second-stage

L-O cascade

L^{th} -order

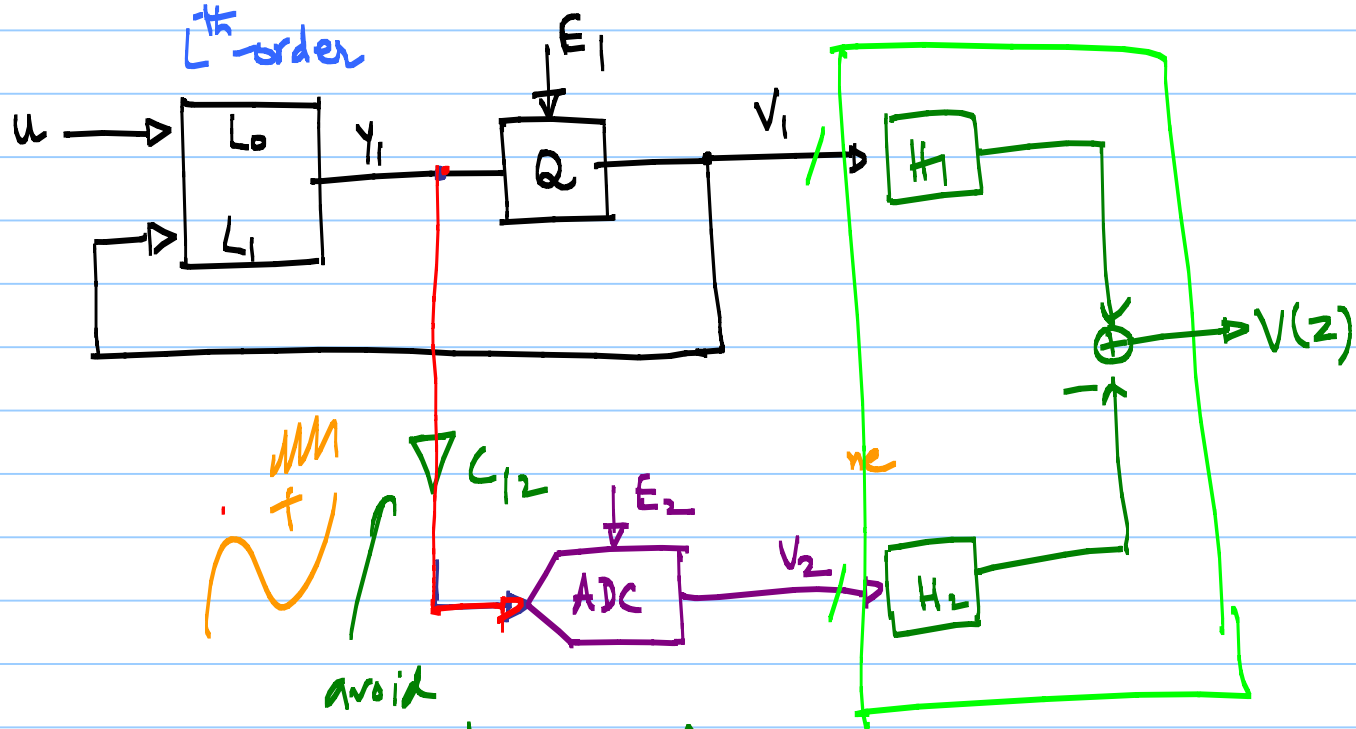

avoid
overloading of ADC_L

$$Y_1(z) = V_1(z) - E_1(z) = \text{STF}_1 \cdot U + (\text{NTF}_1 - 1)E_1 \longrightarrow \textcircled{1}$$

Digital NCF_s ⇒ $H_1(z) = z^{-k}$

$$H_2(z) = \frac{\text{NTF}_1(z)}{\text{NTF}_1(z) - 1} \quad \text{to ensure pole cancellation}$$

$$V(z) = z^{-k} [\text{STF}_1 \cdot U + \text{NTF}_1 \cdot E_1] - \frac{\text{NTF}_1}{\text{NTF}_1 - 1} \cdot z^{-k} \{ \text{STF}_1 \cdot U + (\text{NTF}_1 - 1)E_1 + E_2 \}$$

=

$$V(z) = \frac{z^{-k} \text{STF}_1(z)}{1 - \text{NTF}_1(z)} \cdot U(z) + \left(\frac{z^{-k} \text{NTF}_1(z)}{1 - \text{NTF}_1(z)} \right) \cdot E_2(z)$$

$\frac{\text{NTF}_1}{1 - \text{NTF}_1} \Rightarrow$ in the signal band
 $|\text{NTF}_1| \ll 1$

\approx NTF_1 in the
signal band

$$H_2(z) = \frac{NTF_1(z)}{NTF_1(z) - 1}$$

$$= \frac{1 - 2z^{-1} + z^{-2}}{\cancel{1 - 2z^{-1} + z^{-2}} - 1}$$

IIR

more complexity in NCF

$$NTF_1 = (1 - z^{-1})^2$$

$$H_{2, \text{original}} = 1 - 2z^{-1} + z^{-2}$$


↑
FIR
filter

* If the first-stage is a low-distortion modulator
(STF = 1)

$$X_N(z) = -(1 - \text{NTF}(z)) E(z)$$

$$x_2(z)$$

9th
2-nd order GFF

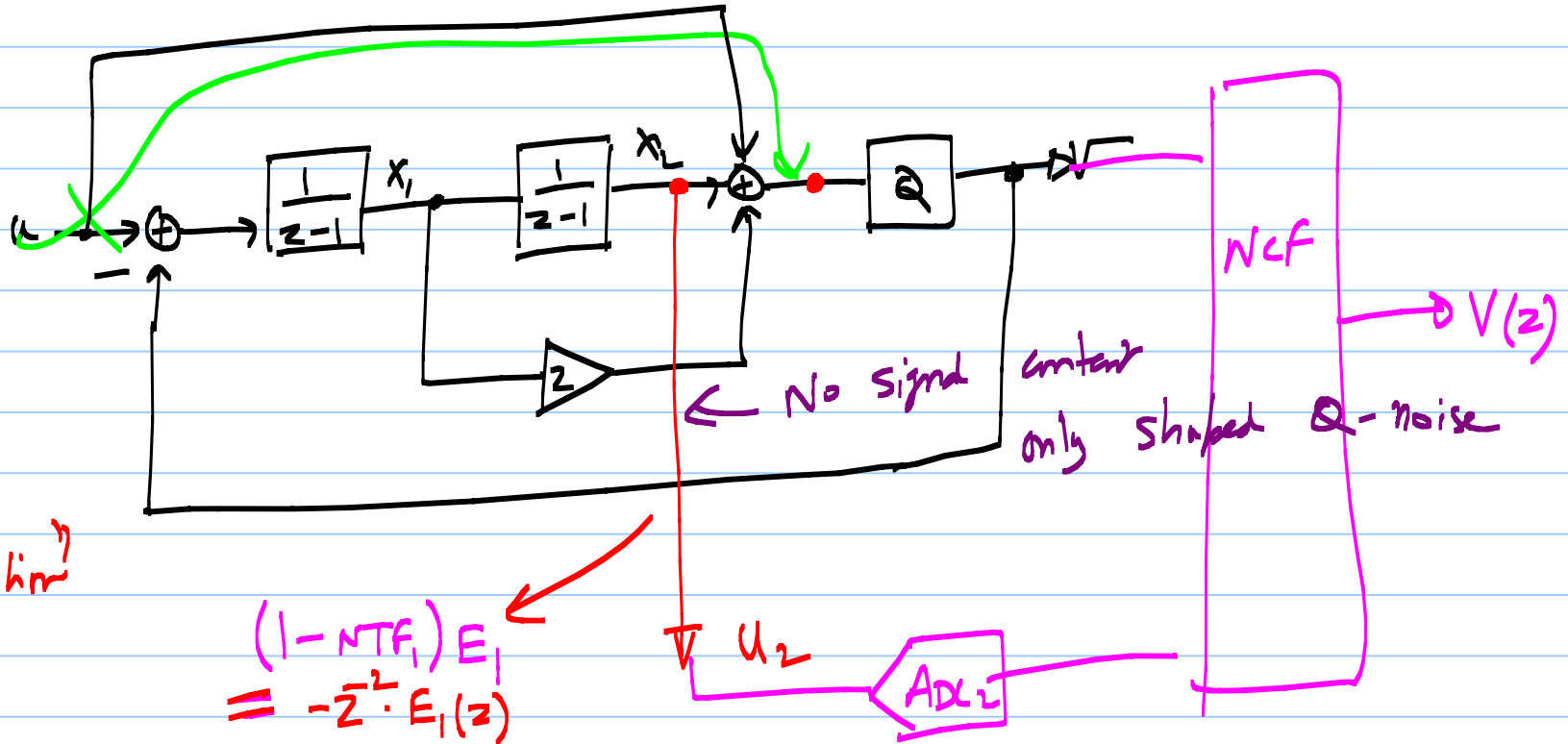

Multi Stage Noise Shaping (MASH)

2-1 MASH \Rightarrow 3rd-order noise-shaping

2-2-1 MASH \Rightarrow 5th-order \gg