

ECE 615 - Lecture 18

"Wireless LANs"

Note Title

11/5/2013

Continuous-time $\Delta\Sigma$ Modulation

802.11 a/b/g/n

ac




40/80/160 BW




6-9 GHz

≥ 12 bits

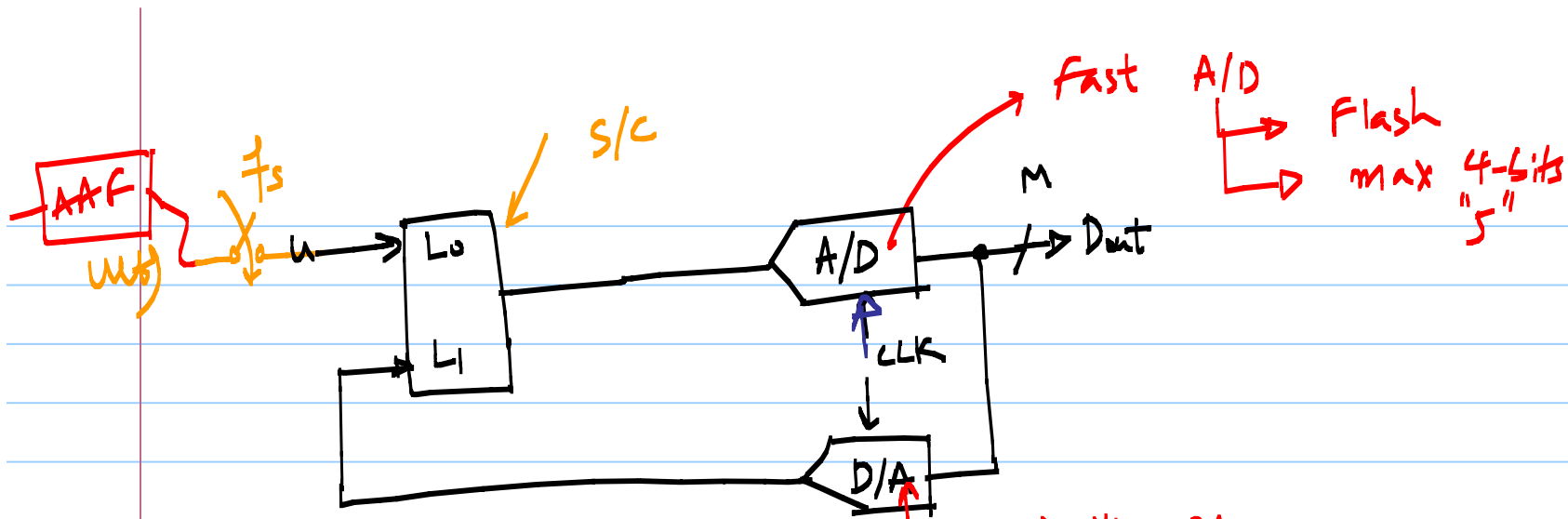


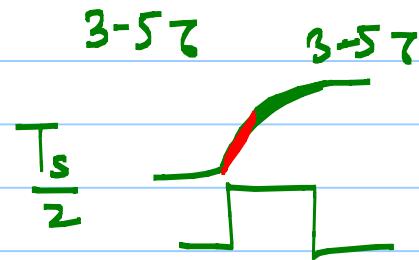S/C \Rightarrow opamp setting \Rightarrow f_{in}
 SR
 A_v





* opamp can only slew for 25% of settling time


* Opamp power consumption

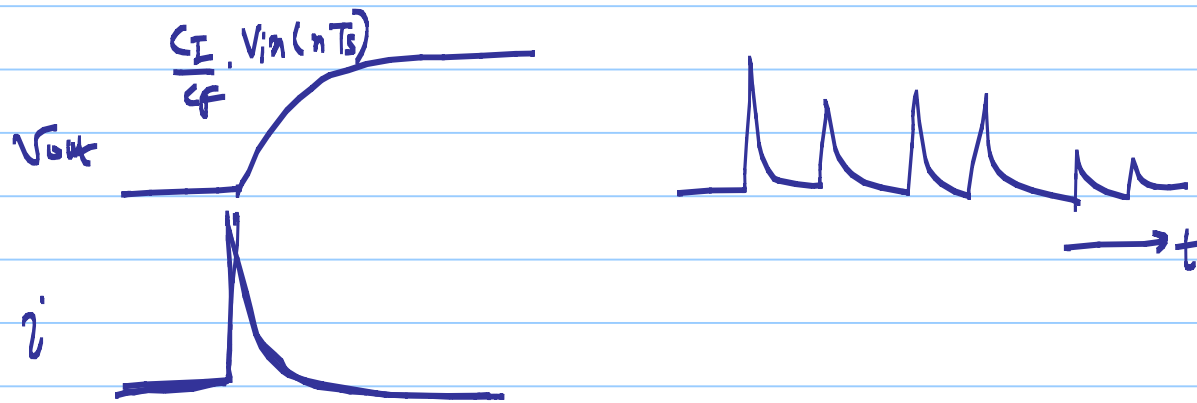


Opamp o/p is changing discretely.

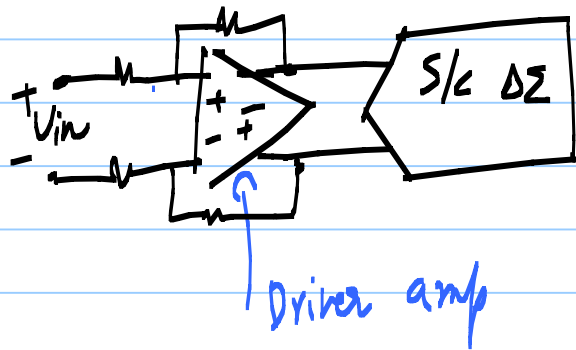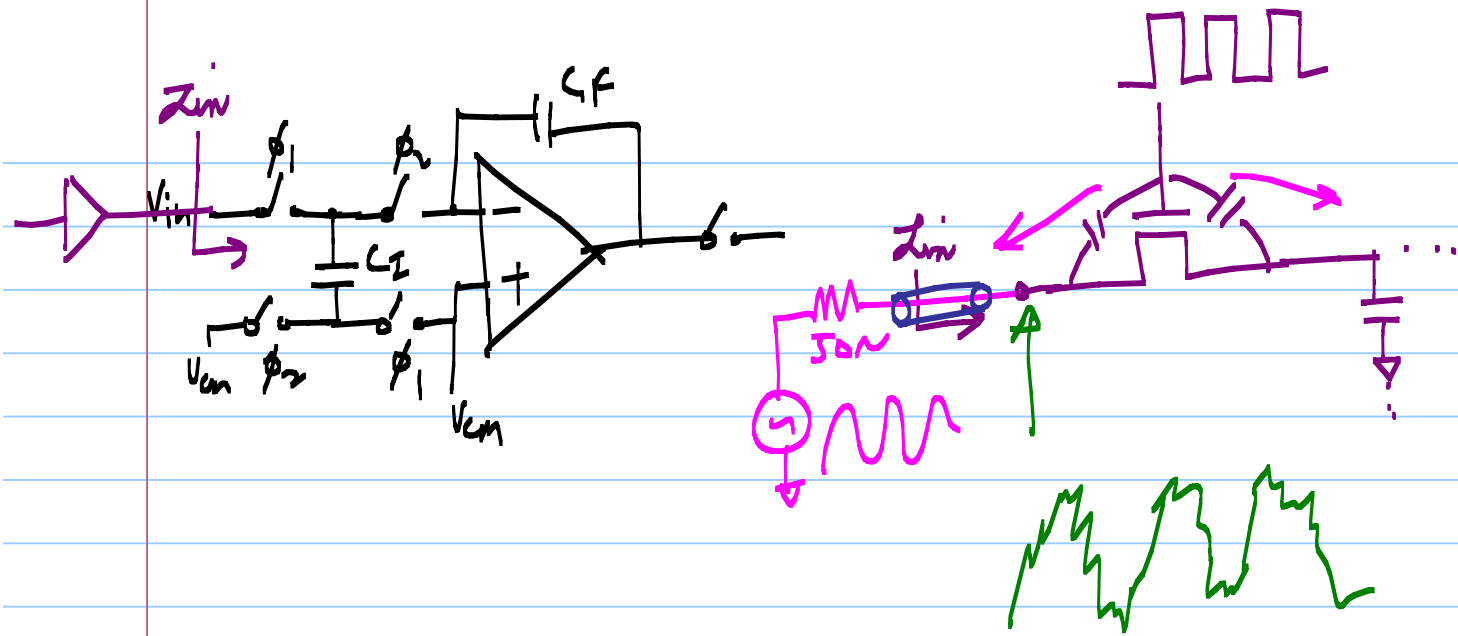


input impedance is not constant

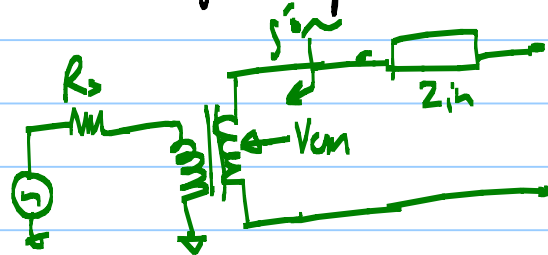

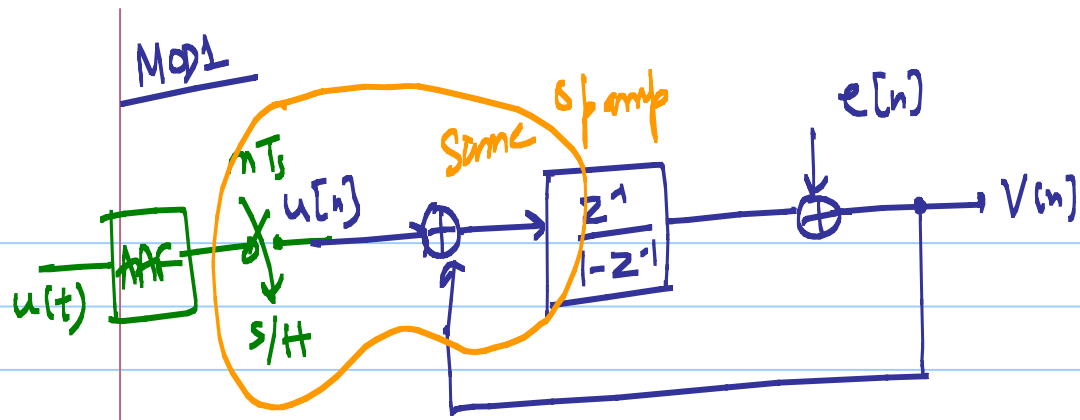

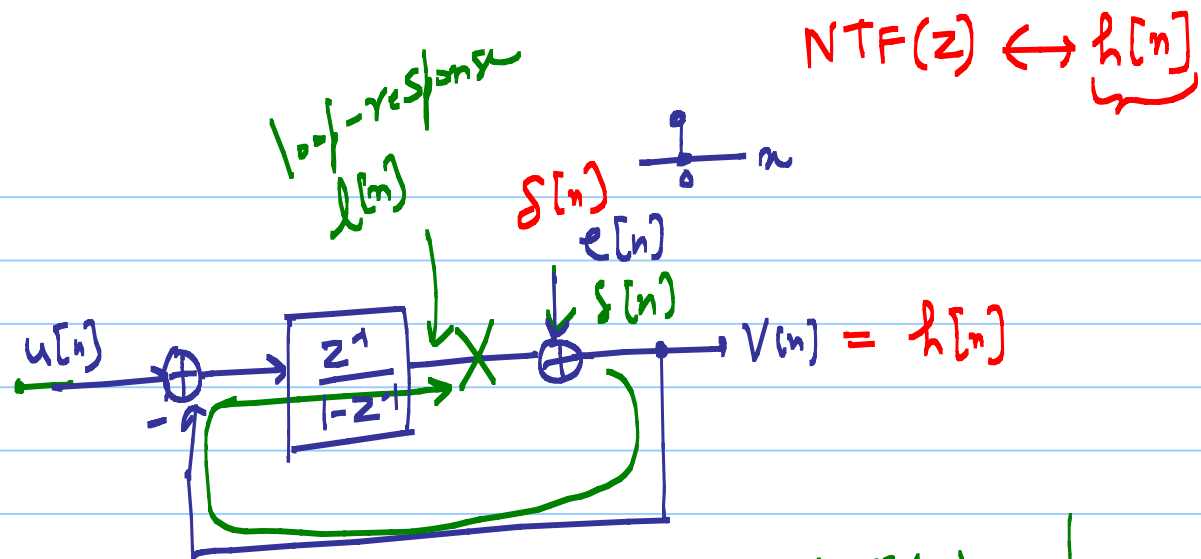- Bottom plate sampling
- delayed clock-phase for charge-injection



$$NTF(z) = \frac{1}{1 + L(z)}$$

loop response
seen by quantization
noise

$$L(z) = \frac{1}{NTF(z)} - 1$$


$$= \frac{1}{1-z^{-1}} - 1 = \frac{1 - 1 + z^{-1}}{1 - z^{-1}}$$



$$= \frac{z^{-1}}{1 - z^{-1}}$$

$$e[n] = \delta[n] = \{1, 0, 0, \dots\}$$

$$f_s = 1 \text{ Hz}$$

$$x[n] = \{0, 1, 1, 1, \dots\}$$

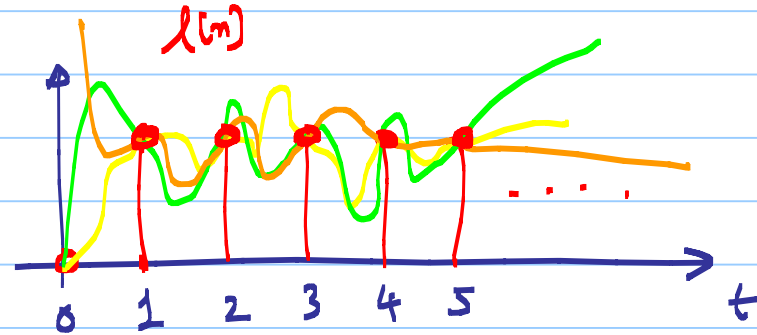

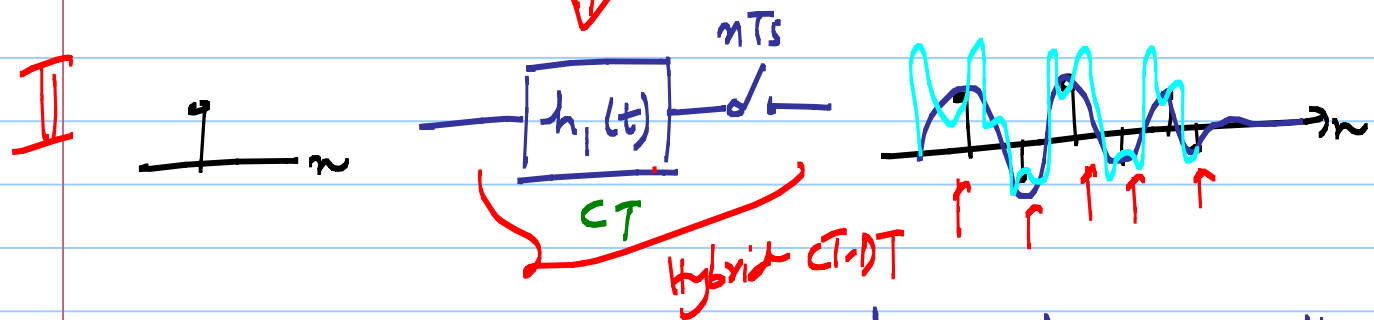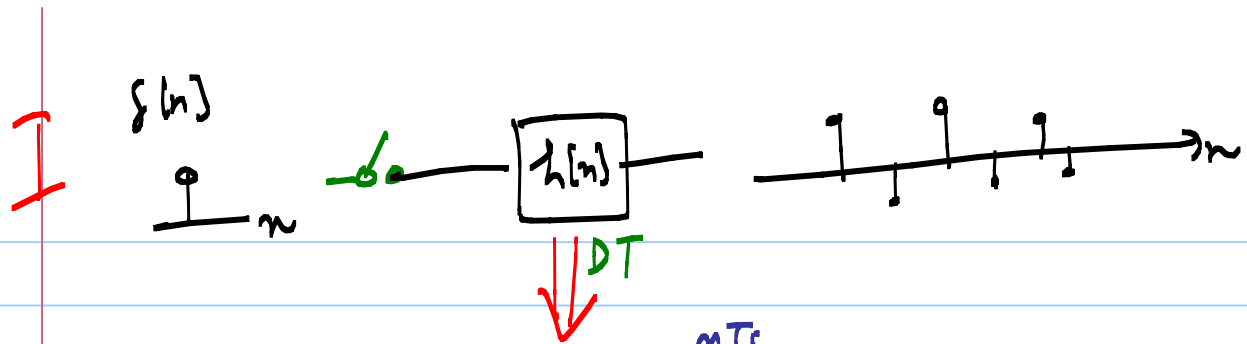


* Can use a CT impulse response $h_1(t)$ p.t. the sampled response is $h[n]$


↳ many $h_1(t)$ possibilities

↳ impulse invariance transformation

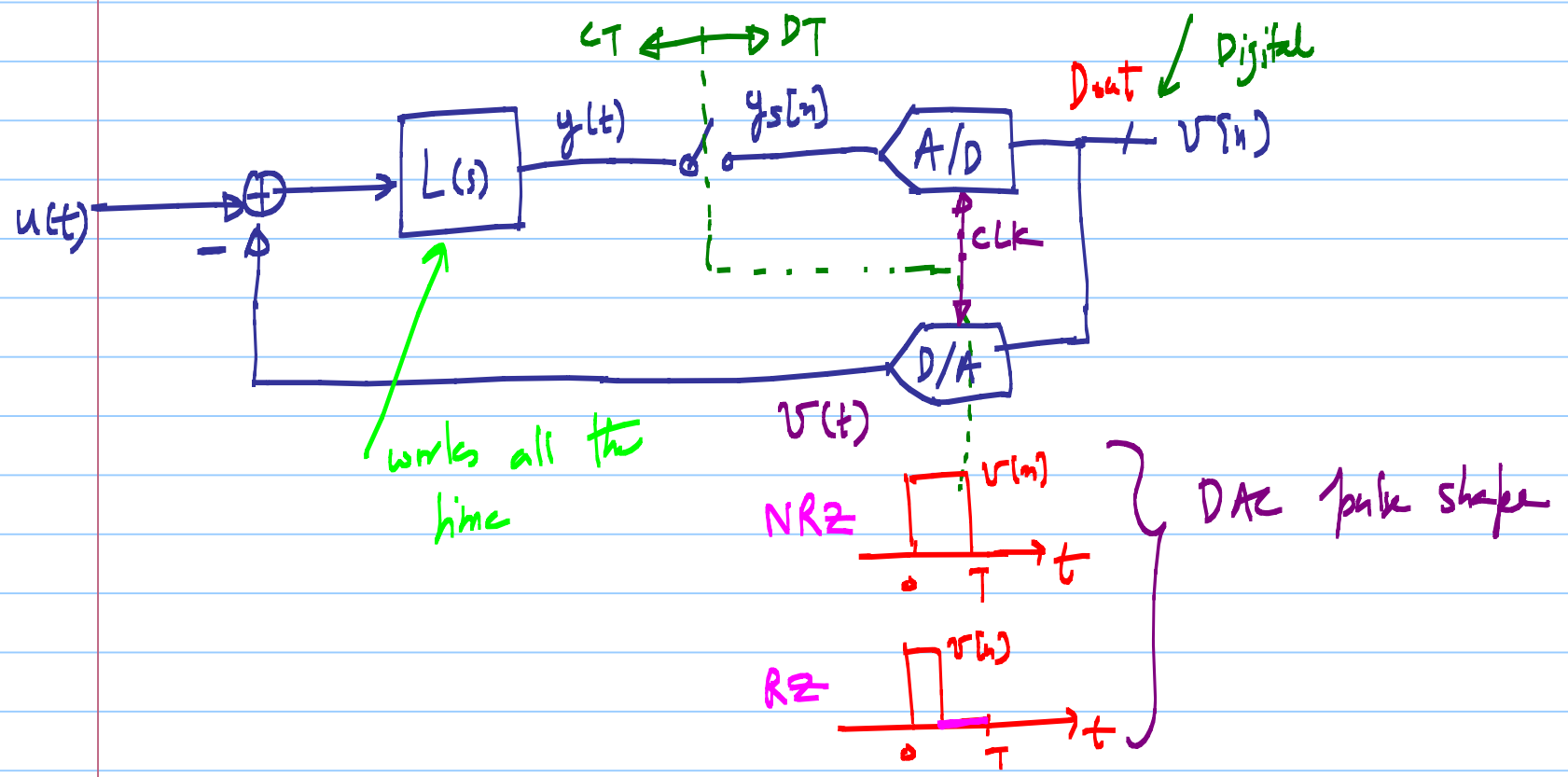Basic idea \Rightarrow find a CT filter whose sampled impulse response is same as the DT filter



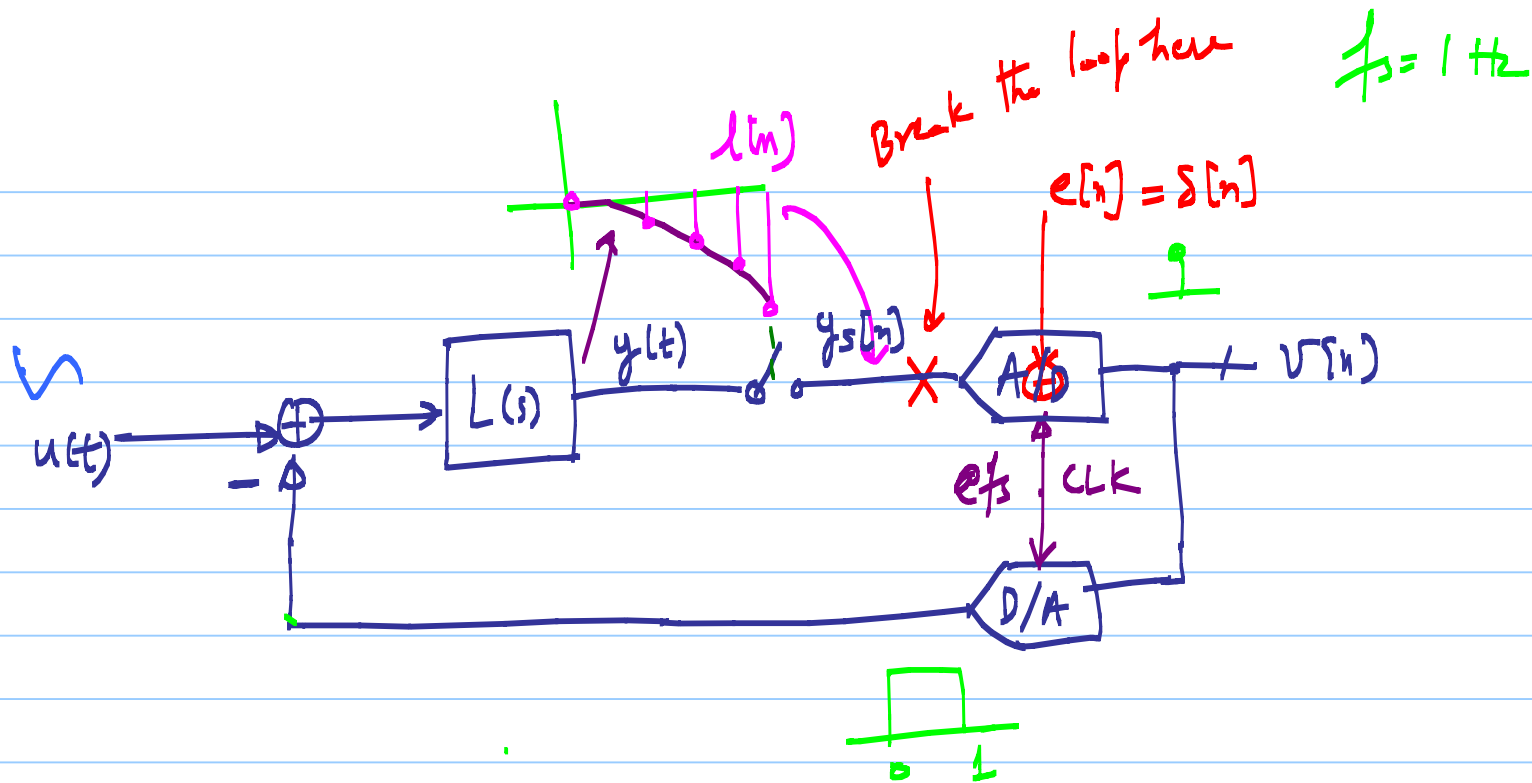* The loop-filter is realized using CT circuits, but made to look like a DT loop response





Overall system is DT

↳ A/D can't distinguish if the loop reference is DT or CT

Advantages of CT $\Delta\Sigma$ ADCs

↳ lower power dissipation \Leftrightarrow high speed implementation
of GHz-sampling $\Delta\Sigma$ ADCs

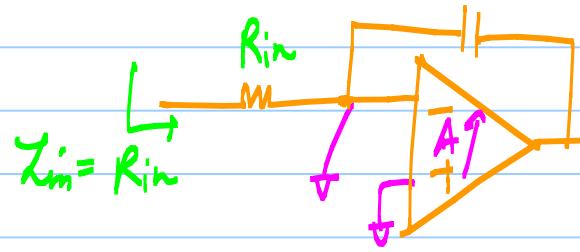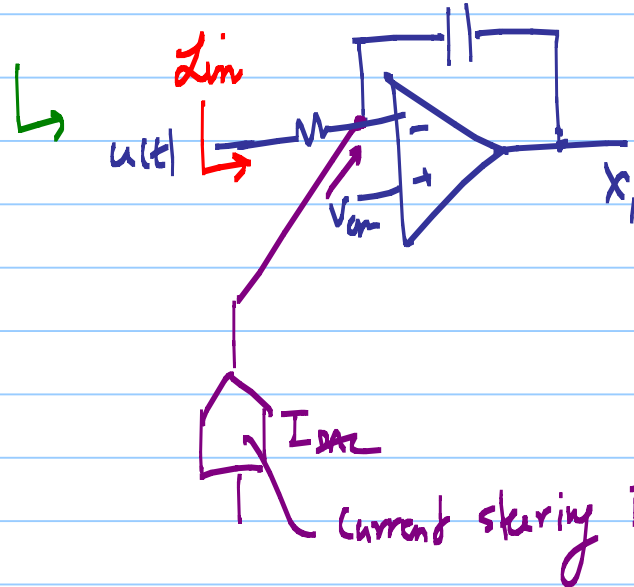↳ ~~*~~ Inherent anti-aliasing (free AAF)





* fixed input impedance
 \Rightarrow great for on-chip integration

1-bit CT \rightarrow BJTs
2nd-order



\downarrow 2nd-order S/c

\downarrow 5th-order S/c

\downarrow 5th-order CT

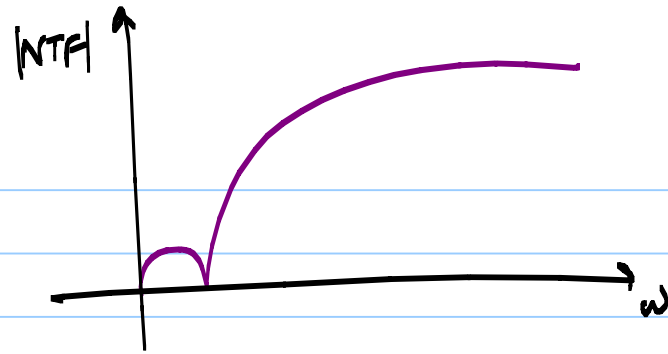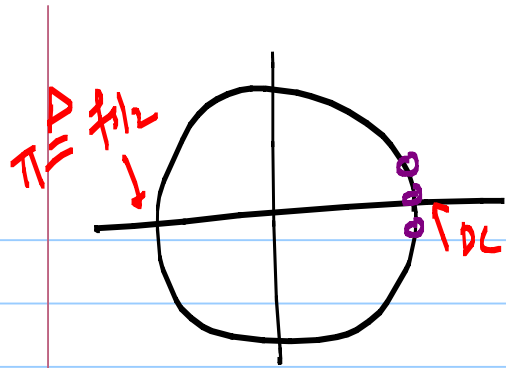

LP- $\Delta\Sigma$

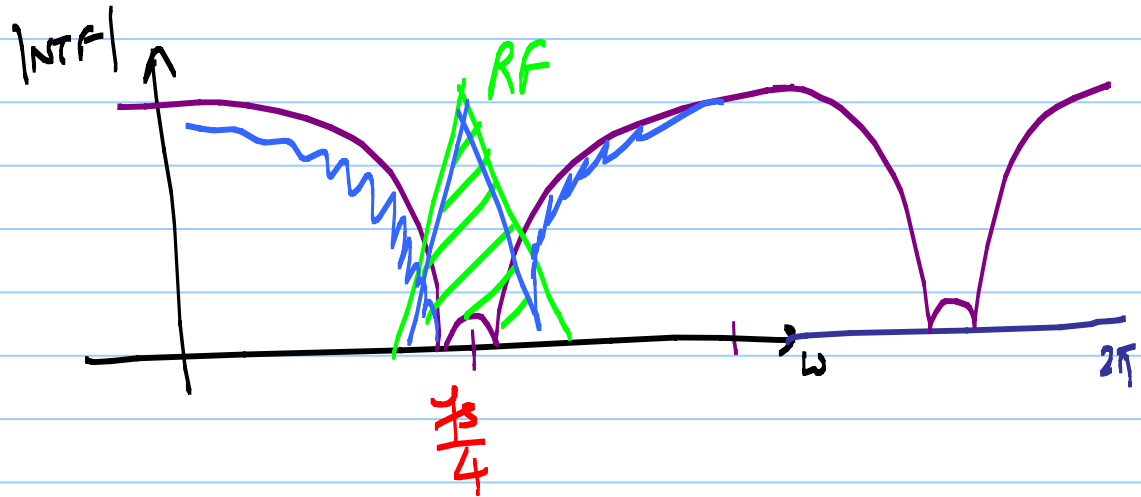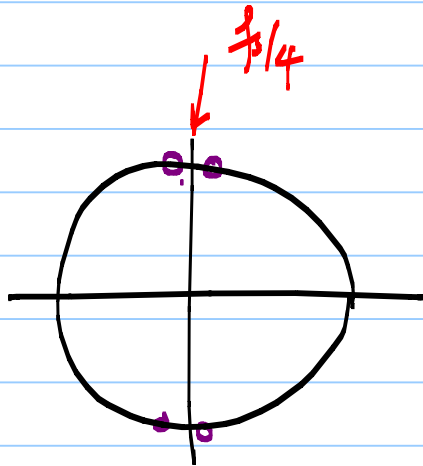

BP- $\Delta\Sigma$

"RF \rightarrow Digital Converter"
L(1)
L(2)

