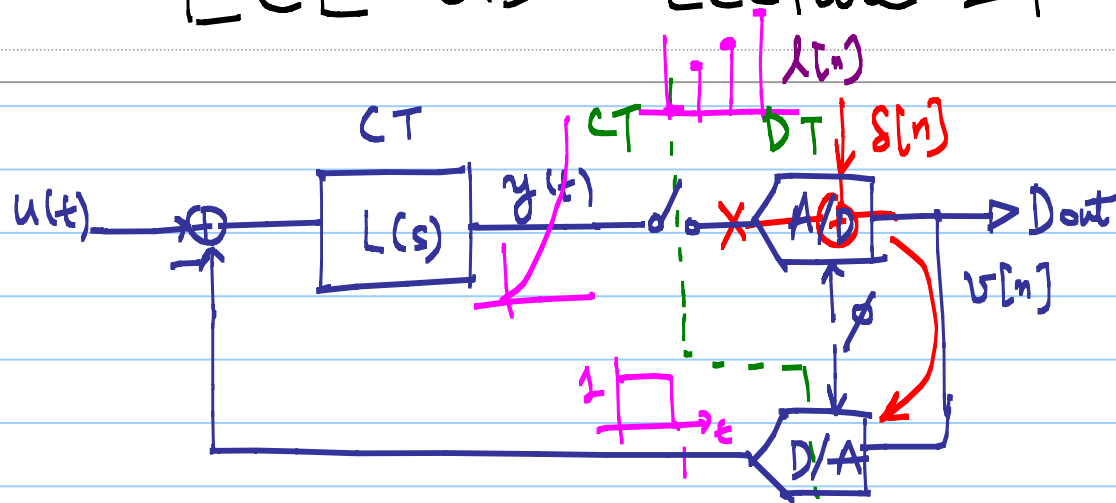


ECE 615 - Lecture 19

Note Title


11/7/2013




$f_s = 1 \text{ Hz}$

Overall, the system is discrete-time

$$NTF(z) = \frac{1}{1+L(z)}$$

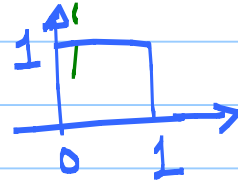



D/A pulse shape

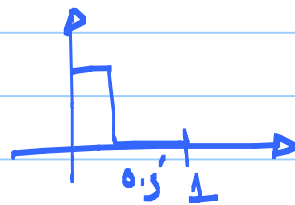

~~NTF(s)~~

1st - order CT $\Delta\Sigma$ Modulator


Normalized to
 $f_s = 1 \text{ Hz}$

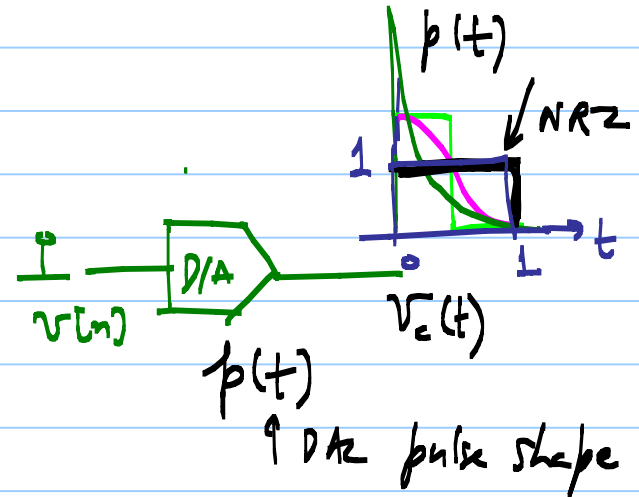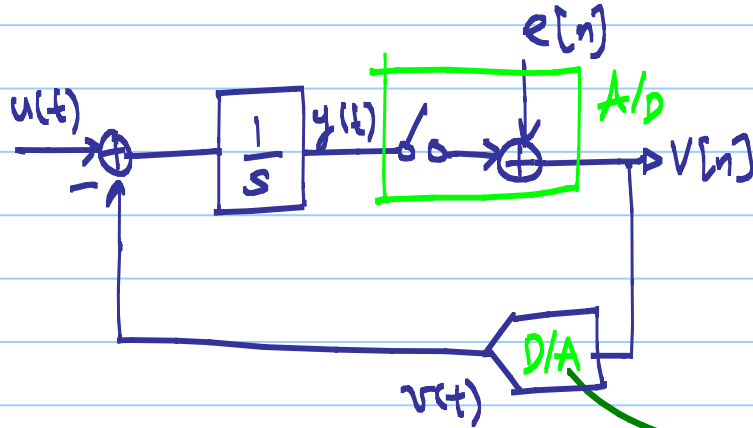



* DAC is converting a DT signal
to a CT signal

$\hookrightarrow p(t) \leftarrow$ pulse shape

NTF ??
..

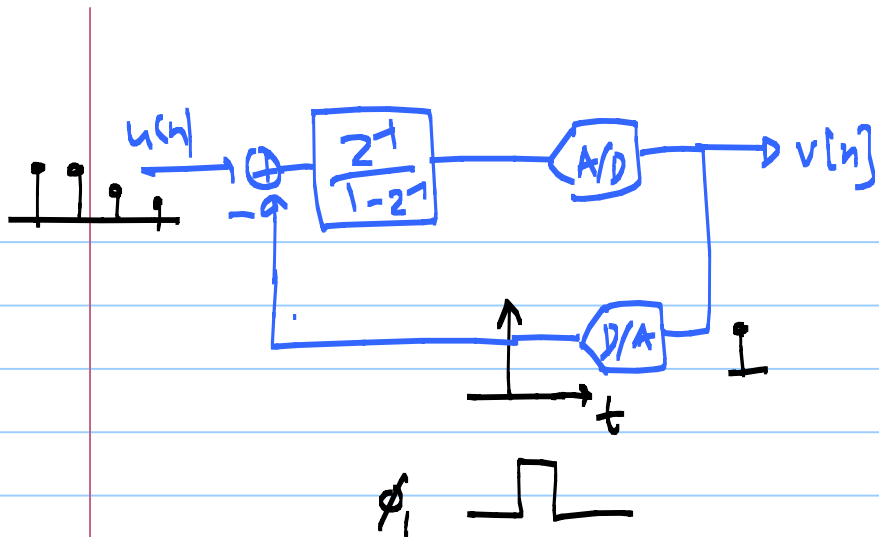




A/D

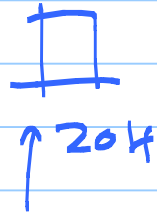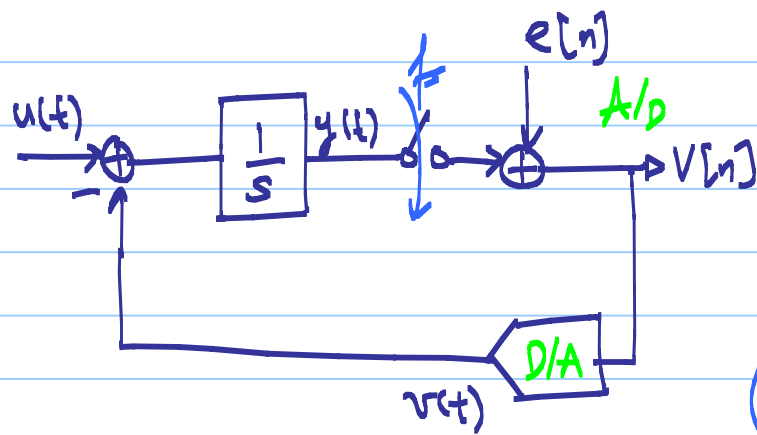

$$u(t) - u(t-T)$$



~~$$(U(s) - V(s)) \frac{1}{s} + E(s) = V(s)$$

$$\frac{1}{s} (1 - e^{-sT})$$~~

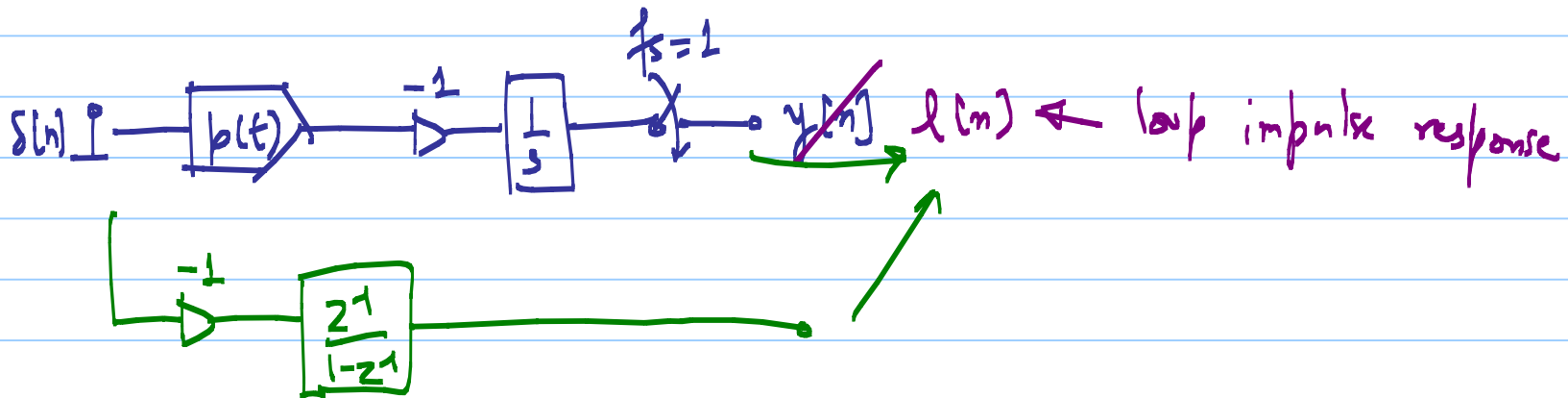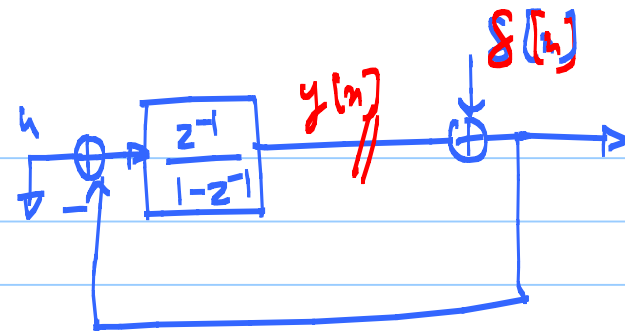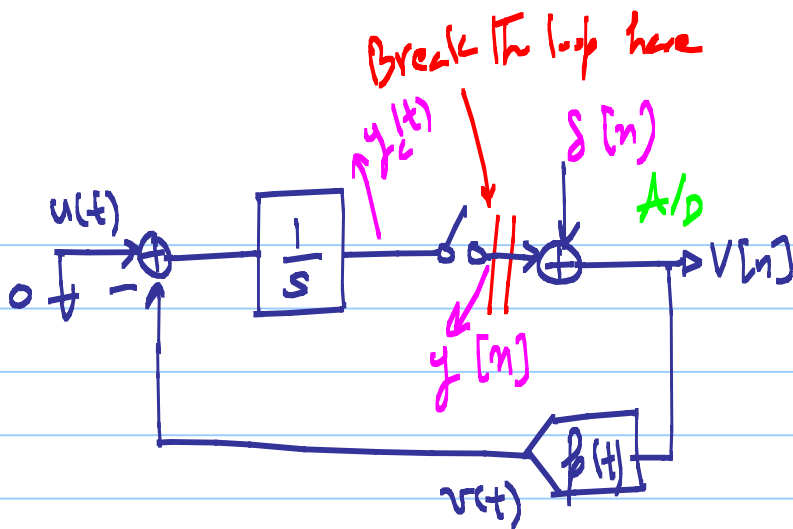

$l[n] \xleftrightarrow{Z} L(z)$ should be the same for the CT & DT loops


The DT impulse response

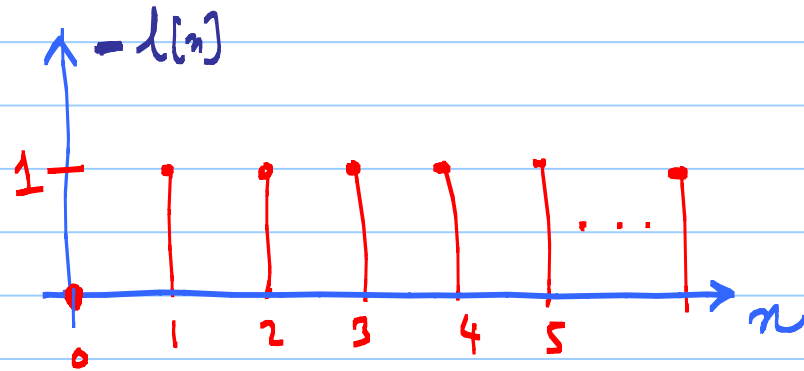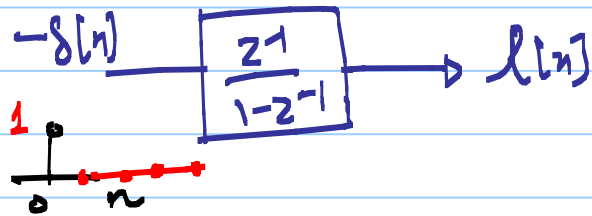


$\{0, 1, 1, \dots\}$

The CT impulse response


$$f_s = \frac{1}{T_s} = 1$$

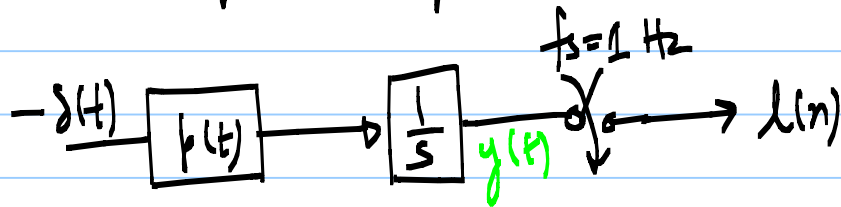

$$\{0, 1, 1, 1, \dots\}$$

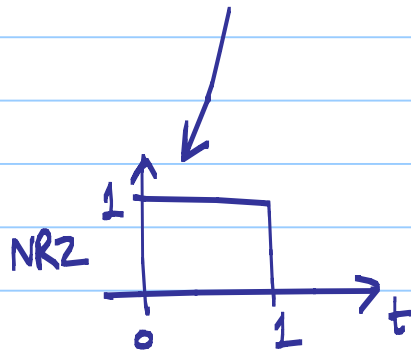

$\frac{1}{s}$

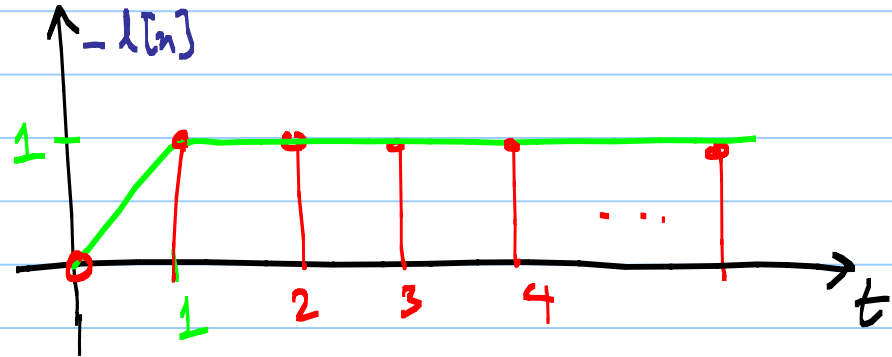


$$L(z) = -\left(\frac{z^{-1}}{1-z^{-1}}\right)$$

$$\left(\sum_{n=0}^{\infty} x^n = \frac{1}{1-x} \right)$$


$|x| < 1$

$$NTF(z) = \frac{1}{1-L(z)} = (1-z^{-1})$$

$$f_s = \frac{1}{T_s} = 1$$

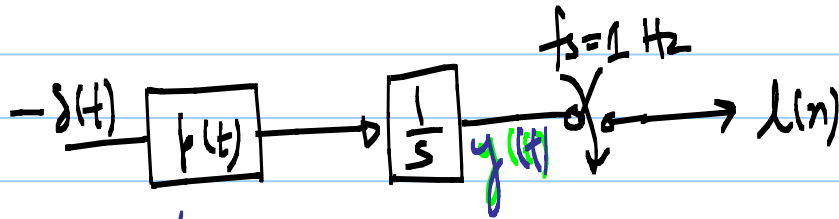



$$\{0, 1, 2, \dots\}$$

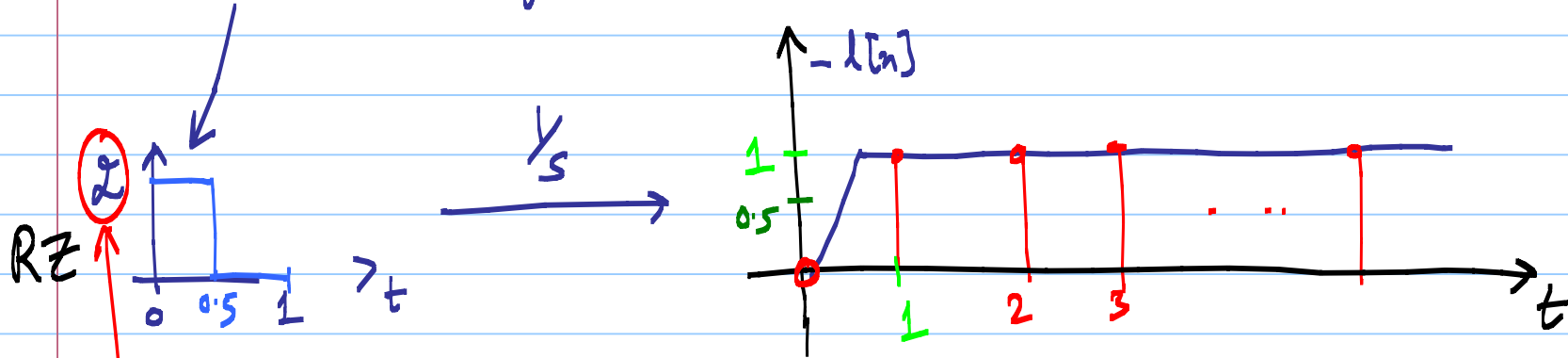


scale the DAZ pulse
amplitude by $\times 2$
to get the same
impulse response

Many possibilities for
 $\{p(t), L(s)\}$ for the same NTF(s)

Time-scaling (change the sampling rate)

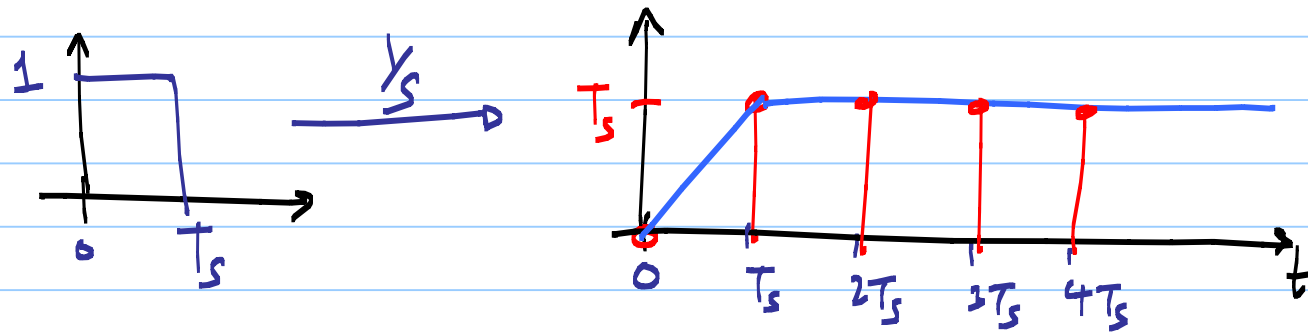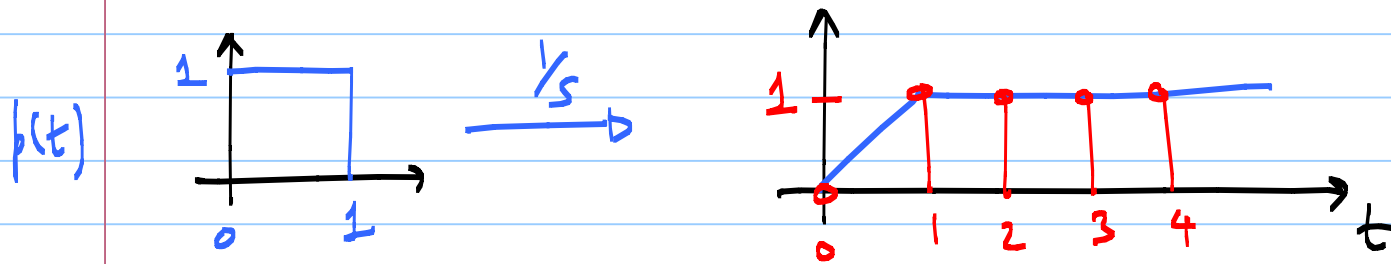



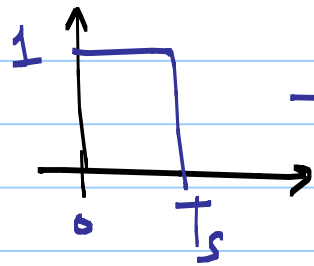


$$\frac{1}{sT_s} = \frac{1}{s}$$





time scaling
of the loop filter

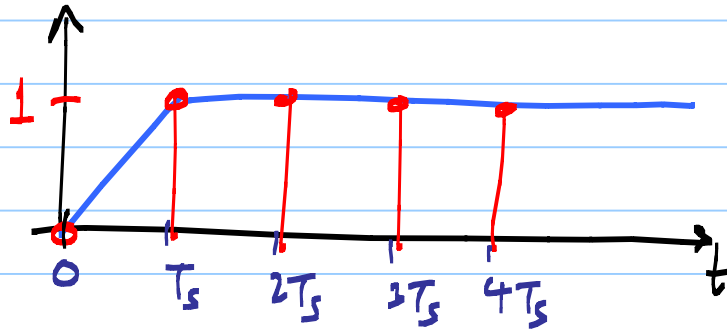

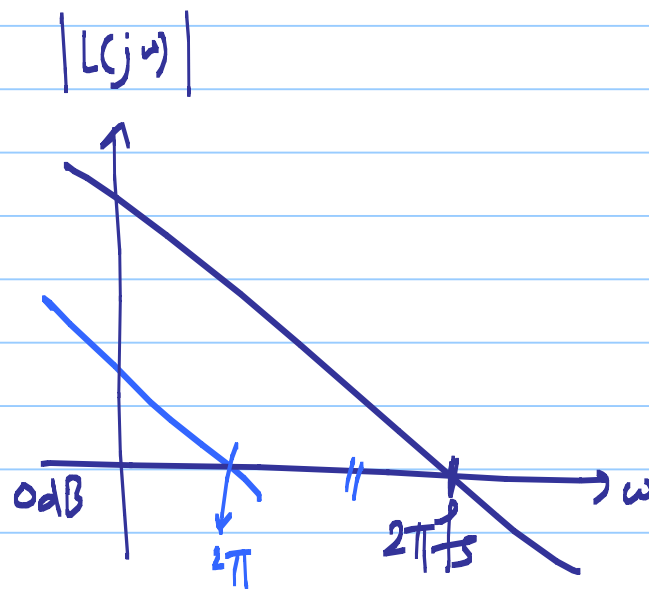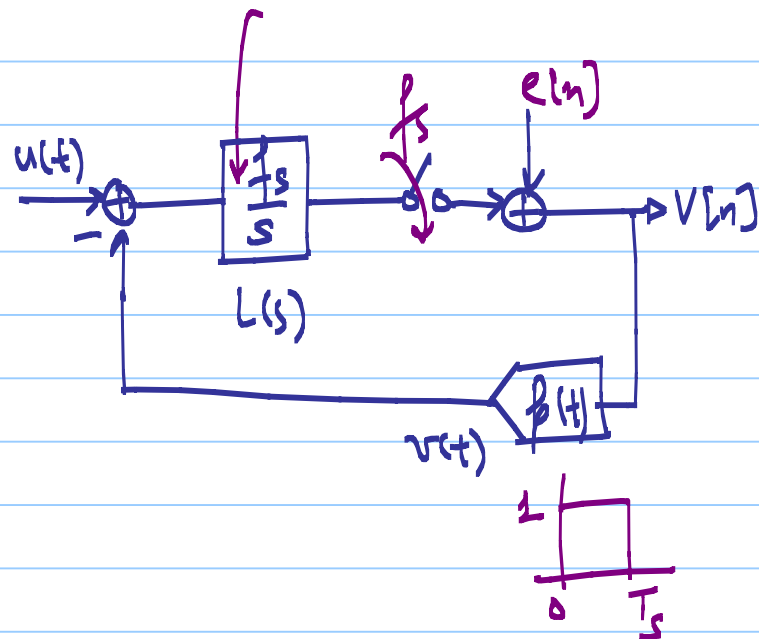

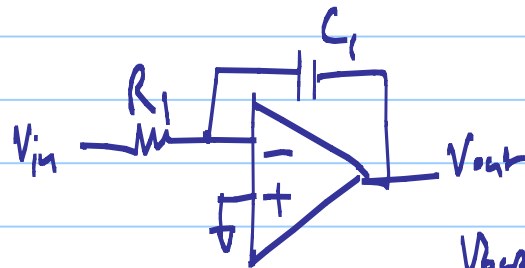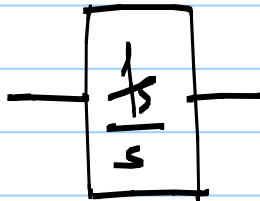" we have scaled fun of the Integrator"
 ↳ not the opamp



Ortmanns
CT & Z Book

$$\frac{V_{out}}{V_{in}} = - \frac{1}{R_1 C_1} \cdot \frac{1}{s}$$

Why $\frac{1}{s}$ and not $\frac{1}{RCs}$

$$\frac{1}{RC} = f_s$$

$$\Rightarrow RC = \frac{1}{f_s}$$

For $f_s = 1\text{Hz} \Rightarrow RC = 1\text{s} \Rightarrow 1\mu\text{F} \times 1\text{M}\Omega$

For $f_s = 1\text{GHz} \Rightarrow RC = 1\text{ns} \Rightarrow 1\text{pF} \times 1\text{k}\Omega$


9m MATLAB

Design CT filters with $f_s = 1 \text{ Hz}$

↓ Time-scaling → scale all the coefficients

Circuit Schematics

Impulse Invariant Transformation

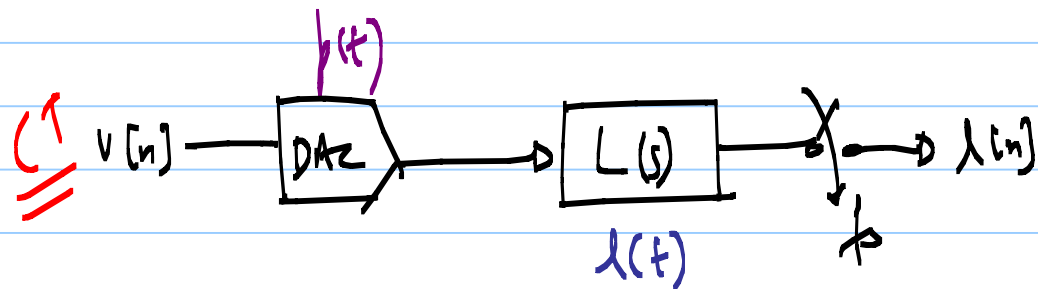

$$p(t) \otimes \lambda(t) \Big|_{t=nT_s} = \lambda[n]$$

$$\mathcal{L}^{-1}\{P(s) \cdot L(s)\} \Big|_{t=nT_s} = \mathcal{Z}^{-1}\{L(z)\}$$

I.T.T.

Synthesis of higher-order CT $\Delta\Sigma$ Modulators

$$x[n] = \mathcal{Z}^{-1}\{L(z)\} = \mathcal{L}^{-1}\{R_D(s) \cdot L(s)\} \Big|_{t=nT_s}$$

NTF(z) \rightarrow L(z) \rightarrow How do we get L(s) for any $R_D(s)$
3rd order

Using IIT Table
"Symbolic Math"

Impulse Response fitting
(Numerical)

↓
J.A. Cherry, Books

↓
ΔΣ Toolbox
realizeNTF_ct