


# ECE 615 - Lecture 20

Note Title

11/12/2013


Impulse Invariant Transform  
based symbolic calculation

Numerical fitting

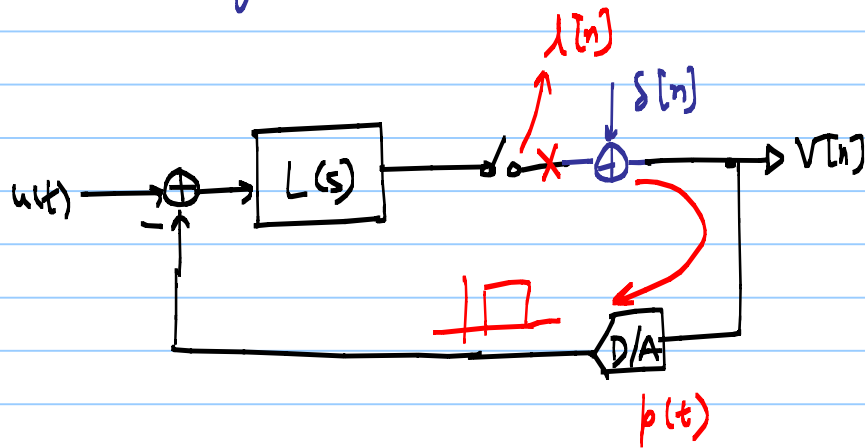

$\lambda[n]$

|

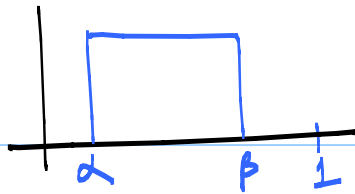

Normalized to  $T_s = 1s$   
(1Hz)

I.I.T.

$$x[n] = \mathcal{Z}^{-1}\{L(z)\} = \mathcal{L}^{-1}\{R_D(s) \cdot L(s)\} \Big|_{t=nT_s}$$

① Start with a DT  $\Delta\Sigma$  modulator, with an open loop response

$$L(z) = \frac{1}{NTF(z)} - 1$$

② Map  $L(z)$  to a CT  $\Delta\Sigma$  modulator, with a ~~the~~ pulse shape

$$\hat{y}_D(t) = p(t)$$


$$\{L(z), \hat{r}_D(t)\} \xrightarrow{\text{IIT}} L(s)$$

Use Tables

③ Write  $L(z)$  as a partial fraction expansion

↳ rectangular pulse shape  $t \in [\alpha, \beta]$   $\hat{r}_D(t)$
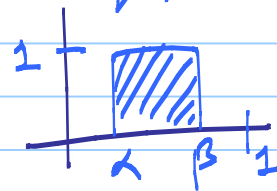
$$\hat{R}_{\alpha, \beta}(s) = \frac{1}{s} [e^{-\alpha s} - e^{-\beta s}]$$



$$u(t-\alpha) - u(t-\beta)$$

J.A. Cherry

④ Use table to convert each of the partial fraction 'poles'  
from z-domain to s-domain  
↳ recombine to obtain  $L(s)$

When using IIT,

a z-domain pole  $z_k$  with multiplicity of  $l$   
maps to a CT pole at  $s=s_k$  with the  
same multiplicity

$$s_k = \ln(z_k)$$

'l' poles at  $z_k \xrightarrow{\text{IFT}} \text{'l' poles at } s_k = \ln(z_k)$

$$\frac{1}{(z-1)^l} \rightarrow \frac{y_0}{s^l - 0} = \frac{y_0}{s^l}$$

scaling coefficient

$$\frac{z^{-1}}{1-z^{-1}} \rightarrow \frac{1}{s}$$

delaying integrator

CT integrator

A poor intuition

$$I(z) = \frac{z^{-1}}{1-z^{-1}} = \frac{1}{z-1} = \frac{1}{e^{sT_s}-1}$$

$$= \frac{1}{e^s - 1}$$


for  $T_s = 1s$

$$= \frac{1}{(1 + s + \frac{s^2}{2!} + \dots) - 1}$$

$$= \frac{1}{s + \frac{s^2}{2!} + \frac{s^3}{3!} + \dots}$$

$$\approx \frac{1}{s}$$

for  $|sT_s| \ll 1$   
 $\Rightarrow \omega \ll \pi$

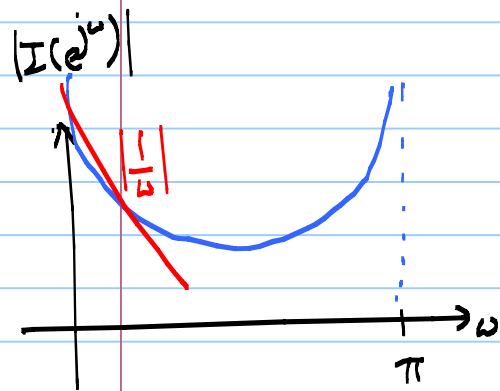

Ex 1

2<sup>nd</sup>-order CT-DSM

NRZ DAZ  $(\alpha, \beta) = (0, 1)$

$$NTF(z) = (1 - z^{-1})^2$$

$$\Rightarrow L(z) = \frac{NTF(z) - 1}{NTF(z)} = \frac{-2z^{-1} + z^{-2}}{(1 - z^{-1})^2}$$

$$L(z) = \frac{-2z + 1}{(z - 1)^2}$$

$$= \underbrace{\frac{-2}{z-1}} + \underbrace{\frac{-1}{(z-1)^2}} \Leftarrow \text{partial fraction expansion of } L(z)$$

$$(\alpha, \beta) = (0, 1)$$

$$4 \quad s_k = h(z_k) = 0$$

$$\frac{1}{(z-1)} \rightarrow \frac{1}{s}$$

$$\frac{1}{(z-1)^2} \rightarrow \frac{1-0.5s}{s^2}$$

} from the IIT Table


$$L(s) = -2 \left( \frac{1}{s} \right) - \left( \frac{1-0.5s}{s^2} \right)$$

$$L(s)_{NRZ} = - \frac{1+1.5s}{s^2}$$

for an NRZ DAC



For an RZ DAC  $(d, s) = (0, 0.5)$

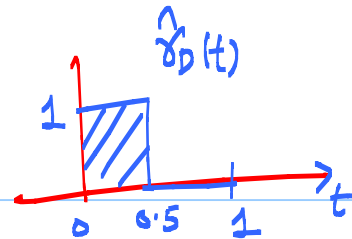

$$L(s)_{RZ} = - \left( \frac{2 + 2 \cdot 5s}{s^2} \right)$$

\* Numerator coefficients are higher for RZ pulse-shape

Numerical Determination of Loop filter coefficients

$$r_1 \begin{bmatrix} 0 \\ \vdots \\ 0 \\ \vdots \end{bmatrix} + r_2 \begin{bmatrix} 0 \\ 0.5 \\ 1.5 \\ 2.5 \\ \vdots \end{bmatrix} = \begin{bmatrix} 0 \\ 2 \\ 3 \\ 4 \\ 5 \\ \vdots \end{bmatrix}$$

$C_1$                        $C_2$                        $L[n]$

$N$  is our choice  
 $\swarrow$   
 $N \times 1$

$$\begin{bmatrix} C_1 & C_2 \end{bmatrix} \begin{bmatrix} r_1 \\ r_2 \end{bmatrix} = \begin{bmatrix} l(0) \\ l(1) \\ \vdots \\ l(n) \end{bmatrix}$$

$N \times 2$                        $2 \times 1$                        $N \times 1$

"optimization"

$$Ck = l$$

$$(C^T C)k = C^T l$$

$$\vec{k} = [k_1, k_2]$$

$$\vec{k}^* = (C^T C)^{-1} (C^T l)$$

pseudo-inverse


least mean square  
(LMS) data fitting

In  $\Delta\Sigma$  Toolbox  $\rightarrow$  `realize_NTF_ct()`

$\uparrow$   $L(z), (k, \beta)$

$\downarrow$   $L(s)$

$\leftarrow$  use numerical fitting

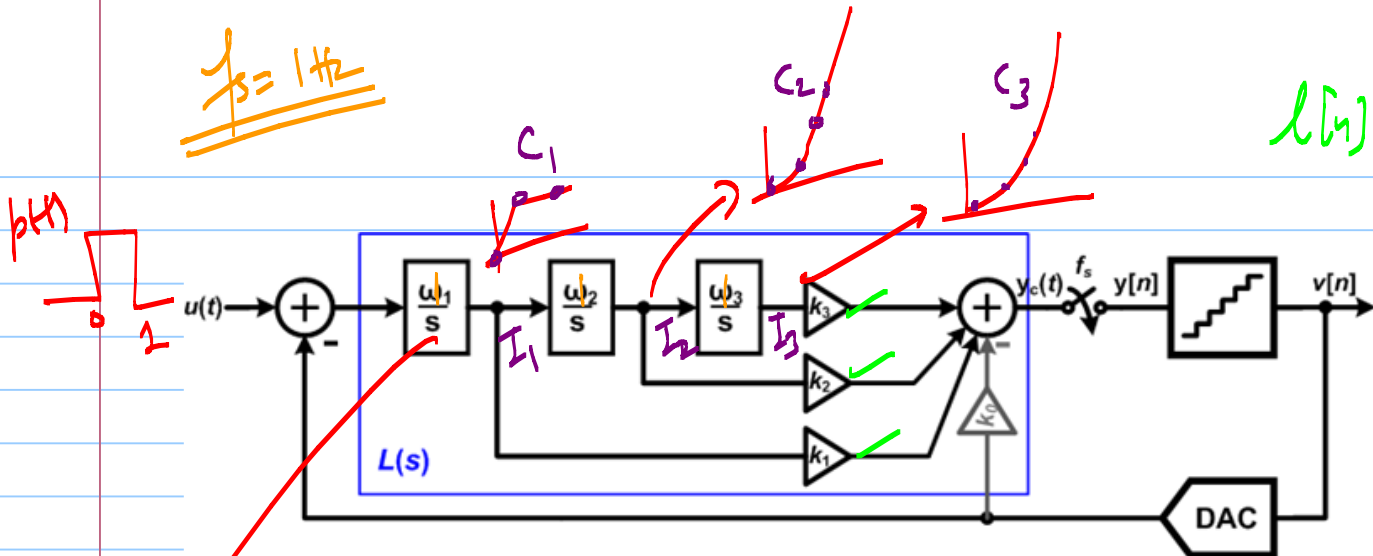

$$\begin{bmatrix} c_1 & c_2 & c_3 \end{bmatrix} \begin{bmatrix} k_1 \\ k_2 \\ k_3 \end{bmatrix} = \begin{bmatrix} \lambda(0) \\ \lambda(1) \\ \lambda(2) \\ \vdots \end{bmatrix}$$

