


ECE615 Mixed-Signal IC Design

Discrete-Time $\Delta\Sigma$ Modulator Implementation



Vishal Saxena
(vishalsaxena@boisestate.edu)

Analog Mixed Signal IC Laboratory
Boise State University

Review: A $\Delta\Sigma$ ADC System


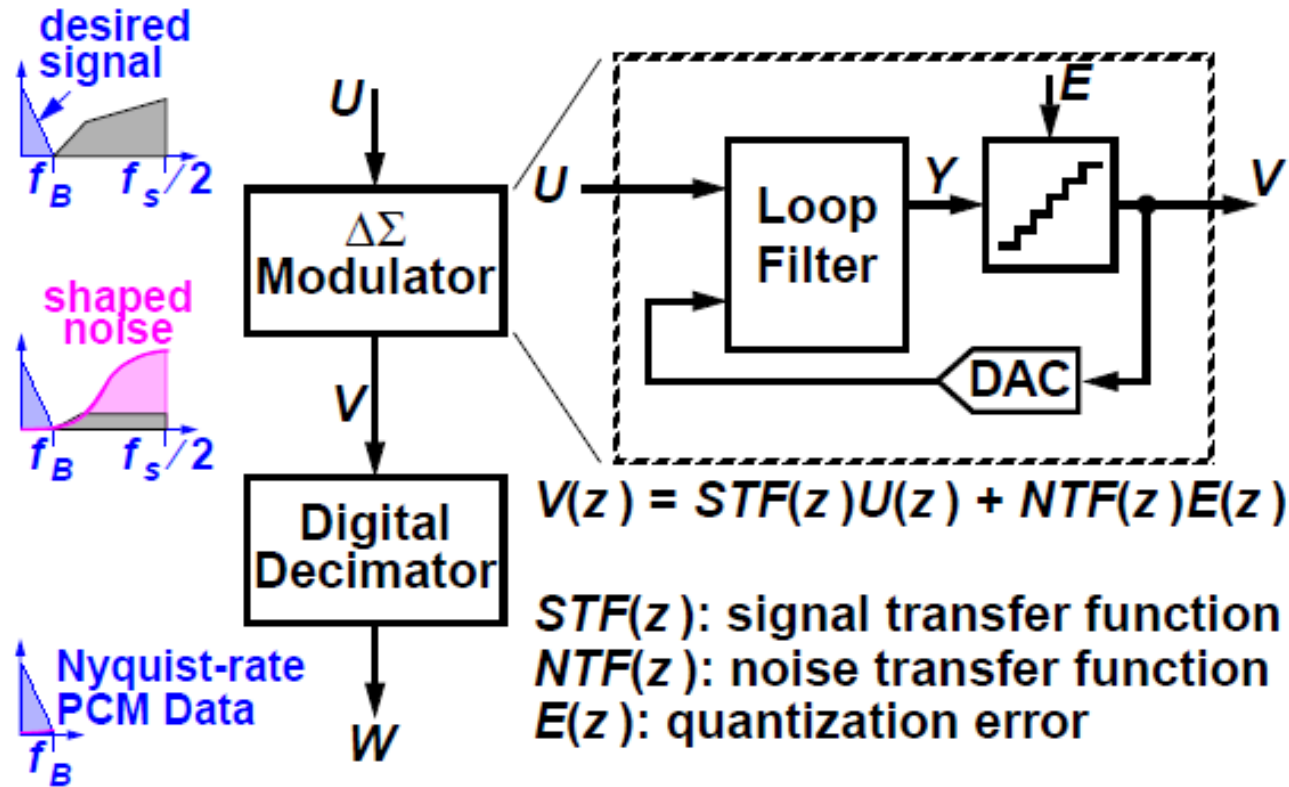


Review: MOD1

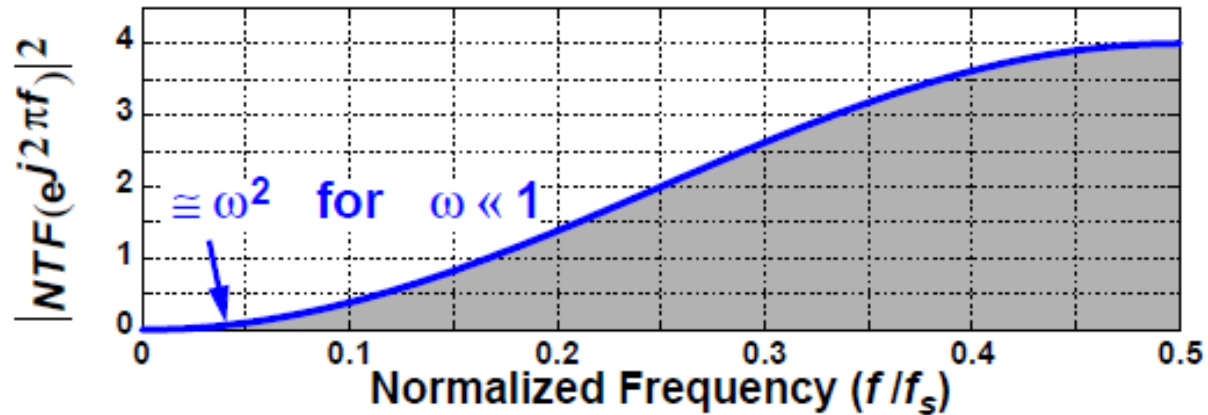 

- Doubling OSR improves SQNR by 9 dB
Peak SQNR $\approx \text{dbp}(9 \cdot \text{OSR}^3 / (2\pi^2))$; $\text{dbp}(x) \equiv 10\log_{10}(x)$


Review: MOD2

  

- **Doubling OSR improves SQNR by 15 dB**
Peak SQNR $\approx \text{dbp}((15 \cdot \text{OSR}^5)/(4\pi^4))$


Review: Simulated MOD2 PSD

Input at 50% of FullScale

 


Example Design: 2nd-order Modulator

Parameter	Symbol	Value	Units
Bandwidth	f_B	1	kHz
Sampling Frequency	f_s	1	MHz
Signal-to-Noise Ratio	SNR	100	dB
Supply Voltage	VDD	3	V

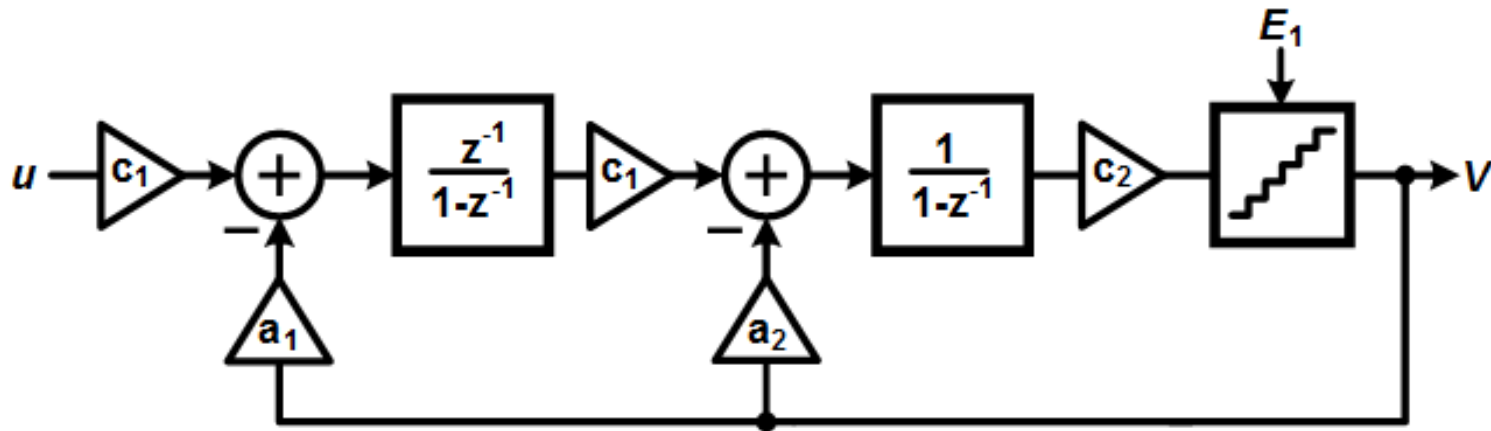

NTF Design


Block Diagram

 


- ❑ Summation blocks
- ❑ Delaying and non-delaying discrete-time integrators
- ❑ Quantizer (1-bit)
- ❑ Feedback DACs (1-bit)
- ❑ Decimation filter (not shown)
 - Digital and therefore “easy”

Switched-Capacitor Integrator

Single-ended circuit:

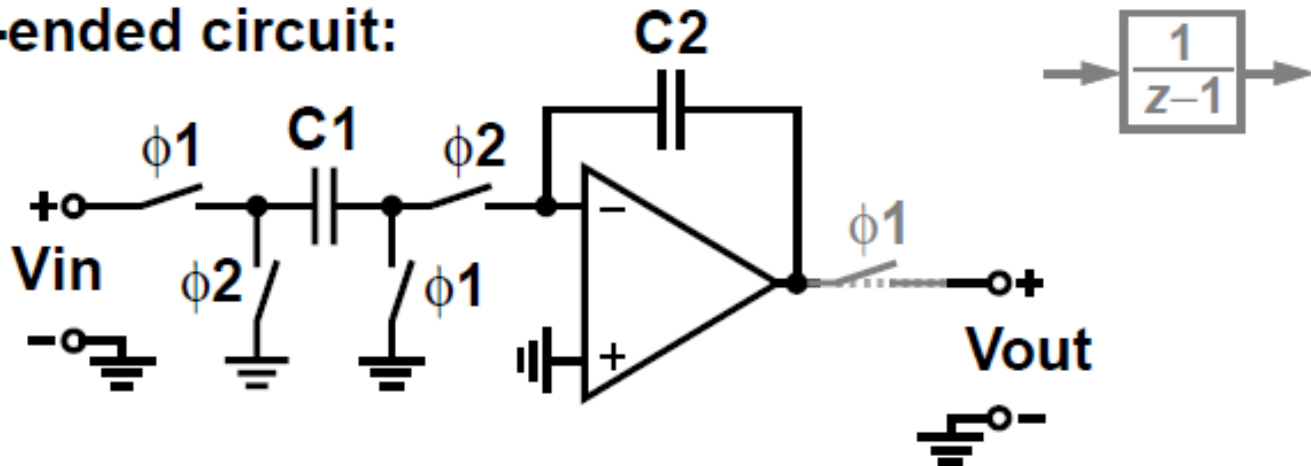


Timing:

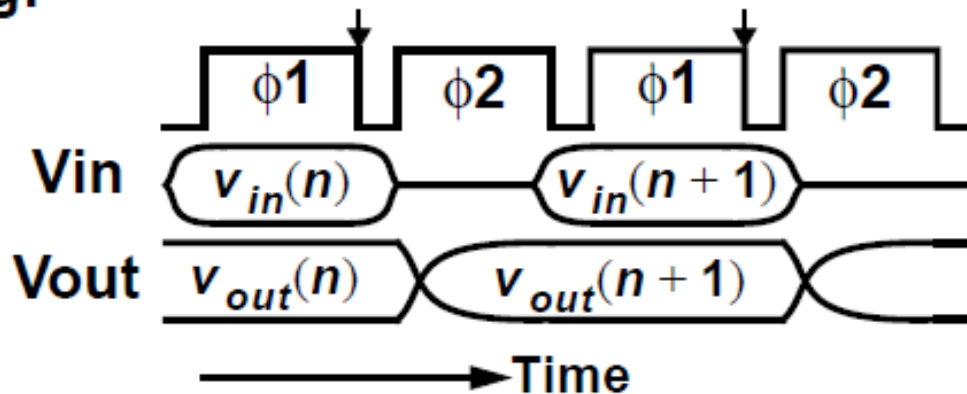


Switched-Capacitor Integrator contd.


Single-ended circuit:

 


Timing:

 

$\phi 1$:

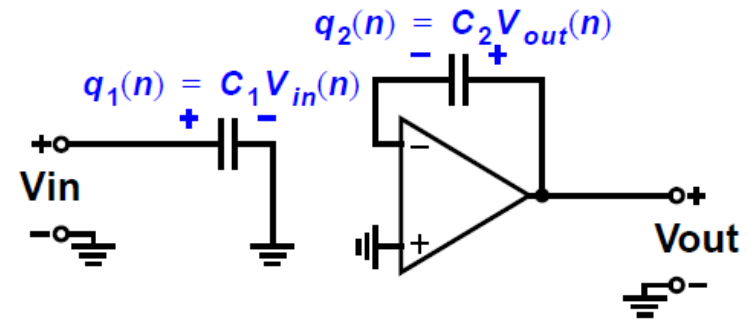

$\phi 2$:

 

Switched-Capacitor Integrator contd.

$$q_2(n+1) = q_2(n) + q_1(n)$$

$$zQ_2(z) = Q_2(z) + Q_1(z)$$


$$Q_2(z) = \frac{Q_1(z)}{z-1}$$

- This circuit integrates charge
- Since $Q_1 = C_1 V_{in}$ and $Q_2 = C_2 V_{out}$

$$\frac{V_{out}(z)}{V_{in}(z)} = \frac{C_1/C_2}{z-1}$$


- Note that the voltage gain is controlled by a *ratio* of capacitors
With careful layout, 0.1% accuracy is possible.

Summation and Integration

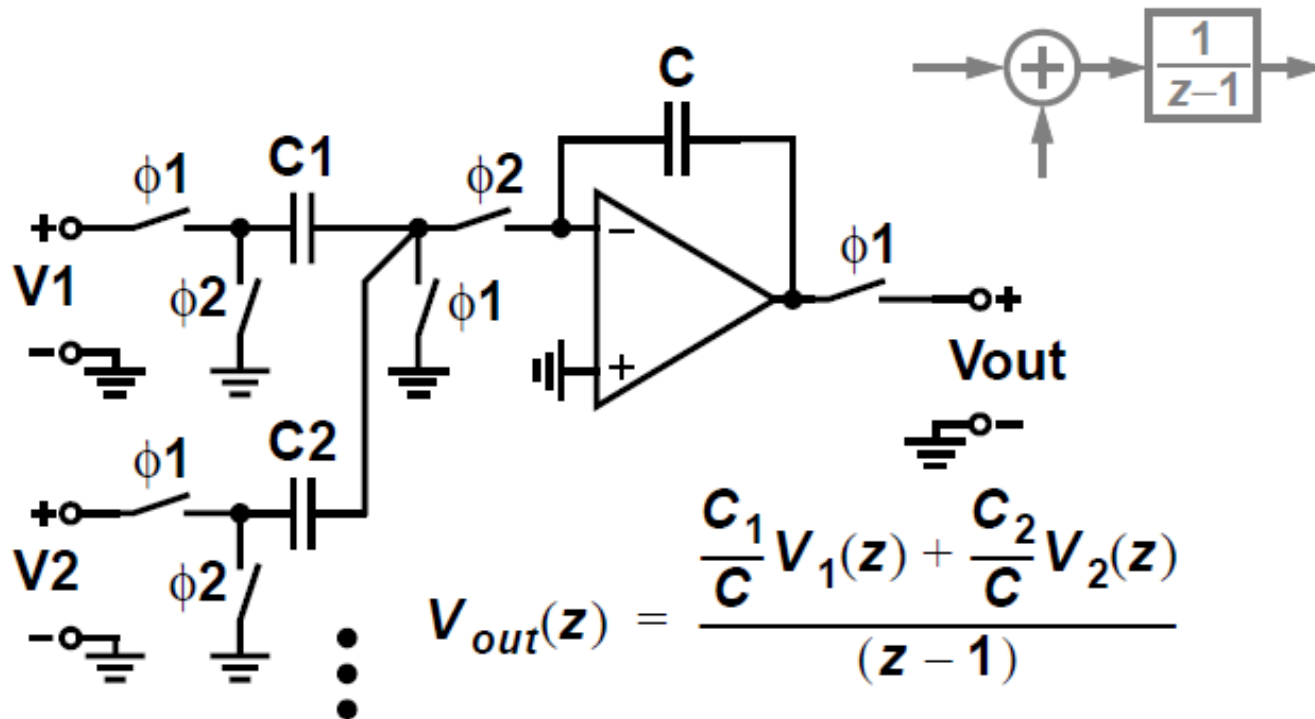


- Adding an extra input branch accomplishes addition, with weighting

1-bit DAC + Summation + Integration

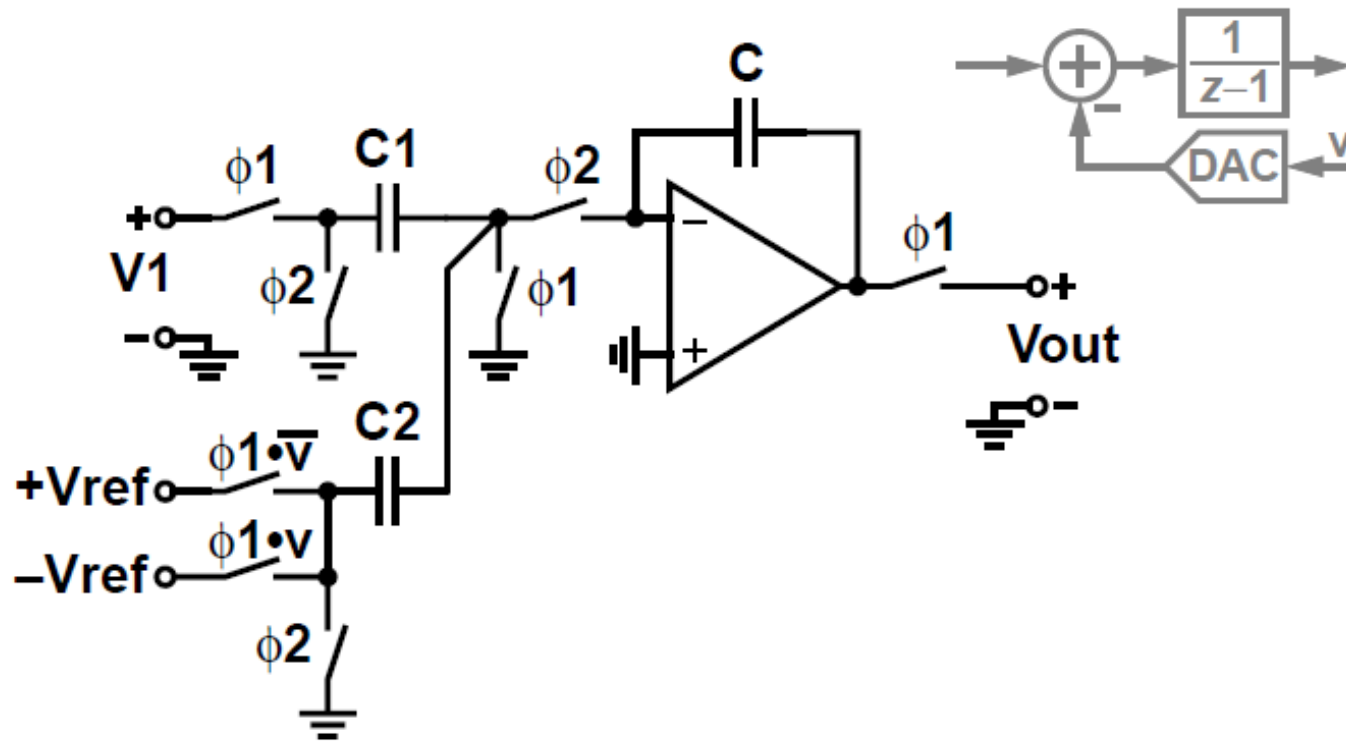


- 1-bit DAC by switching between references ($\pm V_{ref}$)

Fully-Differential Integrator

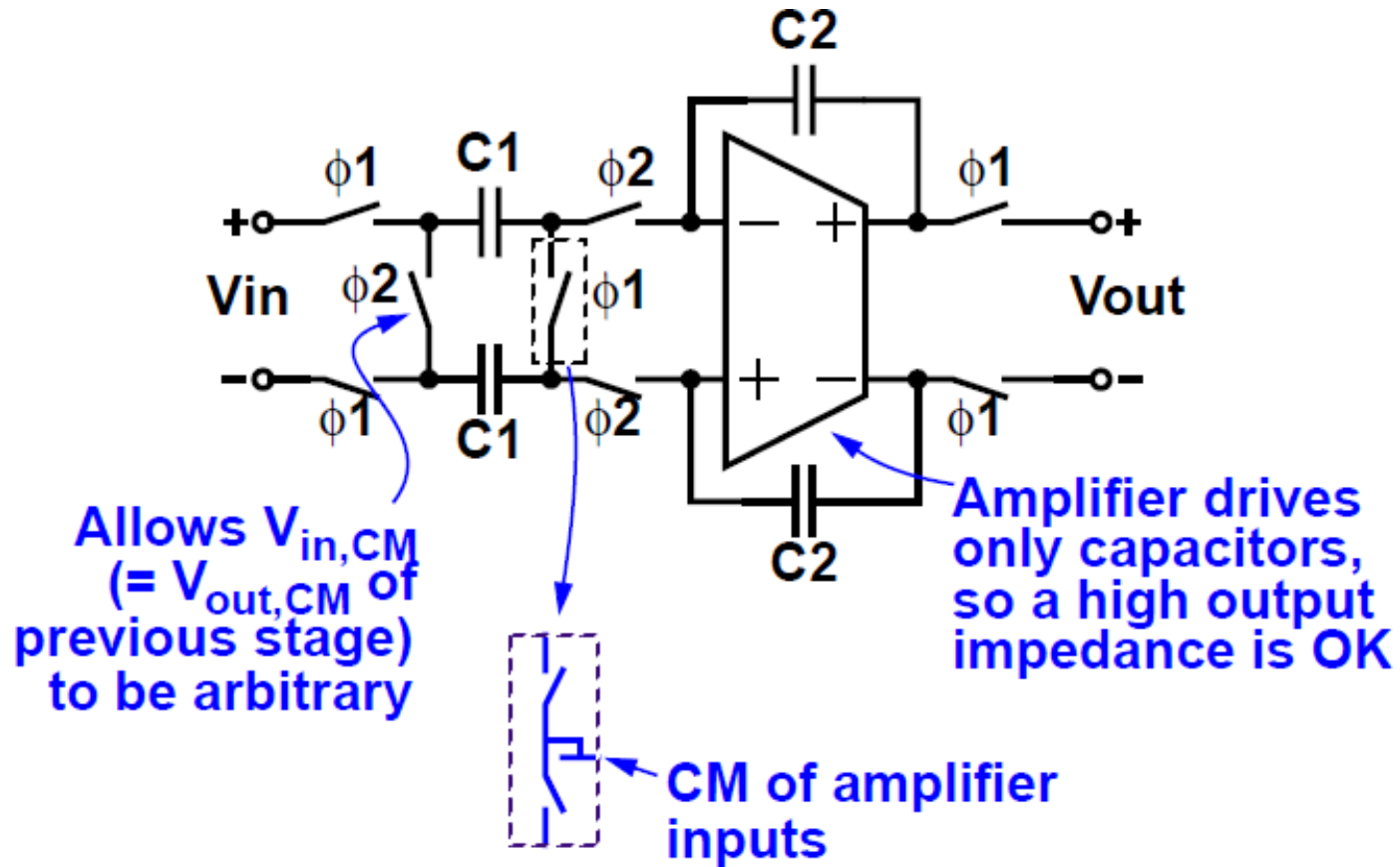


Non-Delaying Integrator

Single-ended circuit:

 


Timing:

 


Non-Delaying Integrator contd.


Single-ended circuit:

 


Timing:

 

$\phi 2$:

 

$\phi 1$:

 

Non-Delaying Integrator contd.

$$q_2(n+1) = q_2(n) - q_1(n+1)$$

$$zQ_2(z) = Q_2(z) - zQ_1(z)$$


$$\frac{Q_2(z)}{Q_1(z)} = -\frac{z}{z-1}$$

$$\frac{V_{out}(z)}{V_{in}(z)} = -\left(\frac{C_1}{C_2}\right)\frac{z}{z-1}$$


- **Delaying (and inverting) integrator**

Half-Delay Integrator

Single-ended circuit:

 

Timing:

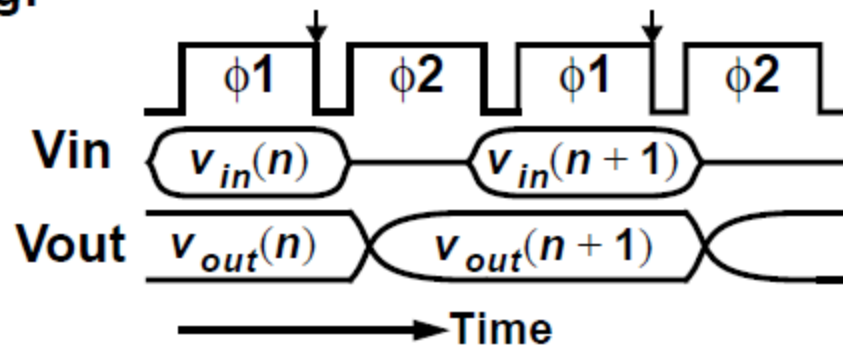

Half-Delay Integrator

- Output is sampled on a different phase than the input
- Some use the notation to denote the shift in sampling time


$$H(z) = \frac{z^{-1/2}}{z - 1}$$

- An alternative method is to declare that the border between time n and $n+1$ occurs at the end of a specific phase, say φ_2
- A circuit which samples on φ_1 and updates on φ_2 is non-delaying, i.e. $H(z) = z/(z - 1)$

whereas a circuit which samples on φ_2 and updates on φ_1 is delaying, i.e. $H(z) = 1/(z - 1)$

Timing in a $\Delta\Sigma$ Modulator

 - The safest way to deal with timing is to construct a timing diagram and verify that the circuit implements the desired difference equations
- E.g. MOD2:




- Difference Equations:


Eq.0: $v(n) = Q(x_2(n))$

Eq.1: $x_1(n+1) = x_1(n) - v(n) + u(n)$

 
Eq.2: $x_2(n+1) = x_2(n) - v(n) + x_1(n+1)$



Switched-Capacitor Realization

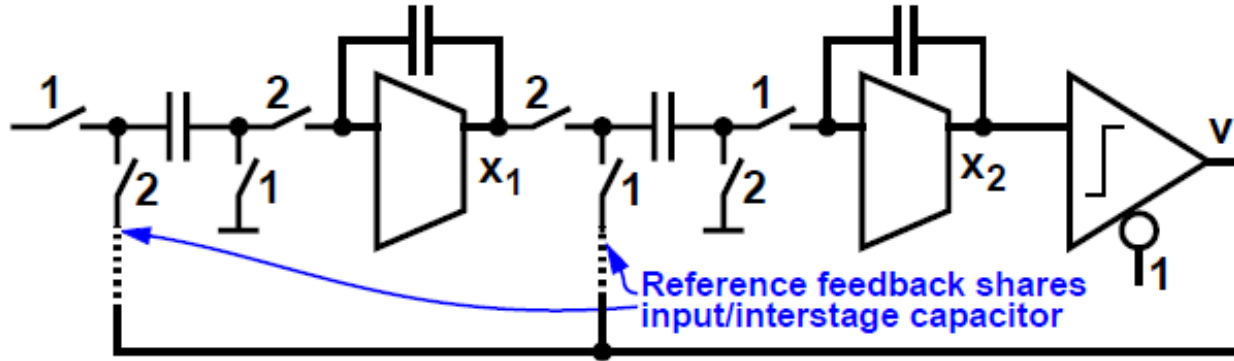

Timing

 


Timing looks OK!

Difference Equations:

Eq.0: $v(n) = Q(x_2(n))$

Eq.1: $x_1(n+1) = x_1(n) - v(n) + u(n)$

 Eq.2: $x_2(n+1) = x_2(n) - v(n) + x_1(n+1)$




Signal Swing

- So far, we have not paid any attention to how much linear swing the op amps can support, or to the magnitudes of u , V_{ref} , x_1 and x_2
- For simplicity, assume:
 - the full-scale range of u is $\pm 1\text{V}$
 - the opamp swing is also $\pm 1\text{V}$ and
 - $V_{\text{ref}} = \pm 1\text{V}$
- We still need to know the ranges of x_1 and x_2 in order to accomplish *dynamic-range scaling*


Dynamic Range Scaling

- In a linear system with known state bounds, the states can be scaled to occupy any desired range
- Use state-space similarity transform for dynamic range scaling

e.g. one state of original system

 


The state scaled by $1/k$

 

State Swings in MOD2

- Using linear theory

 

$$V = z^{-1}U + (1 - z^{-1})^2 E$$



$$X_1 = \frac{z}{z-1}(U - V) = U - (1 - z^{-1})E$$

$$X_2 = V - E = z^{-1}U + (-2z^{-1} + z^{-2})E$$



- If u is constant and E is white with power $\sigma_e^2 = 1/3$, then
 - Mean $(x_1) = u$ and $\sigma_{x_1}^2 = 2\sigma_e^2 = 2/3$
 - Mean $(x_2) = u$ and $\sigma_{x_2}^2 = 5\sigma_e^2 = 5/3$

Simulated Histograms

$u = -0.1$

  


$u = 0.7$

  



Scaled MOD2

- Take $\|x_1\|_\infty=3$ and $\|x_2\|_\infty=9$
 - The first integrator should not saturate
 - The second integrator will not saturate for DC inputs up to -3 dBFS and possibly as high as -1 dBFS.
- Our scaled version of MOD2 is then

 

First Integrator (INT1)

- Share Input and Reference Caps

  

- What is the optimal value for C ?

Obtaining the Coefficients

```
H = synthesizNTF(2,500,0,2);  
form = 'CIFB';  
[a,g,b,c] = realizNTF(H,form);  
b(2:end) = 0;  
ABCD = stuffABCD(a,g,b,c,form);  
[ABCDs umax] = scaleABCD(ABCD);  
[a,g,b,c] = mapABCD(ABCDs,form);
```



Voltage Scaling from the Toolbox

- ❑ **Translation of toolbox block diagram to a practical circuit.**
 - **Toolbox assumes the input of a single-bit modulator ranges from -1 to +1**
 - **The default DRS is also such that the integrator states occupy the [-1,1] range**
 - **The toolbox quantizer LSB size is 2 units**
- ❑ **However, in analog circuits the range must have physical units and match the voltage limits set by the technology**
- ❑ **Example:**
 - **Lets say the FS input is 3V, whereby the toolbox value is 2**
 - **Lets assume that the amplifier supports a diff swing of 2Vpp (same as the toolbox)**

Voltage Scaling Example

  Example:

- Lets say the FS input is 3V, whereby the toolbox value is 2
- Lets assume that the amplifier supports a diff swing of 2V_{pp} (same as the toolbox)



- Relationship between the circuit variables and the state variables are

$$x_1 = \frac{v_{x1}}{1V},$$

$$u = \frac{v_{in} - 1.5V}{1.5V}$$

$$v = 2v_d - 1$$

Voltage Scaling Example contd.

- The difference equation we need to implement is

$$x_1(n+1) = x_1(n) + b_1 u(n) - a_1 v(n)$$

where $a_1 = b_1 = 1/4$. The circuit equation becomes

$$\begin{aligned} v_{x1}(n+1) &= v_{x1}(n) + \frac{b_1 [v_{in}(n) - 1.5 \text{ V}]}{1.5} - a_1 [2v_d(n) - 1] \cdot 1 \text{ V} \\ &= v_{x1}(n) + \frac{v_{in}(n)}{6} - 0.5 \text{ V} \cdot v_d(n) \end{aligned}$$

The equation from the circuit implementation


$$v_{x1}(n+1) = v_{x1}(n) + \frac{2C_1}{C_2} v_{in}(n) - \frac{2C_1}{C_2} V_{DD} v_d(n)$$

The capacitor ratio of the input and integrating capacitors needs to be

$$C_1/C_2 = 1/12.$$

With $V_{DD} = 3 \text{ V}$, the above ratio also gives the correct coefficient for v_d .

Thermal - kT/C - Noise

 

□ **From ECE 614 Noise Analysis:**


Regardless of the value of R , the mean square value of the voltage on C is

$$\overline{v_n^2} = \frac{kT}{C}$$

where $k = 1.38 \times 10^{-23}$ J/K is *Boltzmann's constant* and T is the temperature in Kelvin


Noise in SC Integrator

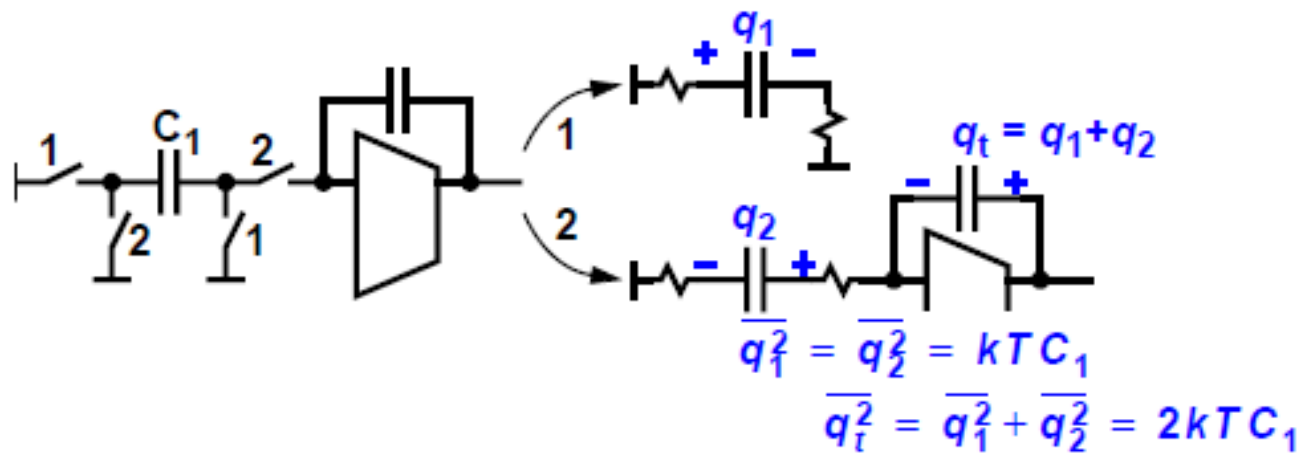- Each charge/discharge operation has a random component
 - The amplifier plays a role during phase 2, but lets assume that the noise in both phases is just kT/C .
- For a given cap, these random components are essentially uncorrelated, so the noise is white




Noise in SC Integrator contd.

 - This noise charge is equivalent to a noise voltage with ms value $v_n^2 = 2kT/C_1$ added to the input of the integrator:



- This noise power is spread uniformly over all frequencies from 0 to $f_s/2$
- The power in the signal band $[0, f_B]$ is v_n^2/OSR

Differential Noise

 

- Twice as many switched caps
⇒ twice as much noise power
- The input-referred noise power in our differential integrator is
- $V_n^2 = 4kT/C_1$

INT1 Cap Sizes

For SNR = 100 dB @ -3-dBFS input

- The signal power is

$$\overline{v_s^2} = \frac{1}{2} \cdot \frac{(1 \text{ V})^2}{2} = 0.25 \text{ V}^2$$

-3 dBFS $\frac{A^2}{2}$



- Therefore we want $\overline{v_{n, \text{in-band}}^2} = 0.25 \times 10^{-10} \text{ V}^2$
- Since $\overline{v_{n, \text{in-band}}^2} = \overline{v_n^2} / \text{OSR}$

$$C_1 = \frac{4kT}{\overline{v_n^2}} = 1.33 \text{ pF}$$

- If we want 10 dB more SNR, we need 10x caps


Second Integrator (INT2)

- Separate Input and Feedback Caps

 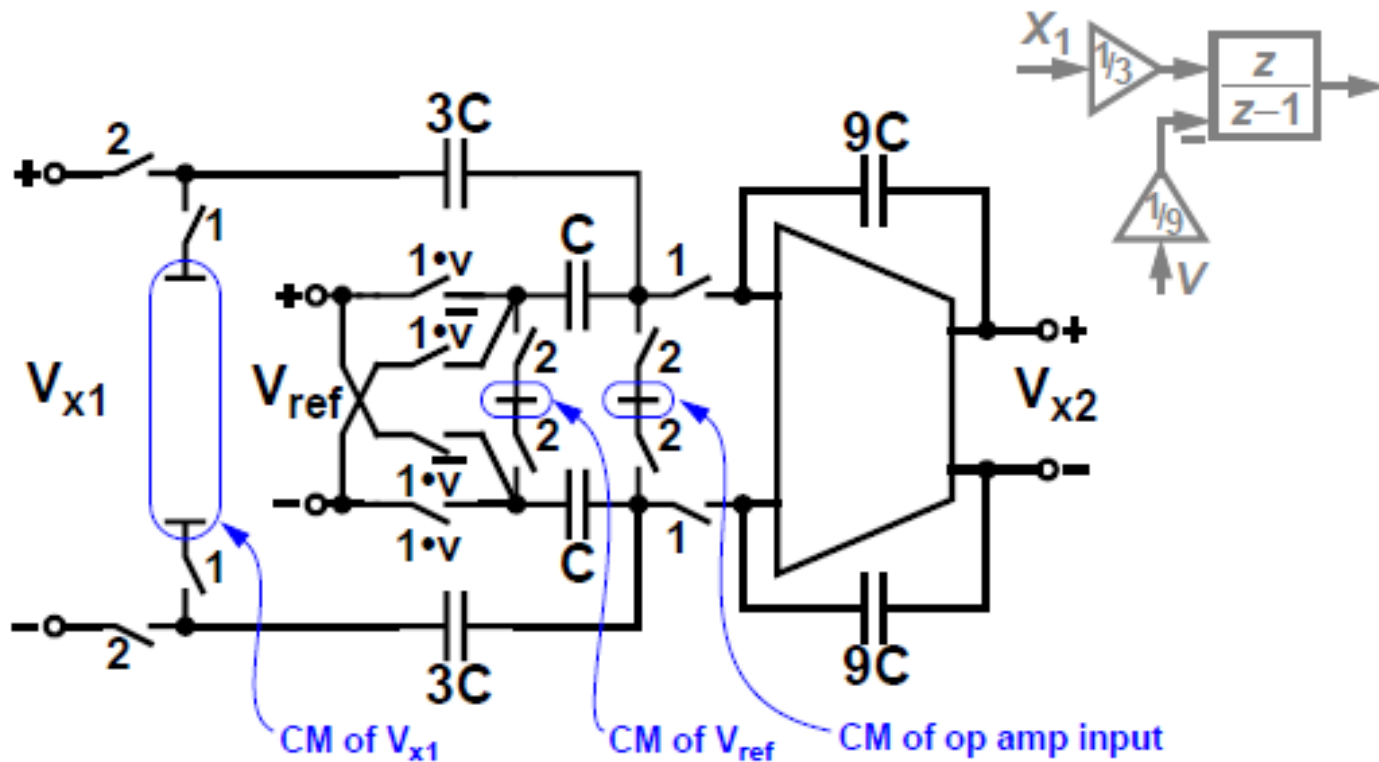

2nd Integrator Cap Sizes

 - In-band noise of second integrator is greatly attenuated



$$\omega_B = \frac{\pi}{OSR}$$

$$\text{INT1 gain @ pb edge: } A = \frac{1/3}{\omega_B} = \frac{OSR}{3\pi}$$


$$\text{INT2 noise attenuation: } > OSR \cdot A^2 \approx 10^6$$

⇒ Capacitor sizes not dictated by thermal noise

- Charge injection errors and desired ratio accuracy set absolute size

A reasonable size for a small cap is currently ~10 fF.

Behavioral Schematic for SwitCap MOD2

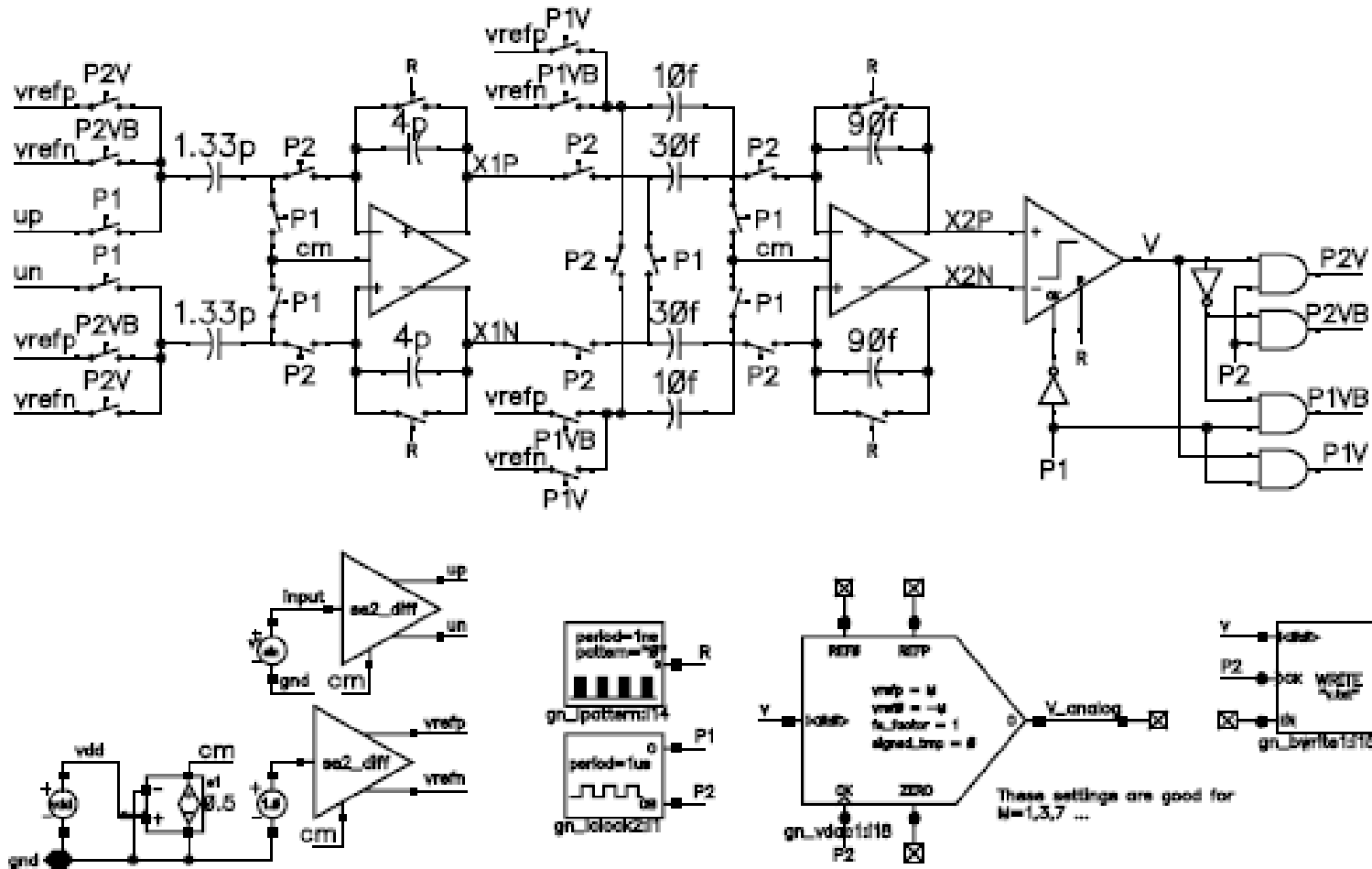


Verification

- ❑ **Open-loop Verification**
- ❑ **Loop filter**
- ❑ **Comparator**
 - In case of a single-bit integrator only polarity and timing can go wrong
- ❑ **Closed-loop Verification**
 - Swing of internal states
 - Spectrum: SQNR, STF gain
 - Sensitivity, start-up, overload recovery,...

Loop-Filter Check - Theory

 - Open-loop the feedback loop, set $u=0$, and drive an impulse through the feedback path




$$X_2 = \frac{-1}{z-1} \left(1 + \frac{z}{z-1} \right) Y$$

$$\therefore y(n) = \{1, 0, 0, \dots\} \Rightarrow x_2(n) = \{-2, -3, -4, \dots\}$$

- If $y=x_2$ is as predicted then the open-loop response, $-L(z)$, is correct
=> The correct NTF will be realized by the circuit

Loop-Filter Check - Simulation

□ But....

 


Loop-Filter Check - Specifics


- ❑ An impulse response is $\{1,0,0,0\}$, but a binary DAC can only output ± 1 , i.e. it can't produce a zero
- ❑ **Q:** So how can we determine the impulse response of the loop filter through simulation?
- ❑ **A:** Do two simulations: one with $v=\{-1,-1,-1,\dots\}$ and one with $v=\{+1,-1,-1,\dots\}$.
- ❑ Then take the difference.
- ❑ According to linear superposition, the result is the response to $v=\{2,0,0,\dots\}$, so divide by 2.
 - To keep the integrator states from growing too quickly, one could also use $v=\{-1,-1,+1,-1,\dots\}$ and then $v=\{+1,-1,+1,-1,\dots\}$

Simulated State Swings

- **-3-dBFS ~300-Hz sine wave**

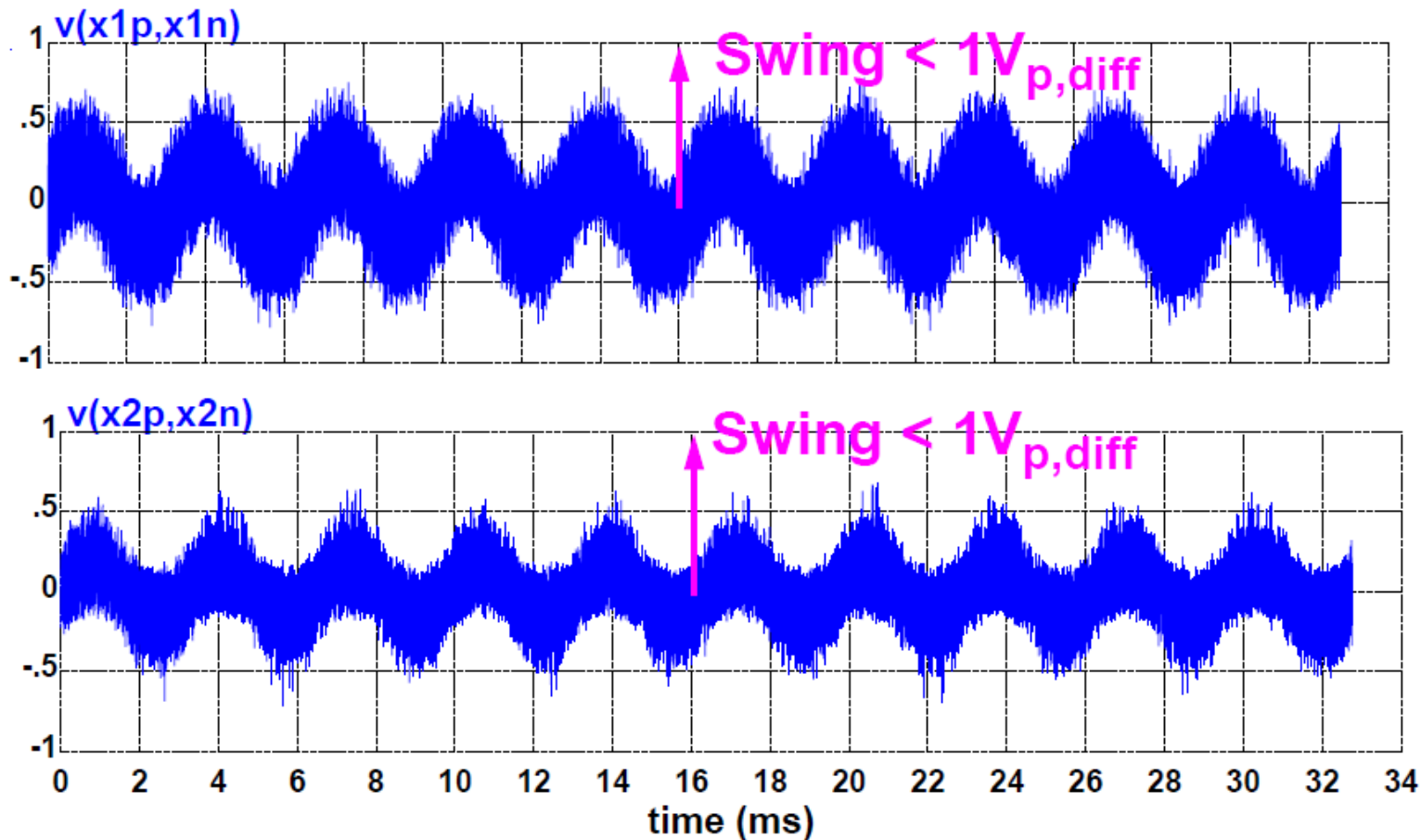


Rookie Spectrum

 

Professional Spectrum

- SNDR dominated by -109-dBFS 3rd harmonic

Professional Spectrum

 


Implementation Summary

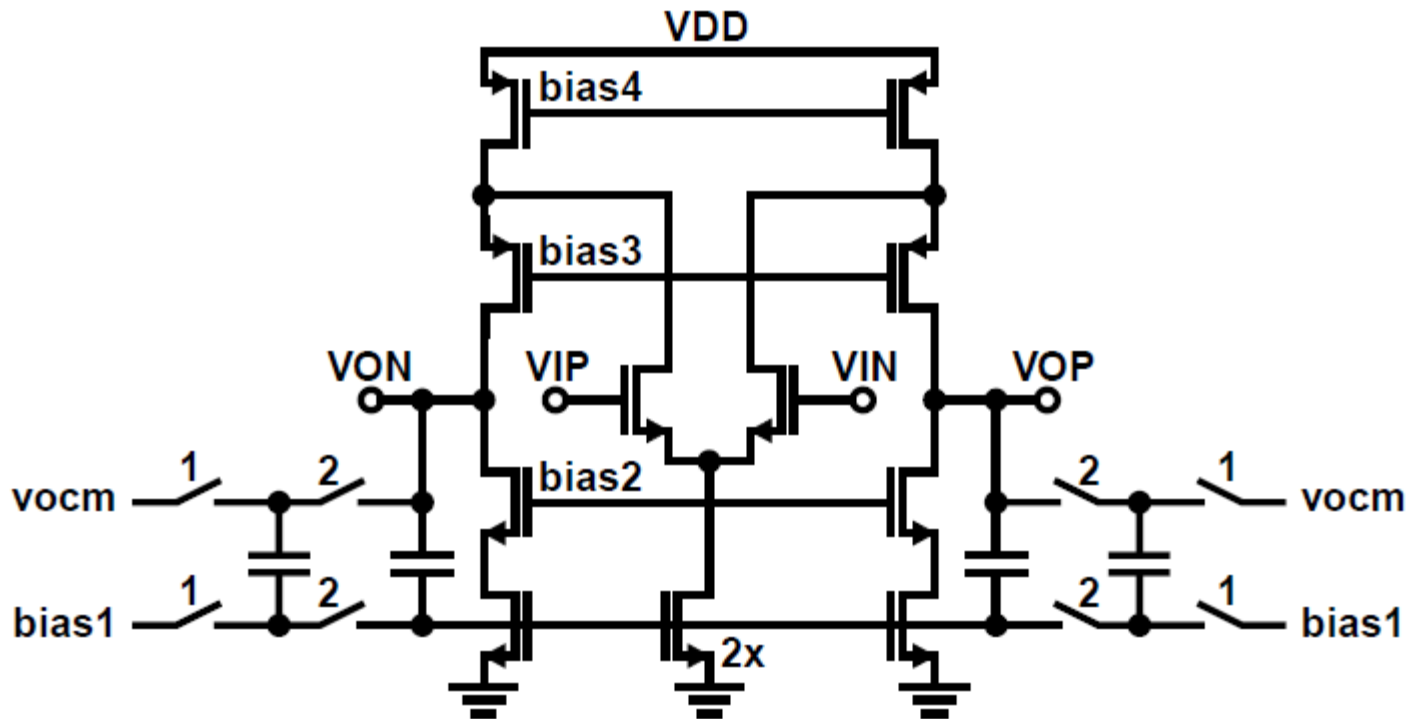1. **Choose a viable SC topology and manually verify timing**
2. **Do coefficient quantization and dynamic-range scaling**
 - You now have a set of capacitor ratios.
 - Verify operation: loop filter, timing, swing, spectrum.
3. **Determine absolute capacitor sizes**
 - Verify noise.
4. **Determine op-amp specs and construct a transistor-level schematic**
 - Verify everything.
5. **Layout, fabricate, debug, publish/market!**

Building Block - Opamp


- **Folded-cascode op-amp with switched-capacitor common-mode feedback**



Effect of Finite Opamp Gain

Linear Theory

 - Suppose that the amplifier has finite DC gain A . Define $\mu = 1/A$.
- To determine the effect on the integrator pole, let's look at our SC integrator with zero input:



Effect of Finite Opamp Gain


- A fraction of q_2 leaks away each clock cycle:

$$q_2(n+1) = (1 - \varepsilon)q_2(n),$$

$$\text{where } \varepsilon = \mu C_1 / C_2$$

- Thus, the integrator is lossy, with a pole at $z = 1 - \varepsilon$

 Q: How big can ε get before the effect becomes significant?



Linear Theory

- According to the linear theory, finite op amp gain should not degrade the noise significantly as long as

$$A > (C_1 / C_2)(OSR / \pi)$$

- For our implementation of MOD2, in which $C_1 / C_2 = 1/4$ and $OSR = 500$, this leads to

$$A > 40 = 32 \text{ dB},$$


which is quite a lax requirement!

- As OSR is decreased, the gain requirement goes down

Opamp Transconductance

Settling time

- Model the op amp as a simple g_m :

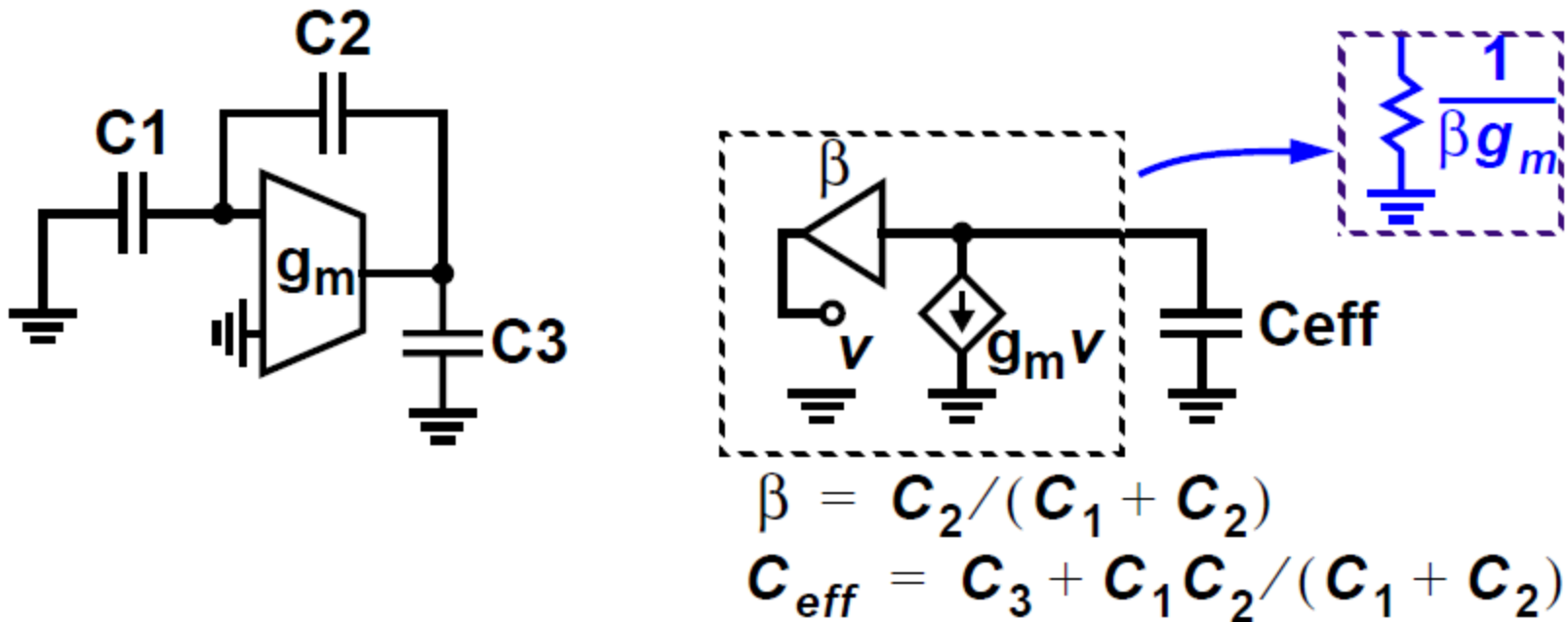

- This is a single-time-constant-circuit with $\tau = C_{eff} / (\beta g_m)$

Opamp Settling Requirements

- If g_m is linear, incomplete settling has the same effect as a coefficient error and thus g_m can be very low
- In practice, the g_m is not linear and we need to ensure nearly complete settling
- As a worst case scenario, let's require transients to settle to 1 part in 10^5
This should be more than enough for -100 dBc distortion.

Opamp Settling Requirements contd.

- If linear settling is allocated 1/4 of a clock period,

we want $\exp\left(-\frac{T/4}{\tau}\right) = 10^{-5}$, or $\tau = \frac{T}{4 \ln 10^5} = 20 \text{ ns}$

and thus $g_m = \frac{C_{eff}}{\beta \tau} = \frac{C_{eff}}{\beta} 4 f_s \ln 10^5$

- For INT1 of our MOD2:

$$C_{eff} = 0.5 \left(\frac{4\text{p} \cdot 1.33\text{p}}{4\text{p} + 1.33\text{p}} + 30\text{f} \right) = 0.5 \text{ pF}^*$$

$$\beta = 3/4$$


$$f_s = 1 \text{ MHz}$$

$$\Rightarrow g_m = 30 \mu\text{A/V}$$

*. 0.5 comes from the single-ended to differential translation.

Opamp Slewing

 - The maximum charge transferred through C1 is




- If we require the slew current to be enough to transfer q_{max} in $1/4$ of a clock period, then

$$I_{slew} = \frac{q_{max}}{T/4} \approx 5\ \mu\text{A}$$

Opamp Design – Bias Current

Bias Currents

Slew Currents

 

- Slew constraint dictates $I > 5\mu\text{A}$

