


# ECE615 Mixed-Signal IC Design

## Lecture 20: Discrete-Time $\Delta\Sigma$ Modulator Implementation



Vishal Saxena, Boise State University  
([vishalsaxena@boisestate.edu](mailto:vishalsaxena@boisestate.edu))

Analog Mixed Signal IC Laboratory  
Boise State University

# Review: A $\Delta\Sigma$ ADC System


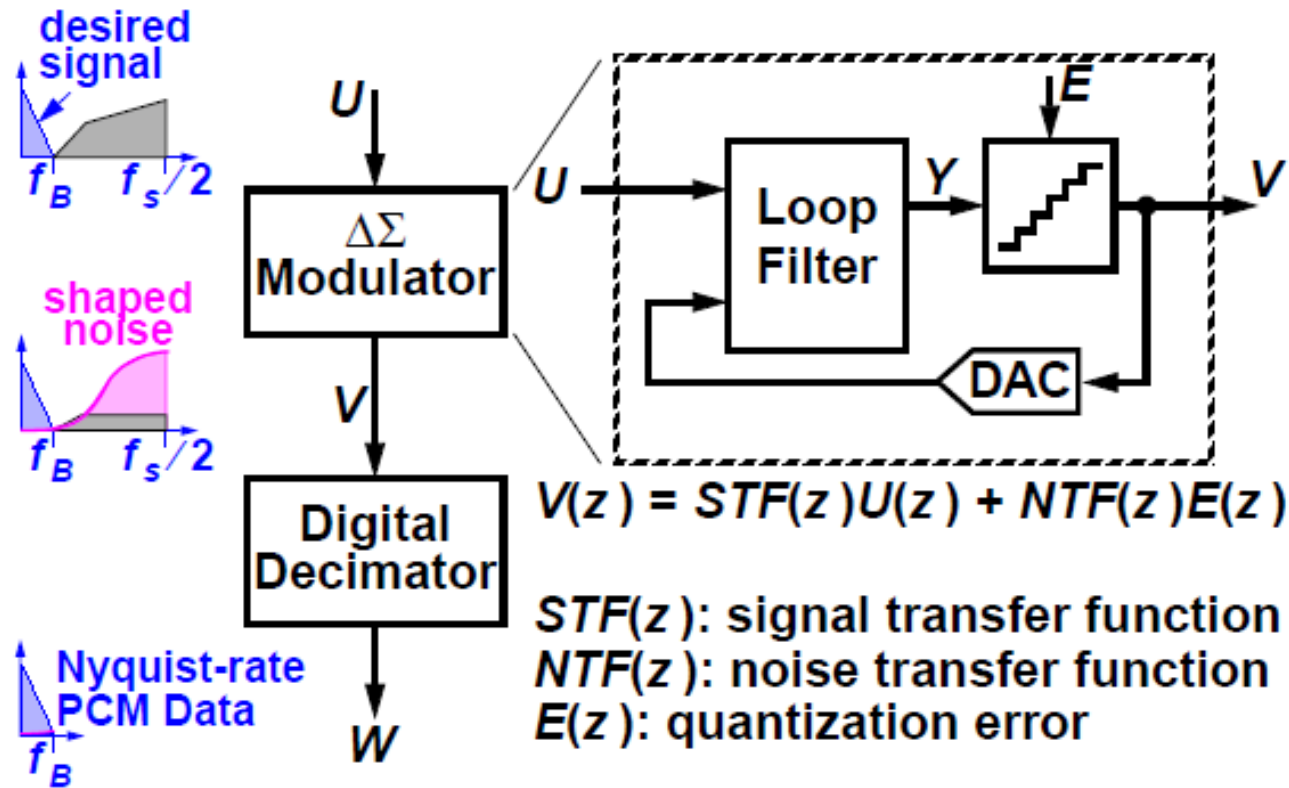


# Review: MOD1

  

- Doubling OSR improves SQNR by 9 dB  
Peak SQNR  $\approx \text{dbp}(9 \cdot \text{OSR}^3 / (2\pi^2))$ ;  $\text{dbp}(x) \equiv 10\log_{10}(x)$


# Review: MOD2

  

- **Doubling OSR improves SQNR by 15 dB**  
Peak SQNR  $\approx \text{dbp}((15 \cdot \text{OSR}^5)/(4\pi^4))$

# Review: Simulated MOD2 PSD

Input at 50% of FullScale

 

# Example Design 1

- Clock at  $f_s = 1 \text{ MHz}$ .

Assume  $BW = 1 \text{ kHz}$ .

$$\Rightarrow OSR = f_s / (2 \cdot BW) = 500 \approx 2^9$$


- MOD1: SQNR  $\approx 9 \text{ dB/octave} \cdot 9 \text{ octaves} = 81 \text{ dB}$
- MOD2: SQNR  $\approx 15 \text{ dB/octave} \cdot 9 \text{ octaves} = 135 \text{ dB}$

Actually more like 120 dB.

- SQNR of MOD1 is not bad, but SQNR of MOD2 is awesome!

MOD2 is usually preferred over MOD1 because MOD2's quantization noise is more well-behaved.


# Block Diagram

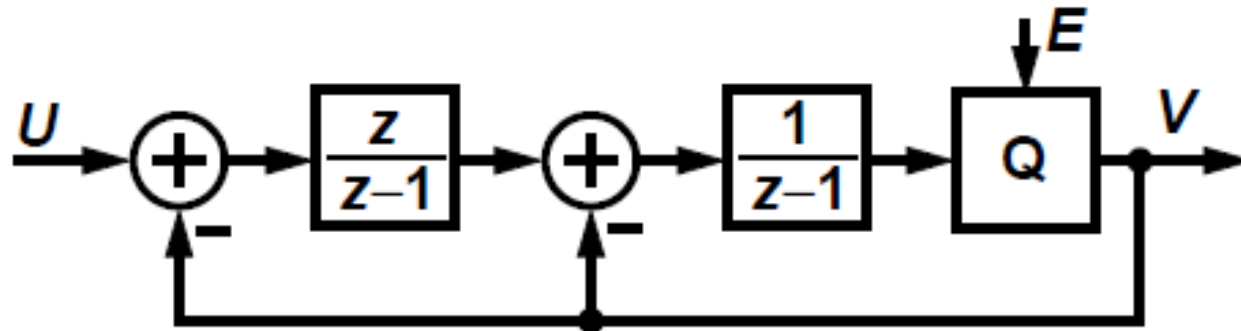


- ❑ Summation blocks
- ❑ Delaying and non-delaying discrete-time integrators
- ❑ Quantizer (1-bit)
- ❑ Feedback DACs (1-bit)
- ❑ Decimation filter (not shown)
  - Digital and therefore “easy”

# Switched-Capacitor Integrator

Single-ended circuit:

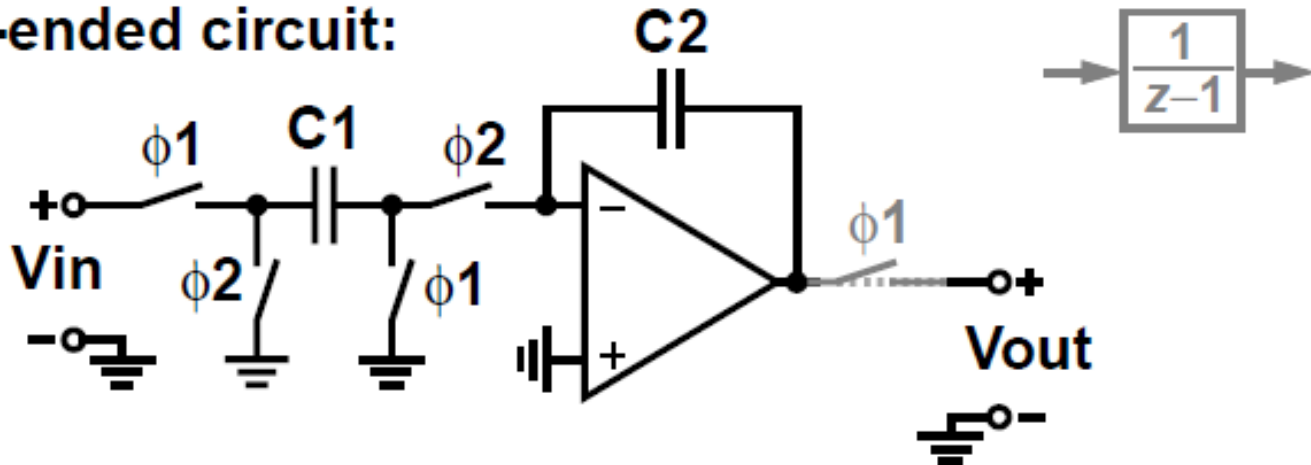


Timing:

 




# Switched-Capacitor Integrator contd.


Single-ended circuit:

 


Timing:

 

$\phi 1$ :

 

$\phi 2$ :

 

# Switched-Capacitor Integrator contd.

$$q_2(n+1) = q_2(n) + q_1(n)$$

$$zQ_2(z) = Q_2(z) + Q_1(z)$$


$$Q_2(z) = \frac{Q_1(z)}{z-1}$$

- This circuit integrates charge
- Since  $Q_1 = C_1 V_{in}$  and  $Q_2 = C_2 V_{out}$

$$\frac{V_{out}(z)}{V_{in}(z)} = \frac{C_1/C_2}{z-1}$$


- Note that the voltage gain is controlled by a *ratio* of capacitors  
With careful layout, 0.1% accuracy is possible.

# Summation and Integration

 


- Adding an extra input branch accomplishes addition, with weighting

# 1-bit DAC + Summation + Integration

 


- 1-bit DAC by switching between references ( $\pm V_{ref}$ )

# Fully-Differential Integrator

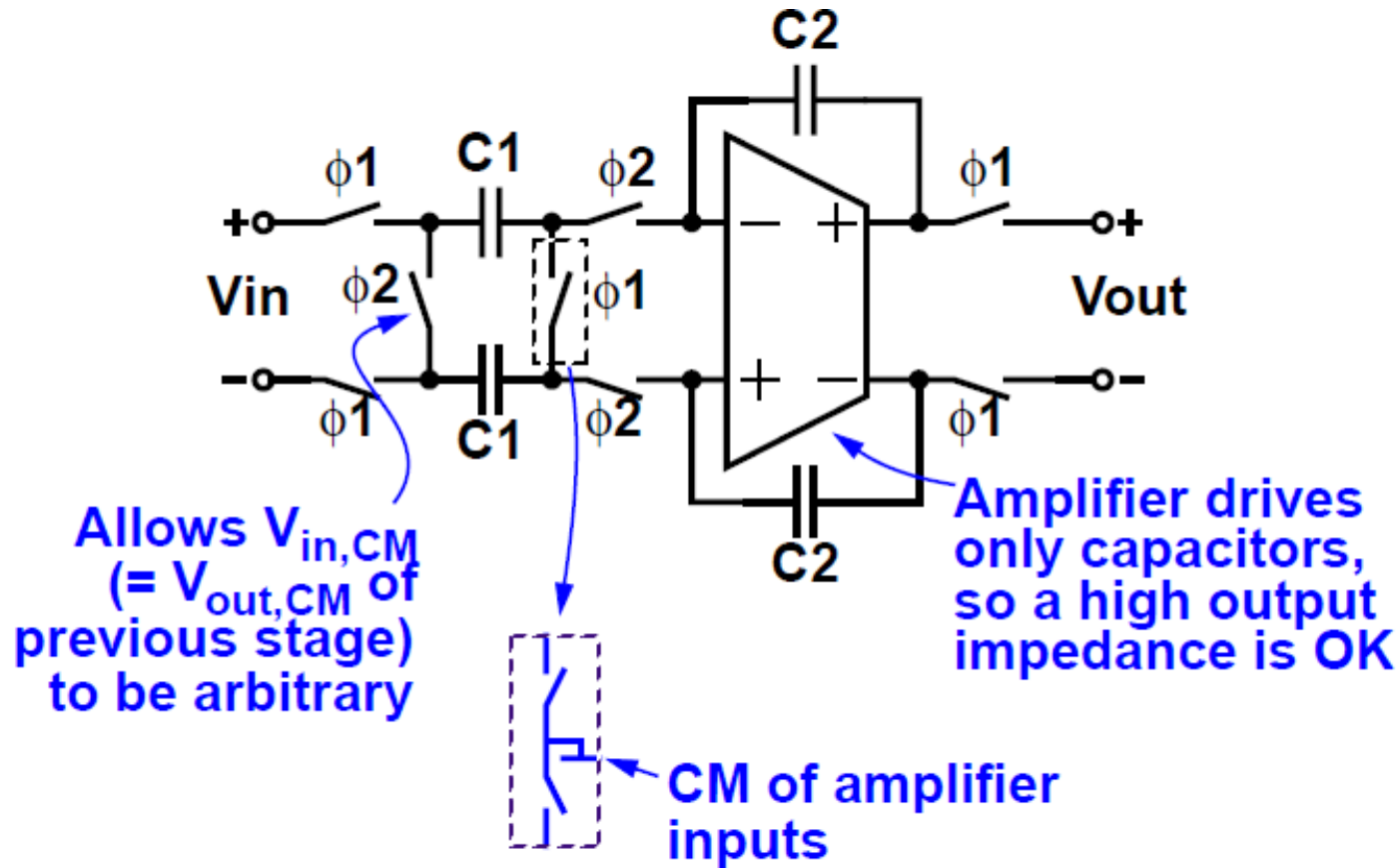


# Non-Delaying Integrator

Single-ended circuit:

 


Timing:

 


# Non-Delaying Integrator contd.


Single-ended circuit:

 


Timing:

 

$\phi 2$ :

 

$\phi 1$ :

 

# Non-Delaying Integrator contd.

$$q_2(n+1) = q_2(n) - q_1(n+1)$$

$$zQ_2(z) = Q_2(z) - zQ_1(z)$$

$$\frac{Q_2(z)}{Q_1(z)} = -\frac{z}{z-1}$$


$$\frac{V_{out}(z)}{V_{in}(z)} = -\left(\frac{C_1}{C_2}\right)\frac{z}{z-1}$$

- **Delaying (and inverting) integrator**




# Half-Delay Integrator

Single-ended circuit:

 

Timing:

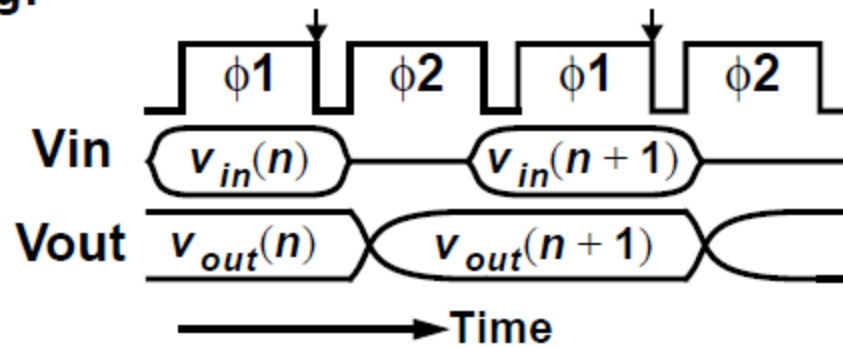

# Half-Delay Integrator

- Output is sampled on a different phase than the input
- Some use the notation to denote the shift in sampling time


$$H(z) = \frac{z^{-1/2}}{z - 1}$$

- An alternative method is to declare that the border between time  $n$  and  $n+1$  occurs at the end of a specific phase, say  $\varphi_2$
- A circuit which samples on  $\varphi_1$  and updates on  $\varphi_2$  is non-delaying, i.e.  $H(z) = z/(z - 1)$

whereas a circuit which samples on  $\varphi_2$  and updates on  $\varphi_1$  is delaying, i.e.  $H(z) = 1/(z - 1)$
 
# Timing in a $\Delta\Sigma$ Modulator

- The safest way to deal with timing is to construct a timing diagram and verify that the circuit implements the desired difference equations
- E.g. MOD2:




- Difference Equations:


**Eq.0:**  $v(n) = Q(x_2(n))$

**Eq.1:**  $x_1(n+1) = x_1(n) - v(n) + u(n)$

 
**Eq.2:**  $x_2(n+1) = x_2(n) - v(n) + x_1(n+1)$



# Switched-Capacitor Realization

 

Timing

 


Timing looks OK!

Difference Equations:

**Eq.0:**  $v(n) = Q(x_2(n))$

**Eq.1:**  $x_1(n+1) = x_1(n) - v(n) + u(n)$

 **Eq.2:**  $x_2(n+1) = x_2(n) - v(n) + x_1(n+1)$




# Signal Swing

- So far, we have not paid any attention to how much linear swing the op amps can support, or to the magnitudes of  $u$ ,  $V_{\text{ref}}$ ,  $x_1$  and  $x_2$
- For simplicity, assume:
  - the full-scale range of  $u$  is  $\pm 1\text{V}$
  - the opamp swing is also  $\pm 1\text{V}$  and
  - $V_{\text{ref}} = \pm 1\text{V}$
- We still need to know the ranges of  $x_1$  and  $x_2$  in order to accomplish *dynamic-range scaling*


# Dynamic Range Scaling

- In a linear system with known state bounds, the states can be scaled to occupy any desired range
- Use state-space similarity transform for dynamic range scaling

e.g. one state of original system

 


The state scaled by  $1/k$

 

# State Swings in MOD2

## □ Using linear theory

 

$$V = z^{-1}U + (1 - z^{-1})^2 E$$

$$X_1 = \frac{z}{z-1}(U - V) = U - (1 - z^{-1})E$$



$$X_2 = V - E = z^{-1}U + (-2z^{-1} + z^{-2})E$$

## □ If $u$ is constant and $E$ is white with power $\sigma_e^2 = 1/3$ , then



- Mean  $(x_1) = u$  and  $\sigma_{x_1}^2 = 2\sigma_e^2 = 2/3$
- Mean  $(x_2) = u$  and  $\sigma_{x_2}^2 = 5\sigma_e^2 = 5/3$

# Simulated Histograms

$u = -0.1$

  


$u = 0.7$

  





# Scaled MOD2

- Take  $\|x_1\|_\infty=3$  and  $\|x_2\|_\infty=9$ 
  - The first integrator should not saturate
  - The second integrator will not saturate for DC inputs up to  $-3$  dBFS and possibly as high as  $-1$  dBFS.
- Our scaled version of MOD2 is then

 


# First Integrator (INT1)

- Share Input and Reference Caps

  

- What is the optimal value for  $C$  ?

# Thermal - $kT/C$ - Noise

 


- From ECE 614 Noise Analysis: Regardless of the value of  $R$ , the mean square value of the voltage on  $C$  is

$$\overline{V_n^2} = \frac{kT}{C}$$

where  $k = 1.38 \times 10^{-23}$  J/K is *Boltzmann's constant* and  $T$  is the temperature in Kelvin

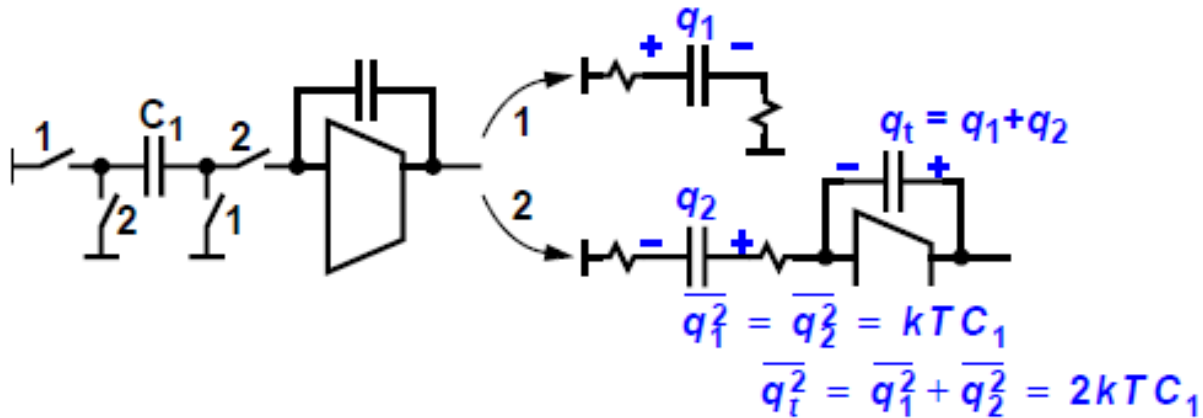
# Noise in SC Integrator

- Each charge/discharge operation has a random component
  - The amplifier plays a role during phase 2, but lets assume that the noise in both phases is just  $kT/C$ .
- For a given cap, these random components are essentially uncorrelated, so the noise is white



 
# Noise in SC Integrator contd.

- This noise charge is equivalent to a noise voltage with ms value  $v_n^2 = 2kT/C_1$  added to the input of the integrator:



- This noise power is spread uniformly over all frequencies from 0 to  $f_s/2$
- The power in the signal band is  $v_n^2/OSR$

# Differential Noise

 

- Twice as many switched caps  
⇒ twice as much noise power
- The input-referred noise power in our differential integrator is
- $V_n^2 = 4kT/C_1$

# INT1 Cap Sizes

**For SNR = 100 dB @ -3-dBFS input**

- The signal power is

$$\overline{v_s^2} = \frac{1}{2} \cdot \frac{(1 \text{ V})^2}{2} = 0.25 \text{ V}^2$$

-3 dBFS                       $\frac{A^2}{2}$


- Therefore we want  $\overline{v_{n, \text{in-band}}^2} = 0.25 \times 10^{-10} \text{ V}^2$
- Since  $\overline{v_{n, \text{in-band}}^2} = \overline{v_n^2} / \text{OSR}$

$$C_1 = \frac{4kT}{\overline{v_n^2}} = 1.33 \text{ pF}$$

- If we want 10 dB more SNR, we need 10x caps

# Second Integrator (INT2)


- Separate Input and Feedback Caps

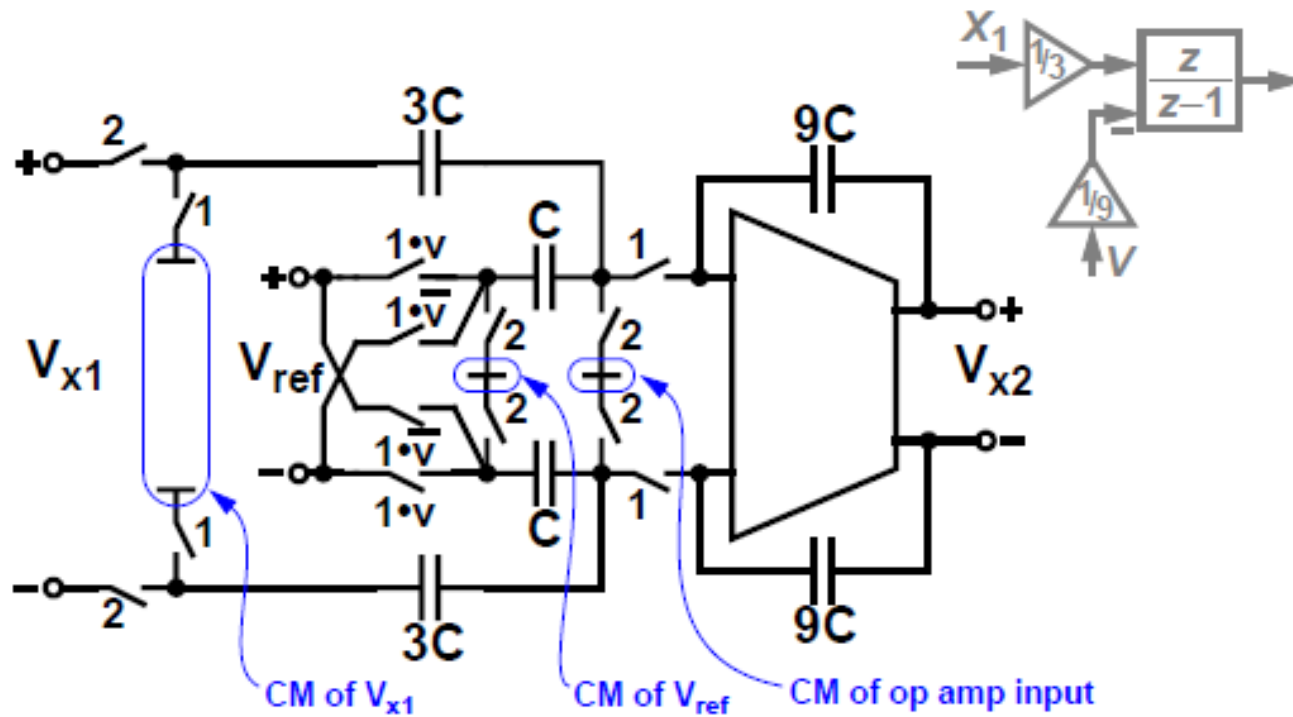


 
# INT2 Cap Sizes

- In-band noise of second integrator is greatly attenuated



$$\omega_B = \frac{\pi}{OSR}$$

$$\text{INT1 gain @ pb edge: } A = \frac{1/3}{\omega_B} = \frac{OSR}{3\pi}$$

$$\text{INT2 noise attenuation: } > OSR \cdot A^2 \approx 10^6$$

⇒ Capacitor sizes not dictated by thermal noise

- Charge injection errors and desired ratio accuracy set absolute size

A reasonable size for a small cap is currently ~10 fF.

# Behavioral Schematic for S/C MOD2

