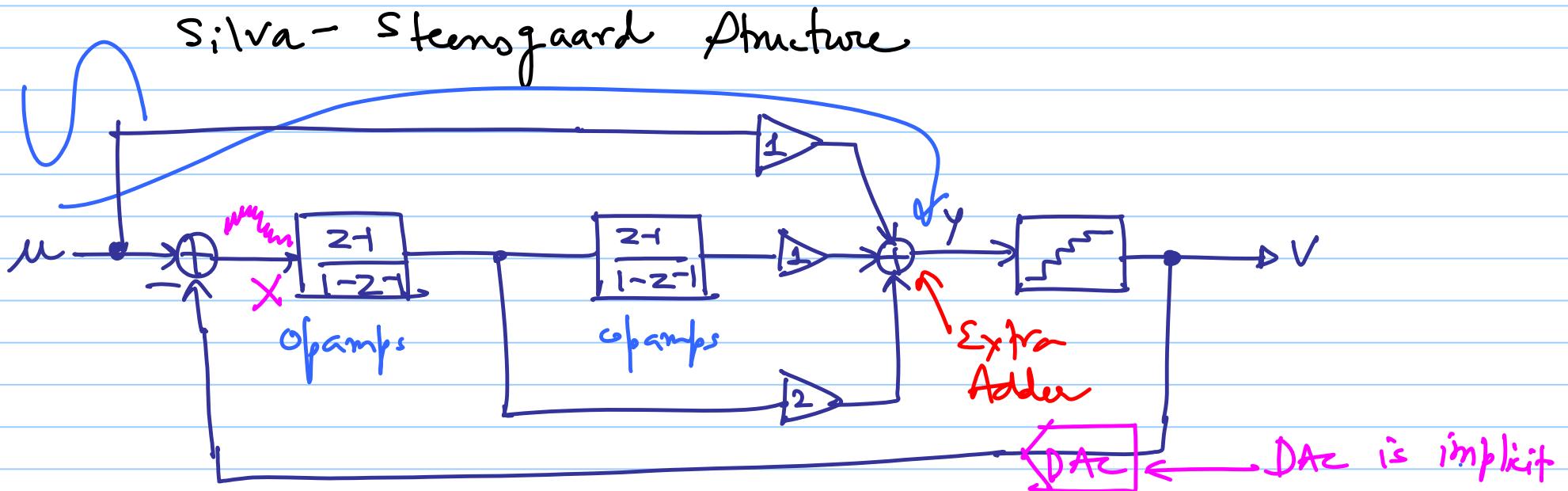


# ECE 615 - Lecture 12

Note Title

2/18/2016




$$V(z) = \underline{u(z)} + (1-z^{-1})^2 E(z)$$


$$X(z) = u(z) - v(z) \leftarrow \text{loop filter input}$$

$$= - (1-z^{-1})^2 E(z) \sim \text{contains only shaped noise term}$$

- (+) ① loop filter only processes Quantization Noise
  - ↳ signal swing at  $X$  is reduced
    - ↳ lower SR ( $\therefore$  linearity) requirement from the opamps
- (-) Extra ADDER before the quantizer
  - ↳ passive switched capacitor adder

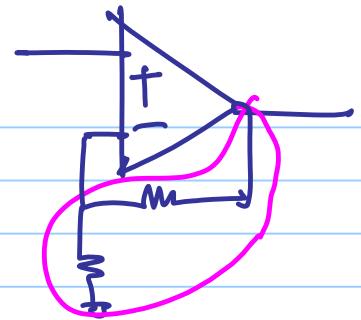\* The linearity of the feedback  
DAC is very critical



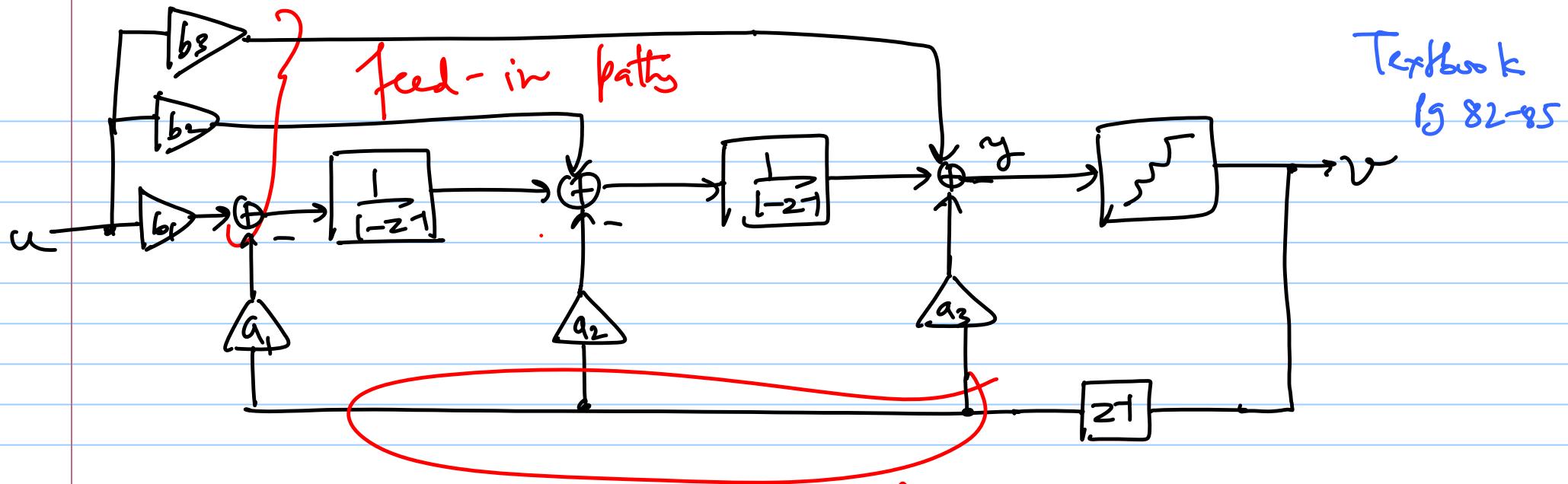

$$NTF(z) = \frac{(1-z^{-1})^2}{A(z)}$$

$\uparrow a'_s$

$$STF(z) = \frac{B(z)}{A(z)}$$


$\uparrow b'_s$        $\uparrow a'_r$

$$B(z) = b_1 + b_2 (1-z^{-1}) + b_3 (1-z^{-1})^2$$

$$A(z) = 1 + (a_1 + a_2 + a_3 - 2)z^{-1} + (-a_2 - 2a_3)z^{-2} + \underbrace{a_3 z^{-3}}$$

$a_3 \approx 0$  is  
 $DT - \Delta \Sigma$

$$NTF(z) = \frac{(1-z^{-1})^2}{A(z)}$$

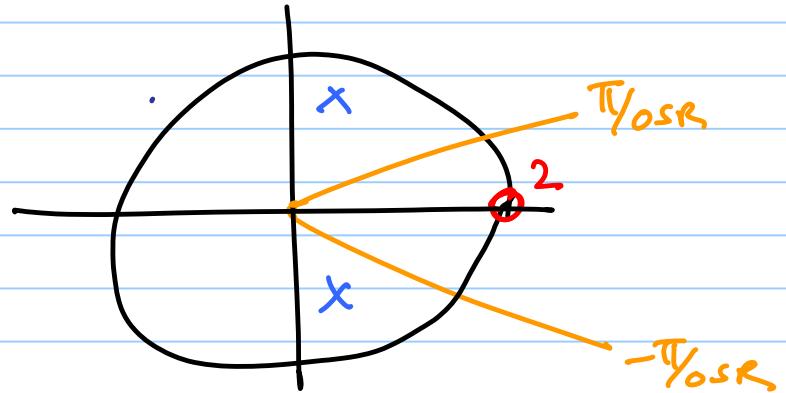



so far

$$|NTF(z)| = \frac{|(1-z)^2|}{|A(z)|} \approx \frac{\omega^2}{|A(j)|} \quad \text{for } \omega \ll \pi$$

$$= k \omega^2 \Rightarrow k = \frac{1}{|A(j)|}$$

$|A(j)|$  is the DC gain  
of  $A(z)$

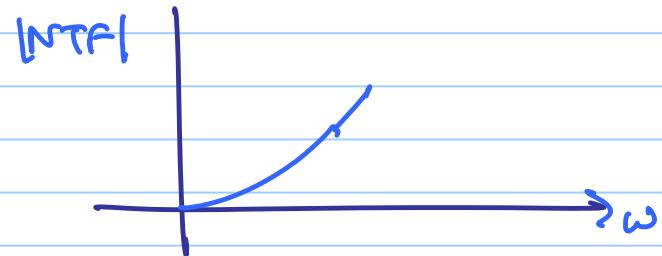

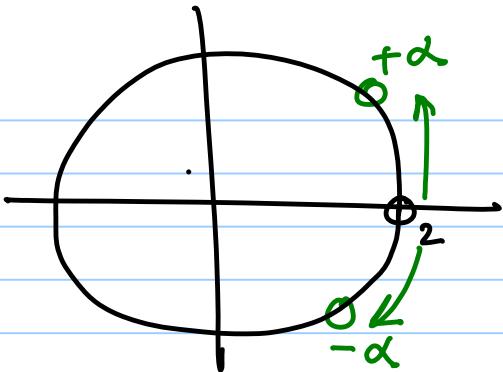


Move the NTF zeros from  $z=1$  to  $z=e^{\pm j\omega}$

$$|NTF(z)| \text{ is the } \cong k(w+\alpha)(w-\alpha)$$

Signal band  
∴  $w \ll \pi$

$$= k(w^2 - \alpha^2)$$

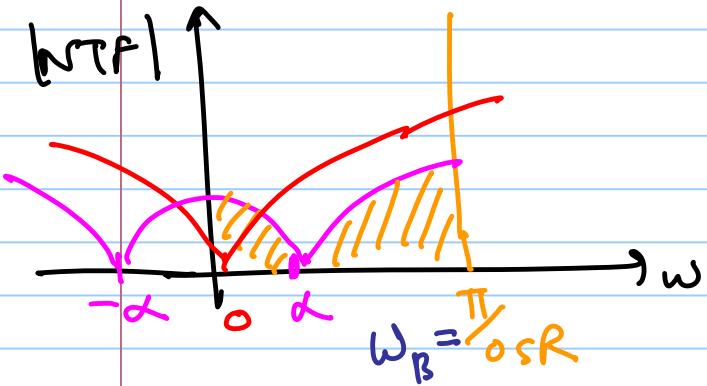

$$\Rightarrow I_{BN} = \frac{\Delta^2}{2\pi} \int_{-\alpha}^{\omega_B} |k(w^2 - \alpha^2)|^2 dw$$

$$= \frac{\Delta^2 R^2}{12\pi} \int_0^{\omega_B} (w^2 - \alpha^2)^2 dw = \frac{\Delta^2 k^2 \cdot I(\alpha)}{12\pi}$$

The

Integral

$$I(\alpha) = \int_{0}^{\omega_B} (\omega^2 - \alpha^2)^2 d\omega$$

for the least I<sub>BN</sub>, I( $\alpha$ ) must be minimized

$$\Rightarrow \frac{d I(\alpha)}{d \alpha} = 0$$

$$\Rightarrow \frac{d}{d \alpha} \int_{0}^{\omega_B} (\omega^2 - \alpha^2)^2 d\omega = 0$$

$$\Rightarrow \int_{0}^{\omega_B} \frac{d}{d \alpha} (\omega^2 - \alpha^2)^2 d\omega = 0$$

$$= 4\alpha \int_0^{\omega_B} (\omega^2 - \alpha^2) d\omega = 0$$


$$\Rightarrow \frac{\omega_B^3}{3} - \alpha^2 \omega_B^2 = 0$$

$$\Rightarrow \boxed{\alpha^* = \frac{\omega_B}{\sqrt{3}}}$$

$$\Rightarrow \alpha = \frac{\pi}{osR} \cdot \frac{1}{\sqrt{3}}$$

$$\frac{I(0)}{I(\alpha^*)} = \frac{9}{4} \Rightarrow$$

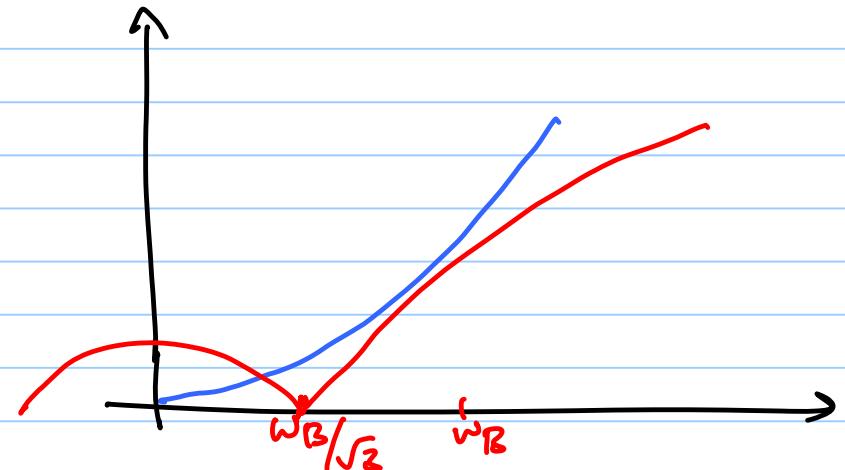SQNR improvement  
of  $\log_{10}(9/4) = 3 \cdot 5 \text{ dB}$




pole locations determine

OBG

↳ determines stability

will come back to  
this later

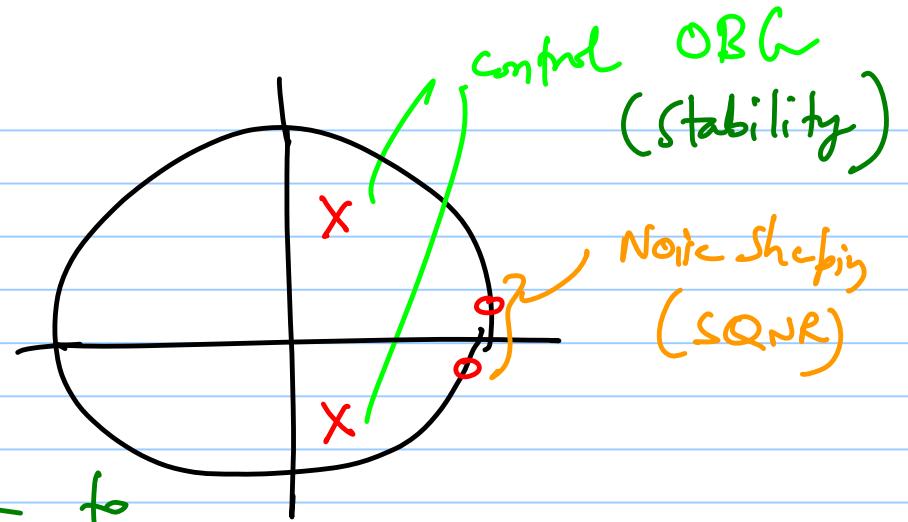


$$(a+b)^3 = a^3 + b^3 + 3ab(a+b)$$

Let's say

$$NTF(z) = (1-z^{-1})^3$$

$$OBG = \sum |h(n)| = 8$$

## Describing function Analysis

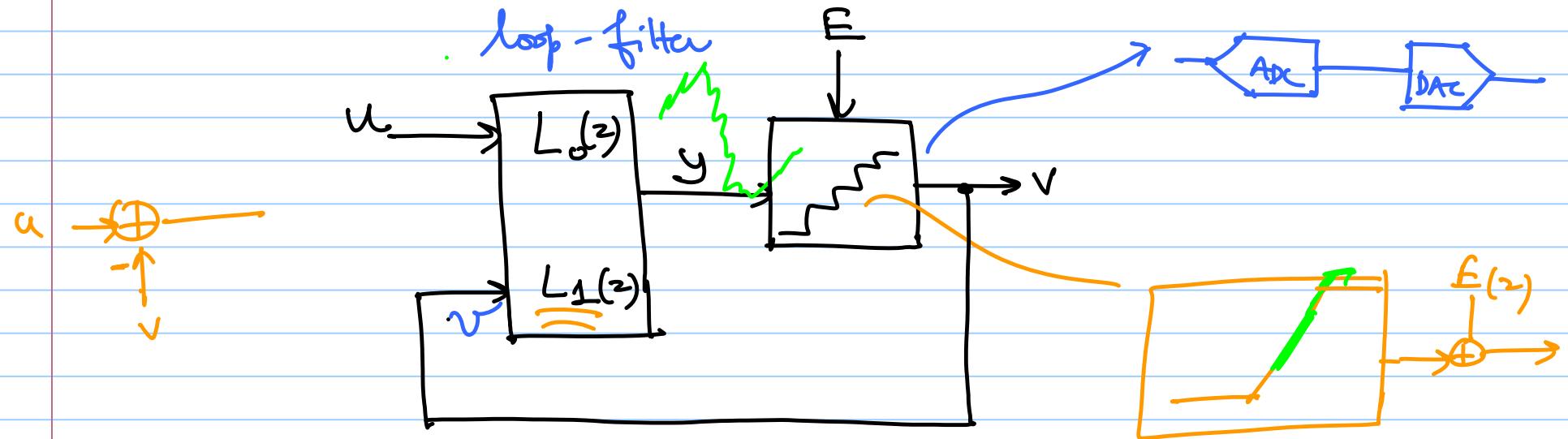

$$\gamma(z) = L_0(z) u(z) + L_1(z) v(z)$$

$$\therefore V(z) = \gamma(z) + E(z)$$

$$\Rightarrow V(z) = L_o(z) U(z) + L_i(z) V(z) + E(z)$$

Uncarried model

$$\Rightarrow V(z) = \frac{L_o(z)}{1-L_i(z)} U(z) + \frac{L_i(z)}{1-L_i(z)} \cdot E(z)$$

minus  
absorbed by  $L_i(z)$

$$= STF(z) U(z) + NTF(z) E(z)$$

$$L_o(z) = \frac{STF(z)}{NTF(z)}$$

$$L_i(z) = \frac{NTF(z)-1}{NTF(z)}$$

Ex. for 2<sup>M</sup>-order modulator

$$L_0(z) = \frac{1}{(1-z)}^2$$

$$L_1(z) = \frac{-z^1}{(-z)^1} - \frac{z^1}{(1-z)^1}^2$$