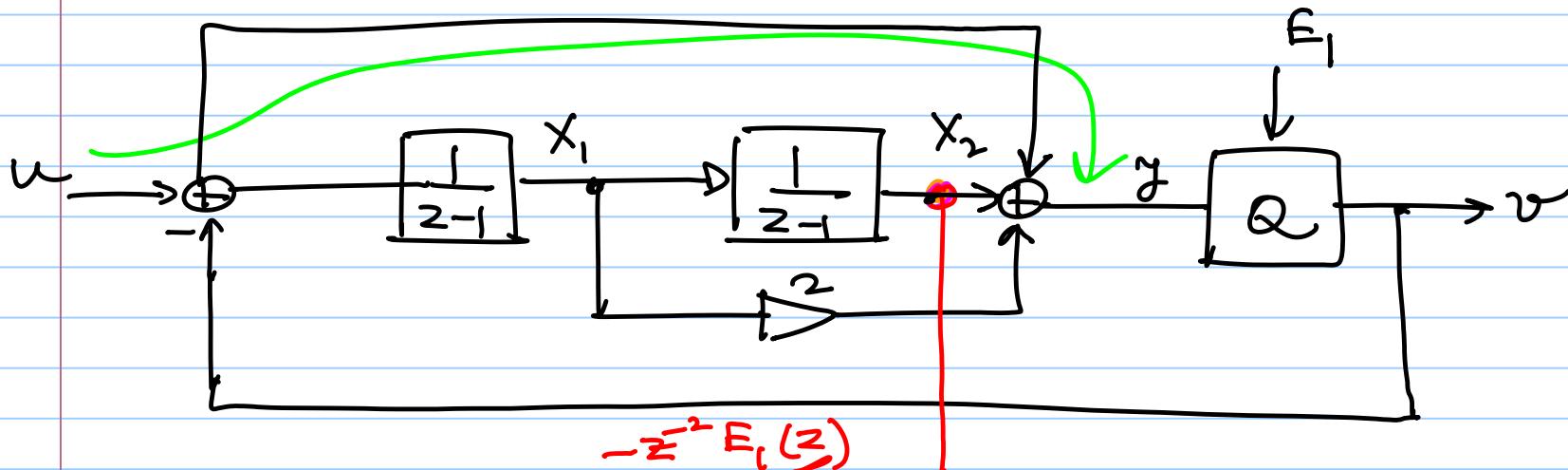


# ECE 615 - Lecture 22

Note Title

3/31/2016



$$-z^{-2} E_1(z)$$

feed forward modulation  $\Rightarrow$  2<sup>nd</sup> order

$$NTF = (-z^{-1})^2$$

$$STF = 1$$

$$\rightarrow x_2 = -z^{-2} \cdot E_1(z) \rightarrow \text{low distortion topology}$$

Ex.

2-2 MASH


(SOSO)

$$STF_1 = STF_2 = z^{-2} , NTF_1 = NTF_2 = (1-z^1)^2$$

$$V(z) = z^4 U(z) - \boxed{(1-z^1)^4 E_2(z)} \rightarrow E_1(z) \text{ is cancelled (ideally)}$$

$$NTF(z) = (1-z^1)^4$$

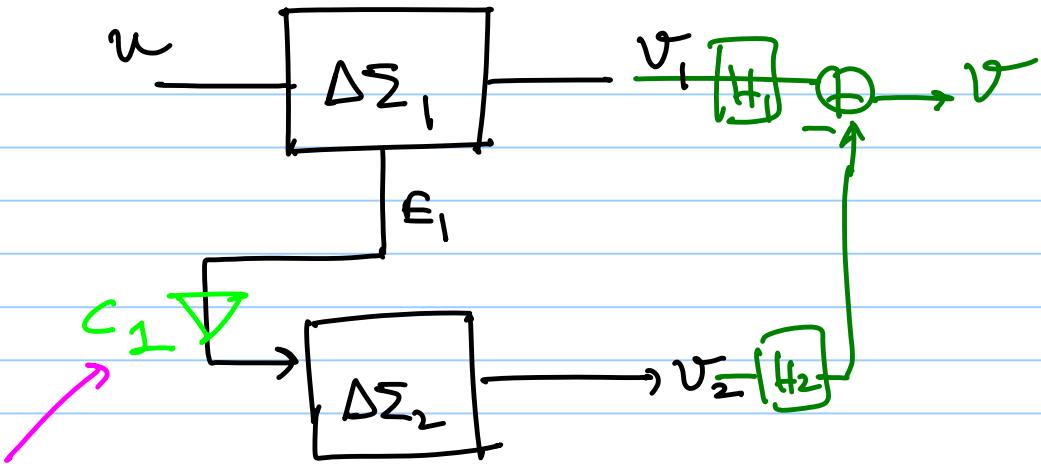↳ stability is still governed by  
 $OBC = 4$ .



if

$$|E_{\text{fil}}|_{\max} > \text{MSA}_2$$

↳ instability or  
SNDR drop

interstage  
coupling  
coeff.

"single-bit"

\* for a 2<sup>m</sup>-order first stage ΔΣM, usually  $c_1 = \frac{1}{4}$

$$|E_{\text{fil}}|_{\max} \ll \text{MSA}_2$$

↳ low SNR in the  
2<sup>nd</sup> modulator

\* for multi-bit quantizer in the first-stage  
 $c_1 \geq 1$

\* The inverse of scaling factor ( $c_1$ ) needs to be included in  $H_2$  to cancel  $E_1(z)$

$$H_1 = STF_{2,d}$$

$$H_2 = \frac{1}{c_1} NTF_{1,d}$$

$$V(z) = STF_1 \cdot STF_{2,d} V(z) + \boxed{\frac{1}{c_1} NTF_{1,d} NTF_2 \cdot E_2(z)}$$

NTF

In general:


$$NTF_{\text{casc}} = \frac{(1-z^*)^{N_{\text{casc}}}}{\prod_{i=1}^n c_i}$$

In band noise

$$IBN = \frac{\pi c^L}{\pi} \int_0^{\pi/2} |NTF_1(\omega)|^2 |NTF_2(\omega)|^2 d\omega = \frac{IBN_o}{\pi c_i^2}$$


for single-bit MASH  $c_i < 1 \Rightarrow IBN \downarrow \Rightarrow SNR \downarrow$

2-2 MASH

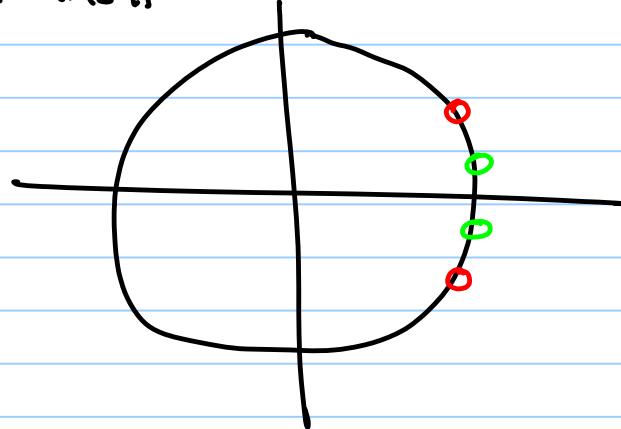

zero pairing in MASH

↳ NCF may be more complicated.

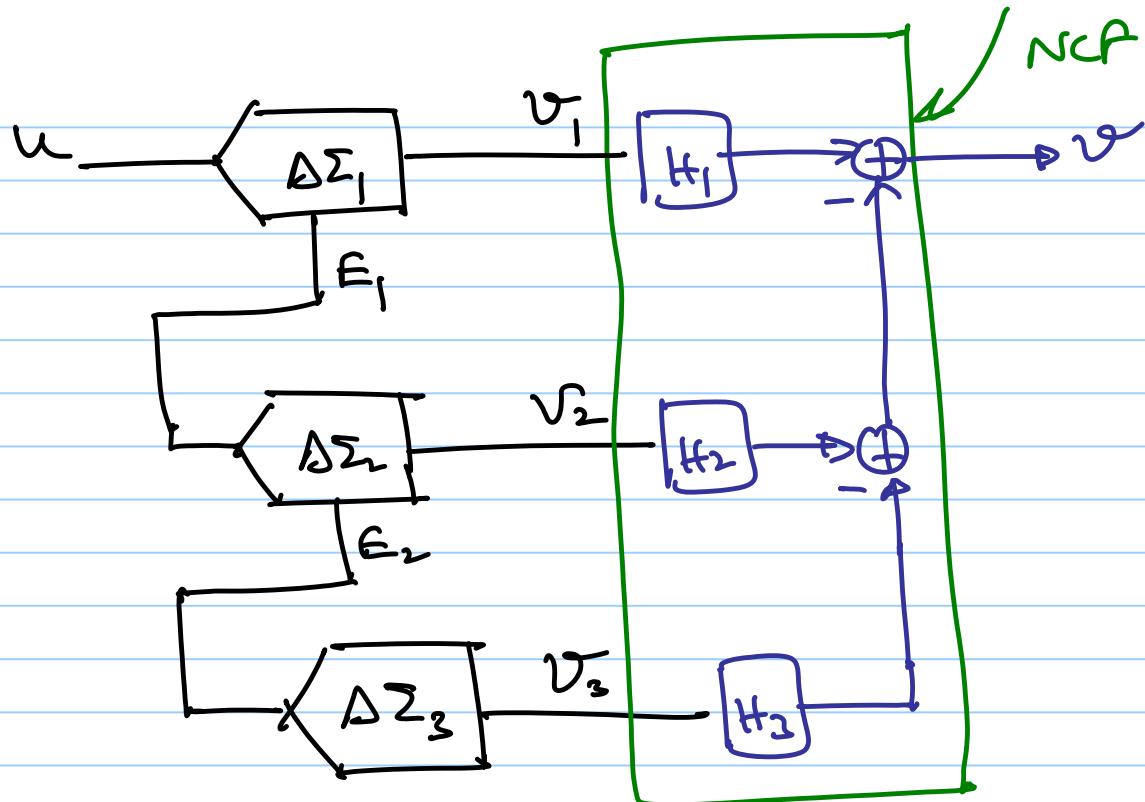

Goal: Cancel  $E_1$  &  $E_2$

$$\begin{aligned} H_1 \cdot NTF_1 - H_2 \cdot STF_2 &= 0 \\ H_2 \cdot NTF_2 - H_3 \cdot STF_3 &= 0 \end{aligned} \quad \rightarrow ①$$

If  $E_1 + E_2$  are perfectly cancelled

$$V = STF_1 \cdot H_1 \cdot U + NTF_3 \cdot H_3 \cdot E_3$$

$$H_1 = STF_2, \quad H_2 = NTF_1$$

$$H_3 = \frac{NTF_1 \cdot NTF_2}{STF_3}$$

$$STF_3 = z^k$$

$$NTF = \frac{NTF_1 \cdot NTF_2 \cdot NTF_3}{STF_3}$$

2-1-1 MASH

2-2-1 MASH

S didn't consider  $C_i$ 's

## Analysis of Noise Leakage:


In a single-loop  $\Delta\Sigma$  modulator, the issues are:

- ↳ imperfect matching of capacitors ( $C$ 's)

- ↳ finite gain of opamps

- ↳ incomplete settling & slew rate in opamps

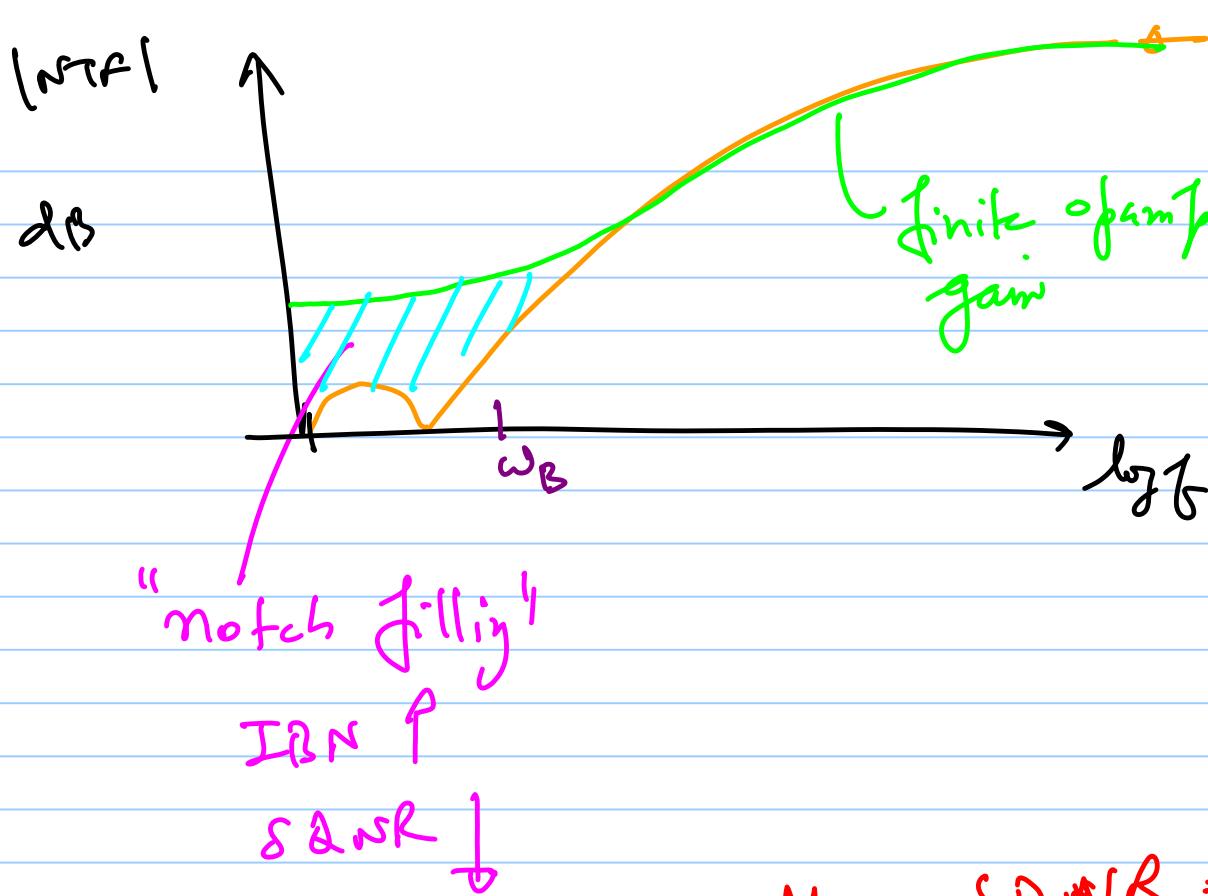→ These anomalies change the NTF + STF, and thus the SNR



$$|NTF| \approx \frac{1}{|L|} \text{ loop gain}$$




More S&NR  $\Rightarrow$  opamp DC gain ↑



(First order settling)  
Linear settling.


$V_{out}$


$$A_L(1-e^{-t/\tau})u(t)$$

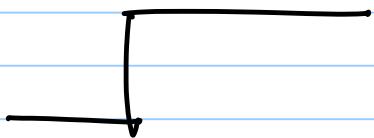

$$i_{out} = C_L \frac{dV_{out}}{dt}$$

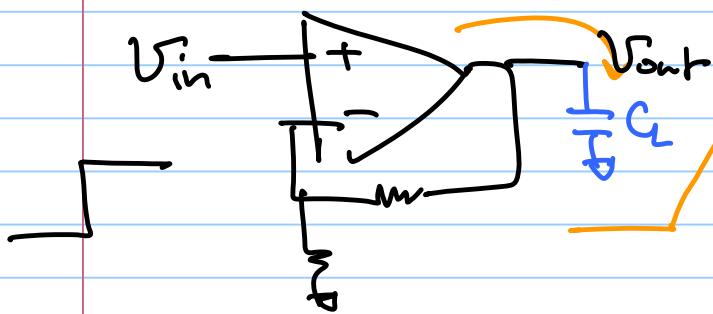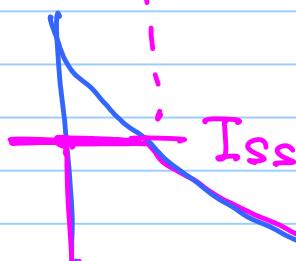

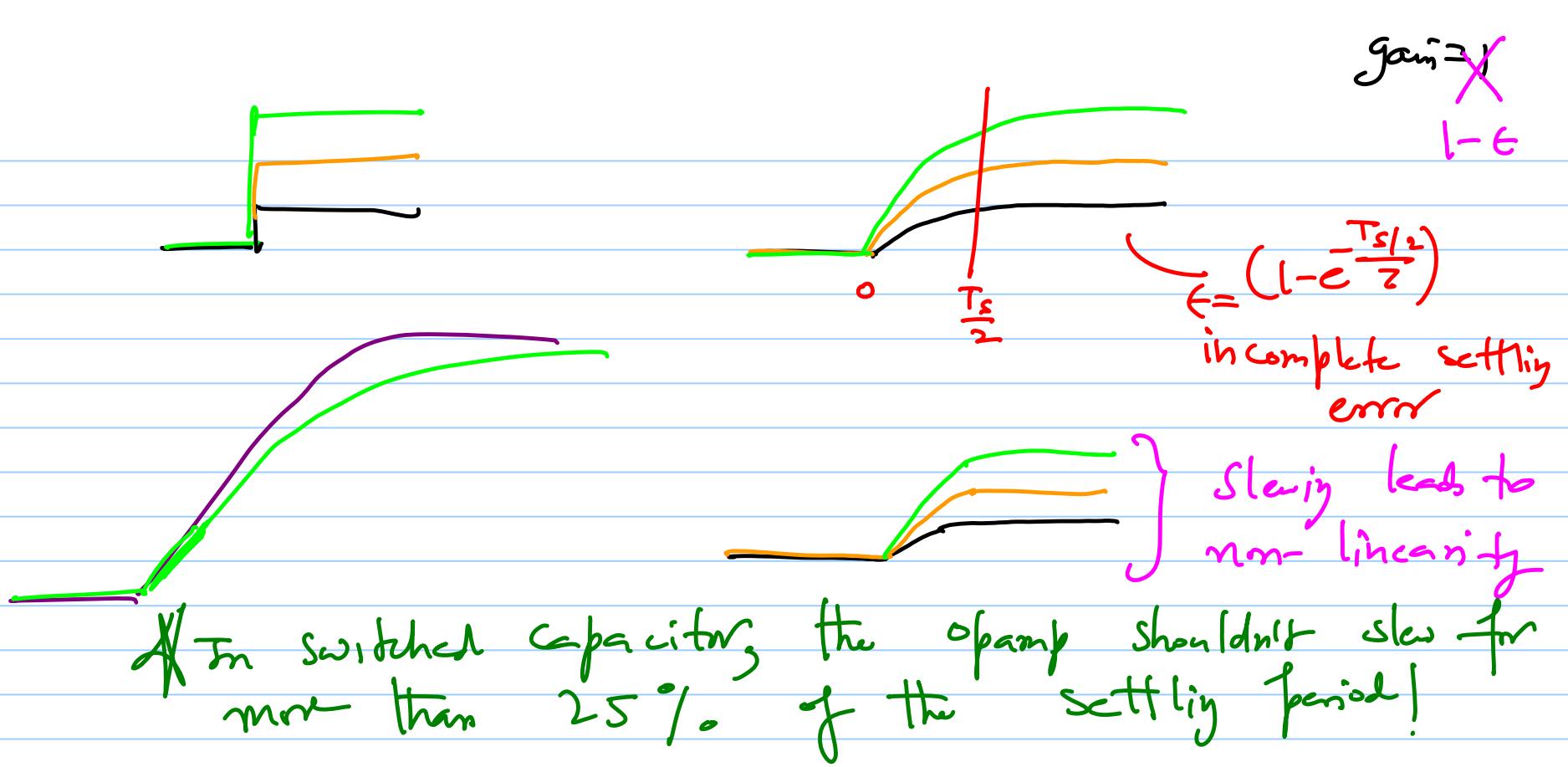

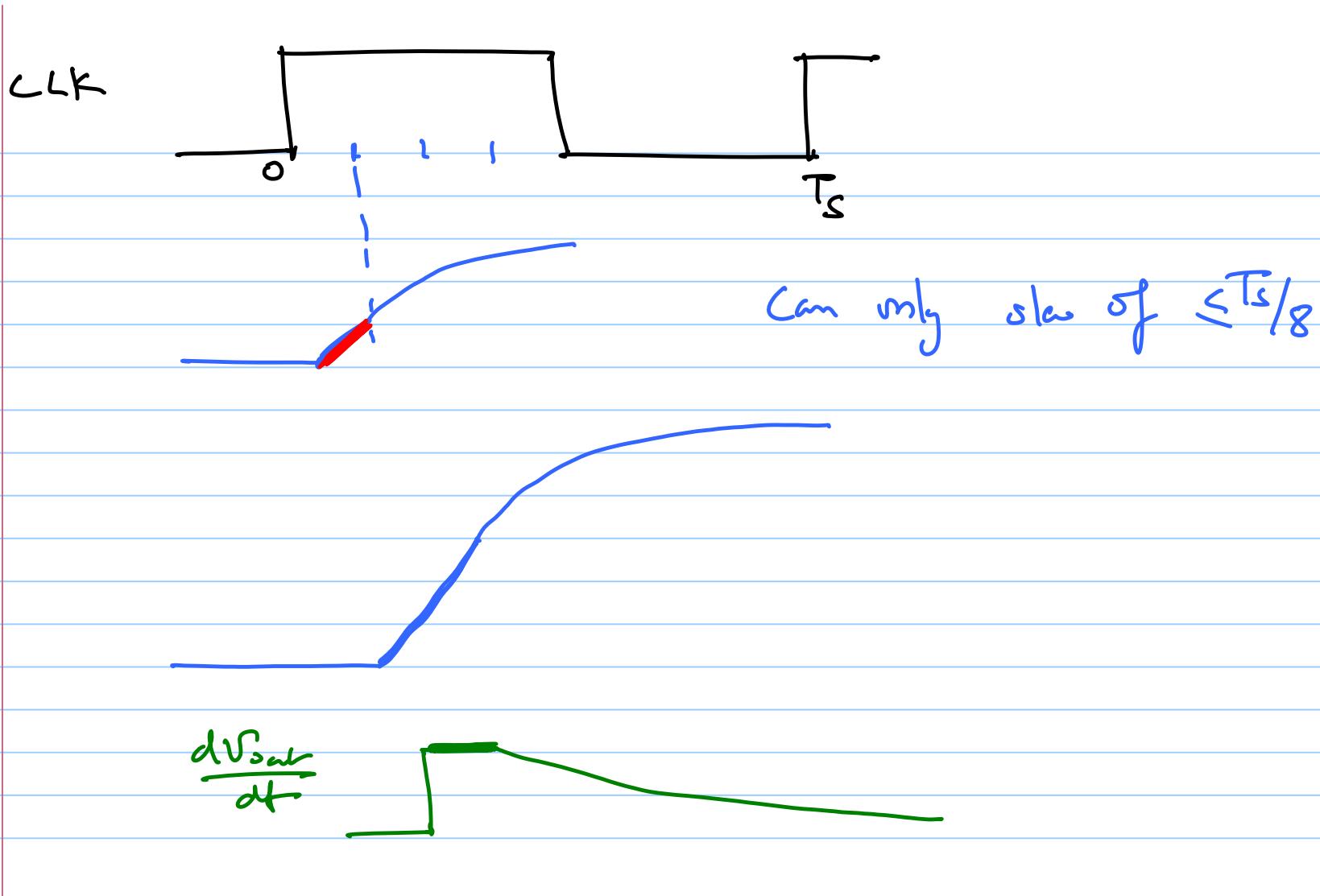

In a MAST to cancel  $E_1$

$$H_{1,i} \cdot NTF_{1a} - H_{2,i} \cdot STF_{2a} \xrightarrow{?} 0$$

$$\Rightarrow H_{e_1} = \underline{H_1} \cdot \underline{NTF_1} - H_2 \cdot \underline{STF_2}$$

$H_{e_1} \neq 0$  due to imperfect analog components

$$|H_{e_1}| = ?$$

$$H_1 = STF_2 \xrightarrow{\text{flat in the signal band}}$$

$$H_2 = NTF_1$$

$$|H_{e_1}| \approx |NTF_1 - H_2| = |NTF_{1a} - NTF_{1i}|$$

ideal

leakage

$$|b_{L1}| \approx |NTF_{1,a} - NTF_{1,i}|$$

first-stage should be  
as close to ideal response  
as possible  
↳  $E_1$  leakage

$$I_i(z) = \frac{a}{z-1}$$

integrator gain =  $G_{C_2}$

$$I_a(z) = \frac{a'}{z-p'} \quad \text{or model for imperfect integrator}$$

$$a' = a(1+D)$$

$$|H_{E_1}| \approx \frac{1}{A} + z^2(1-z) \left[ \frac{D}{a} + (1+\frac{1}{a}) \frac{1}{A} \right]$$

direct noise

feedthrough

from  $E_1$  to  $V$

1<sup>st</sup>-order

noise-shaper