
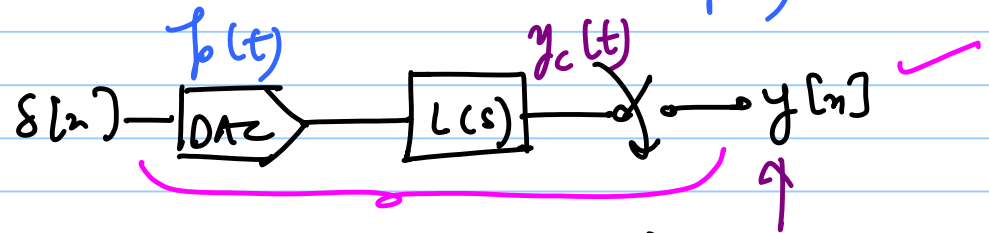
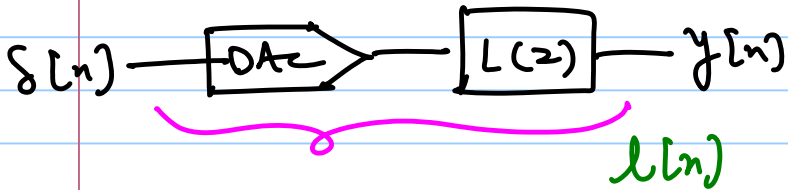
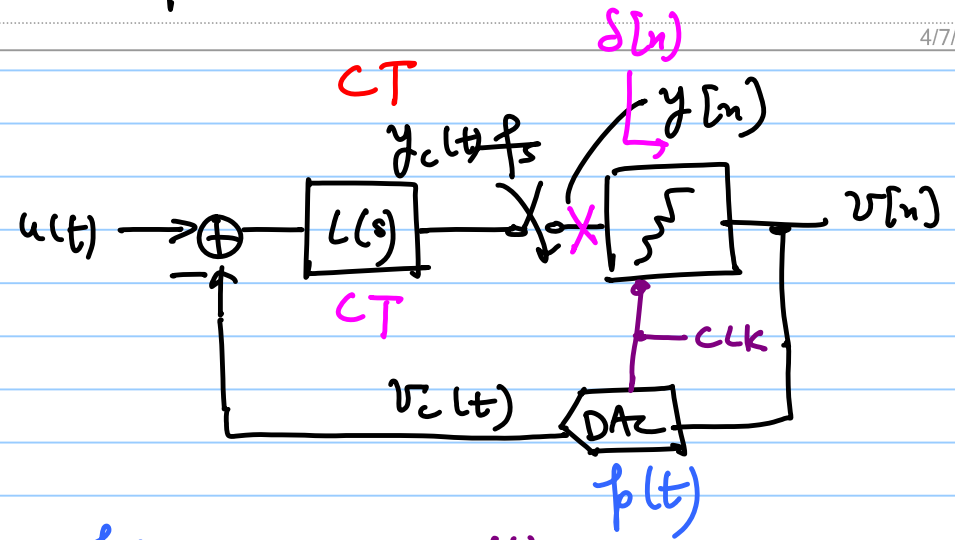


# ECE 615 - Lecture 24

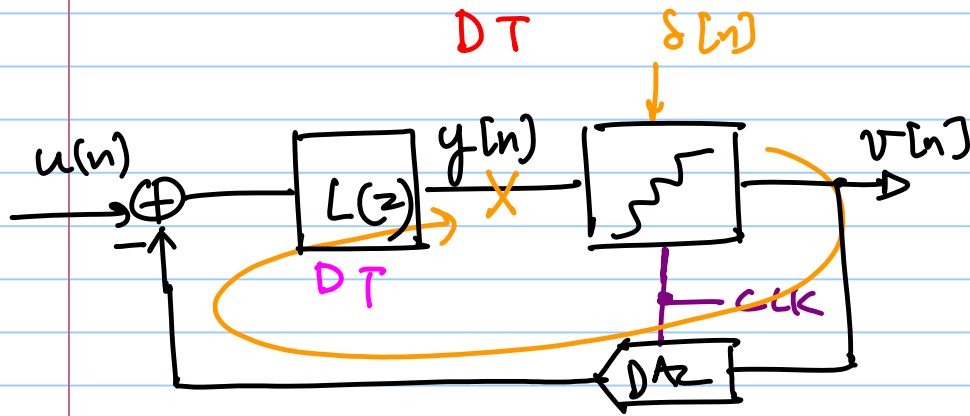

Impulse invariant Transformation (IIT)

$$y[n] \stackrel{\Delta}{=} y_c(t) \Big|_{t=nT_s}$$

if  $c[n] = \delta[n]$

$$x[n] \stackrel{\Delta}{=} y(t) \Big|_{t=nT_s}, v[n] = \delta[n]$$

I.I.T.

$$\Rightarrow \mathcal{Z}^{-1}\{L(z)\} = \left\{ \mathcal{Z}^{-1}\left( L(s) \cdot R_{\text{DAZ}}(s) \right) \right\} \Big|_{t=nT_s}$$


DT prototype

$$\text{NTF}(z) = \frac{1}{1+L(z)}$$


loop filter



$\mathcal{Z}\{\beta(t)\}$

DAZ pulse shape


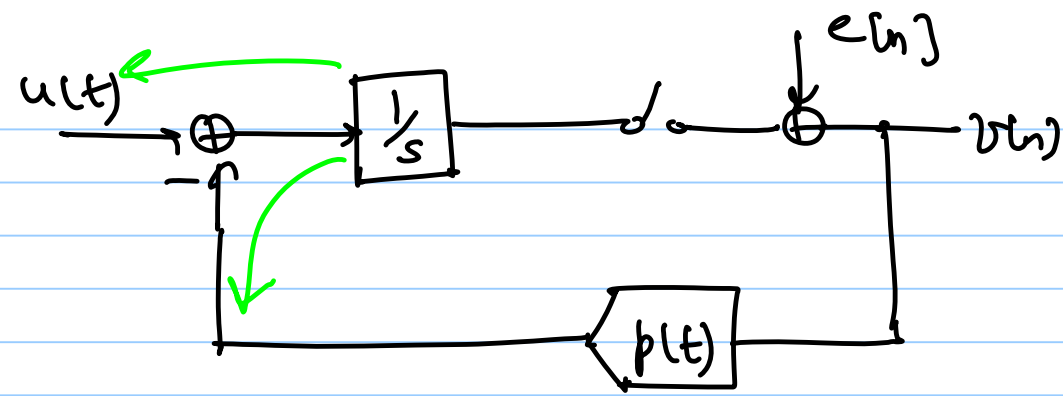



$$f_s = 1 \text{ Hz}$$

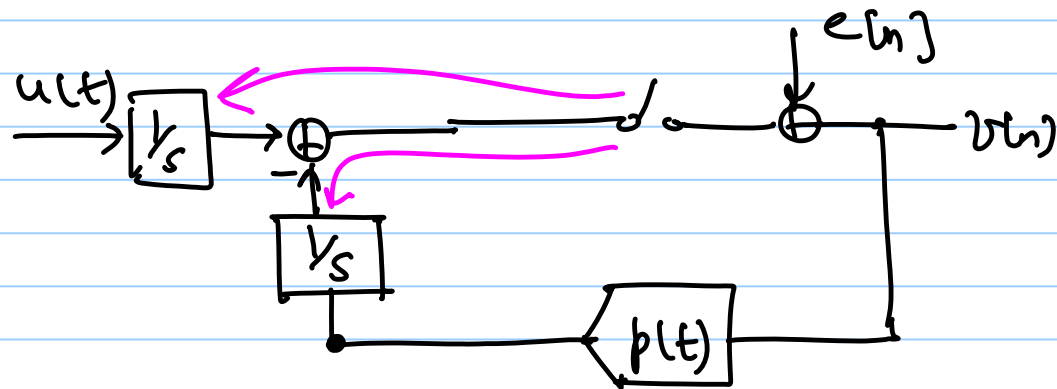

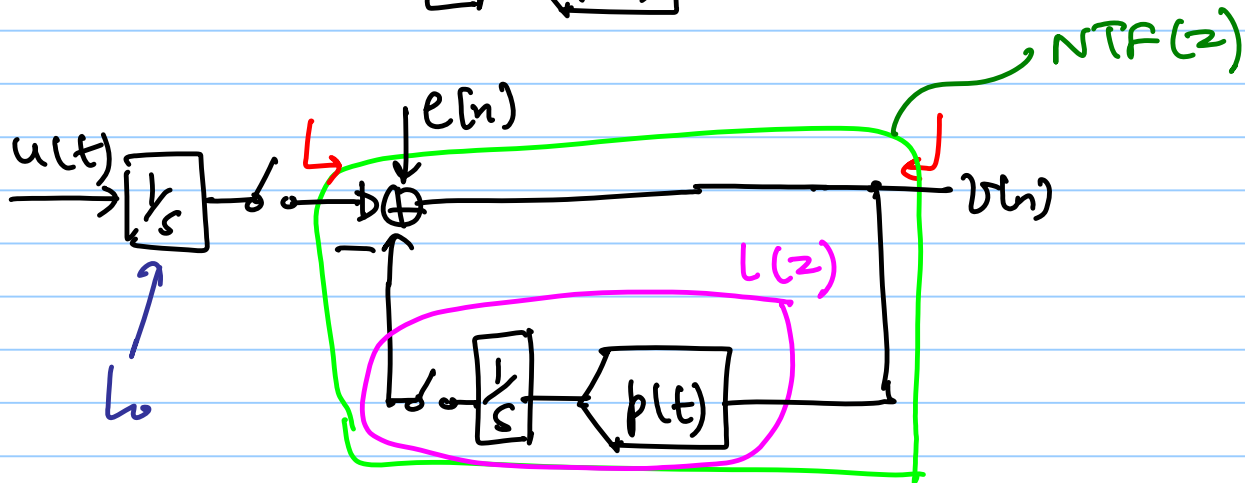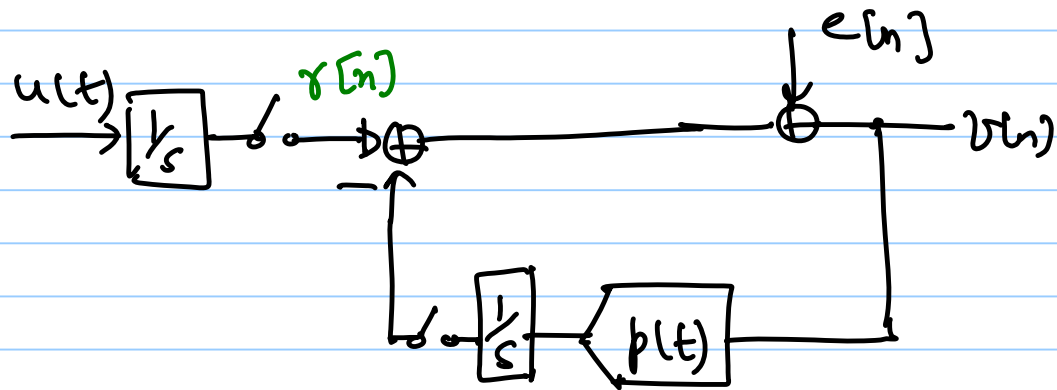

$$\frac{1}{1+L(z)} = \text{NTF}(z)$$

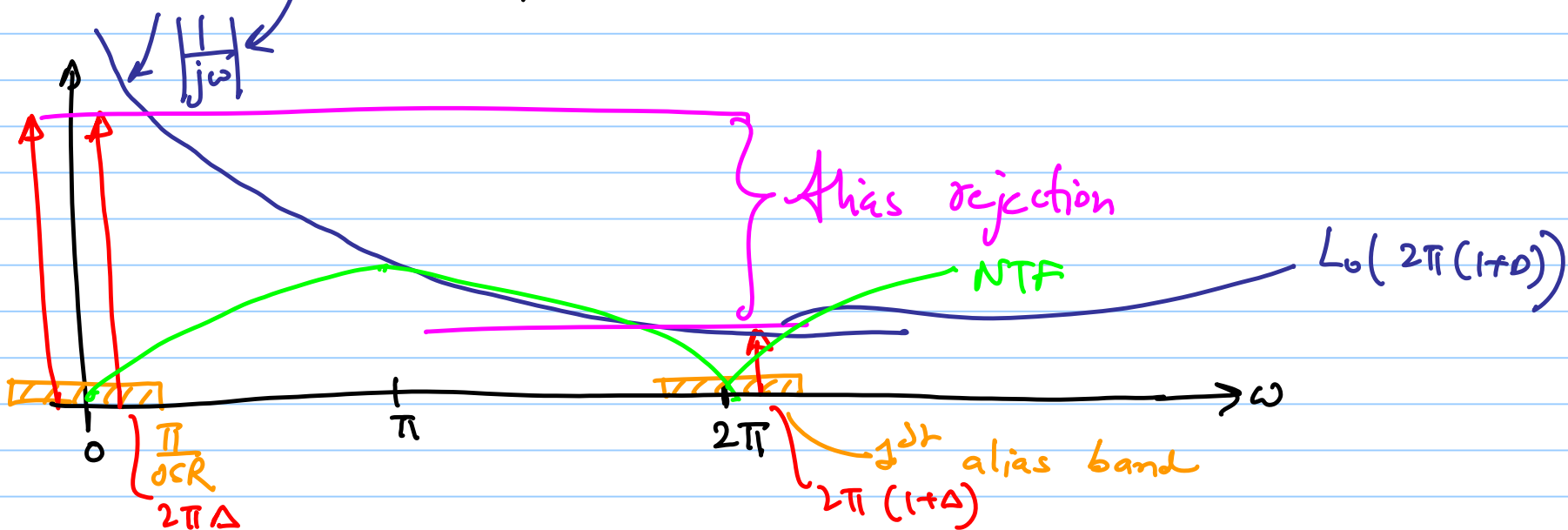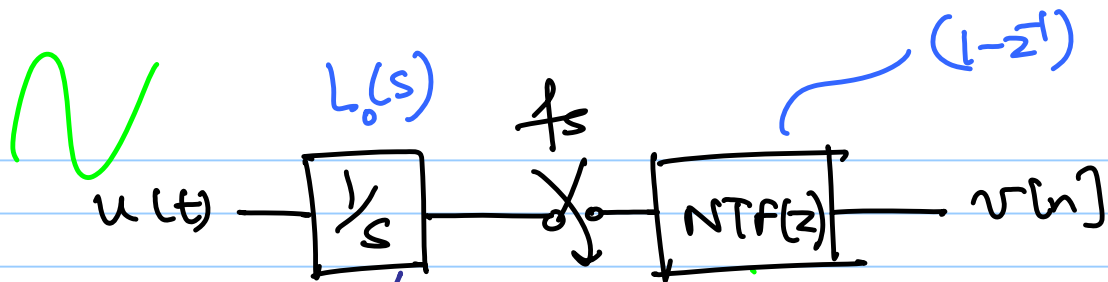

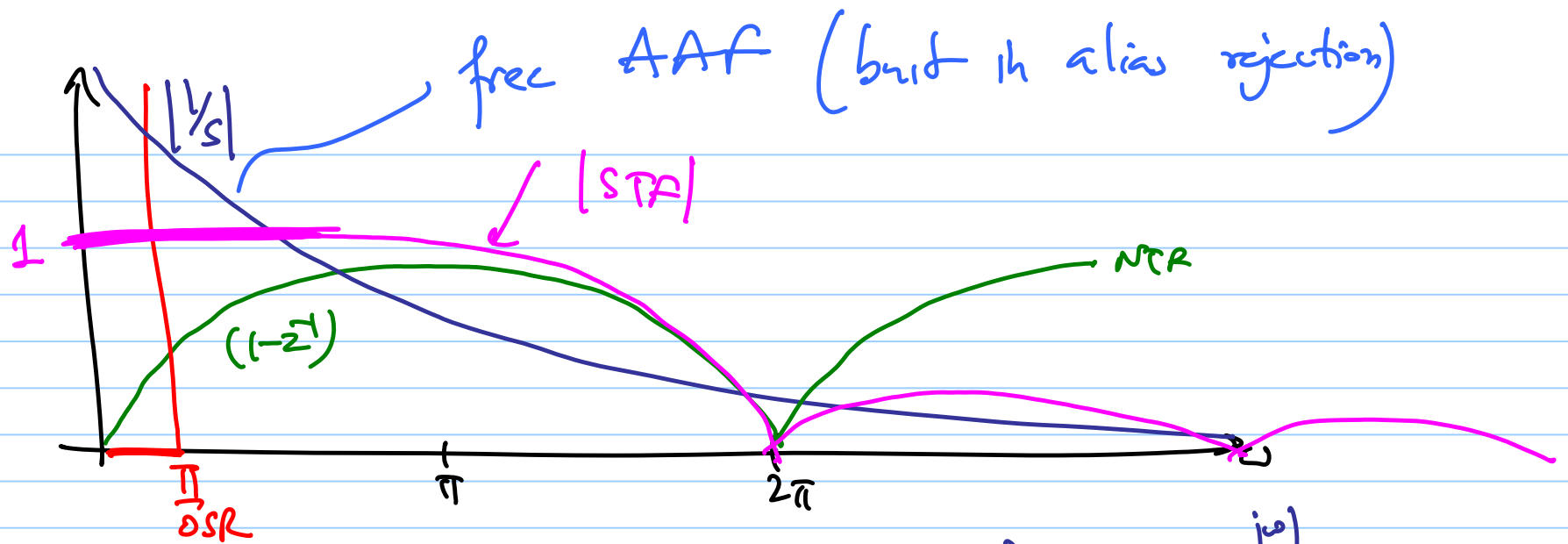


In general  $STF(j\omega) = L_0(j\omega) \cdot NTF(e^{j\omega})$

AAF  $\rightarrow L_0(j\omega)$


$\hookrightarrow$  implicit anti-aliasing in CT- $\Delta\Sigma$  Modulators

this alias rejection is

$$\frac{|L(2\pi(f+\Delta))|}{|L(2\pi\Delta)|}$$

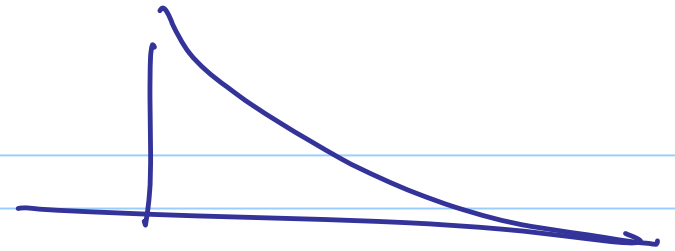
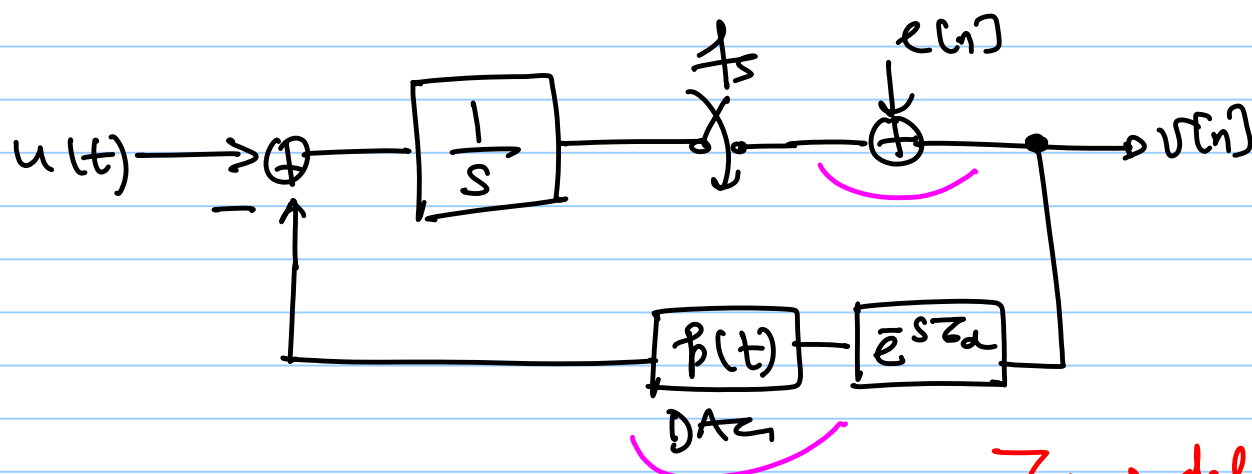
# Excess loop-delay in CT- $\Delta\Sigma$ :




$f_s = 1 \text{ Hz}$


ADC + DAC will have finite delay.

$T_d \rightarrow$  delay in quantizer

$0 < T_d < T_s$

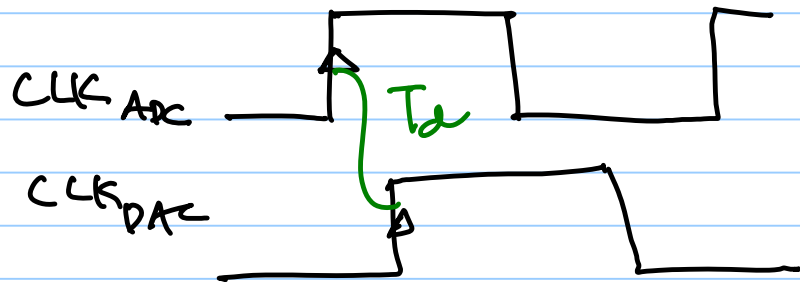




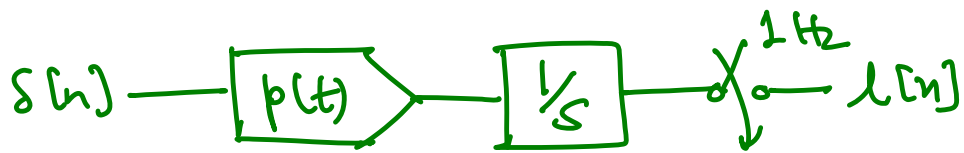


$$l[n] \xleftrightarrow{Z} L(z)$$

$$l[n] = \{0, 1, 1, \dots\}$$

Ideal Case

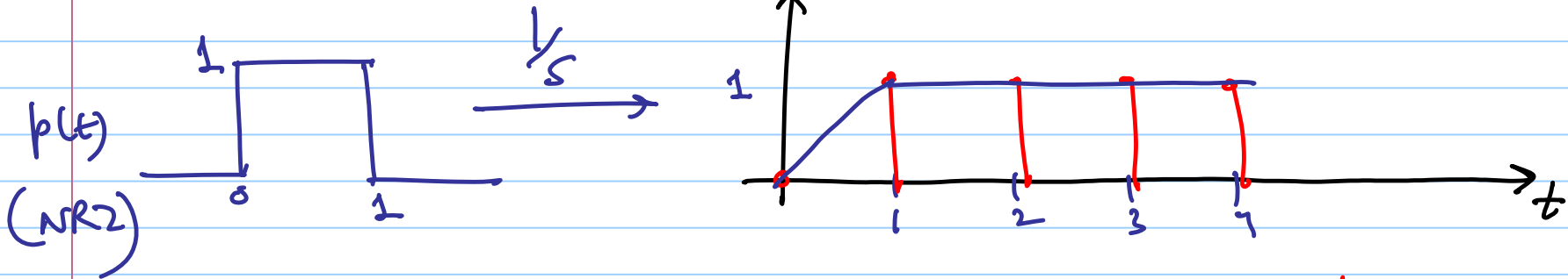


with delays

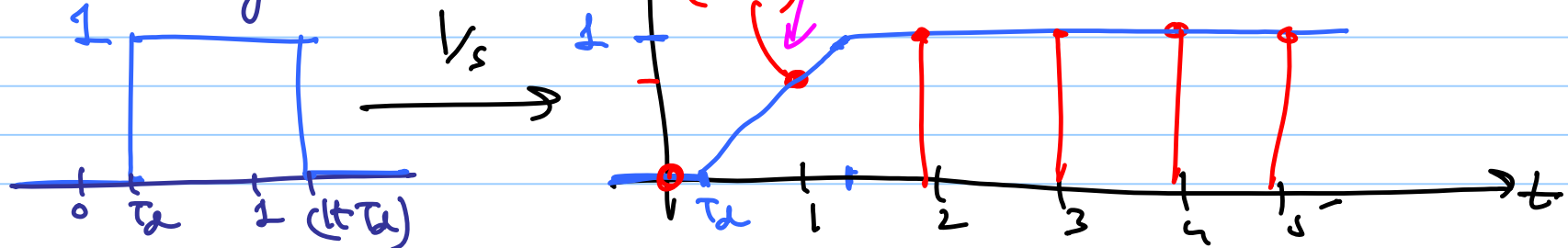

$$l[n] = \{0, 1-T_a, 1, 1, \dots\}$$

$$L(z) = \frac{z^T}{1-z^{-1}} - T_a z^{-1}$$

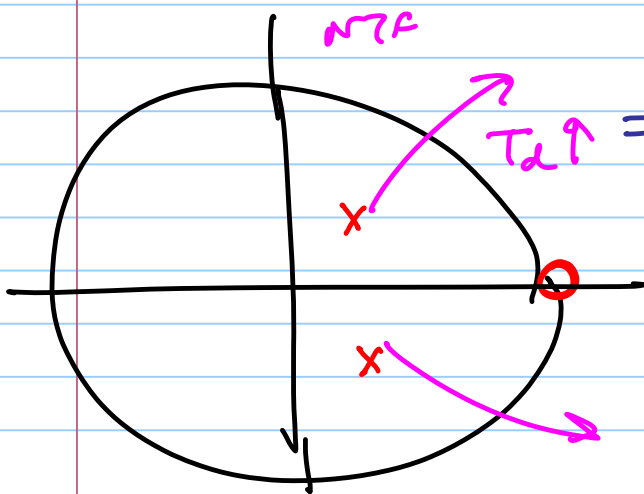
$$NTF(z) = \frac{1}{1+L(z)} = \frac{1}{1 + \frac{z^T}{1-z^{-1}} - T_a z^{-1}} = \frac{(1-z^{-1})}{(-T_a z^{-1})(1-z^{-1})}$$



$$T_a \uparrow = \frac{(1-z^{-1})}{1 - T_a z^{-1} + T_a z^{-2}}$$

ideally  $\rightarrow (1-z^{-1})$

with delay

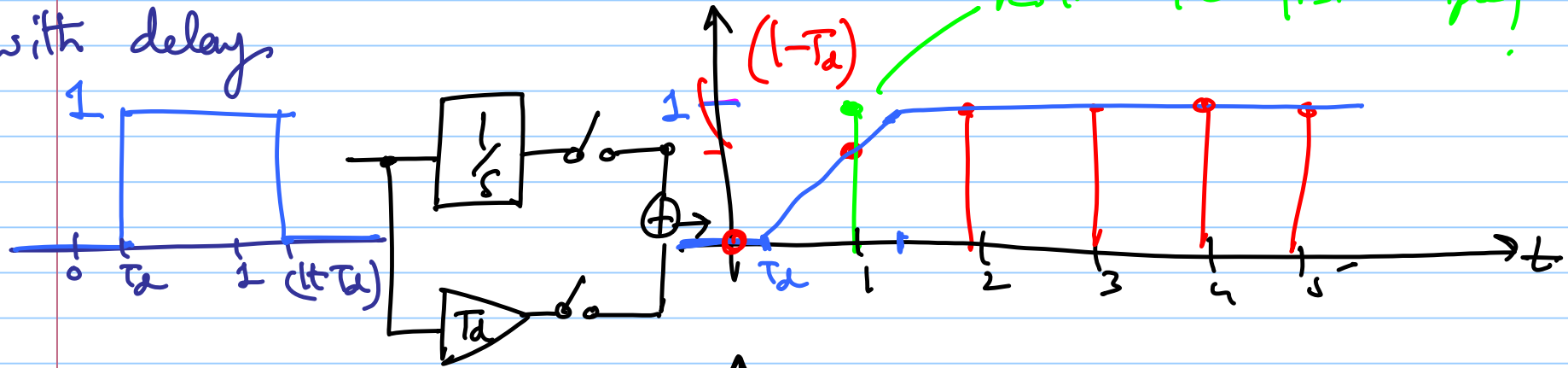

restore the first samples



$\delta(n)$  "ELD Compensation"

