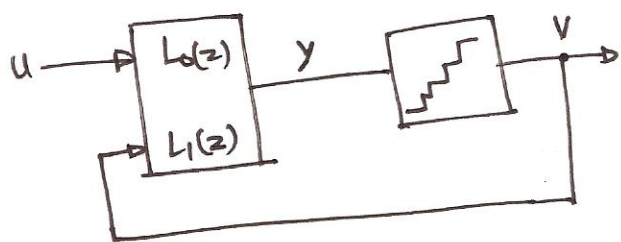


# Higher-Order $\Delta\Sigma$ Modulators



$$NTF(z) = \frac{1}{1 - L_1(z)}$$

$$STF(z) = \frac{L_0(z)}{1 - L_1(z)}$$

- $L_1(z)$  has high gain in the signal band  
 ↳ reduces quantization noise in the signal-band  
 $\Rightarrow |NTF| \approx \frac{1}{|L_1|}$
- $\Rightarrow L_0(z)$  must also be large in the signal band in order to keep STF close to 1 in the signal band.  
 $\Rightarrow |STF| \approx \frac{|L_0|}{|L_1|} \approx 1$  in signal band  
 ↳ both  $L_0$  and  $L_1$  should have their poles in the signal band.  
 ↳  $L_0$  and  $L_1$  have different zeros in general.

$$NTF(z) = \frac{1}{1 - L_1(z)} = \frac{1}{1 - \frac{N_1(z)}{D(z)}} = \frac{D(z)}{D(z) - N_1(z)}$$

$$L_0(z) = \frac{N_0(z)}{D(z)}$$

$$L_1(z) = \frac{N_1(z)}{D(z)}$$

$\Rightarrow$  poles of  $L_1(z) \Rightarrow$  zeros of  $NTF(z)$  ← important!

- $NTF(z)$  and  $STF(z)$  share the same poles  
 ↳ i.e. the roots of  $1 - L_1(z) = 0$   
 ↳ zeros of  $L_0(z)$  may cancel some/all poles in  $D(z)$ .

• A contrived example (not necessarily stable NTF):

$$STF(z) = z^{-k} \quad NTF(z) = (1 - z^{-1})^N$$

$\Rightarrow |STF| = 1$

$\Rightarrow L_0(z) = \frac{STF(z)}{NTF(z)} = z^{-k} (1 - z^{-1})^{-N} = \frac{z^{N-k}}{(z-1)^N}$

$\rightarrow$  N-poles at  $z=1$   
 (N-k) zeros @  $z=0$   
 k zeros @  $z=\infty$ .

~~NTF(z)~~

$$L_1(z) = \frac{1}{NTF(z)} - 1 = (1-z^{-1})^{-N} - 1 = \frac{1 - (1-z^{-1})^N}{(1-z^{-1})^N}$$

$$= \frac{z^N - (z^{-1})^N}{(z-1)^N} \Rightarrow N\text{-poles at } z=1$$

what about the zeros?

• for finding  $L_1(z)$  zeros i.e.  $z_i$

$$(1-z^{-1})^N = 1 = e^{j2\pi} \leftarrow N^{\text{th}}\text{-roots of unity}$$

$$\Rightarrow (1-z_i^{-1}) = e^{j\frac{2\pi i}{N}}, i=0 \text{ to } N-1$$


$$\Rightarrow z_i = \frac{1}{1 - e^{j\frac{2\pi i}{N}}} = \frac{1}{2} \left[ 1 + j \cot\left(\frac{\pi i}{N}\right) \right], i=1, \dots, (N-1).$$

for  $i=0 \Rightarrow z_0$  is at  $\infty$ .

$\Rightarrow$  1 zero @  $\infty$

$(N-1)$  zeros given by

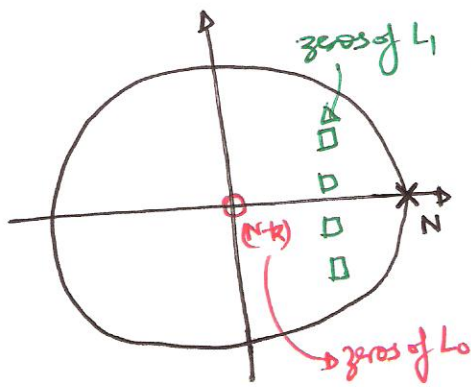
(MATLAB may show zeros at  $\infty$  differently)



- \* Both  $L_0$  &  $L_1$  have  $N$ -poles at  $z=1$  (i.e. DC)
- \*  $(N-k)$  zeros of  $L_0$  lie on  $z=0$ , and other  $k$  zeros @  $\infty$ .
- \* zeros of  $L_1$  are located within the unit circle at  $z_i = \frac{1}{1 - e^{j\frac{2\pi i}{N}}}$

# Loop-Filter Architectures:

## CIFB

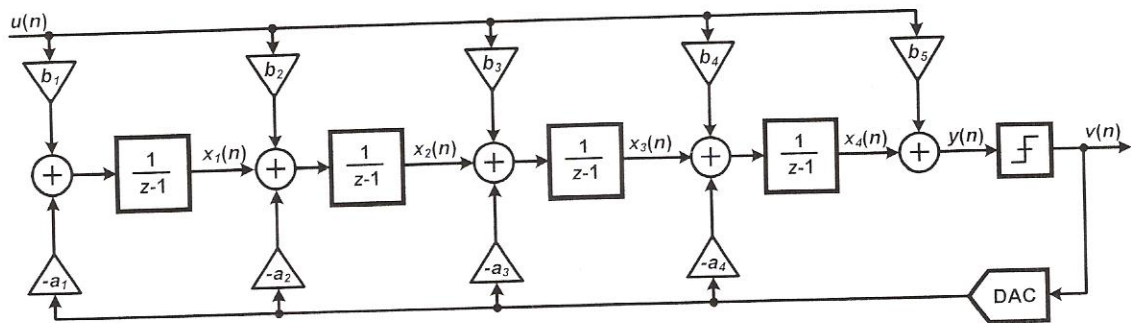

CIFB → Cascaded integrators with distributed feedBack.

↳ Cascade of  $N$  delaying integrators.

↳ feedback from the quantizer to the input of each integrator.

↳ Multiple feed-in branches possible.

By inspection,

$$L_o(z) = \left( \left( \frac{b_1}{(z-1)} + b_2 \right) \frac{1}{(z-1)} + b_3 \right) \frac{1}{(z-1)} + \dots \frac{1}{(z-1)} + b_{N+1}$$

$$= \sum_{i=1}^{N+1} \frac{b_i}{(z-1)^{N+1-i}}$$

$$= \frac{b_1 + b_2(z-1) + \dots + b_{N+1}(z-1)^N}{(z-1)^N}$$

$$L_i(z) = - \left( \frac{a_1}{(z-1)^N} + \frac{a_2}{(z-1)^{N-1}} + \dots + \frac{a_N}{(z-1)} \right)$$

$$= - \sum_{i=1}^N \frac{a_i}{(z-1)^{N+1-i}}$$

$$= - \frac{a_1 + a_2(z-1) + \dots + a_N(z-1)^{N-1}}{(z-1)^N}, \quad a_i, b_i > 0.$$

$\Rightarrow NTF(z) = \frac{1}{1-L(z)} = \frac{(z-1)^N}{D(z)}$ , where!

Note that the multiplier is 1 for  $(z-1)^N$ .

$D(z) = a_1 + a_2(z-1) + \dots + a_N(z-1)^{N-1} + a_{N+1}(z-1)^N$

$\Rightarrow$  All the NTF zeros lie at DC  $\Rightarrow z=1$

$\hookrightarrow$  Since  $NTF(\infty)=1 \Rightarrow$  the NTF is realizable.

$\hookrightarrow$   **$a_i$ 's** introduce finite non-zero poles into the NTF to control OBG or  $|H|_{\infty}$ .

$\hookrightarrow$  also determine the zero of  $L(z)$ .

$\hookrightarrow$  found by comparing  $D(z)$  with the denominator of the required  $NTF(z)$ .  $a_i > 0 \forall i$

$\bullet$   $STF(z) = \frac{L_0(z)}{1-L_1(z)} = \frac{b_1 + b_2(z-1) + \dots + b_{N+1}(z-1)^N}{D(z)}$

$\hookrightarrow$   **$b_i$ 's** determine the zeros of the STF and  $a_i$  its poles.

$\hookrightarrow$  poles of NTF and STF are shared.

$\hookrightarrow$  STF zeros can be placed in such a way so as to cancel some of the poles, allowing STF to have a lower roll-off rate than set by  $\frac{b_1}{D(z)}$ .

$\bullet$  This NTF can be implemented using a Butterworth response as all the zeros are at DC.

$\hookrightarrow$  non-zero values of  $a_i$ 's are required to realize the prescribed poles

$\Rightarrow$  No flexibility in choosing  $a_i$  branches

$\bullet$  More flexibility in choosing the values of  $b_i$ 's  $\rightarrow b(2:end)=0$  in MATLAB

$\hookrightarrow$  All  $b_i$ 's except  $b_1$  can be chosen to be zero  $\Rightarrow$  only one feed-in branch

Ex. for  $b(z: \text{end}) = 0$

$$STF(z) = \frac{b_1}{D(z)} \Rightarrow \text{for } |STF|=1 \text{ at low frequencies } b_1 = D(0).$$

↳ All the zeros of STF lie at  $\infty$ .

- $b$ 's are obtained by coefficient matching of the numerators.
- when only  $b_1$  is used, we need to make sure that  $|D(e^{j\omega})|$  is maximally flat in the signal band to make  $|STF|$  constant in this region. ← Important!


**Low-Distortion CTFB case:**

when  $b_i = a_i$  for  $i \leq N$  and  $b_{N+1} = 1$

↳  $STF = 1$  (for all frequencies)

$$\Rightarrow V(z) = U(z) + NTF(z) \cdot E(z) \leftarrow \text{important equation for Low-Dist Modulators}$$

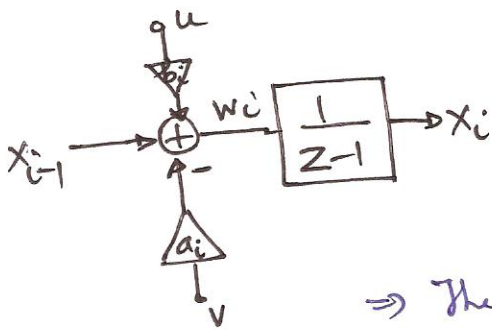⇒ input to the  $i$ th integrator for this case is:




$$\begin{aligned} W_i(z) &= X_{i-1}(z) - a_i V(z) + b_i U(z) \\ &= X_{i-1}(z) + a_i (U(z) - V(z)) \\ &= X_{i-1}(z) - a_i NTF(z) \cdot E(z) \end{aligned}$$

No signal here!



- ⇒ The input signal is not present in any integrator input.
- ⇒ The loop filter only processes the quantization noise  $e[n]$ .
  - ↳ reduced opamp output swings, especially for multibit quantizers.
- ⇒ integrator non-linearities will not introduce harmonic distortion into the output signal  $V(z)$ .

• This also results in lesser amount of dynamic range scaling (DRS).  
 ↳ more convenient element (caps) values. ← Verify this point yourself.

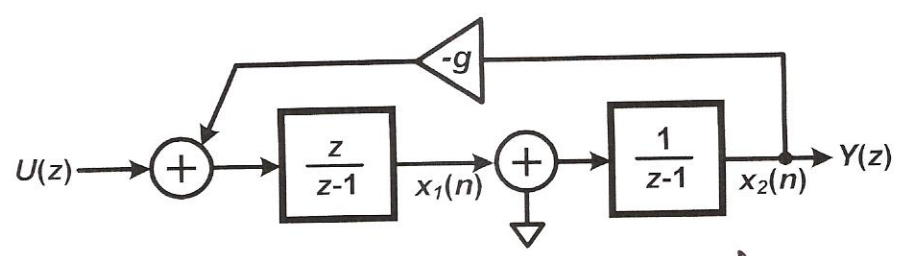- How to implement complex zeros?
- Use feedback around pairs of integrators to form resonators.



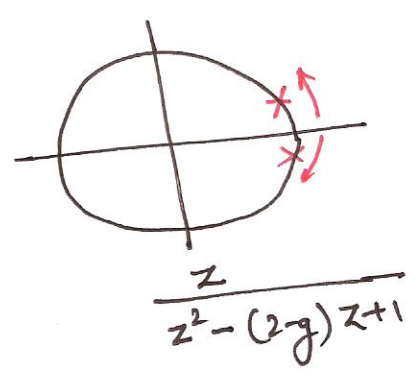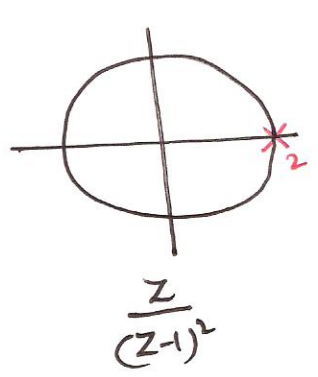- Non-delaying + delaying integrator pair
- Add a small amount of negative-feedback around the integrator pair to form a resonator.
  - ↳ Move the open-loop poles away from the  $z=1$  (DC) point along the unit circle.
  - ↳  $L_1(z)$  poles eventually become NTF(z) zeros.



$$U \frac{z}{(z-1)^2} - \frac{g z}{(z-1)^2} Y = Y$$

$$\Rightarrow R(z) = \frac{Y}{U} = \frac{z}{(z-1)^2 + g z} = \frac{z}{z^2 - (2-g)z + 1}$$

$$= \frac{z}{z^2 - (2 \cos \alpha)z + 1}$$

$$= \frac{z}{(z - e^{j\alpha})(z - e^{-j\alpha})}$$

$$\Rightarrow \cos \alpha = 1 - \frac{g}{2}$$

$$\Rightarrow \alpha = \cos^{-1} \left( 1 - \frac{g}{2} \right)$$

$\Rightarrow$  complex roots at  $\omega = \pm \alpha = \pm \cos^{-1} \left( 1 - \frac{g}{2} \right)$ .

Now, consider,

$$\cos \alpha = 1 - \frac{g}{2}$$

$$1 - 2\sin^2 \frac{\alpha}{2} = 1 - \frac{g}{2}$$

$$\Rightarrow \sin\left(\frac{\alpha}{2}\right) = \pm \frac{\sqrt{g}}{2}, \quad \text{using for } \alpha \ll \pi, \sin(\alpha) \approx \alpha.$$

$$\Rightarrow \boxed{\alpha \approx \pm \sqrt{g}}$$


$\Rightarrow$  the roots are precisely on the unit-circle irrespective of the value of  $g$ .

$\Rightarrow$  Resonator poles are located at

$$z = e^{\pm j\sqrt{g}}$$

- Combine the integrator pairs in the CIFB topology to form the CRFB (Cascade of Resonators with distributed feedback)
  - $\hookrightarrow$  Note that the resonator has one non-delaying integrator
- for odd-order, the first integrator is not paired-up.
  - $\hookrightarrow$  reduce noise coupling from the 'g' branch.
- The value of  $g$ 's can be directly obtained from the optimized zero locations.
- Now, we can implement either inverse-chebyshev or any other NTF response with complex zeros.

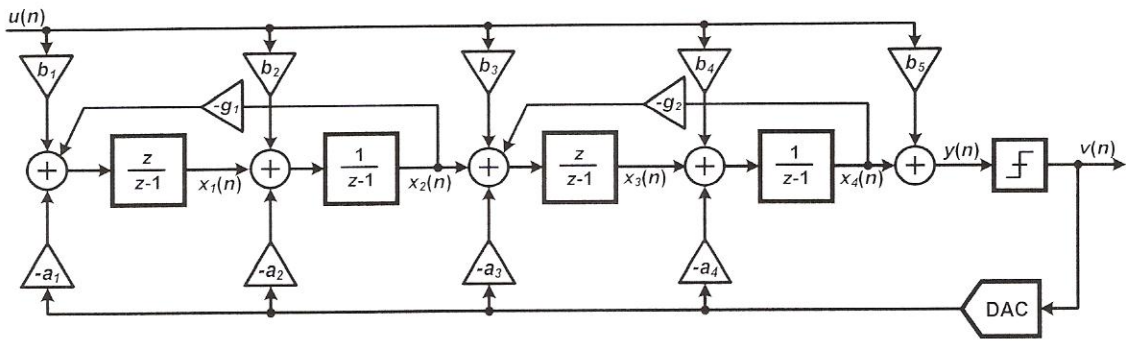• Consider the 4<sup>th</sup> order CRFB topology



• Here, 1<sup>st</sup> and 3<sup>rd</sup> integrators are delay-free to keep the  $L_1(z)$  poles on the unit circle.

• In this topology, the transfer function from  $V$  to  $X_2$  is

$$R_1(z) = \left. \frac{X_2(z)}{V(z)} \right|_{U(z)=0} = \frac{-a_1 z + a_2(z-1)}{z^2 - (2-g_1)z + 1}$$


• Now, for wideband ADC's realized using switched-capacitor integrators, it is advantageous to have a delay in each of the integrators.

↳ relaxes speed requirements on the amplifiers used.

↳ Now, the resonator will need to accommodate two delaying integrators!



• Resonator with delaying integrators.

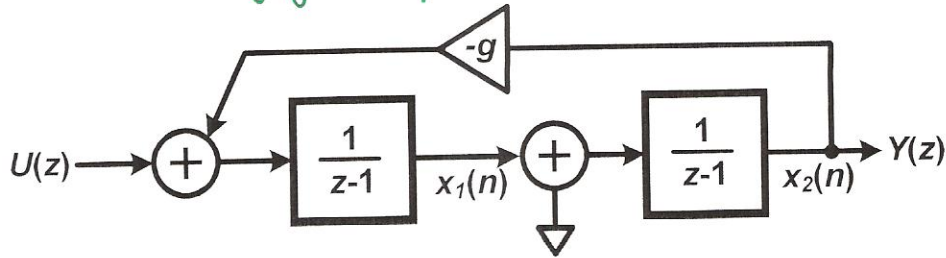


$$\Rightarrow R_1(z) = \frac{Y(z)}{U(z)} = \frac{1}{z^2 - 2z + (g+1)}$$

$\Rightarrow$  the poles are at  $z_{\pm} = 1 \pm j\sqrt{g}$

$\Rightarrow |z_{\pm}| = \sqrt{1+g} > 1 \Rightarrow$  outside the unit circle

•  $\tan \alpha = \pm \sqrt{g_1}$

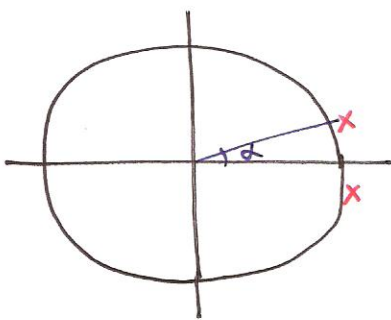$\Rightarrow \alpha = \pm \tan^{-1}(\sqrt{g_1}) \approx \pm \sqrt{g_1}$  for  $\omega_i \ll \pi$




This leads to the topology called "CIFB with Resonators" or simply CIFB in the  $\Delta\Sigma$  toolbox.

• These resonators by themselves unstable, ( $\because$  poles are outside the unit circle) but they are embedded in an overall stable feedback system which prevents oscillations.  
 $\hookrightarrow$  overall the loop is stable.

• The value of  $(g_i)$  comes from the  $\omega_i$  (or  $\alpha$ ).  
 $\hookrightarrow$  The rest of the parameters ( $a_i$  &  $b_i$ ) are found by equating the polynomials of  $L_0(z)$  and  $L_1(z)$ .  
 $\hookrightarrow$  Done using software tools (ie.  $\Delta\Sigma$  toolbox)  
 • realizeNTF() function

### CIFB topology with resonators.

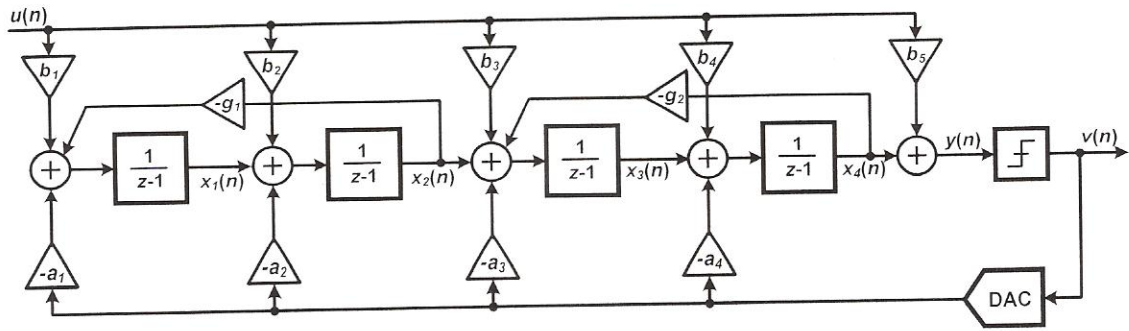

Now to complete the analysis,

$$R_2(z) = - \frac{a_3 z + a_4 (z-1)}{z^2 - (2-g_2)z + 1} = \frac{X_4(z)}{X_2(z)} \Big|_{u(z)=0}$$

\*  
 $\frac{X_4(z)}{V(z)} \Big|_{U(z)=0} = R_1(z) \cdot R_0(z) + R_2(z)$  ← think superposition for!  
 $= R_1(z) \left( \frac{z}{z^2 - (2-g_2)z + 1} \right) + R_2(z)$

$V \rightarrow X_2$     $X_2 \rightarrow X_4$     $V \rightarrow X_4$  directly

$$\Rightarrow L_1(z) = - \frac{(a_3 z + a_4 (z-1))z + [z^2 - (2-g_1)z + 1] \cdot (a_3 z + a_4 (z-1))}{(z^2 - (2-g_1)z + 1)(z^2 - (2-g_2)z + 1)}$$

$L_0(z) \Rightarrow$  negative of above, with  $b_i$ 's replacing  $a_i$  in  $R_1(z)$  and  $R_2(z)$  and  $b_5$  added as a constant term

$$\Rightarrow L_0(z) = \frac{(b_1 z + b_2 (z-1))z + [z^2 - (2-g_1)z + 1] (b_3 z + b_4 (z-1)) + b_5}{(z^2 - (2-g_1)z + 1)(z^2 - (2-g_2)z + 1)}$$

• Note the MATLAB warnings when 'CIFB' topology is used with optimized zeros.

# ECE 697 Delta-Sigma Converters Design

## Lecture#15 Slides

Vishal Saxena  
([vishalsaxena@u.boisestate.edu](mailto:vishalsaxena@u.boisestate.edu))



## Fourth-Order Loop-Filter Example

$$NTF(z) = (1 - z^{-1})^4$$



$$STF(z) = z^{-1}$$

$$L_0(z) = \frac{STF(z)}{NTF(z)} = \frac{z^{-1}}{(1 - z^{-1})^4}$$
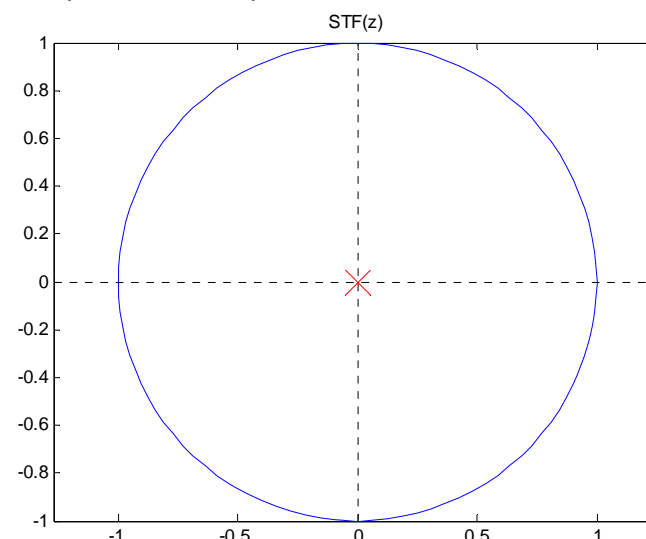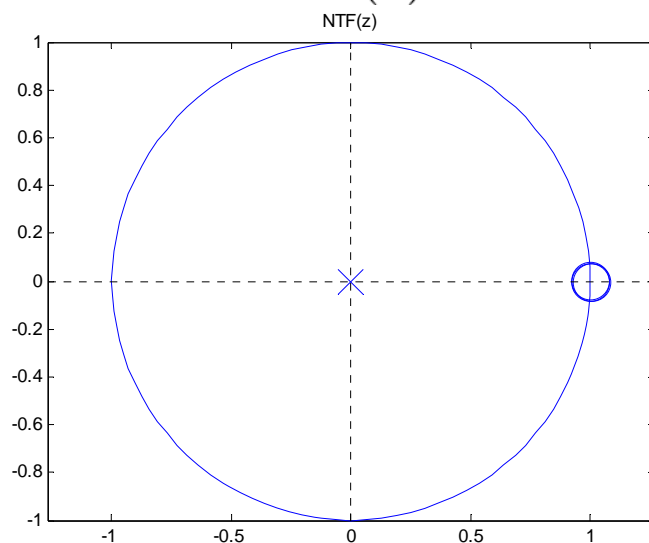
$$L_1(z) = \frac{1}{NTF(z)} - 1 = \frac{4z^{-1} \left(1 - \frac{1}{2}z^{-1}\right) \left(1 - z^{-1} + \frac{1}{2}z^{-2}\right)}{(1 - z^{-1})^4}$$





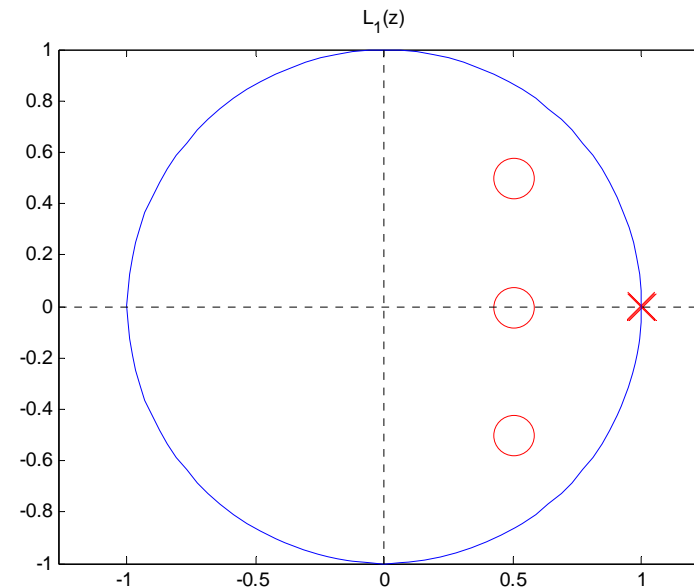
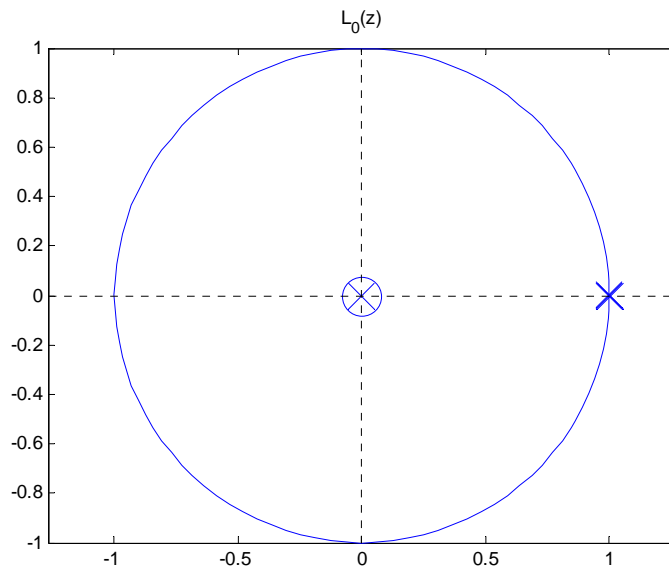
## Fourth-Order Loop-Filters: $L_0$ and $L_1$





- $L_0$  and  $L_1$  share same poles.
  - ✓ These poles become NTF zeros.
- $L_1$  zeros combined with the poles, give rise to NTF poles.
- $L_0$  zeros are different from those of  $L_1$ .
- Refer to the notes for details.
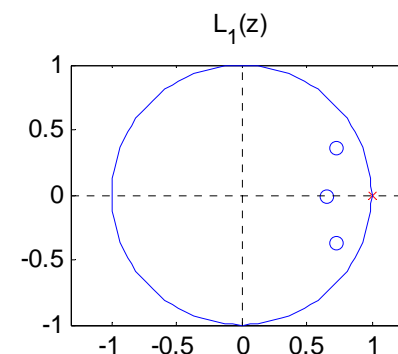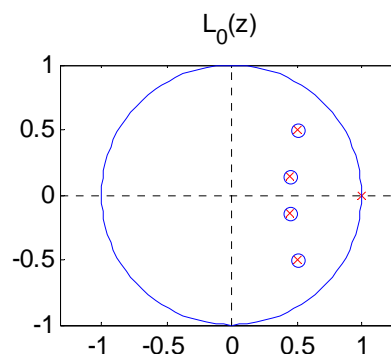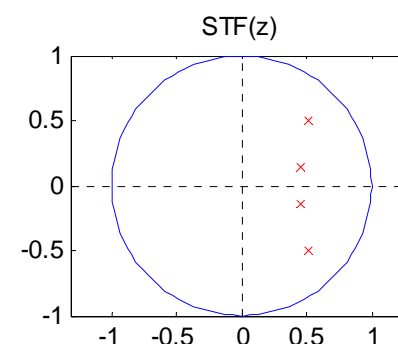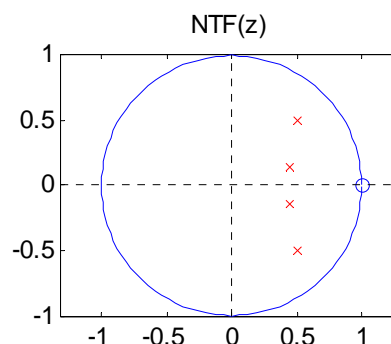
# CIFB Example 1



- ❑ CIFB, order = 4
- ❑ All NTF zeros at  $z=1$ , i.e.  $\text{opt} = 0$ .
- ❑ OBG = 3, OSR = 16, nLev = 15.
- ❑ Only single input coupling is used
  - ✓  $\mathbf{b}(2:\text{end}) = 0$
  - ✓ Maxflat poles in STF
- ❑  $\mathbf{a} = [0.16 \ 0.86 \ 1.9 \ 2.1]$
- ❑  $\mathbf{b} = [0.16 \ 0 \ 0 \ 0]$
- ❑  $\mathbf{c} = [1 \ 1 \ 1 \ 1]$
- ❑  $\mathbf{g} = [0 \ 0]$



# CIFB Example 1 contd. : NTF and STF

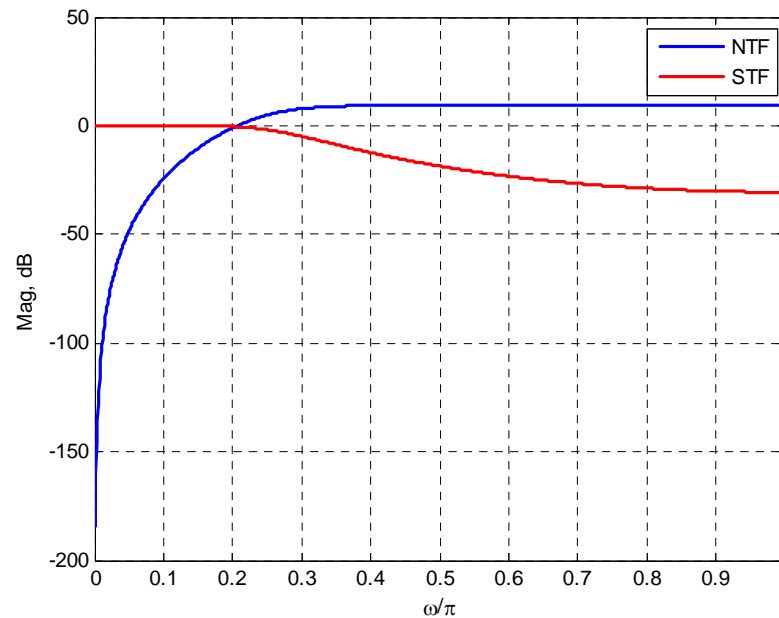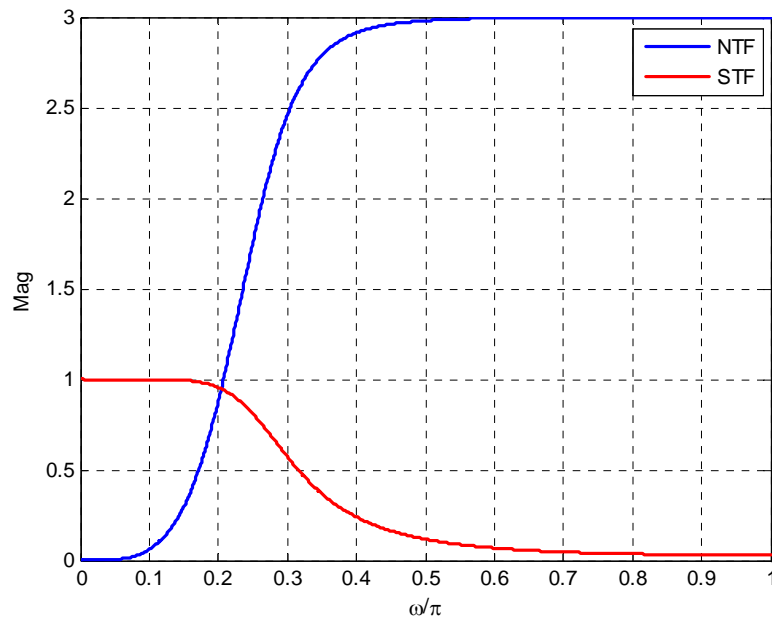

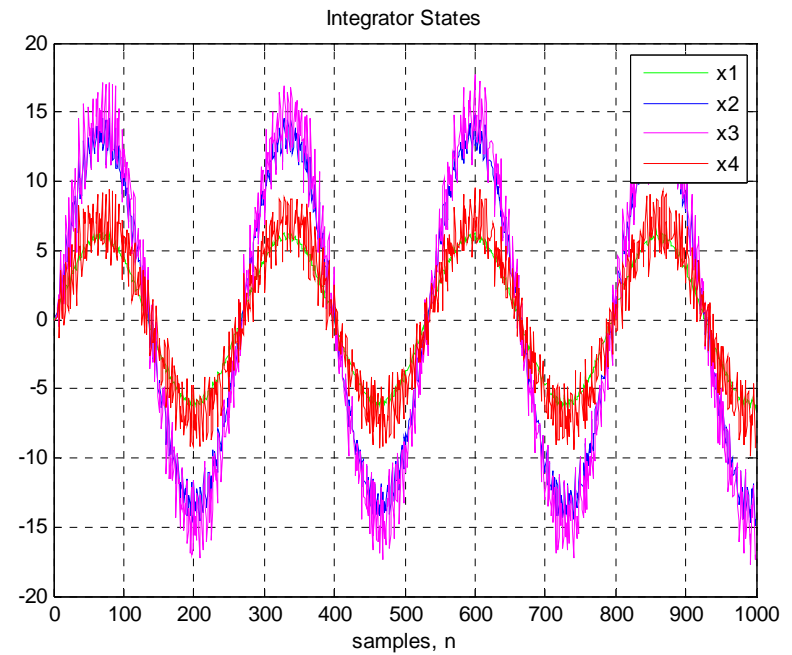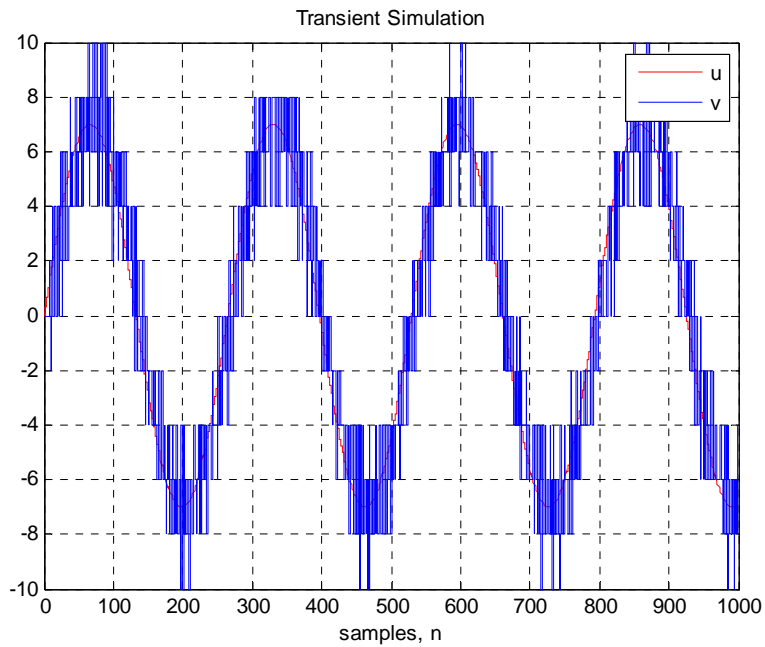
# CIFB Example 1 contd. : Loop-Filter States








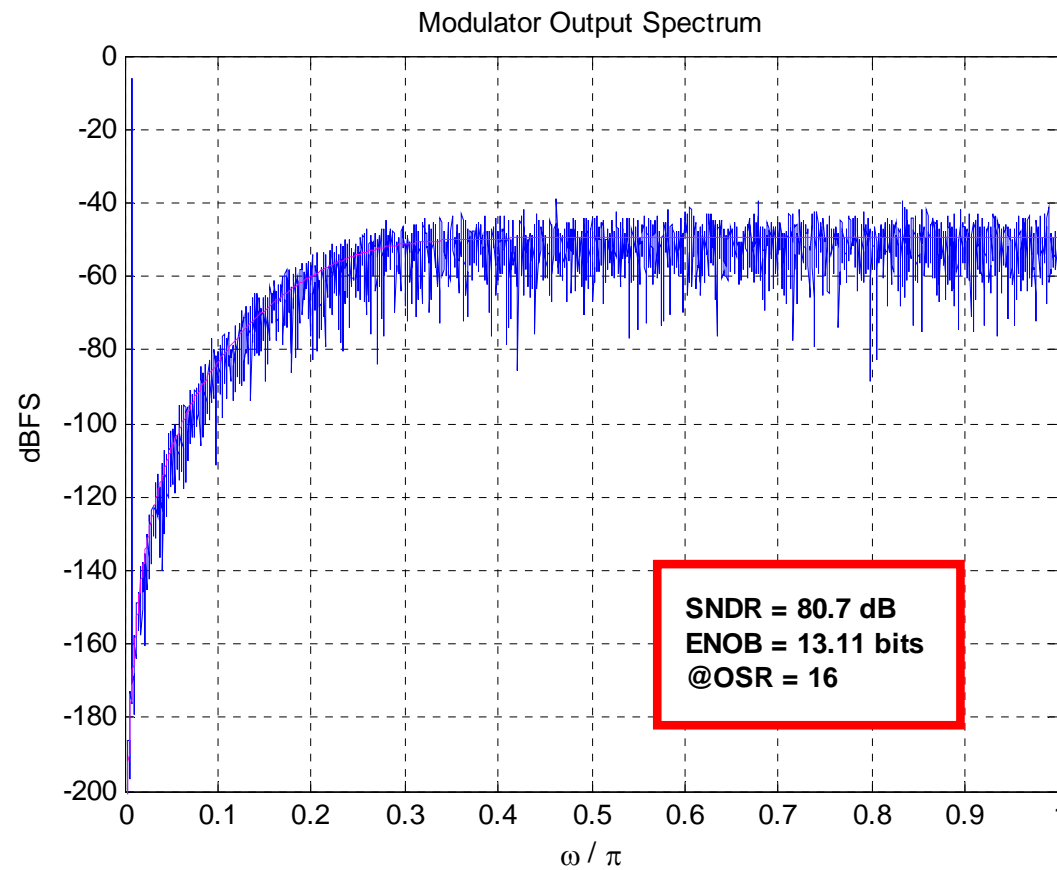
# CIFB Example 1 contd. : Simulated Spectrum




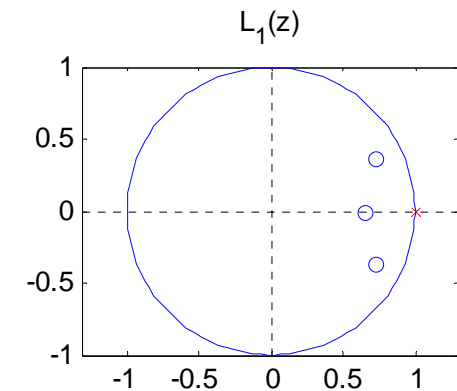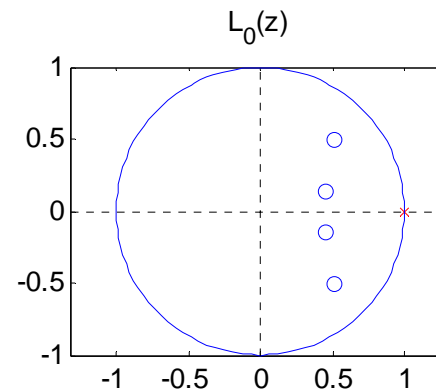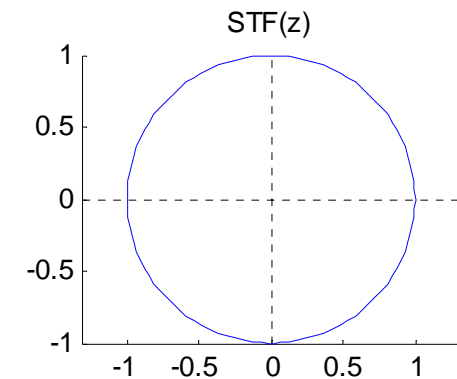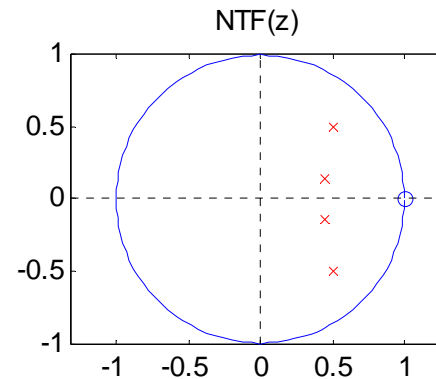
# CIFB Example 2



- ❑ CIFB, order = 4
- ❑ All NTF zeros at  $z=1$ , i.e.  $\text{opt} = 0$ .
- ❑ OBG = 3, OSR = 16, nLev = 15.
- ❑ Low-distortion topology
  - ✓  $b_i = a_i$
  - ✓ Maxflat poles in STF
- ❑  $\mathbf{a} = [0.16 \ 0.86 \ 1.9 \ 2.1]$
- ❑  $\mathbf{b} = [0.16 \ 0.86 \ 1.9 \ 2.1]$
- ❑  $\mathbf{c} = [1 \ 1 \ 1 \ 1]$
- ❑  $\mathbf{g} = [0 \ 0]$



# CIFB Example 2 contd. : NTF and STF

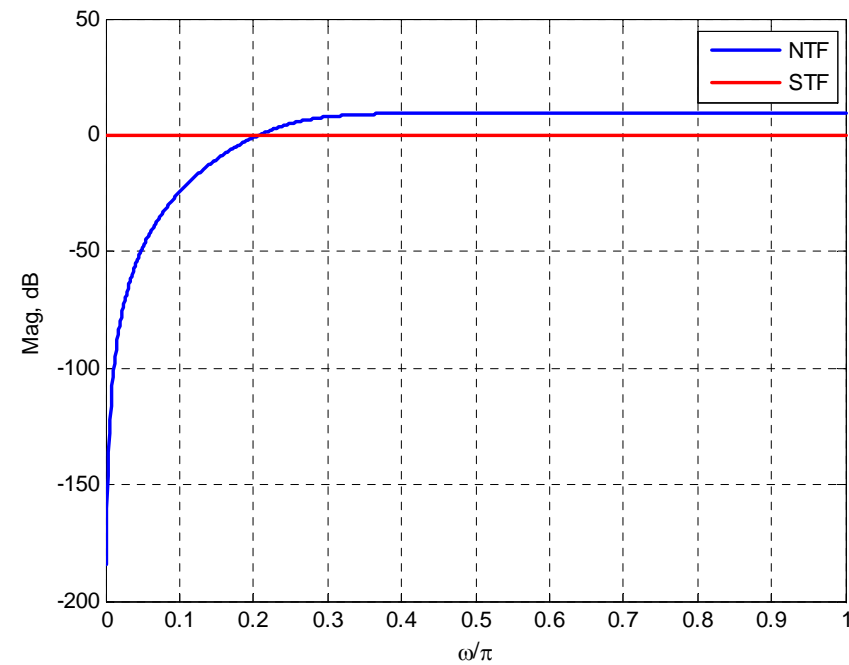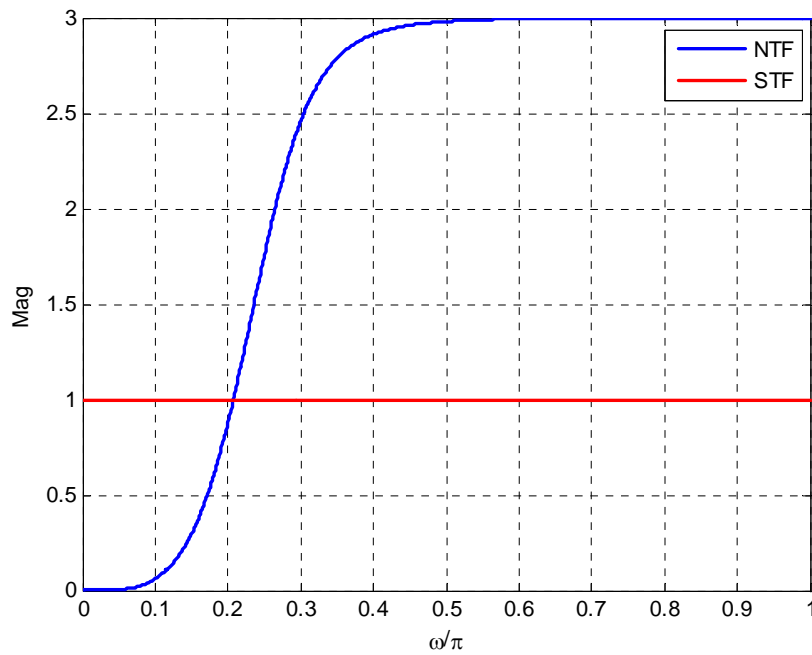

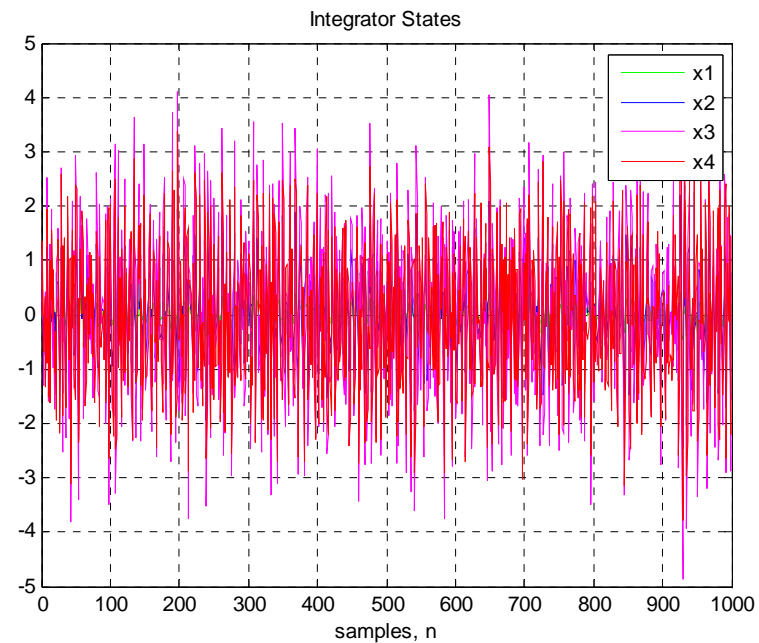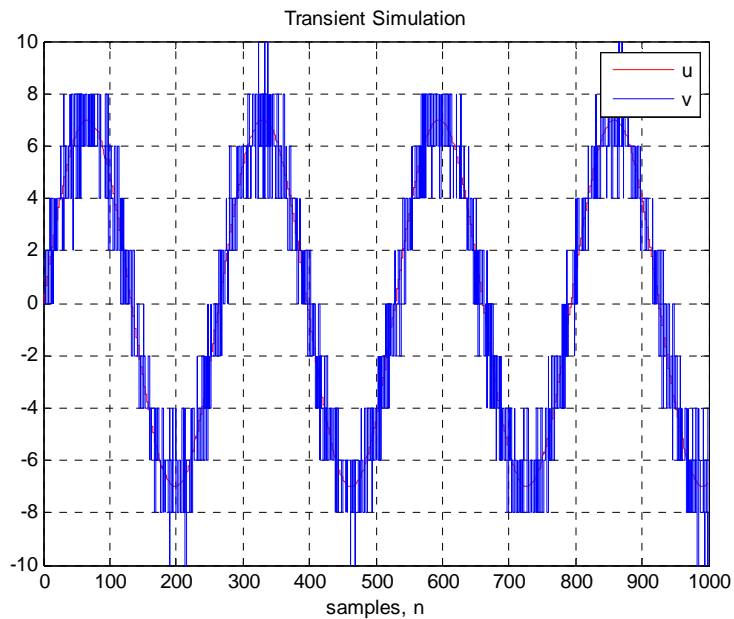
# CIFB Example 1 contd. : Loop-Filter States



□ Note that the integrator state excursions are drastically reduced.
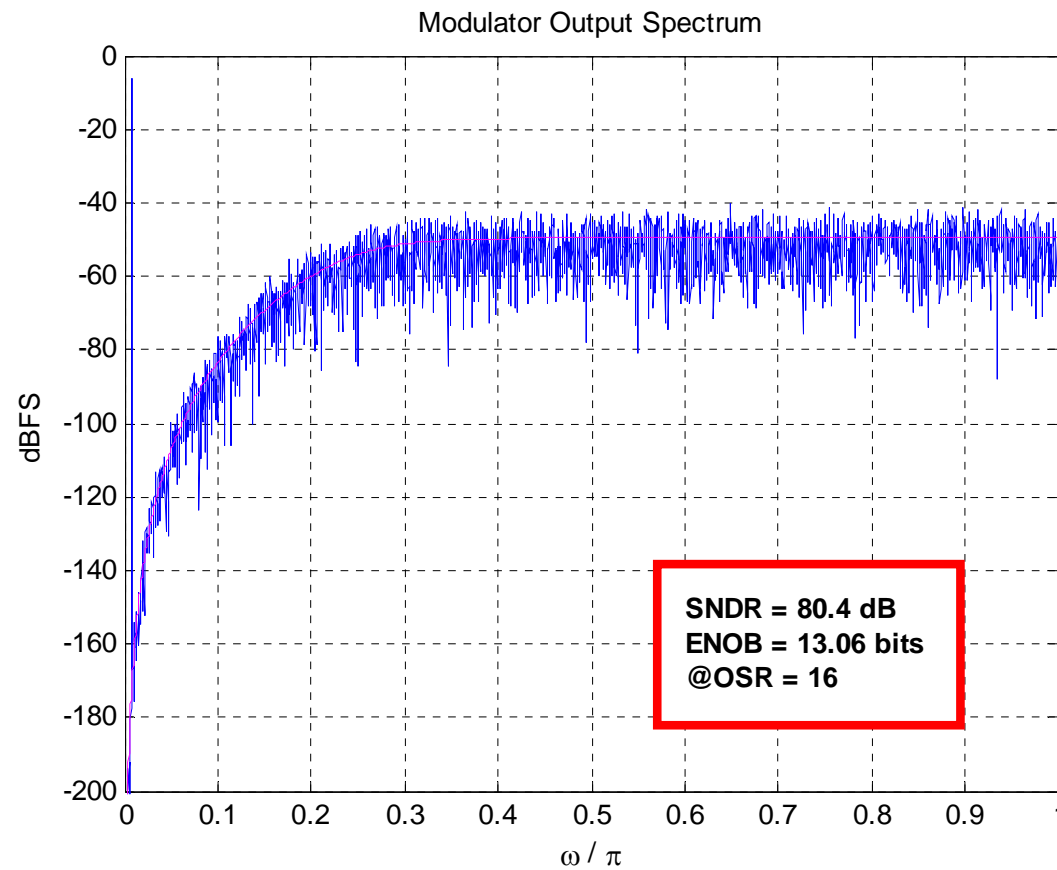
# CIFB Example 2 contd. : Simulated Spectrum



## Other Examples of Feedback Topologies

- ❑ CRFB with single feed-in
  - ✓ CRFB\_4<sup>th</sup>\_Order\_1.m
- ❑ Low-distortion CRFB topology
  - ✓ CRFB\_4<sup>th</sup>\_Order\_2.m
- ❑ CIFB with single feed-in and optimized NTF zeros
  - ✓ CIFB\_Opt\_4<sup>th</sup>\_Order\_1.m
- ❑ Low-distortion CIFB topology with optimized NTF zeros
  - ✓ CIFB\_Opt\_4<sup>th</sup>\_Order\_2.m