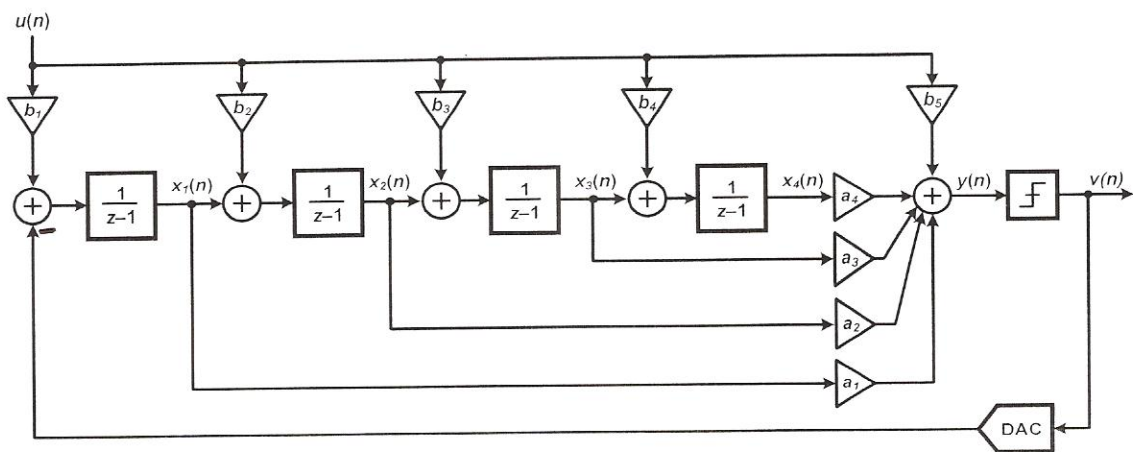


# feedforward Loop-filter Topologies

①

## CIFF



### Cascade of Integrators with feedforward summation (CIFF)

↳ Use feedforward paths rather than feedback ones to create the zeros of the NTF.

By inspection!

If  $I(z) = \frac{1}{z-1} = \frac{z^{-1}}{1-z^{-1}}$  ← delaying integrator / accumulator.

$$L_1(z) = -a_1 I(z) - a_2 I^2(z) - \dots - a_N I^N(z)$$

$$L_0(z) = b_1 (a_1 I + a_2 I^2 + \dots + a_N I^N) + b_2 (a_2 I + \dots + a_N I^{N-1}) + b_3 (a_3 I + \dots + a_N I^{N-2}) + \dots + b_{N+1}$$

$$\Rightarrow L_1(z) = - \frac{a_1 + a_2(z-1) + \dots + a_N(z-1)^{N-1}}{(z-1)^N} \quad \leftarrow \begin{array}{l} L_1 \text{ same as in CIFB} \\ \Rightarrow \text{Same NTF} \end{array}$$

$$L_0(z) = \frac{\gamma_1 + \gamma_2(z-1) + \dots + \gamma_N(z-1)^{N-1} + \gamma_{N+1}(z-1)^N}{(z-1)^N}$$

$$\gamma_{N+1} = b_{N+1}$$

$$\gamma_N = b_1 a_1 + b_2 a_2 + b_3 a_3 + \dots$$

$$\gamma_{N-1} = b_2 a_1 + b_3 a_2 + b_4 a_3 + \dots$$

$$\vdots$$


$$\gamma_1 = b_1 a_N$$

} complicated  
 ← This generic case is not used in the Toolbox.

- Now, consider the case when  $b_2=b_3=\dots=b_N=0$  and  $b_1=b_{N+1}=1$  ②  
 $\hookrightarrow$  input coupling, and full input feedforward.

Note!

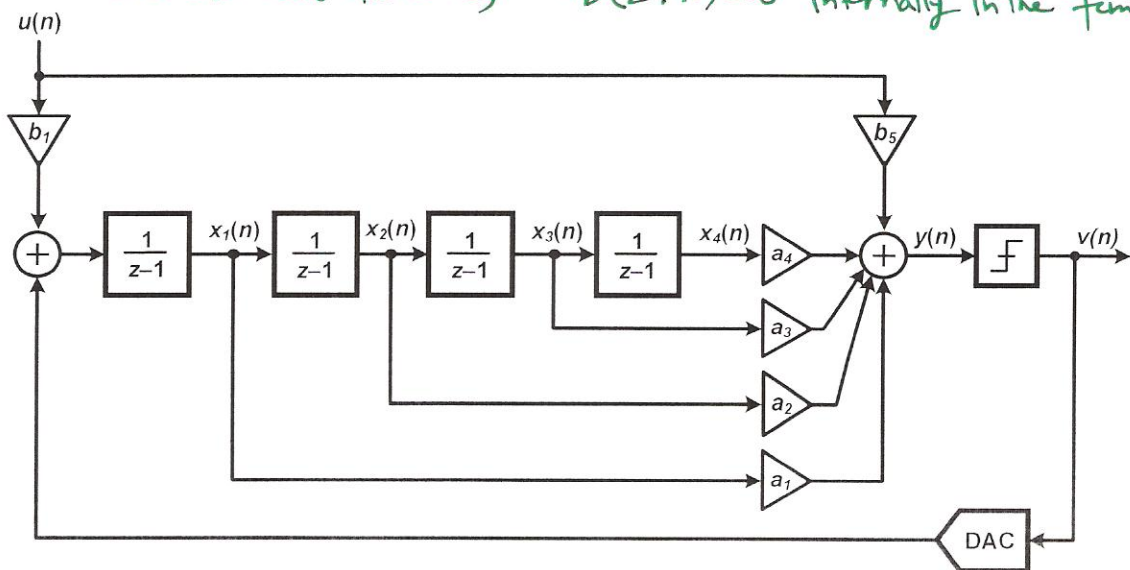- Toolbox `realizeNTF()` function only uses  $b_1$  and  $b_{N+1}$ , rest  $b$ 's are set to 0  $\Rightarrow b(2:N)=0$  internally in the function.



Now, the  $L_0(z)$  simplifies to

$$\begin{aligned} L_0(z) &= (a_1 I + a_2 I^2 + \dots + a_N I^N) + 1 \\ &= 1 - (-a_1 I - a_2 I^2 - \dots - a_N I^N) \\ &= 1 - L_1(z) \end{aligned} \quad \longrightarrow \textcircled{1}$$

$$\Rightarrow \begin{cases} L_0(z) = 1 - L_1(z) & \text{when } b_{N+1} = 1 \\ L_0(z) = -L_1(z) & \text{when } b_{N+1} = 0. \end{cases}$$

from ①, we have when  $b_{N+1} = 1$  (full input feedforward case)

$$\boxed{STF(z) = \frac{L_0(z)}{1 - L_1(z)} = 1}, \text{ Also } NTF(z) = \frac{1}{1 - L_1(z)}$$

when  $b_{N+1} = 0$ , (only input is coupled)

$$\boxed{STF(z) = 1 - NTF(z) = \frac{-L_1(z)}{1 - L_1(z)}, \text{ } NTF(z) = \frac{1}{1 - L_1(z)}$$

• when  $b_1 = b_{N+1} = 1$

STF = 1

$$\Rightarrow U(z) - V(z) = U(z) - \underbrace{[U(z) + NTF(z)E(z)]}_{V(z)}$$

$$\Rightarrow NTF(z) \cdot E(z)$$

→ Loop-filter doesn't process the input signal  $U(z)$  at all.

↳ low distortion case

↳ same results apply to relaxed integrator implementation as seen for the CIFB low-distortion case.

• Note that implementing the low-distortion condition is easier with CIFF (only 2 branches) as opposed to  $(N+1)$  input coupling branches required for the CIFB case.

• when  $b_{N+1} = 0 \Rightarrow$  only input coupling is used then we saw that

STF(z) = 1 - NTF(z)


⇒ results in high-frequency peaking in the STF.

↳ add pre-filter to the inputs in this range to avoid overloading in the modulator.

or modify the ~~NTF~~ NTF/STF


↳ can use other  $b_i$ 's to attenuate the noise peaking.

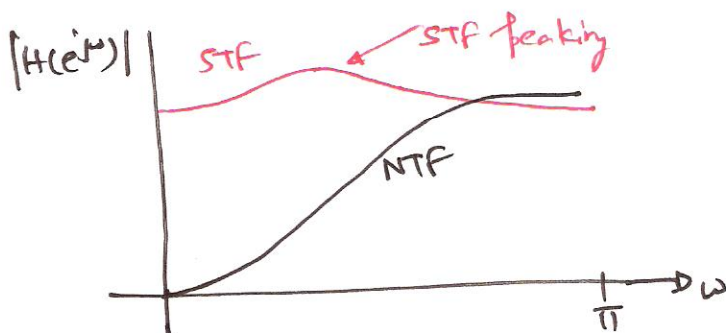↳ figure this out for CIFF/CRFB topologies.




↪

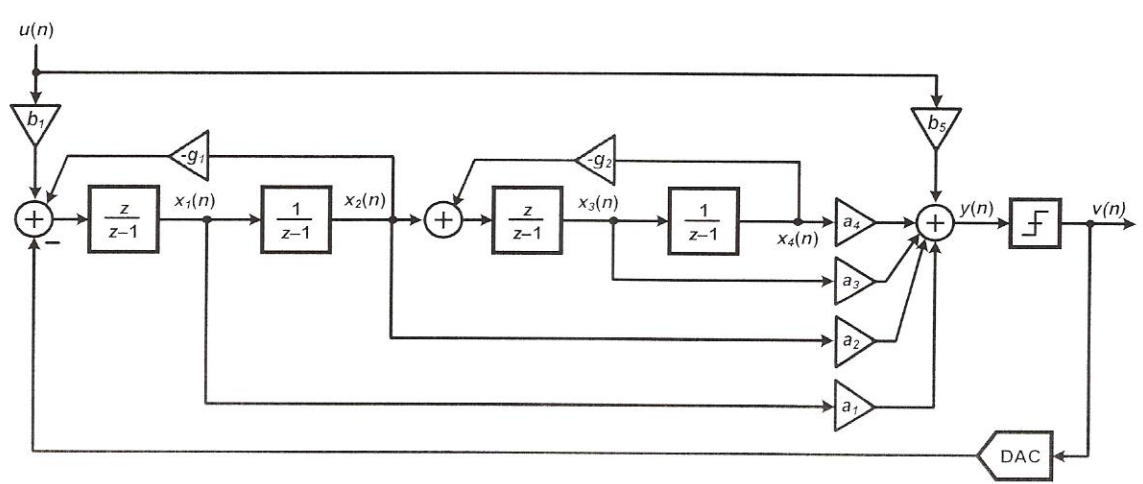- Add resonator feedbacks to create complex NTF zeros  
 ↳ CRFF (Cascade of Resonators with feedforward summation)



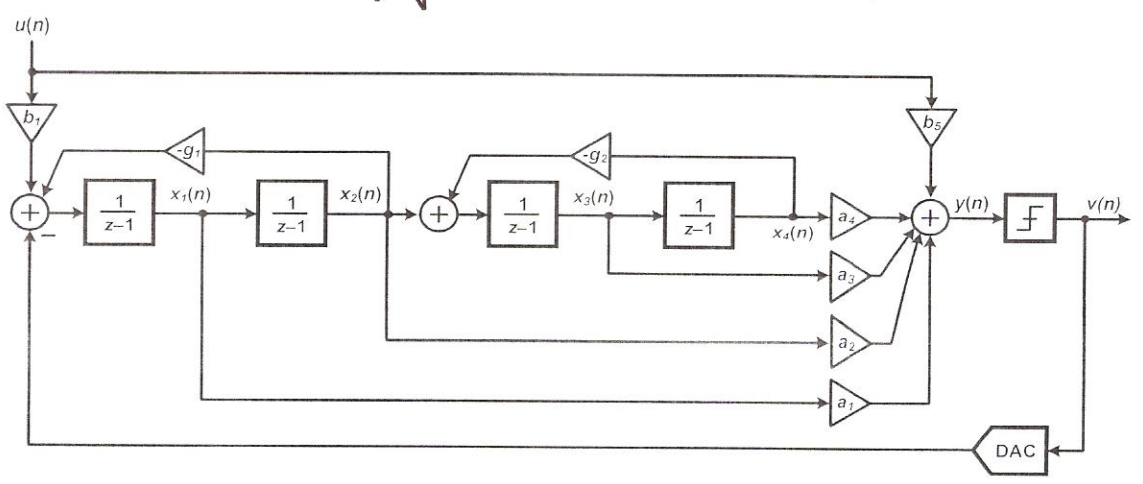- Can also use double-delaying resonators to modify the CRFF topology.



- Same analysis for resonators as seen for the CRFB/CEFB cases.
- Here, multiple input feed-in branches are also possible.  
 using  $b(2:N)$   
 ↳ modify toolbox function?



# Comparison between FB and FF topologies:

5

## Feed forward

- ① FF has relaxed dynamic range requirements.
- ② If full-FF is not used ( $b_{n+1} \neq 0$ ) STF peaking occurs.  
↳ a problem in CT-DSMs
- ③ only one DAC required
- ④ Needs a summation block
- ⑤ Timing can be tricky  
↳ need to quantize  $u$  and feed it back in zero time.
- ⑥ First integrator is fastest
- ⑦ First opamp is power hungry (noise reasons)  
⑥ & ⑦ → Best optimization for opamp power consumption
- ⑧ Small capacitor area

## FeedBack.

Integrator outputs contain significant amount of input signal as well as filtered quantization noise (Typically)

STF has good attenuation beyond the signal band

↳ Better AAF in CT-DSMs.

Requires many feedback DACs.

No extra summer required.

Not an issue

Last integrator is fastest (has large signal content)

First opamp is power hungry (noise reasons)

⑥ & ⑦ ⇒ first and last opamps are power hungry → more power is burnt.

Large capacitor area to accommodate the large signal swings

↳ DRS results in large c's.


↳ more power burnt in opamps

↳ Larger layout size.

If STF/AAF is not an issue, C<sub>IFF</sub> (CRFF) architecture is generally preferred.

• Intuition for larger integrator swings in CIFB/CRFB topology. (6)

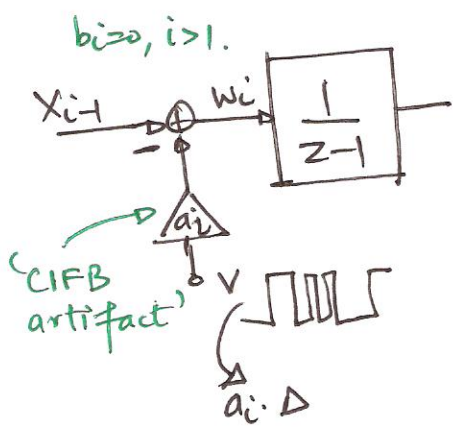Consider a DC input to the CIFB modulator with  $b_i = 0$  for  $i > 1$  and 1-bit quantizer feedback.



- Each integrator has  $\infty$  gain at DC
- $\Rightarrow$  Sum of all inputs  $= 0$  to prevent any dc component from appearing at the integrator input  $\rightarrow$  else loop-filter will saturate
- $\Rightarrow$  one input is the 1-bit feedback path another is the output of the previous integrator i.e.  $(X_{i-1})$ .

$\Rightarrow X_{i-1}$  must have a DC component to counteract the DC component of the 1-bit feedback.

$\Rightarrow$  Each integrator output contains a combination of filtered quantization noise and a low frequency component equal to the input signal.

• from simulations, the signal component in  $X_i$  is significantly larger than the noise component

$\hookrightarrow$  larger integrator swings ( $\max(X_i) > \max(X_{i-1})$ )  
(verify yourself)

$\hookrightarrow$  need larger integrator feedback caps to limit the swings, as a result of dynamic range scaling (DRS)

$\hookrightarrow$  requires large  $c_2$  values.

$\Rightarrow$  CIFB circuits tend to be larger and more power hungry than the FF ones.

# Multi-stage Modulators

①

- For low-OSR values, it's no longer possible to obtain high SNR values in a single (quantizer) loop modulator by raising the order of the loop-filter.

↳ MSA ↓ as order ↑

↳ can increase quantizer resolution

↳ Flash ADC design becomes complicated


↳ DAC → linearity issues (complex ~~DEM~~ DEM for large n/ler)

↳ complexity ↑ as  $2^N$

- max 4-5 bits quantizer is employed.

- Use digital cancellation of noise, rather than filtering, by using a multistage (cascade) structure of the modulator.
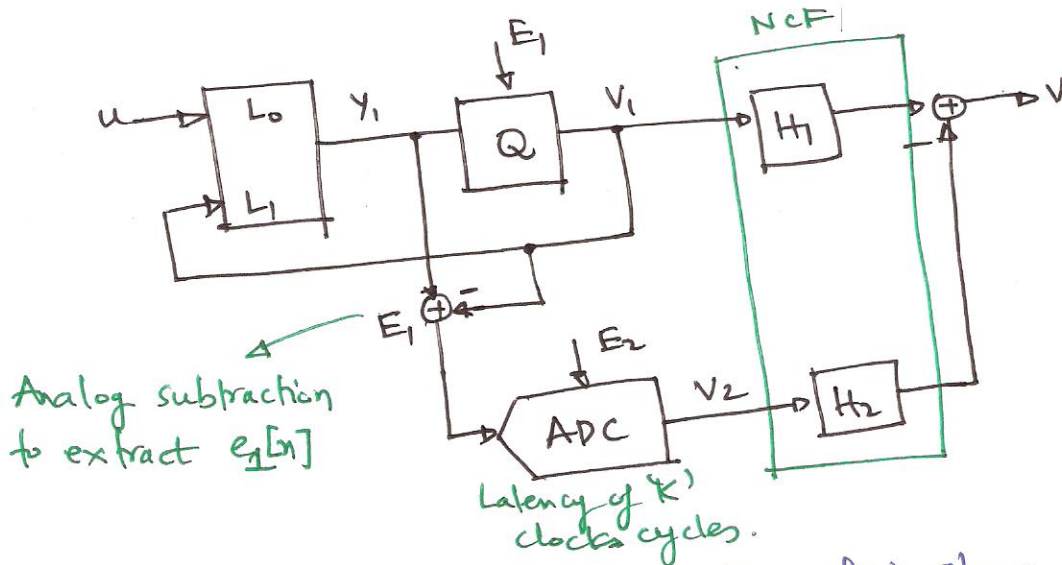
## ① L-0 Cascade (Leslie-Singh Structure).



- $L^{\text{th}}$ -order  $\Delta\Sigma$  modulator in the first stage. followed by a static (zero-order) ADC as the second-stage → eg. a pipelined ADC of 10-bit resolution.
- Combine the outputs of the two stages  $v_1$  &  $v_2$  to obtain the overall output  $v$ .



↳  $e_1[n]$  is extracted in analog form by

$$e_1 = V_1 - y_1$$

⇒  $e_1$  is then converted to digital form by a multibit (say 10 bits) ADC forming the 2<sup>nd</sup>-stage.

↳ introduces a second-quantization noise  $e_2[n]$ .

- $|e_2[n]| \ll |e_1[n]|$

- 2<sup>nd</sup>-stage can have arbitrary latency (no feedback loop around it)

↳ realized using a low complexity pipelined ADC.

•  $V_1$  and  $V_2$  are filtered by digital stages  $H_1$  and  $H_2$  respectively and then "added" together.

↳  $H_1(z) = z^{-k}$  simply ⇒ matches the latency of the 2<sup>nd</sup>-stage.

↳  $H_2(z)$  ⇒ digital equivalent of the first-stage NTF.

$$\Rightarrow V(z) = H_1(z) \cdot V_1(z) - H_2(z) \cdot V_2(z)$$

$$= \underbrace{z^{-k}}_{H_1} [STF_1 \cdot U + NTF_1 \cdot E_1] - \underbrace{NTF_1 \cdot z^{-k}}_{H_2} \cdot \underbrace{[E_1 + E_2]}_{u_2 = e_1}$$

$$\cong z^{-k} [STF_1 \cdot U - NTF_1 \cdot E_2]$$

if  $E_1$  is perfectly cancelled. i.e.  $H_2 = NTF_1$

• Compare  $V(z)$  with  $V_1(z)$ :

Except for the delay of  $z^{-k}$ ,

- $E(z)$  is replaced by  $-E_2(z)$

- PSD level  $E_2(z)$  is much smaller than that of  $E_1(z)$

↳ it's cheaper to construct a pipelined ADC than a multibit-loop quantizer.


↳ Enhances SNR by as much as 25-30dB.



Subtraction Implementation!

• To obtain  $e_1[n]$  by subtraction, the operation of the quantizer must be delay-free, which may not be practical.

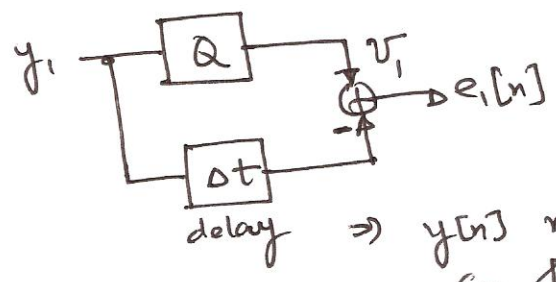$\therefore e_1[n] = \underbrace{v_1[n]}_{n=t} - y_1[n]$   
possible with finite quantizer delay



$\Rightarrow y_1[n]$  must be delayed before subtraction can be carried out  
 $\hookrightarrow$  done using switched-cap techniques.

• To avoid the subtraction altogether, the input signal of the second-stage can be chosen as  $y_1[n]$ , instead of  $e_1[n]$ .

Then, we have

$$Y_1(z) = V_1(z) - E_1(z) = STF_1 \cdot U + (NTF_1 - 1) E_1$$

keeping  $H_1(z) = z^{-k}$ , but choosing  $H_2$  as

$$H_2(z) = \frac{NTF_1(z)}{NTF_1(z) - 1}, \text{ the overall output now becomes}$$

$$V(z) = z^{-k} [STF_1 \cdot U + NTF_1 \cdot E_1] - \frac{NTF_1}{NTF_1 - 1} z^{-k} \{STF_1 \cdot U + (NTF_1 - 1) E_1 + E_2\}$$

• Assuming ideal cancellation of terms, we get

$$V(z) = \frac{z^{-k} STF_1(z)}{1 - NTF_1(z)} \cdot U(z) + \frac{z^{-k} NTF_1(z)}{1 - NTF_1(z)} \cdot E_2(z)$$

$\therefore$  In the signal band  $|NTF| \ll 1$  then

$$\frac{NTF_1}{1 - NTF_1} \approx NTF_1 \text{ in the signal band}$$

$\hookrightarrow$  can get SQNR close to the ~~value~~ one obtained earlier.

Disadvantage:

$y_1(n)$  contains  $u(n)$  as well as  $f_1(n)$

↳ second-stage must be able to handle a larger input signal.

↳ Also the second-stage must have lower distortion in processing the  $u(n)$  input.

↳ Not very attractive overall.

Consider one of the low distortion structures

- Eg. CIFB with  $b_i = a_i$  and  $b_{N+1} = 1$ ,

or CFF with  $b_1 = b_{N+1} = 1$  and  $b(2:N) = 0$

⇒ both cases have  $STF = 1$ .

↳ output of the last integrator in the <sup>low-dist CIFB</sup> case is:

$$X_N(z) = Y(z) - b_N U(z)$$

$$= STF(z) \cdot U(z) - (1 - NTF(z)) E(z) - b_N U(z)$$

$$\Rightarrow X_N(z) = -(1 - NTF(z)) \cdot E(z)$$


This signal  $X_N(z)$  can be used as the input for the second-stage of the L-O cascade.

↳ doesn't contain any  $u(n)$

↳ second-stage need not very linear

Example topology:

• 2<sup>nd</sup> order CFF

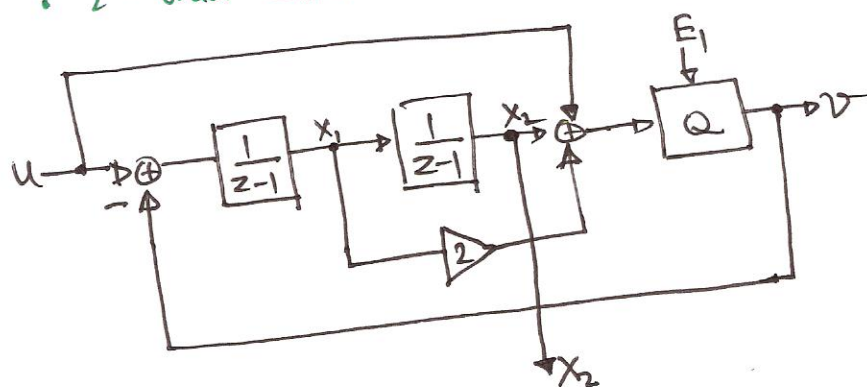

$$NTF = (1 - z^{-1})^2$$

$$STF = 1$$

$$X_2 = -z^{-2} E(z)$$

↳ feed directly to the second stage input.

# ECE 697 Delta-Sigma Converters Design





## Lecture#16 Slides

Vishal Saxena  
([vishalsaxena@u.boisestate.edu](mailto:vishalsaxena@u.boisestate.edu))




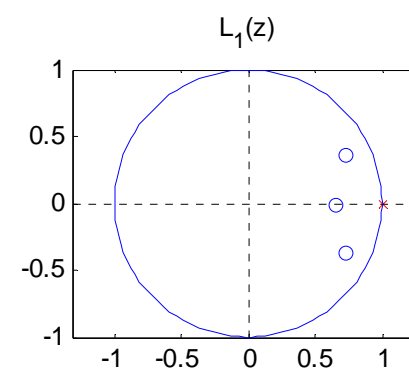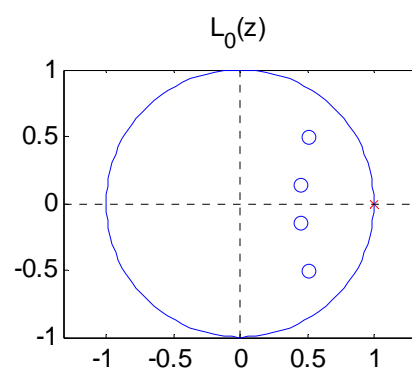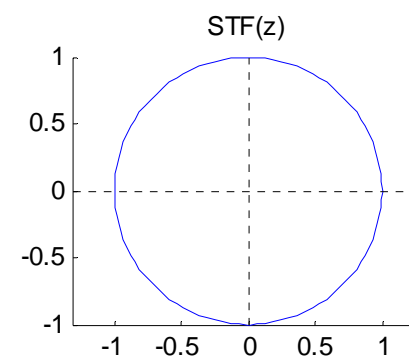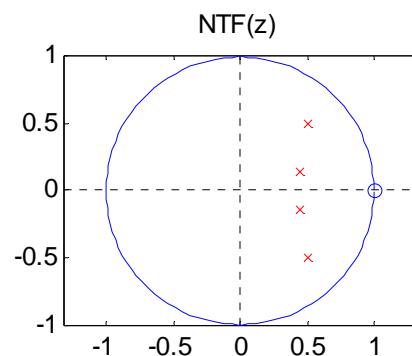
# CIFF Example 1



- ❑ CIFF, order = 4
- ❑ All NTF zeros at  $z=1$ , i.e.  $\text{opt}=0$ .
- ❑ OBG = 3, OSR = 16, nLev = 15.
- ❑ Low-distortion topology
  - ✓  $b(1)=b(5)=1$
  - ✓  $b(2:4)=0$
- ❑  $\mathbf{a} = [2.1 \ 1.9 \ 0.86 \ 0.16]$
- ❑  $\mathbf{b} = [1 \ 0 \ 0 \ 0 \ 1]$
- ❑  $\mathbf{c} = [1 \ 1 \ 1 \ 1]$
- ❑  $\mathbf{g} = [0 \ 0]$



# CIFF Example 1 contd. : NTF and STF

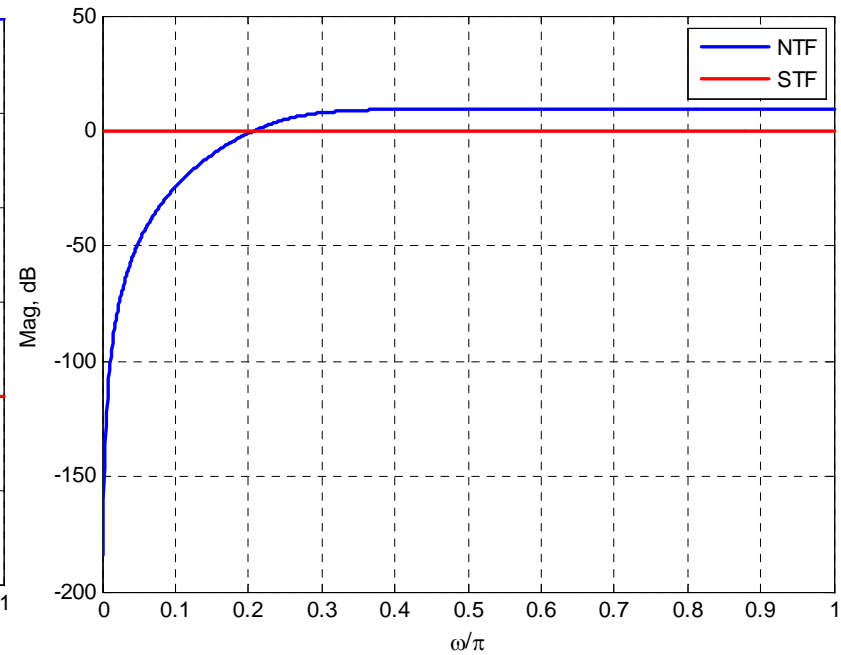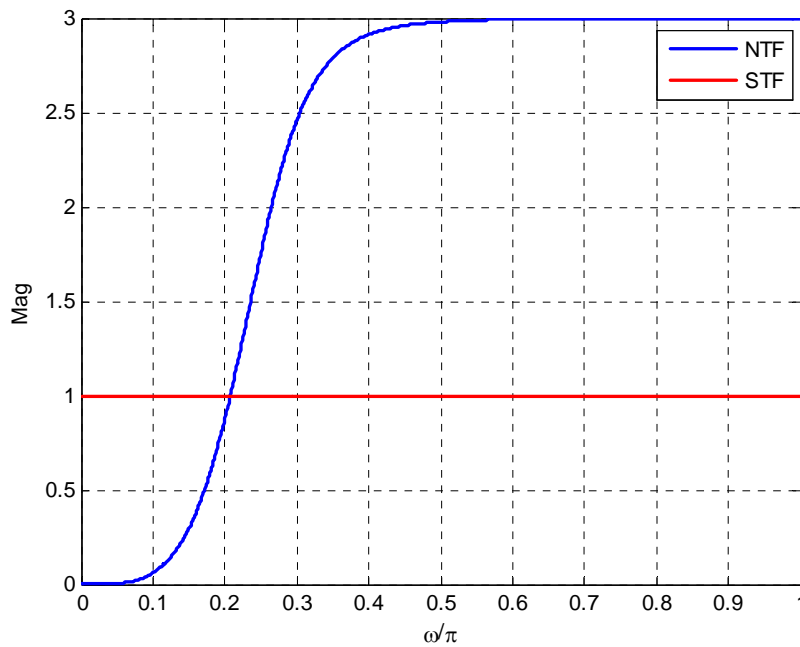

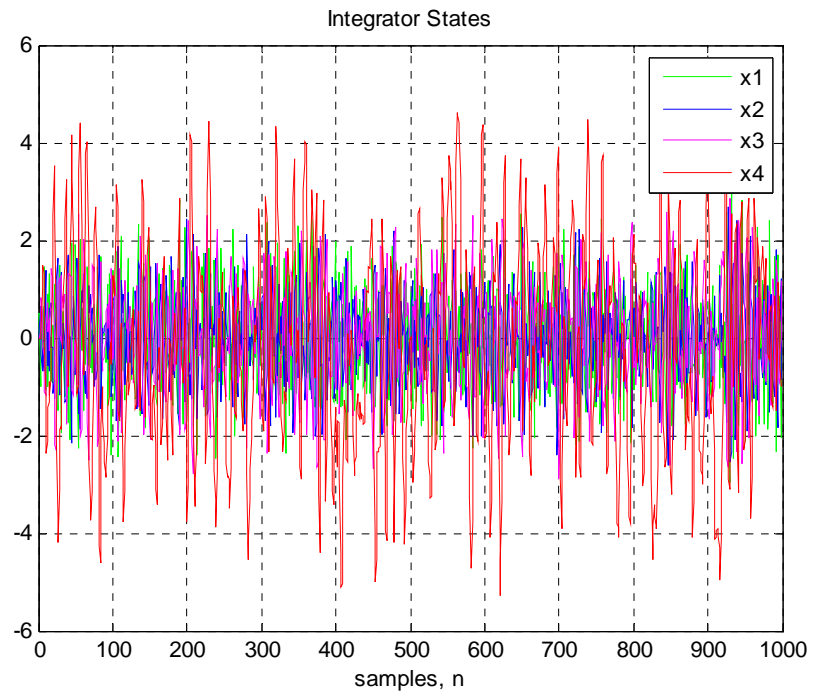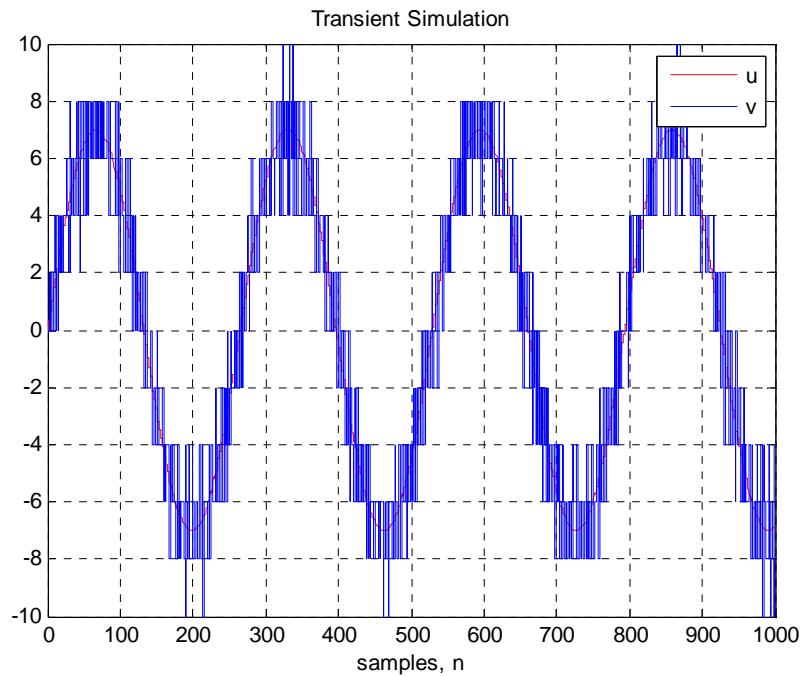
# CIFF Example 1 contd. : Loop-Filter States








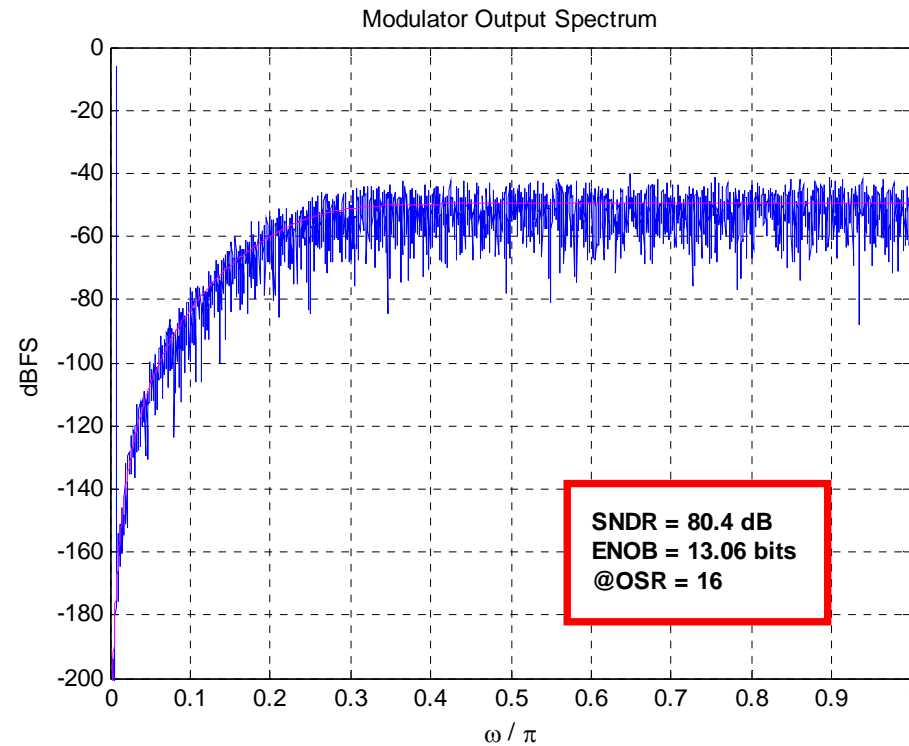
# CIFF Example 1 contd. : Simulated Spectrum




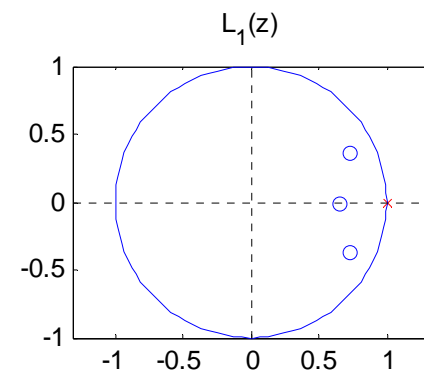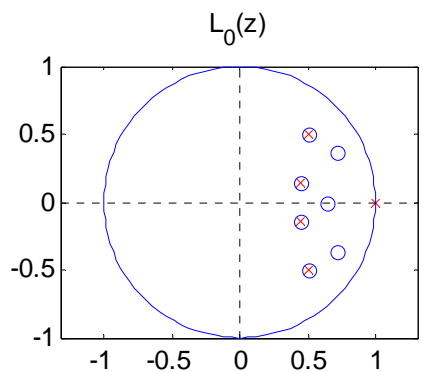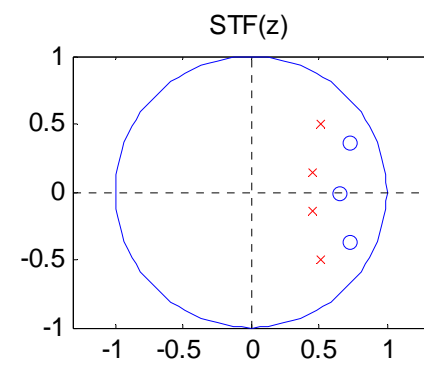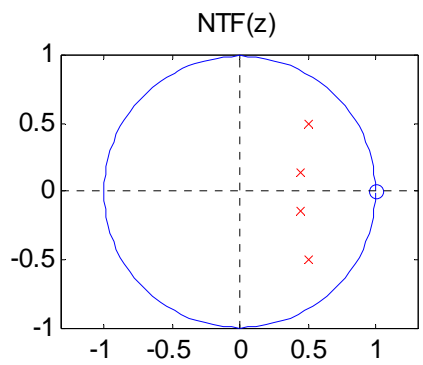
# CIFB Example 2

- CIFB, order = 4
- All NTF zeros at  $z=1$ , i.e.  $\text{opt}=0$ .
- OBG = 3, OSR = 16, nLev = 15.
- Only single input feed-in used
  - ✓  $b(2:\text{end})=0$
- $\mathbf{a} = [2.1 \ 1.9 \ 0.86 \ 0.16]$
- $\mathbf{b} = [1 \ 0 \ 0 \ 0]$
- $\mathbf{c} = [1 \ 1 \ 1 \ 1]$
- $\mathbf{g} = [0 \ 0]$





# CIFF Example 2 contd. : NTF and STF

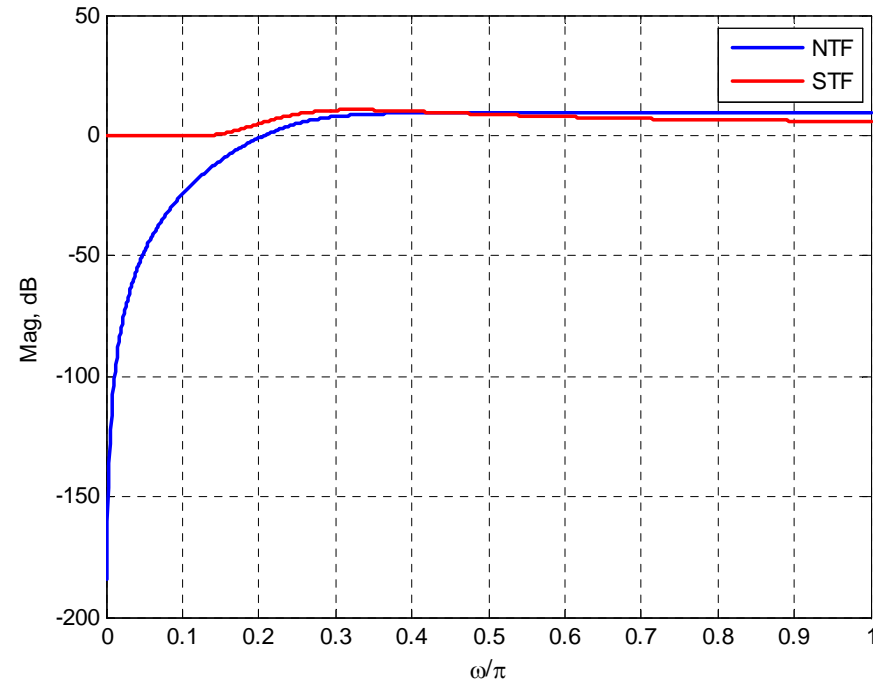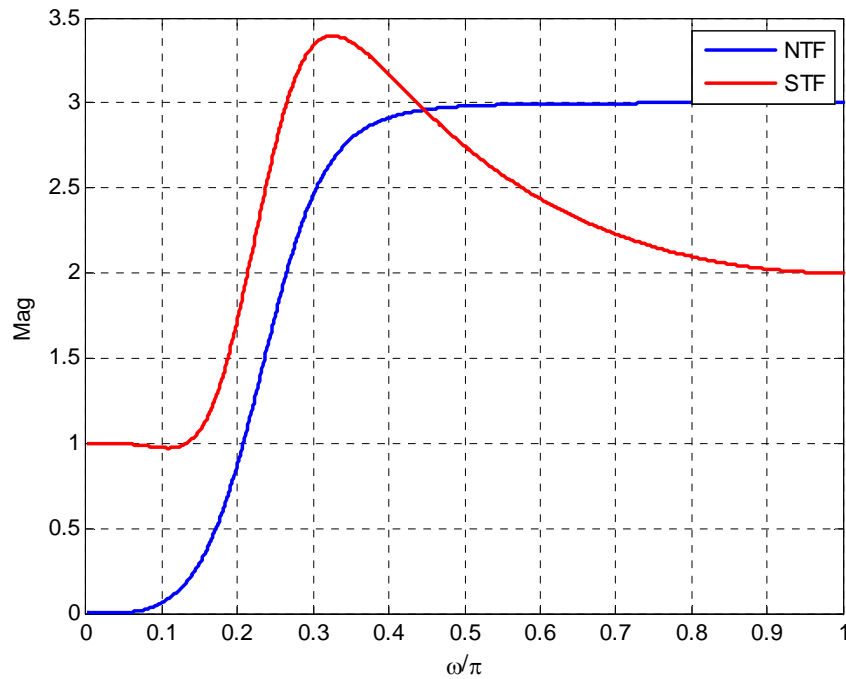

☐ Notice the significant STF peaking !



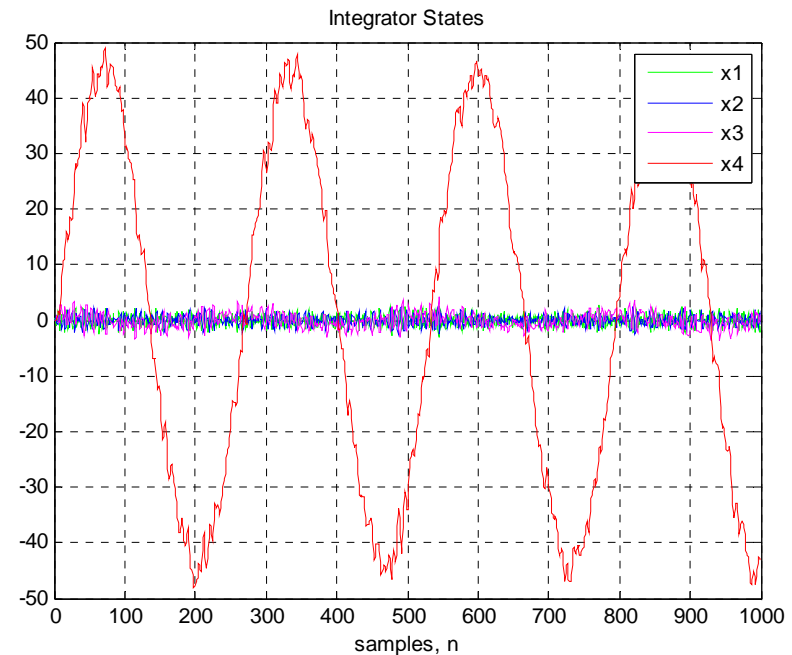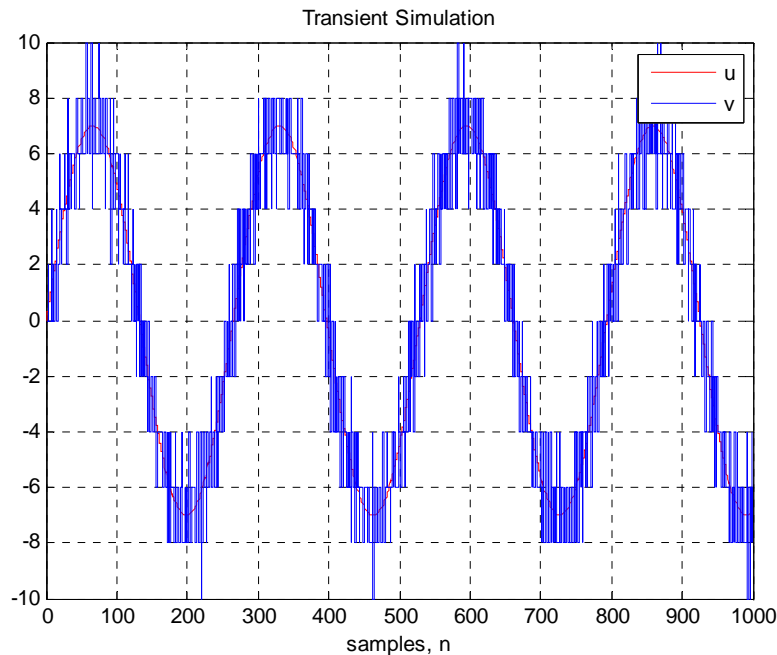
# CIFF Example 2 contd. : Loop-Filter States



- ❑ Last integrator output has significant signal content
  - ✓ Use dynamic range scaling.
  - ✓ Last integrator will burn more power in this case.
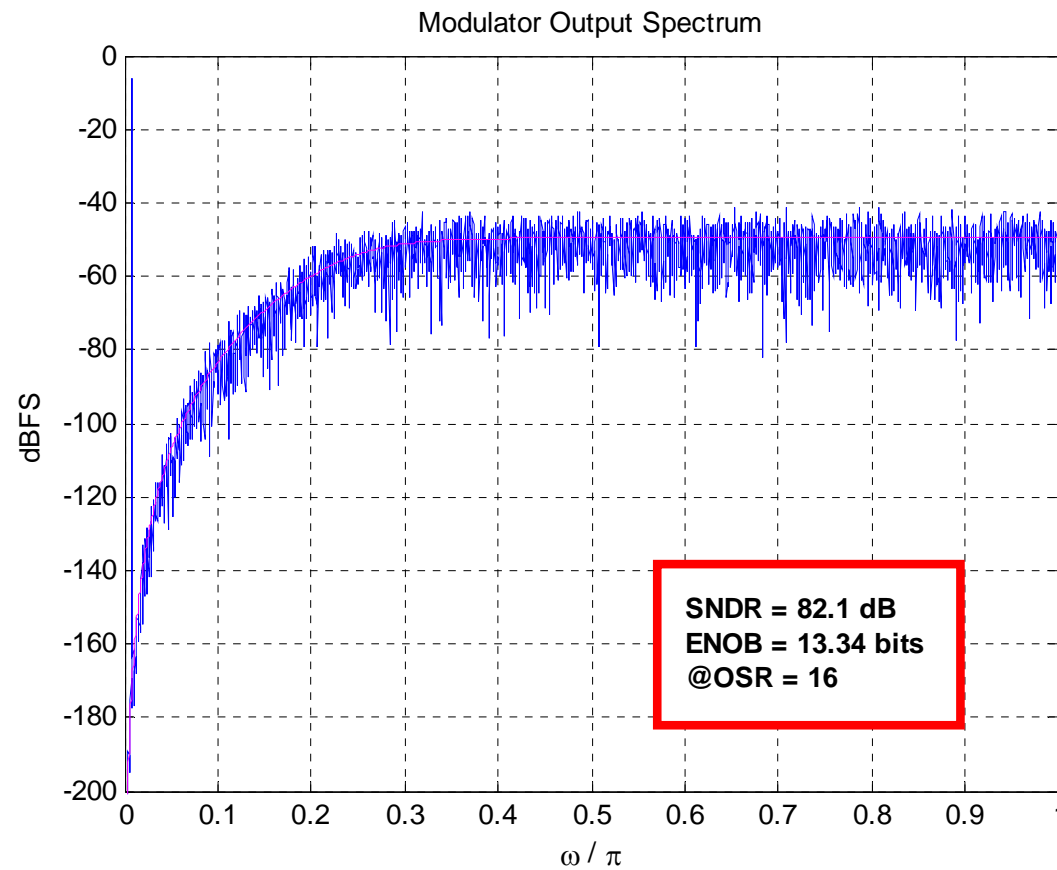
# CIFF Example 2 contd. : Simulated Spectrum



## Other Examples of Feed-forward Topologies

- ❑ Low-distortion CRFF topology
  - ✓ CRFF\_4<sup>th</sup>\_Order\_1.m
- ❑ CRFF with single feed-in
  - ✓ CRFF\_4<sup>th</sup>\_Order\_2.m
- ❑ Low-distortion CIFF topology with optimized NTF zeros
  - ✓ CIFF\_Opt\_4<sup>th</sup>\_Order\_1.m
- ❑ CIFF with single feed-in and optimized NTF zeros
  - ✓ CIFF\_Opt\_4<sup>th</sup>\_Order\_2.m
- ❑ STF peaking in FF topologies with single feed-in is an issue
  - ✓ CT FF DSM will have STF peaking as full-feedforward branch can't be used.
  - ✓ The feed-in coefficients  $b$ 's can be strategically used to realize CIFF/CRFB topology with better out-of-band STF attenuation.



# L-0 Cascade Simulation

□ TBD