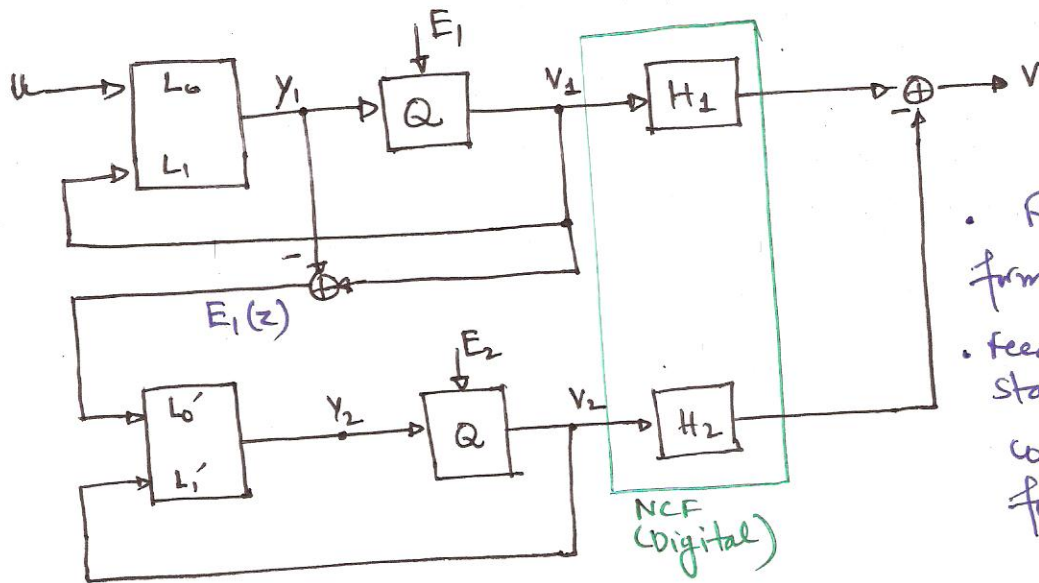


Cascaded (MASH) Delta-Sigma Modulators

①

Multi Stage Noise Shaping (MASH)

• Second stage in the cascade is another $\Delta\Sigma$ modulator.



- Find $e_1[n]$ in analog form by subtracting $e_1 = v_1 - y_2$
- feed $e_1[n]$ to the second stage of the modulator and convert it to its digital form.

1st stage: $V_1(z) = STF_1(z) U(z) + NTF_1(z) \cdot E_1(z)$

2nd stage: $V_2(z) = STF_2(z) E_1(z) + NTF_2(z) \cdot E_2(z)$


Final output:

$$\begin{aligned}
 V(z) &= H_1 V_1 - H_2 V_2 \\
 &= H_1 (STF_1 \cdot U + NTF_1 \cdot E_1) - H_2 (STF_2 \cdot E_1 + NTF_2 \cdot E_2) \\
 &= (H_1 STF_1 U - H_2 \cdot NTF_2 \cdot E_2) + \underbrace{H_1 NTF_1 \cdot E_1 - H_2 \cdot STF_2 \cdot E_1}_{\text{unwanted terms}} \\
 &= (H_1 STF_1 U - H_2 \cdot NTF_2 \cdot E_2) + \underbrace{(H_1 \cdot NTF_1 - H_2 \cdot STF_2)}_{\rightarrow 0} E_1
 \end{aligned}$$

• for cancelling E_1 , we MUST satisfy

$$H_1 \cdot NTF_1 = H_2 \cdot STF_2$$

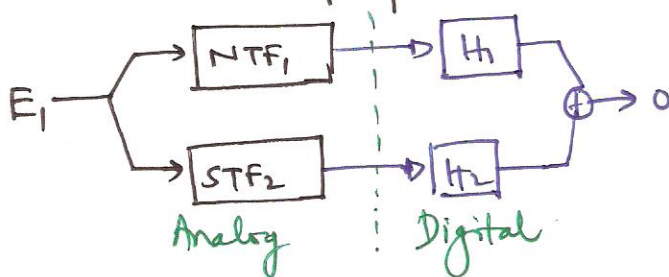\Rightarrow The two paths seen by ' E_1 ' must be identical for perfect cancellation of noise $e_1[n]$.



- The perfect noise cancellation never really occurs due to the mismatch between analog and digital circuitry, and due to the 'tonal' nature of the quantization noise $e_1(n)$.

- The simplest and most practical choice for H_1 and H_2 is

$$H_1 NTF_1 = H_2 STF_2$$

$$\Rightarrow \begin{cases} H_1 = STF_{2,d} \\ H_2 = NTF_{1,d} \end{cases} \text{ All digital filters}$$

- Since STF_2 is often just a delay $\Rightarrow H_1$ is easy to realize

The overall output, then, is given by

$$V = H_1 V_1 - H_2 V_2 = STF_1 \cdot STF_2 \cdot U - NTF_1 \cdot NTF_2 \cdot E_2$$

$$\begin{aligned} NTF &= \prod_i NTF_i \\ STF &= \prod_i STF_i \end{aligned}$$

Example: 2-2 MASH, aka (SOSO) ← second-order - second-order cascade

$$\Rightarrow STF_1 = STF_2 = z^{-2}, \quad NTF_1 = NTF_2 = (1-z^{-1})^2$$


$$\Rightarrow V(z) = z^{-4} U(z) - \underbrace{(1-z^{-1})^4}_{\text{fourth order noise shaping}} E_2(z)$$

↳ stability restrictions of only a 2nd-order loop!

Important:

- E_1 input to the second modulator stage needs to be scaled to fit it within the stable range (MSA) of the second $\Delta\Sigma$ modulator.
 - ↳ For a 2nd order, single-bit first-stage $\Delta\Sigma$, the usual scaling factor is $1/4$.
 - ↳ If multi-bit quantization is used, in the first-stage, the scaling factor can be greater than 1.
 - ↳ The inverse of this scaling factor (or coupling factor) needs to be included in H_2 to cancel $E_1(z)$.

Coupling of Stages:

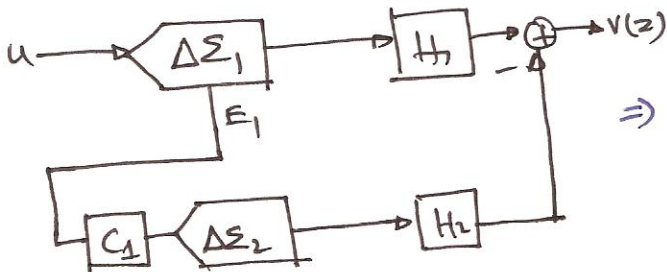

$\Rightarrow H_1 = STF_{1,d}$

$H_2 = \frac{1}{C_1} \cdot NTF_{1,d}$

interstage coupling coefficient

$Y(z) = STF_{1,d} \cdot STF_{2,d} U(z) + \frac{1}{C_1} \cdot NTF_{1,d} \cdot NTF_{2,d} E(z)$

$\Rightarrow NTF_{case} = \frac{(1-z^{-1})^{N_{case}}}{\prod_{i=1}^M c_i}$

$N_{case} = \sum_{i=1}^M N_i$

M = stages

$N_{case} \Rightarrow$ total order of the MASH $\Delta\Sigma$ modulator

- Due to the interstage coupling coefficients, the overall in-band noise is given as

$IBN = \frac{\sigma_e^2}{4\pi} \int_0^{\pi/OSR} \frac{|NTF_1(e^{j\omega})|^2 |NTF_2(e^{j\omega})|^2}{\prod_i c_i^2} d\omega = \frac{IBN_0}{\prod_i c_i^2}$

c_i 's are usually > 1 for single bit MASH first stage.

\Rightarrow if $c_i < 1 \Rightarrow$ IBN is increased


\Rightarrow ~~MASH~~ MASH performance is below the ideal value

- For NTF zero optimization, the complex NTF zeros from the synthesis can be paired-up into individual stage NTFs

$\Rightarrow NTF_1(z) \cdot NTF_2(z) = NTF(z)$ with zero optimization

\hookrightarrow need to think about the pole placement in individual loops.

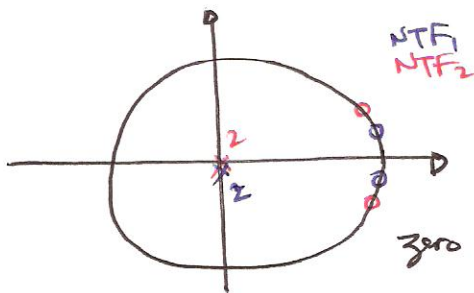\hookrightarrow 2nd order loops are generally stable with a reasonable MSA, even when the poles are at 0.



zero pairing in 2-2 MASH.

Noise leakage in MASH:

- If $H_1 \cdot NTF_1 \neq H_2 \cdot NTF_2$ due to imperfections in the realization of the analog transfer function with the digital logic filters H_1 & H_2 , then

↳ E_1 will appear at the output multiplied by the leakage transfer function $(STF_2 \cdot NTF_{2a} - NTF_1 \cdot STF_{2a})$, where 'a' denotes the actual value of the analog transfer function.

↳ This is known as **Noise leakage** in MASH ADC.

↳ results in serious deterioration in the noise performance of the ADC.

- It is advantageous for MASH system to use a low-distortion loop-filter structure in all stages, especially the one where the quantization noise is isolated by subtraction.

↳ Easy to obtain $e_1[n]$ without any subtraction, i.e. the output of the last integrator.
(See Silva-Steenogaard structure)

- Other advantages:

① $e_2[n]$ is generated by quantizing $e_1[n]$, which itself is "noise-like".

↳ $e_2[n]$ is very close to white noise (uncorrelated with the signal and "itself")
• $R_x(e_2[n]) = \delta[n] \cdot \sigma_{e_2}^2$

↳ $e_2[n]$ behaves like white noise even if $e_1[n]$ is 'tonal'.

see book plot 4.25.

⇒ MASH modulator is less likely to use dithering than a single-loop modulator.

② Allows ^{the} use of a multi-bit quantizer in the second stage of the MASH without any DEM correction for the feedback DAC non-linearity.


↳ as $u_2 = e_1[n]$ is a "noise-like" input and produces much less amount of distortion tones due to the non-linearity in the feedback.

↳ Also, the non-linearity error of the second-stage ^{feedback} DAC (in v_2) is multiplied by $-H_2(z)$ before being added in the output signal v . Since, $H_2(z) = NTF_1(z)$ the DAC₂ non-linearity is suppressed in the baseband.

↳ remnant tones are suppressed, not shaped out so not as good as DWA, but works well as u_2 is a noise-like signal.

↳ "DAC₂ distortion noise/tones is small and tolerable"

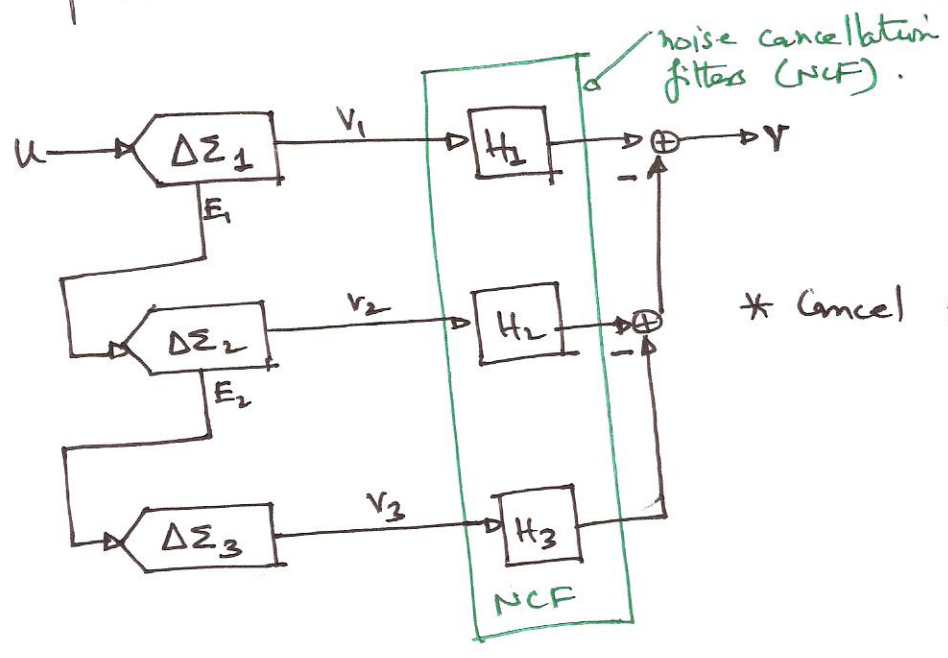• Can further extend MASH to more number of stages (>2).



* Cancel E_1 & E_2 in the NCF.

The cancellation conditions for the 3-stage MASH are:

$$\left. \begin{aligned} H_1 \cdot NTF_1 - H_2 \cdot STF_2 &= 0 \\ H_2 \cdot NTF_2 - H_3 \cdot STF_3 &= 0 \end{aligned} \right\} \rightarrow \textcircled{1}$$

If E_1 & E_2 are perfectly cancelled:

$$\begin{aligned} V &= (STF_1 \cdot U + NTF_1 \cdot E_1) H_1 - (STF_2 \cdot E_1 + NTF_2 \cdot E_2) H_2 \\ &\quad + (STF_3 \cdot E_2 + NTF_3 \cdot E_3) H_3 \\ &= STF_1 \cdot H_1 \cdot U + NTF_3 \cdot H_3 \cdot E_3 \end{aligned}$$

$$\Rightarrow V = STF_1 \cdot H_1 \cdot U + \left(\frac{H_1 \cdot NTF_1 - NTF_2 \cdot NTF_3}{STF_2 \cdot STF_3} \right) E_3$$

• Example NCF design:

$$\Rightarrow H_1 = STF_{2d}, \quad H_2 = NTF_{1d}$$

$$\Rightarrow H_3 = \frac{NTF_{1d} \cdot NTF_2}{STF_3}, \quad \text{choose appropriate } STF_3 = z^{-k}$$

for the overall MASH DSM:

$$\Rightarrow \begin{cases} STF = STF_1 \cdot H_1 = STF_1 \cdot STF_{2d} \\ NTF = \frac{NTF_1 \cdot NTF_2 \cdot NTF_3}{STF_3} \end{cases}$$

↳ Also need to include the interstage coupling coefficients (i.e. β terms).

⇒ H_1 and other STF usually contain simple delays
↳ flat gain in the signal band

⇒ NTF_3 provide 'triple' noise suppression in the signal band.

↳ Ideal the quantization errors of first and second stages (i.e. E_1 & E_2) are cancelled.

Example:
 $\Rightarrow 2-2-2 \Rightarrow 6^{\text{th}}$ order noise-shaping with the stability requirements of only second-order stages!

\hookrightarrow performance is limited by noise leakage of E_1 .

\hookrightarrow ~~and~~ Imperfect matching between analog $NTF_{1,2,3}$, $STF_{1,2,3}$ and digital $h_{1,2,3}$.

Analysis of Noise-leakage in MASH ADCs:

• In the single-loop ΔE modulators, the issues are (assume SC implementation)

\hookrightarrow imperfect matching of capacitors (C's)

\hookrightarrow finite-gain of opamps.

\hookrightarrow incomplete settling and slewing in opamps.

\hookrightarrow these anomalies change the NTF and STF, but will not usually affect the SQNR significantly as long as $L(z)$ is large in the signal band.

$$\therefore |NTF| \approx \frac{1}{|L|} \ll 1$$

eg. for opamp gain as low as $\frac{0.99}{\pi}$, the SQNR decreases only by a few dB's.

• In 2-stage MASH:

\hookrightarrow large SQNR is achieved by accurate cancellation of $E_1(z)$, which is shaped by a low-order $H_2 = NTF_2 z$.

\hookrightarrow requires accurate matching between the analog and digital components. transfer function combinations:

$$H_1: NTF_1 \text{ and } H_2: STF_2$$

\hookrightarrow Designer needs to be aware of the matching between the circuit blocks to keep E_1 -leakage low.

- For a 3-stage MASH, leakage of $E_2(z)$ should also be analyzed.
 - ↳ equations describing leakage become complex.
 - ↳ Need accurate behavioral simulations for characterization.

Simple Analysis:

The 'leakage transfer-functions' for E_1 & E_2 to the overall MASH output

V are:

$$H_{L1} = H_1 \cdot NTF_1 - H_2 \cdot STF_2$$

$$H_{L2} = H_2 \cdot NTF_2 - H_3 \cdot STF_3$$

- Ideally both of these leakage TFs are zero, but due to imperfect analog components (circuit blocks), the NTF & STF will be inaccurate.
 - ⇒ H_{L1} & H_{L2} will be non-zero, allowing E_1 & E_2 to leak into V .

$$H_{L1} = \frac{H_1 \cdot NTF_1}{z^2 (1-z)^2} - \frac{H_2 \cdot STF_2}{(1-z)^2 \cdot z^{-2}} \quad \text{for 2-2-MASH}$$

Simplifying assumptions:

- ① The leakage of E_2 is less important than that of E_1 . Since H_{L2} represents higher-order noise shaping than H_{L1} .

Ex. in a 2-2-1 MASH ⇒ H_{L1} noise-shaping is 2nd order
 H_{L2} noise-shaping is 4th order
 ↳ also if multi-bit quantizer is used in the 2nd-stage
 ⇒ $|E_2| \ll |E_1|$.

- ② In H_{L1} , the effect of imperfect NTF_2 dominates that of imperfect STF_2 , even though the gain-error is same for both.

∴ Since $H_{2d} = NTF_1 \stackrel{\Delta}{=} (-z^{-1})^2$, the errors in STF_2 are inherently noise-shaped. However the errors in NTF_1 are not noise-shaped as $H_1 = STF_{2d} \Rightarrow$ flat in the signal band

③ Using ② $STF_2 = H_1 = 1$ in the signal band, then

$$|H_{e1}| \approx |NTF_1 - H_2| = |NTF_{1a} - NTF_{1i}|$$

$\hookrightarrow i \Rightarrow$ ideal model
 $\hookrightarrow a \Rightarrow$ analog implementation

④ ∴ $NTF_1 = \frac{1}{1-L}$,

Assuming small errors we have, $|L_i| \gg 1$ in the signal band


$$\Rightarrow |H_{e1}| \approx \left| \frac{1}{L_{1i}} - \frac{1}{L_{1a}} \right| \longrightarrow \text{②}$$

\hookrightarrow a much simpler to evaluate than the original $|H_{e1}|$.

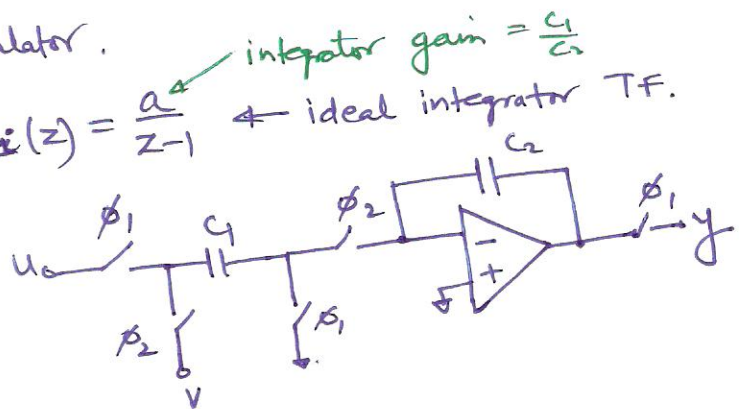Example:

A 1-1 or 1-1-1 MASH modulator.

loop-filter in the 1st stage, $I_2(z) = \frac{a}{z-1}$ ← ideal integrator TF.




errors: • Capacitor ratio error

$$\frac{C_1}{C_2} = (1+D) \rightarrow \text{changes } 'a'$$

- finite op-amp DC gain $A \rightarrow$ changes both 'a' and the pole location.
- finite op-amp $f_{un} \Rightarrow$ changes 'a' due to incomplete settling
 \hookrightarrow effects of slewing ignored for now.
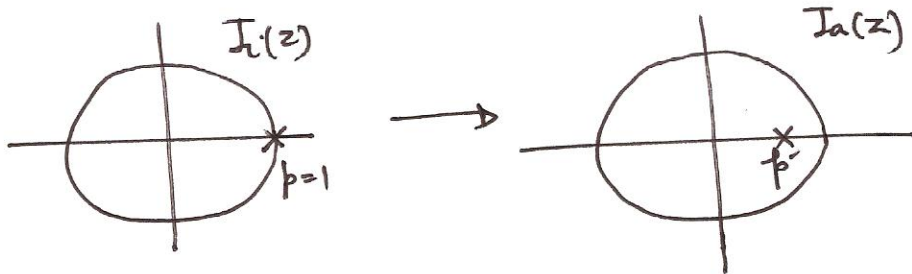
$$\Rightarrow I_a(z) = \frac{a'}{z-\beta'} \leftarrow \text{model for imperfect integrator.}$$



for $D \ll 1$, & $\frac{a}{A} \ll 1$ we can write

$$\begin{cases} a' \stackrel{D}{\approx} a \left[1 - D - \frac{(1+a)}{A} \right] \\ p' = 1 - \frac{a}{A} \end{cases}$$

Here, $L_1(z) = -I(z)$

$$\Rightarrow |H_{e1}| = \left| \frac{(z-1)}{a} - \frac{(z-p')}{a'} \right|$$

$$\approx \left| \frac{1}{a'} \right| \cdot \left| \frac{a}{A} + (z-1) \left(D + \frac{1+a}{A} \right) \right|$$

$$\Rightarrow |H_{e1}| \approx \underbrace{\frac{1}{A}}_{\text{direct noise feedthrough}} + \underbrace{(z-1) \left[\frac{D}{a} + \left(1 + \frac{1}{a}\right) \frac{1}{A} \right]}_{1^{\text{st}}\text{-order filtered}}$$

b) Unfiltered E_1 -leakage component $\approx \boxed{\frac{E_1}{A}}$

and a first-order filtered component

approximately equal to $\boxed{(z-1) \left[\frac{D}{a} + \left(1 + \frac{1}{a}\right) \frac{1}{A} \right] \cdot E_1}$

\Rightarrow for high SNR, \Rightarrow very high opamp gain with excellent settling required to reduce the unfiltered leakage to sufficiently low-level.

\Rightarrow for low-OSR, the second component will also become significant,

\Rightarrow ~~the~~ $(z-1) \frac{E_1}{A}$ becomes larger in signal band.

\hookrightarrow matching accuracy of the caps should be better now. So that $D \ll 1$.

- for a second-order first stage in the MASH, the leakage of ϵ_1 can be reduced. (11)

↳ complicated analysis.

- Assume 2-0 MASH

↳ first-stage is a low-distortion 2nd-order modulator
 ↳ two cascaded integrators

Now, $I_{a_k}(z) = \frac{a_k'}{(z-p_k')}$, for both the integrators, $k=1,2..$

Using Taylor series expansion around $z=1$, we have

$$H_{d1}(z) = A_0 + A_1(1-z^{-1}) + A_2(1-z^{-1})^2 + \dots$$

- Assume $A_2 \gg 1 \Delta D \ll 1$

⇒ for the series coefficients, we get

$$A_0 = \frac{1}{A^2} \rightarrow \text{unfiltered leakage} \propto \frac{1}{A^2} \Rightarrow \text{very small}$$

$$A_1 = \left(\frac{1}{a_1} + \frac{1}{a_2}\right) \frac{1}{A} \rightarrow \text{linearly filtered leakage}$$

$$A_2 = \frac{1}{a_1 a_2} - 1 + 2 \left[1 - \frac{1}{a_1 a_2} - \frac{1}{a_2}\right] \frac{1}{A} + \frac{2D}{a_1 a_2} \rightarrow (1-z^{-1})^2 \text{ filtered leakage.}$$

For $OSR \gg 1$, A_1 & A_2 terms dominate $|H_{d1}|$.

- The derivation above ignored leakage due to the coupling ~~errors~~ branch (c_2) and the errors in the second stage.

↳ these terms only contribute to A_2, A_3, \dots as H_2 is a 2nd-order HPF.

⇒ A second-order first stage is beneficial in a MASH to achieve higher (near-ideal) SNR with reasonable opamp gains (A).

Ref: Textbook pgs 132-136.

Also see the yellow-book of $\Delta\Sigma$.

PS: CT-MASHes to be covered later
 ↳ much more complicated!