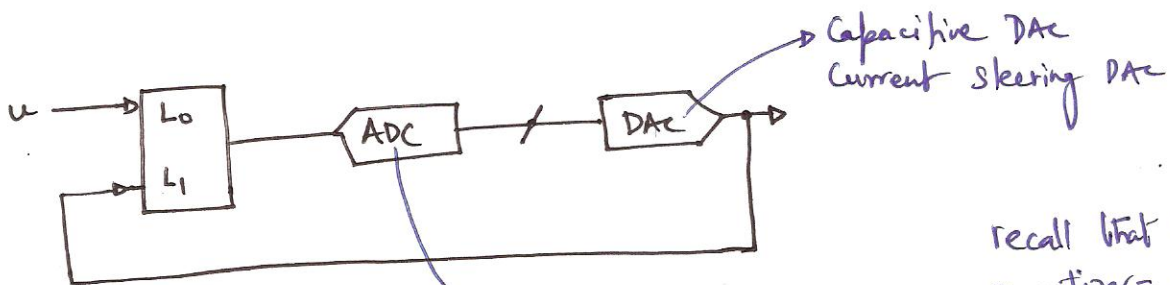



# Continuous-time $\Delta\Sigma$ Modulators



fast ADC  
 ↳ Flash  
 ↳ maximum 4-5 bits.


recall that:  
 quantizer = ADC + DAC

## Discrete-time loop filter:

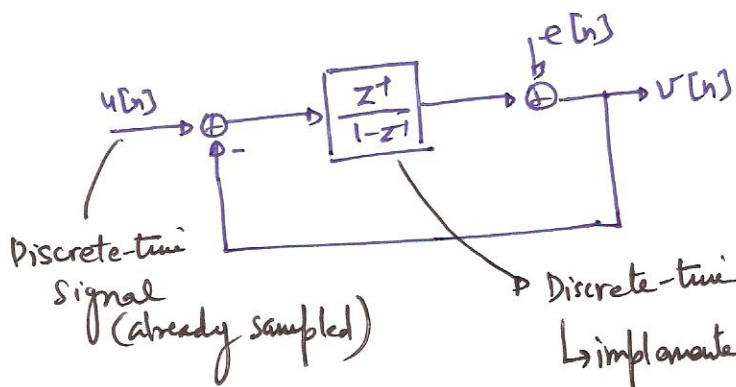


Discrete-time accumulator  
 ↳ implemented using switched capacitor circuits

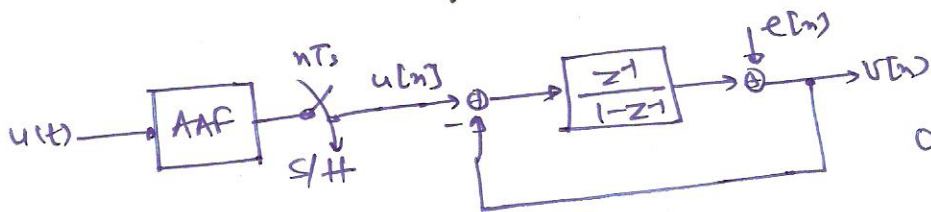DT- $\Delta\Sigma$  → well established technology  
 ↳ initially used for audio recording applications (16-24 bits resolution).  
 ↳ requires AAF in the front-end.




oversampling simplifies the AAF design.

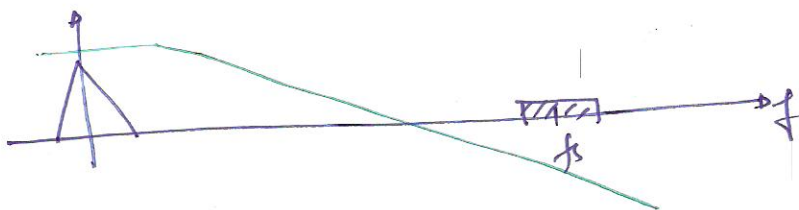

Consider the DT impulse response,  $h[n]$ .




and.

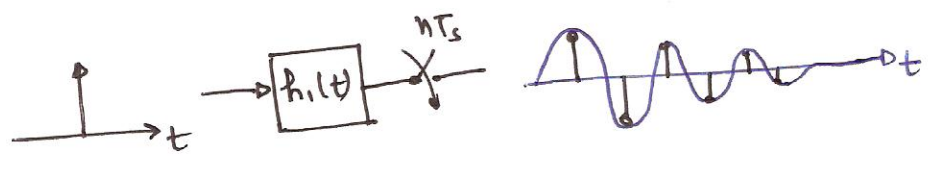

Can use a continuous-time (CT) impulse response  $h_c(t)$  such that the sampled response is  $h[n]$ .

- ↳ many CT responses ' $h_c(t)$ ' are possible.
- ↳ impulse invariance transformation

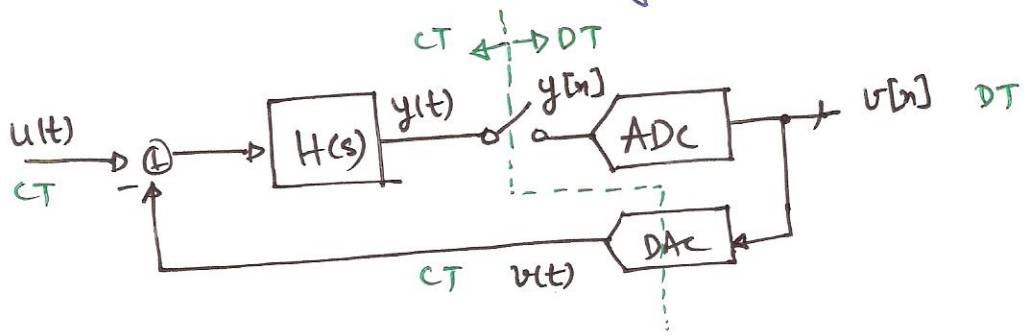Basic idea  $\Rightarrow$  find a CT filter whose sampled impulse response is same as the DT filter.



The loop filter is realized using CT circuitry, but made to look like a discrete-time loop-filter.


- ↳ the quantizer cannot distinguish between the DT or CT loop-filter implementation.

CT-DSM has been gathering interest for past 10 years

↳ lower power dissipation


↳ being actively researched → requires deep understanding of signal and systems.

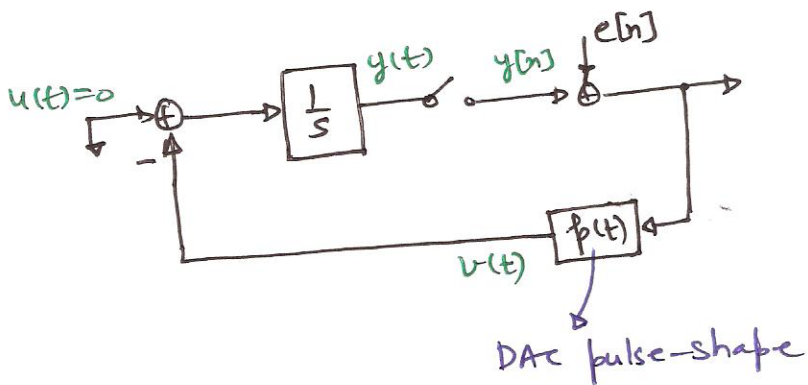- We will initially study first-order CT-DSM and then later generalize to higher-order cases.



The DAC is converting a DT signal to a CT signal  
 ↳ DAC pulse shape needs to be accounted for.  
 ↳ The NTF should be same as the DT NTF.

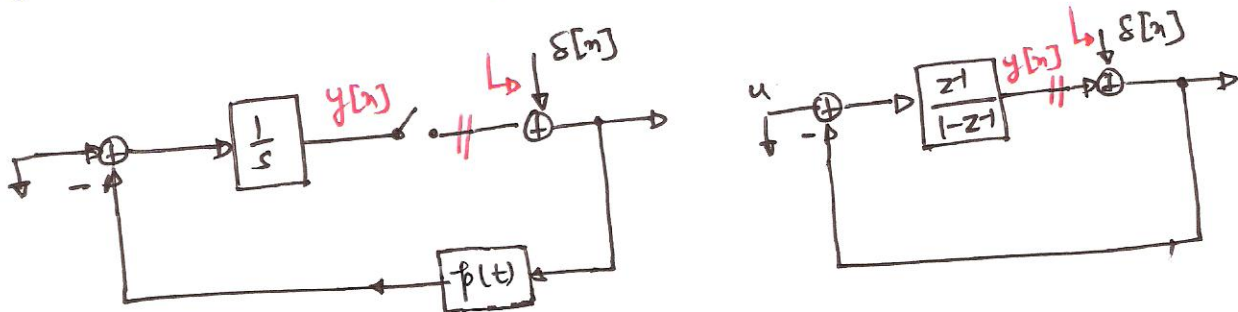Analysis: Break the loop after the sampler and inject a unit impulse.





• If a DT impulse is launched after the sampler, then the returned response after the sampler should be equal to the impulse response in DT modulator.

↳ This impulse response is the loop response seen by the quantization noise i.e.  $L_1(z) \leftrightarrow l_1[n]$ .

• If  $L_1(z)$  is same for the CT & the DT loops  
 ⇒  $NTF(z) = \frac{1}{1-L_1(z)}$  is also guaranteed to be the same.



- Also the STF at low frequencies should be equal to 1.
  - ↳ low frequency components should be the same.
  - ↳ same DC gain.
  - ↳ set  $u=0$  in both cases and just focus on NTF.

The DT impulse response

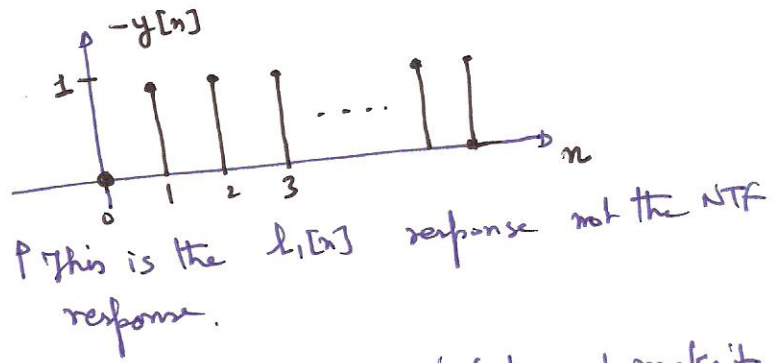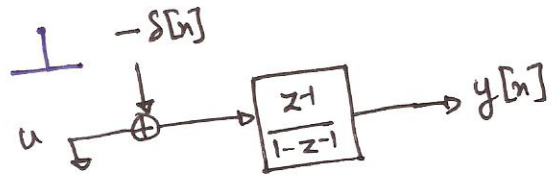

⇒ Rather than working with  $NTF(z) = \frac{1}{1-L_1(z)}$ , deal with  $L_1(z)$  and make it equal for DT as well as the CT ~~loop~~ loop.


DAE response:

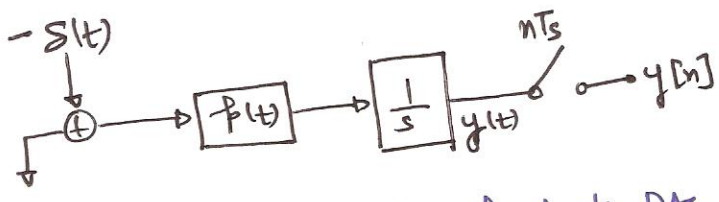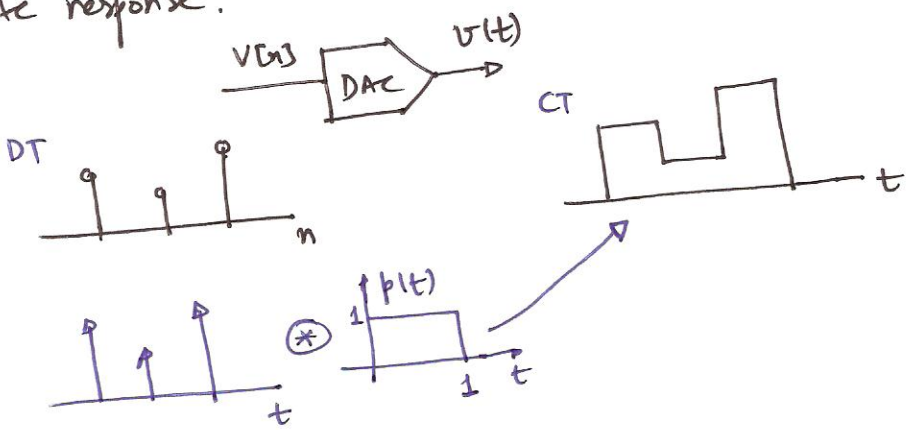


• Pulse shape of the feedback DAC influences the NTF.

## NRZ pulse-shape!


5

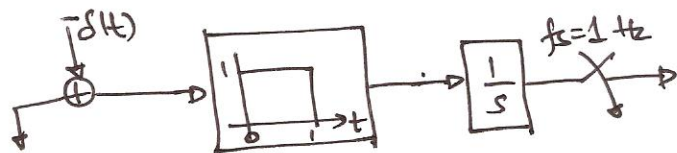

$$T_s = 1s, f_s = 1Hz$$

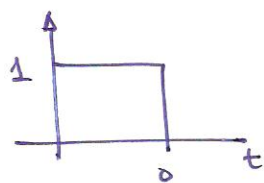

$\frac{1}{s}$


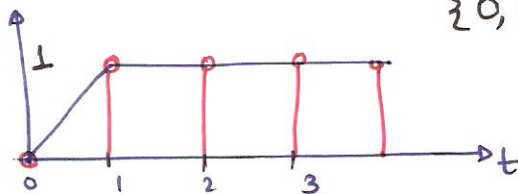


{0, 1, 1, ...}

↳  $L_1$  response is same as in DT case

↳ NTF is also same for DT & CT.

## RZ pulse-shape!

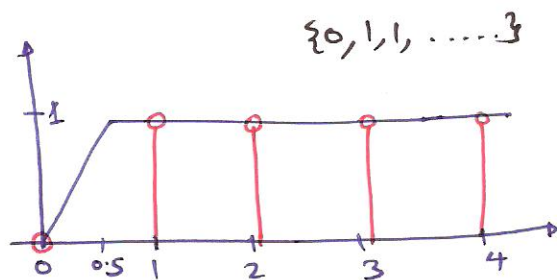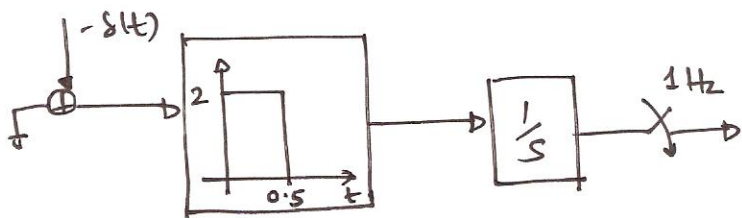

{0, 1, 1, ...}

Need to scale the DAC pulse amplitude (x2) to obtain the same DC gain.



↳ same as DT impulse response

⇒ Can have any number of CT responses to result in the same DT impulse response.


⇒ same NTF(z) for many possibilities of the loop filter  $L(s)$ .

Change the sampling rate

$p(s)$  @ 1Hz

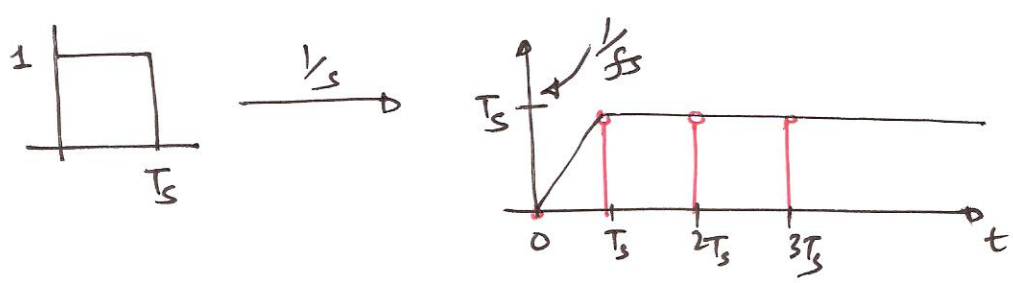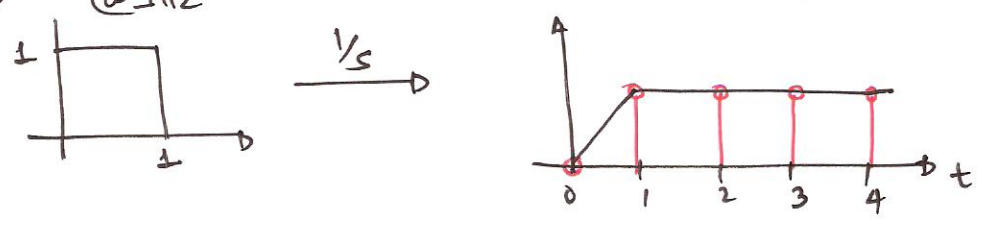

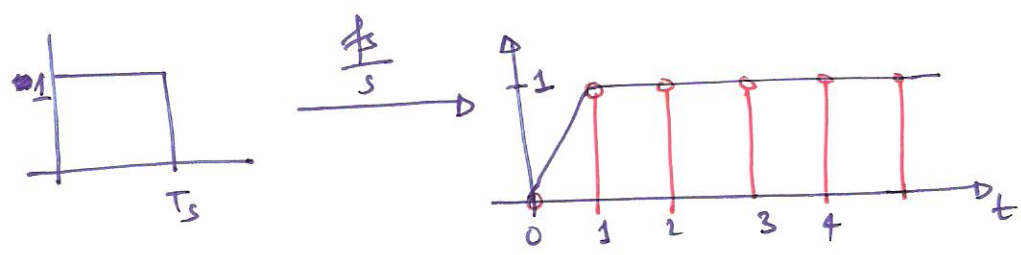⇒ for sampling rate  $f_s > 1$ , the pulse shape width is reduced  
 ↳ loop gain has changed.



⇒  $\boxed{\frac{1}{s}}$  is now  $\boxed{\frac{f_s}{s}}$  or  $\boxed{\frac{1}{sT_s}}$

↳ time-scaling of the loop filter



• Design for  $f_s = 1$  Hz and at the last step scale the loop filter to the appropriate response.

$$\left. \begin{aligned} h(s) &\leftrightarrow H(s/\omega_0) \\ \Rightarrow h(at) &\leftrightarrow \frac{1}{|a|} H\left(\frac{s}{a\omega_0}\right) \end{aligned} \right\} \text{Time scaling of electrical networks.}$$

• Designing CT filter with  $f_s = 1$  Hz also has advantages in MATLAB simulation where very large or very small quantities are avoided.  
 ↳ truncation errors are avoided.
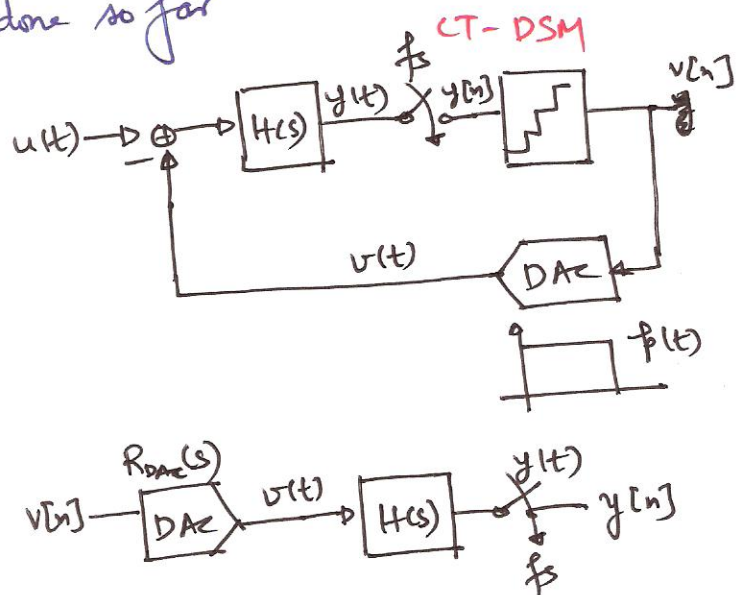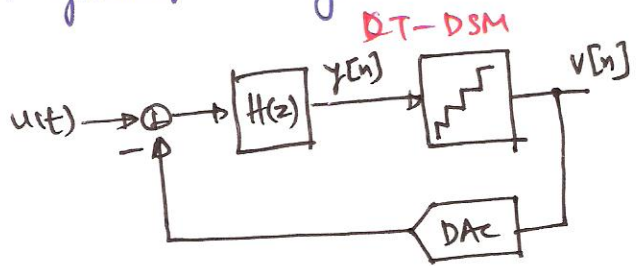
# The Impulse-Invariant Transformation

Generalization of what we have done so far



Both are discrete-time systems

If the input to both the quantizers ( $y[n]$ ) are same at the sampling instants, then for  $v[n] = \delta[n]$ ,

$$y[n] \triangleq y(t) \Big|_{t=nT_s}$$

$$\Rightarrow h[n] \triangleq y(t) \Big|_{t=nT_s, v[n] = \delta[n]}$$

$$\Rightarrow \mathcal{Z}^{-1}\{H(z)\} = \left( \mathcal{L}^{-1}\{R_{\text{DAC}}(s) \cdot H(s)\} \right) \Big|_{t=nT_s}$$

\*  $p(t) \xleftrightarrow{\mathcal{L}} R_{\text{DAC}}(s)$   
is the impulse response of the specific DAC.

In time domain

$$h[n] = [p(t) \otimes h(t)] \Big|_{t=nT_s}$$

$$= \int_{-\infty}^{\infty} p(\tau) \cdot h(t-\tau) d\tau \Big|_{t=nT_s}$$

↳ This is called the impulse invariant transformation (IIT)

↳ impulse responses equal at sampling times.