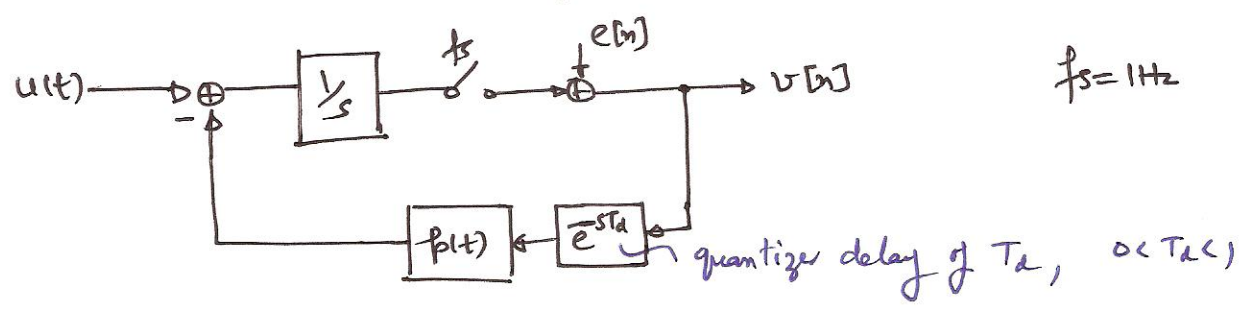




Excess loop-delay in CT-DSMs

Non-idealities \rightarrow Quantizer delay





Ideal (No delay) case

Real case (with quantizer delay)

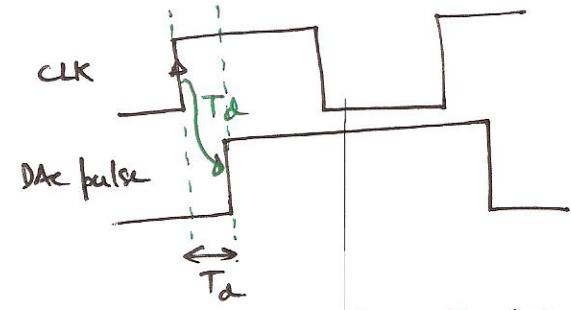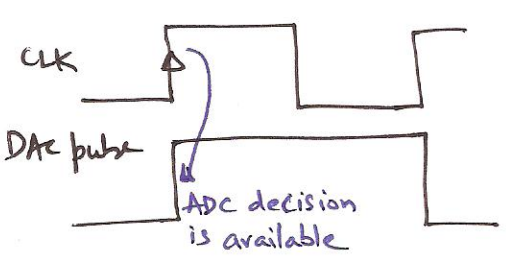

\Rightarrow More delay in the loop \Rightarrow NTF will be affected as $L(z)$ changes.



Ideal case:

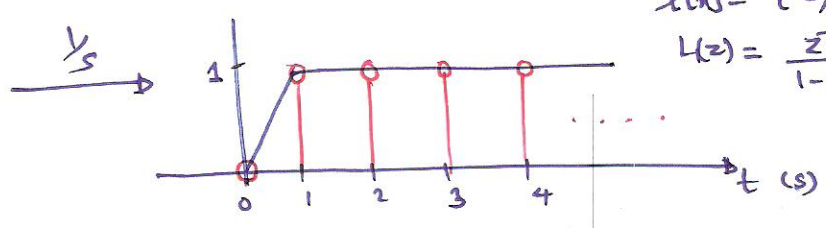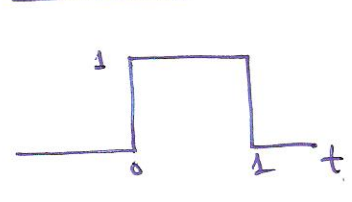

$$l[n] = \{0, 1, 1, \dots\}$$

$$L(z) = \frac{z^{-1}}{1-z^{-1}}$$

with delay:

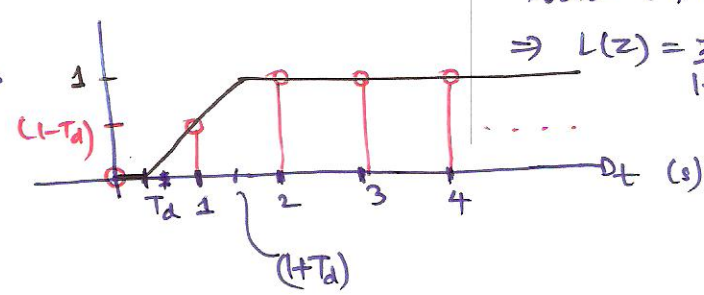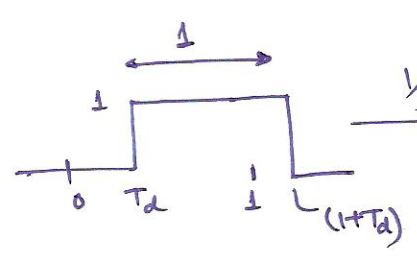

$$l[n] = \{0, (1-T_d), 1, 1, \dots\}$$

$$\Rightarrow L(z) = \frac{z^{-1}}{1-z^{-1}} - T_d z^{-1}$$

\Rightarrow first sample after the unit-delay (T_s) is smaller than expected. ($l[n]$ must always be equal to 0).

with ELD:

(2)

$$\begin{aligned} \text{NTF}(z) &= \frac{1}{1+L(z)} = \frac{1}{1 + \frac{z^{-1}}{1-z^{-1}} - T_d z^{-1}} \\ &= \frac{(1-z^{-1})}{1 - T_d z^{-1} (1-z^{-1})} = \frac{(1-z^{-1})}{1 - T_d z^{-1} + T_d z^{-2}} \end{aligned}$$

for low frequency, $z \approx 1$, $\Rightarrow \text{NTF}(z)|_{z=1} \approx (1-z^{-1})$
 \Rightarrow for DC input the NTF is unchanged.

• poles of the NTF are at $\frac{T_d \pm \sqrt{T_d^2 - 4T_d}}{2}$

\Rightarrow As T_d increases, the poles start moving out of the unit circle.

\hookrightarrow modulator becomes unstable.

\hookrightarrow too much delay \Rightarrow phase of the loop-response is too high

\hookrightarrow loop-becomes unstable.

\Rightarrow As the order of the filter becomes higher, the excess loop delay (ELD) problem gets worse.



\hookrightarrow amount of T_d tolerable, as the loop-order increases, decreases.

\Rightarrow only one NTF zero.

\hookrightarrow noise-shaping is not enhanced



\hookrightarrow but the ~~the~~ order of the modulator is increased.

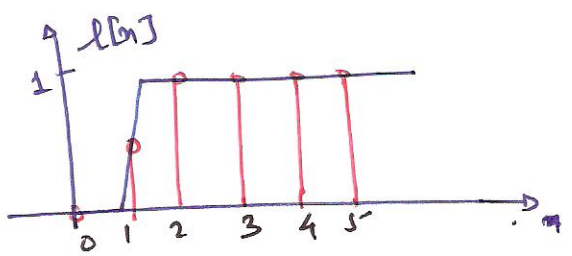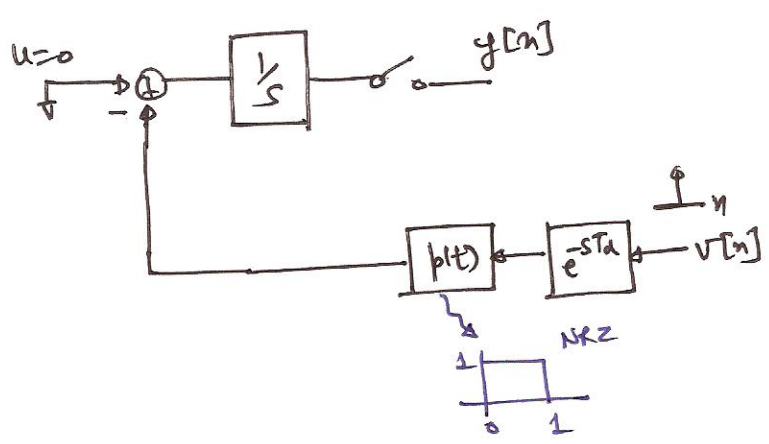A simple fix for the first-order CT-DSM
 ↳ more complicated for higher order topologies



impulse response
 $\frac{z^{-1}}{1-z^{-1}} - T_d z^{-1}$

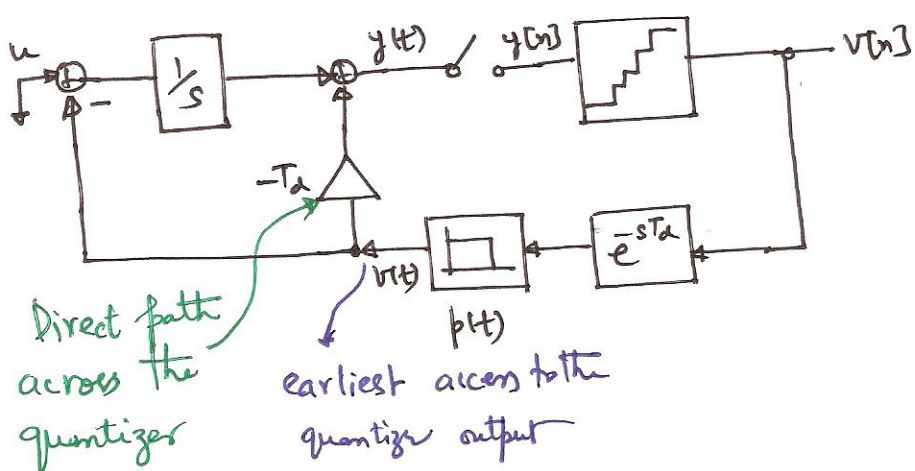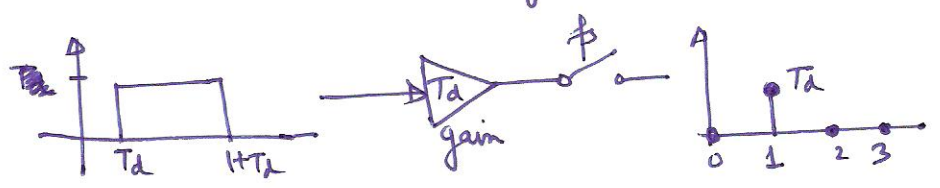- ⇒ Somehow need to add $T_d z^{-1}$ to the impulse response.
- ⇒ Need to add a waveform which after sampling results in ~~the~~ $T_d \cdot z^{-1}$
- ⇒ How about using the DAC pulse itself.
 ↳ many such solutions possible.




$$\Rightarrow \left(\frac{z^{-1}}{1-z^{-1}} - T_d z^{-1} \right) + T_d z^{-1} = \frac{z^{-1}}{1-z^{-1}}$$


$$\Rightarrow L_1(z) \text{ is fixed.}$$

Direct path across the quantizer
 earliest access to the quantizer output


Graphical explanation:

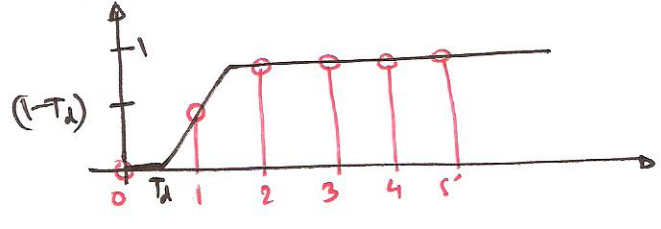

← $y[n]$ with ELD

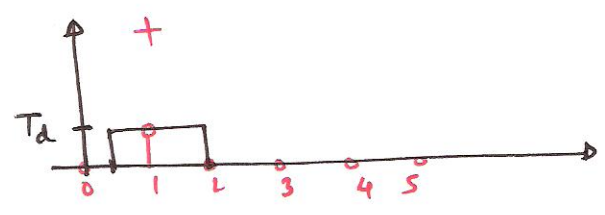

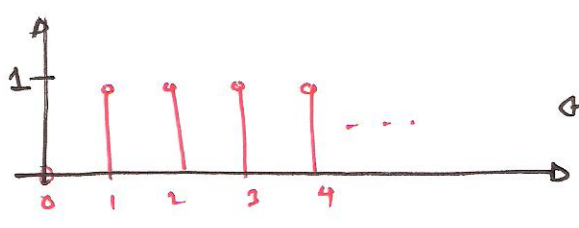← $y[n]$ only due to the direct path around the quantizer



← $y[n]$ after ELD compensation.

⇒ With the excess loop delay, the amount of signal feedback to the quantizer has decreased.

↳ To fix for the delayed feedback, a some amount of direct feedback is provided immediately to the quantizer input in order to stabilize the loop.

o Other way to understand the direct path is that, in order to reduce the excess phase, an LHP zero is added (direct path) to provide quick feedback and stabilize the loop.

Summary:

- o If T_d becomes significant, NTF changes
 - ↳ feedback is delayed → instability
 - ↳ fix by adding a direct path to provide some quick feedback. (generally $T_d < 60\%$ of T_s)
- o Note that when $T_d=0$, the direct path is unacceptable (⇒ zero delay loop)
- o ELD compensation is more complicated for higher-order topologies
 - ↳ (we'll study that later)