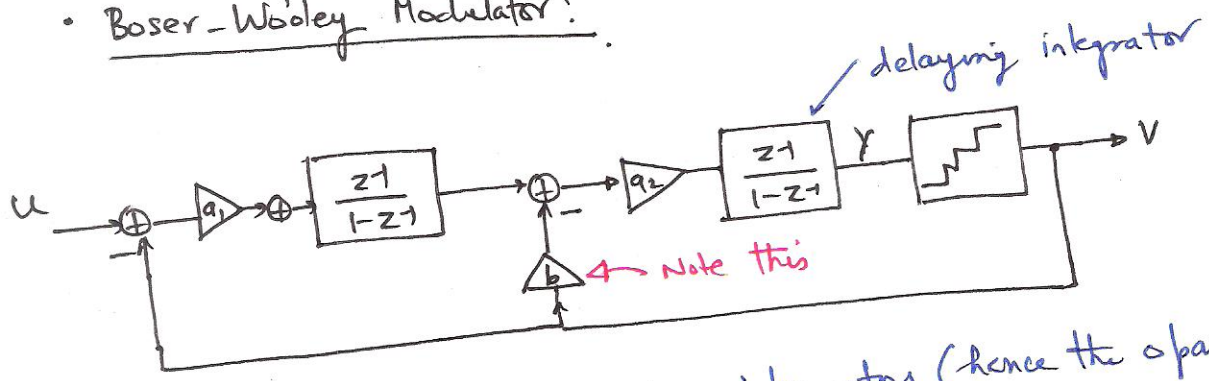


## Alternative 2<sup>nd</sup> order ~~SSM~~ modulators

(2)

- large number of structures for 2<sup>nd</sup> order noise-shaping with  $STF(z) = 1$  or  $z^{-1}$  or  $z^{-2}$ .
- Be careful to avoid delay-free loops.
- Should have reasonable robustness against practical circuit requirements/limitations like finite opamp gm, gain, SR, comparator delay (or quantizer delay), etc.

### Boser-Wooley Modulator:



• Setting requirements on the integrators (hence the opamps) is reduced.

$$NTF(z) = \frac{(1-z^{-1})^2}{D(z)} \quad \text{and} \quad STF(z) = \frac{a_1 a_2 z^{-2}}{D(z)}$$

where,  $D(z) = (1-z^{-1})^2 + a_2 b z^{-1} (1-z^{-1}) + a_1 a_2 z^{-2}$

for  $STF(z) = z^{-2}$  and  $NTF(z) = (1-z^{-1})^2$  we have the conditions  $a_1 a_2 = 1$  and  $a_2 b = 2$ .

$$\Rightarrow D(z) = 1$$


$\Rightarrow$  infinite solutions possible

- Sol<sup>n</sup> ①:  $a_1 = a_2 = 1$  &  $b = 2$
- Sol<sup>n</sup> ②:  $a_1 = 1/2$ ,  $a_2 = 2$ ,  $b = 1$

\* In actual design "Range-Scaling" eliminates these ambiguities in designs

Here,  $U(z) - V(z) = \underbrace{(1-z^{-2}) U(z) - (1-z^{-1})^2 E(z)}_{\hookrightarrow \text{check this spectrum}}$

# The Silva-Stenstaad Structure:

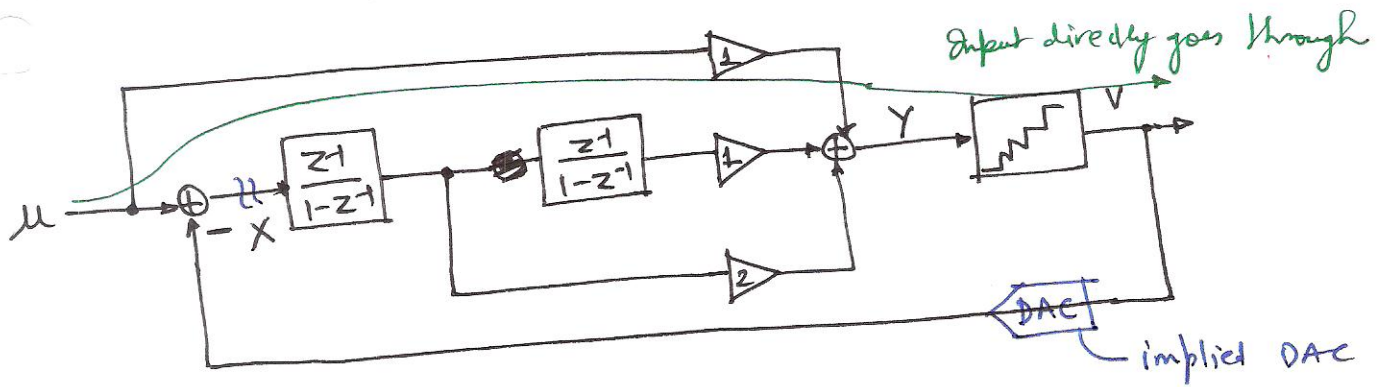

- Note the direct feed-forward path.
- $V(z) = U(z) + (1-z^{-1})^2 E(z)$  ← Note  $U(z)$  is not delayed even when using delaying integrators
- Input signal to the loop filter?
  - $= U(z) - V(z)$
  - $= -(1-z^{-1})^2 E(z)$  ← contain only noise, no signal content


## Advantages:

- ① requirements on loop-filter linearity are reduced.  $\Rightarrow$  Lower power
- ②  $\hookrightarrow$  signal swing at X is reduced  $\rightarrow$  lower SR requirements from the opamps.

- output of the second-integrator:  $-z^2 E(z) \rightarrow$  can be directly used in a MASH without any differencing.
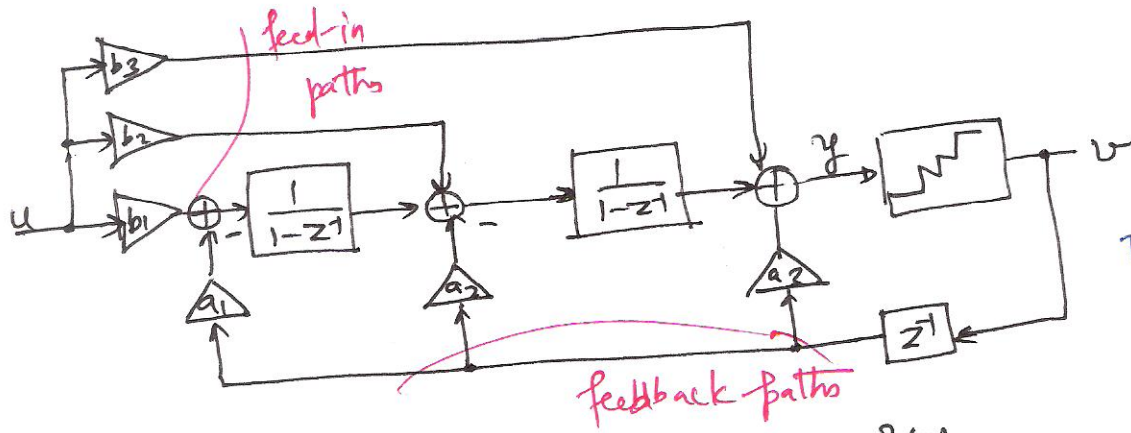
## Disadvantages:

- ① Extra ADDER before the quantizer
  - $\hookrightarrow$  passive adders using capacitors (for s/c design)



TextBook page 82-85.

$$NTF(z) = \frac{(1-z^{-1})^2}{A(z)}, \quad STF(z) = \frac{B(z)}{A(z)}$$

$$B(z) = b_1 + b_2(1-z^{-1}) + b_3(1-z^{-1})^2$$

$$A(z) = 1 + (a_1 + a_2 + a_3 - 2)z^{-1} + (1 - a_2 - 2a_3)z^{-2} + a_3z^{-3}$$

Used only in CT-DSM for Excess-loop delay compensation (zlativ).

By using multiple feedback paths

By using multiple feed-in and feed-back paths, more flexibility is obtained for enhancing stability and Dynamic Range.

Which topology/architecture is the best for 2<sup>nd</sup> order modulator?


↳ what is the optimal NTF? (STF is secondary)

⇒ Find an NTF which minimizes the IN BAND NOISE (IBN) <sup>Quantization</sup>

$$|NTF(z)| = \frac{|(-z^{-1})^2|}{|A(z)|} \approx \frac{\frac{1}{2}\omega^2}{|A(z)|} \text{ for } \omega \ll \pi$$

$$= k\omega^2, \quad k = \frac{1}{|A(1)|}$$

• |A(1)| is the DC gain of A(z)

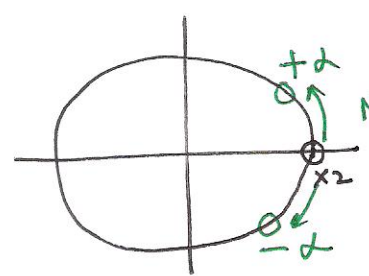

Move the NTF zeros. for  $z=1$  to  $z=e^{\pm j\alpha}$

$$\Rightarrow |NTF(z)| \text{ in the signal band} \approx k(\omega + \alpha)(\omega - \alpha)$$

$$= k(\omega^2 - \alpha^2)$$

$$\omega_B = \frac{\pi}{OSR}$$

$$\Rightarrow IBN = \frac{\Delta^2}{12\pi} \int_0^{\omega_B} k(\omega^2 - \alpha^2)^2 d\omega$$

$$= \frac{\Delta^2 k^2}{12\pi} \int_0^{\omega_B} (\omega^2 - \alpha^2)^2 d\omega = \frac{\Delta^2 k^2}{12\pi} I(\alpha)$$

where the integral  $I(\alpha) = \int_0^{\omega_B} (\omega^2 - \alpha^2)^2 d\omega$

for the least IBN,  $I(\alpha)$  must be minimized

$$\Rightarrow \frac{dI(\alpha)}{d\alpha} = 0$$


$$\Rightarrow \frac{d}{d\alpha} \int_0^{\omega_B} (\omega^2 - \alpha^2)^2 d\omega = 0$$

$$\Rightarrow \int_0^{\omega_B} \frac{d}{d\alpha} (\omega^2 - \alpha^2)^2 d\omega = 0$$

$$\Rightarrow 4\alpha \int_0^{\omega_B} (\omega^2 - \alpha^2) d\omega = 0$$

$$\Rightarrow \frac{\omega_B^3}{3} - \alpha^2 \frac{\omega_B}{1} = 0$$
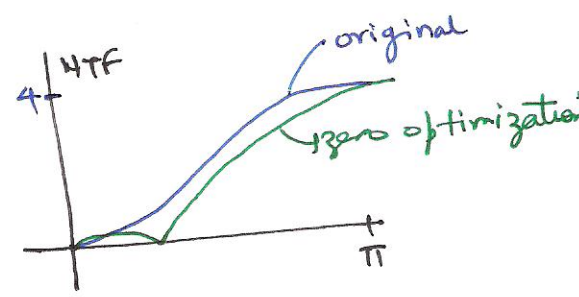
$$\Rightarrow \alpha_{opt} = \frac{\omega_B}{\sqrt{3}}$$




Now find,  $\frac{I(0)}{I(\alpha_{opt})} = \frac{9}{4} \Rightarrow$  SQNR improvement =  $\log_{10}(9/4) = 3.5$  dB

Now, what if we also optimize the pole locations?  
↳ MATLAB based design using exhaustive search.

optimal denominator

$$A_{opt}(z) = 1 - 0.5z^{-1} + 0.16z^{-2}$$


↳ 6 dB higher SQNR.

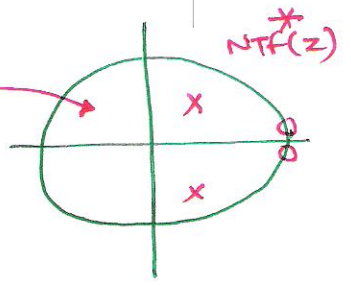

\* We will study this algorithm in detail later.

# Describing Function Analysis

Generalized Block Diagram

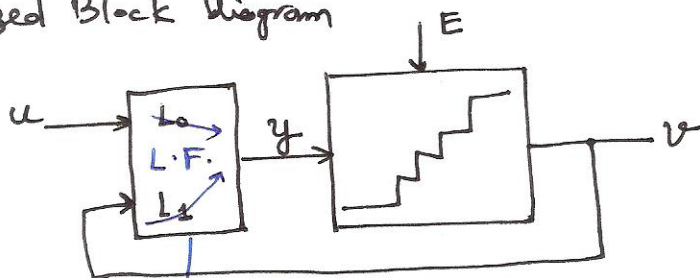

$$Y(z) = L_0(z)U(z) + L_1(z)V(z)$$

where,

$$L_0(z) = \frac{STF(z)}{NTF(z)}$$

$$L_1(z) = \frac{NTF(z) - 1}{NTF(z)}$$

for the whole modulator:

$$\Rightarrow V(z) = Y(z) + E(z)$$

$$= L_0(z)U(z) + L_1(z)V(z) + E(z)$$

$$\Rightarrow V(z) = \underbrace{\frac{L_0(z)}{1 - L_1(z)}}_{STF} \cdot U(z) + \underbrace{\frac{L_1(z)}{1 - L_1(z)}}_{NTF} \cdot E(z)$$

$$= STF(z) \cdot U(z) + NTF(z) \cdot E(z)$$

So far a linear model. But how to model the quantizer so as to understand the effects of its non-linearity.

- Overload (or saturation) of the quantizer causes instability:
  - ↳ when input exceeds the range of the quantizer, the output of the quantizer doesn't change at all.
  - ↳ feedback breaks down!

Definition of stability:  
for LTI systems,

Bounded input  $\rightarrow$  Bounded output (BIBO)  
 $\Rightarrow \sum_n |h(n)| < \infty$

• So far we have assumed Linear Model of noise.

Loop-filter  
↳ 2 inputs & 1 output

\* for second-order DSM  
 $L_0(z) = \frac{1}{(1-z^{-1})^2}$   
 $L_1(z) = \frac{-z^{-1}}{1-z^{-1}} - \frac{z^{-1}}{(1-z^{-1})^2}$

\* for special cases:  
 $L_0(z) = L_1(z) = L(z)$   
 Ex. first-order DSM



# ECE 697 Delta-Sigma Converters Design

## Lecture#9 Slides

Vishal Saxena


([vishalsaxena@u.boisestate.edu](mailto:vishalsaxena@u.boisestate.edu))

# 2<sup>nd</sup> order DSM

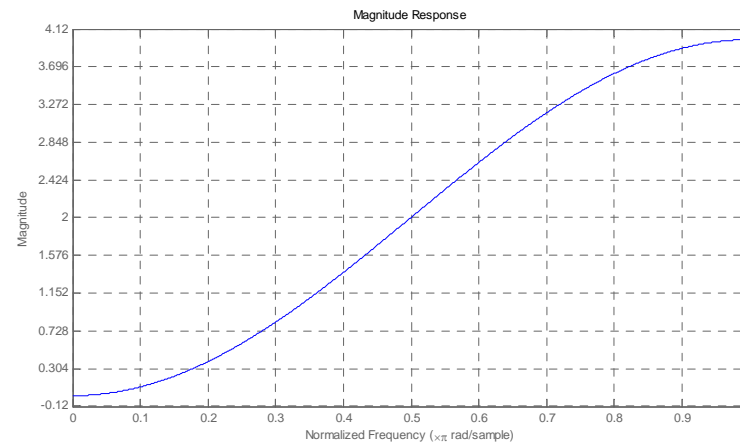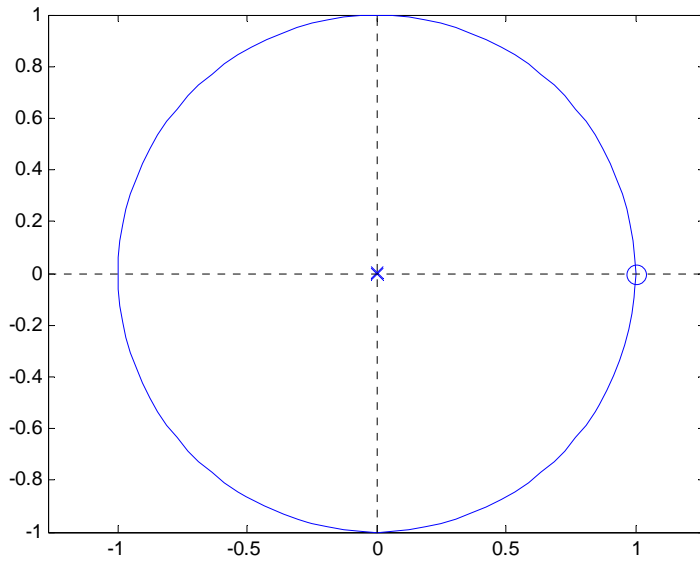


$$NTF(z) = (1 - z^{-1})^2$$

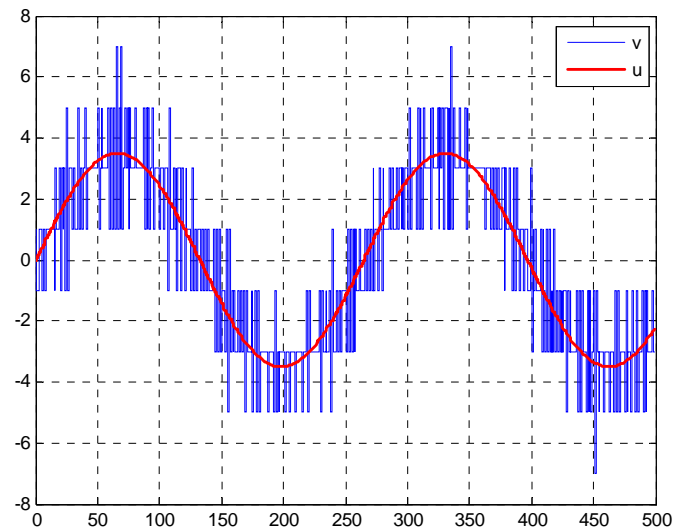File: Second\_Order\_DSM\_Zero\_Opt.m  
Set variable opt=0.





## 2<sup>nd</sup> order DSM: contd.

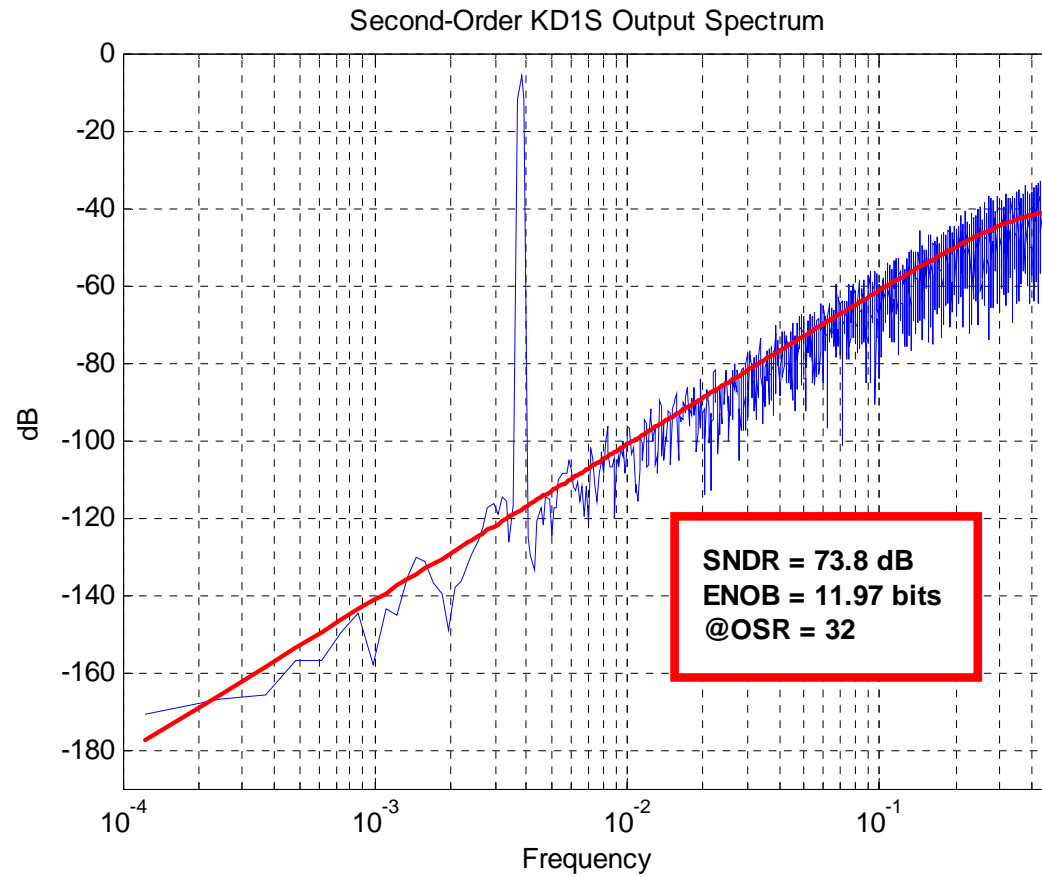



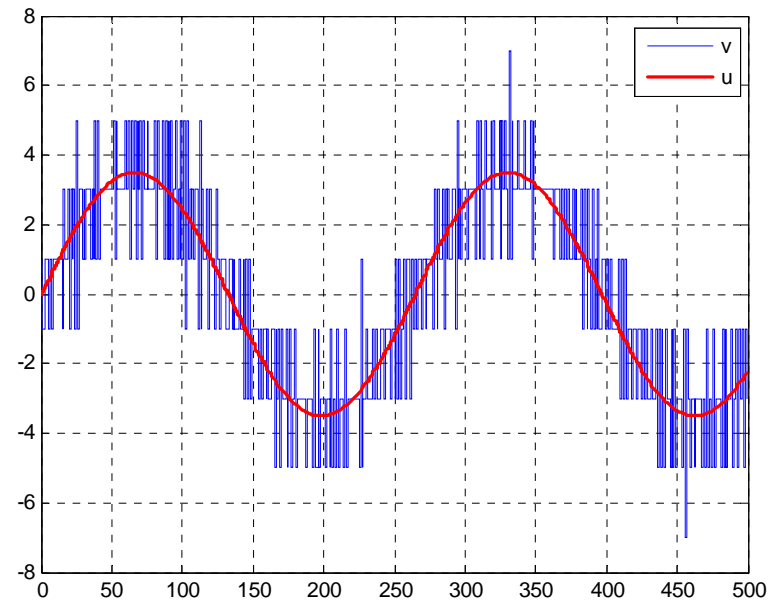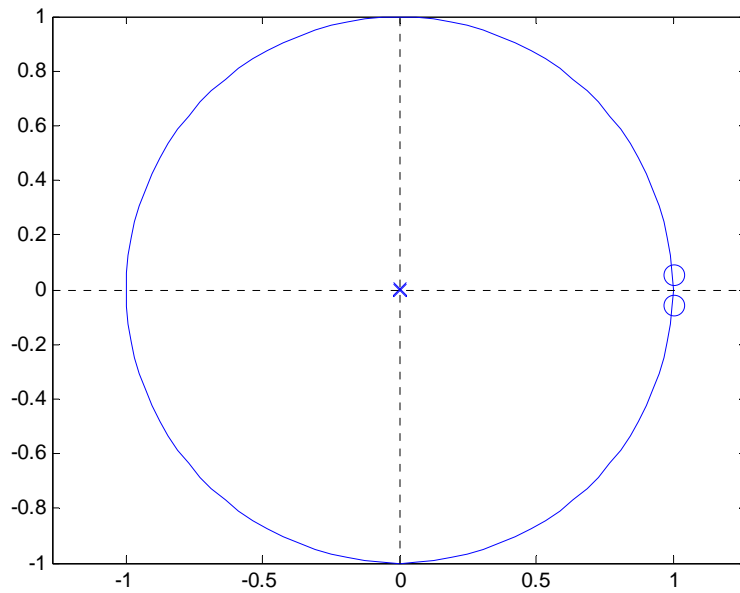
## 2<sup>nd</sup> order DSM: NTF Zero Optimization



$$NTF(z) = (1 - e^{j0.06} z^{-1})(1 - e^{-j0.06} z^{-1})$$

File: Second\_Order\_DSM\_Zero\_Opt.m  
Set variable opt=1.
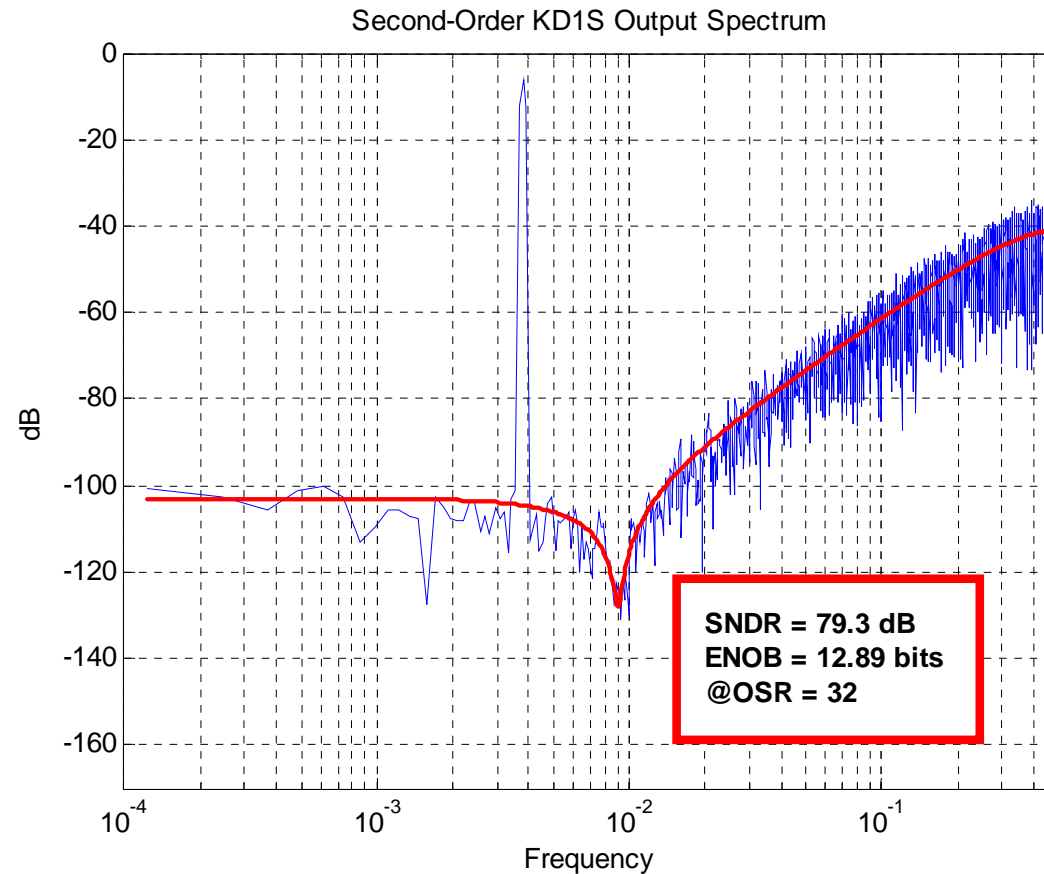
## 2<sup>nd</sup> order DSM: NTF Zero Optimization contd.



- 5.5 dB increase in SQNR.
- NTF pole (if any) optimization to be discussed later.